

JANUARY 1981

Australia \$1.50; Malaysia \$5.10; New Zealand \$1.60

60p

TELEVISION

SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS

**ACCENT
ON VIDEO:**

**THE HITACHI
GP4 CAMERA**

**GII VIDEO
IN/OUT CIRCUIT
VHS TRACKING
MONITOR**

**VCR FAULT
CLINIC**




**PLUS
ALL THE
REGULAR
FEATURES**

PHD COMPONENTS
RADIO & TV COMPONENT DISTRIBUTORS
UNIT 7 CENTENARY ESTATE
JEFFRIES RD ENFIELD MIDDX
SHOP NOW OPEN TELEX 261295

ALL COMPONENTS OFFERED SUBJECT TO AVAILABILITY. WE RESERVE THE RIGHT TO SUBSTITUTE REPLACEMENTS SHOULD THE ORIGINAL PART BE OUT OF STOCK OR UNAVAILABLE!
PLEASE ADD 50p per parcel post and packing.

SEMICONDUCTORS								EHT MULTIPLIERS	
AA113	0.16	AU113	3.00	BF273	0.20	TBA396Q	2.00	TCE950 Doubler	2.00
AA116	0.16	AL103	3.00	BF274	0.25	TDA440	2.50	TCE950/1400 Tripler	5.04
AA117	0.16	AY102	3.00	BF336	0.50	SN76001N	1.50	TCE1400 (Piped System Only)	4.56
AA119	0.16	BC107	0.20	BF337	0.50	TBA520	2.00	TCE1500 Doubler	4.16
OA91	0.12	BC108	0.20	BF338	0.50	TBA120S	1.00	TCE1500 Tripler	4.64
OA95	0.12	BC109	0.20	BF355	0.80	TBA396	2.00	TCE1600 1/2 Wave	3.95
OA202	0.18	BC113	0.15	BF458	1.00	TCA270SQ	2.00	DECCA CS 1730/1B30 Doubler	4.23
BA100	0.18	BC114	0.15	BF459	1.00	TDA2030	8.00	DECCA CS 1910/2213 Tripler	6.67
BA102	0.10	BC115	0.20	BF473	0.50	TDA2140	6.00	DECCA 30 Series Tripler	6.01
BA130	0.15	BC116	0.20	BFX29	0.50	TDA2150	6.00	DECCA 80 Series Tripler	6.43
BA154	0.10	BC117	0.20	BFX84	0.50	TDA2160	6.00	DECCA 100 Series Tripler	6.68
BA155	0.20	BC118	0.20	BFX88	0.50	TDA1230	3.00	GEC Hybrid 2028 Tripler	6.43
BA164	0.16	BC119	0.50	BFY50	0.50	TDA3089	2.00	GEC 2110 Tripler Pre JAN77	7.21
BAX13	0.16	BC125	0.20	BFY52	0.50	TDA1054M	2.00	GEC 2110 Tripler Post JAN77	6.43
BAX16	0.08	BC126	0.20	BFY90	0.50	MC1349P	1.50	ITT CVC 5/8/9 Tripler	6.51
BY38	0.16	BC136	0.40	BF381	0.50	SAA661	0.60	ITT CVC 20/25/30	6.45
BY206	0.20	BC137	0.40	BF389	0.50	SAS560S	2.00	Philips 520 Tripler	6.51
IN4148	0.04	BC138	0.40	BF393	0.40	SAS570S	2.00	Philips 550 Tripler	6.42
BY126	0.20	BC139	0.40	BF399	0.30	SN7400N	0.90	Philips G9 Tripler	6.63
BY127	0.15	BC140	0.40	BF399	0.30	SN7413N	1.00	PYE 691/693/697 Tripler	6.68
BY133	0.22	BC142	0.40	BF399	0.50	SN74122N	1.00	RRI 823 Tripler	5.48
BY164	0.50	BC143	0.40	BF259	0.25	SN74141N	1.00	RRI 2179/823	6.68
SK52/08	1.00	BC147	0.10	BDX32	2.50	TBA395Q	1.80	TCE 3000/3500 Tripler	5.51
BY238	0.15	BC149	0.15	BU206	1.60	TBA950	4.00	TCE 4000 Tripler	8.00
BYX10	0.18	BC153	0.15	BU208/02	2.80	TCAB00	4.00	TCE 8000 Doubler	3.53
IN4001	0.10	BC154	0.15	BU326S	1.00	TCAB00Q	4.00	TCE 8500 Tripler	5.80
IN4002	0.10	BC157	0.15	BU406	2.00	TDA1180	3.00	TCE 9000 Tripler	7.28
IN4003	0.12	BC158	0.15	BU406D	1.70	TDA1190	3.30	TVK 76/13 Continental Sets	3.50
IN4004	0.12	BC159	0.15	BU407	1.70	TDA2002H	3.60	TVK 52 ITT Replacement	6.68
IN4005	0.12	BC160	0.40	BU407D	2.50	TDA2590Q	5.00	Korting 90% Tripler	6.50
IN4006	0.14	BC161	0.40	R2008B	2.50	TDA2600	5.00	Autovox Tripler	6.50
IN4007	0.16	BC170	0.15	R2010B	2.50	TDA2640	3.30	Rediffusion MK 1 Tripler	6.00
IN5407	0.33	BC171	0.15	R2540	3.00	TDA3950	3.00	RRI TV 25 Quadrupler	4.00
BR100	0.30	BC172	0.20	ME0402	0.20	TAA621 AX1	3.30	RRI T20	7.04
BR101	0.60	BC177	0.20	ME0412	0.20	TBA625X5	2.00		
BRV39	0.60	BC178	0.20	ME4003	0.15	TCAB30S	2.00		
TIC1160N	1.50	BC179	0.20	ME6002	0.20	TDA2020/A2	5.00	MULTISECTION CAPACITORS	3.72
BT119	2.00	BC182L	0.15	ME8001	0.20	TDA2020P	5.00	DECCA 400 400/350	
BT120	2.00	BC183L	0.15	MJE2955	1.50	TDA2030V	3.60	DECCA 80/100 400/350	4.00
BYX71/600	0.80	BC184L	0.15	MJE3005	1.50	TDA2030V	3.60	800/250	
2N444	1.50	BC184LC	0.15	MP8113	1.30	TDA2010/BD2	4.50	GEC 200 200 150 50/350	3.00
TV106/2	1.50	BC186	0.30	MPSU05	1.20	TDA2002V	5.00	GEC 100 2000/35	1.10
BYX88 2V7	0.10	BC187	0.30	MPSU55	1.20	TC9A40E	3.00	GEC Philips GB 600/250	2.10
BZY88 3V0	0.10	BC203	0.15	TIP2955	1.30			GEC Philips GB 600/250	2.50
BZY88 3V3	0.10	BC205	0.15	TIP3055	1.30			ITT K8 200 200 75 25/350	3.00
BZY88 3V6	0.10	BC206	0.15	TIS90M	0.30			ITT CVC 20 200/400	2.20
BZY88 3V9	0.10	BC207	0.15	2N2905A	0.50			Philips G11 470/250	1.90
BZY88 4V3	0.10	BC208	0.15	2N2905B	0.50			PYE 691 200 300/350	2.80
BZY88 4V7	0.10	BC209	0.15	2N3505	0.50			PYE 1000 1000/40	0.90
BZY88 5V1	0.10	BC209	0.15	2N3703	0.50			PYE 731 800/250	2.50
BZY88 5V6	0.10	BC212L	0.15	2N3075	0.20			RRI 2500-2500/3	1.30
BZY88 6V2	0.10	BC213L	0.15	2N3710	0.20			RRI 600/300	2.50
BZY88 6V8	0.10	BC214L	0.15	2N3055H	0.60			RRI 300 / 300/300	2.50
BZY88 7V5	0.10	BC225	0.40	TAA350	0.80			TCE 950 100 300 100 16	1.00
BZY88 8V2	0.10	BC237	0.15	TAA550	0.50			TCE 1400 150 100 100	
BZY88 9V1	0.10	BC238	0.15	TAA570	0.50			100 150	3.70
BZY88 10V	0.10	BC251A	0.15	TAA611	1.75			TCE 1500 150 150 100	2.10
BZY88 11V	0.10	BC301	0.40	TAA630S	2.50			TCE 3000/3500 175/400	
BZY88 12V	0.10	BC307	0.15	TAA630S	2.50			100 - 100/350	2.70
BZY88 13V	0.10	BC307	0.15	TAA630S	2.50			TCE 3000/3500 600/70	1.00
BZY88 15V	0.10	BC308	0.15	TAA630S	2.50			TCE 3000/3500 220/100	0.70
BZY88 18V	0.10	BC327	0.15	TAA630S	2.50			TCE 8000/8500 2500-2500/63	1.50
BZY88 20V	0.10	BC328	0.15	TAA630S	2.50			TCE 8000/8500 700/200	1.00
BZY88 22V	0.10	BC337	0.15	TAA630S	2.50			TCE 8000/8500 400/350	1.00
BZY88 27V	0.10	BC338	0.15	TAA630S	2.50			TCE 9000 400/400	3.00
BZY88 33V	0.10	BC547	0.15	TAA630S	2.50			TCE 9500 220/400	2.20
BZX61 7V5	0.20	BC141-10	0.80	TAA630S	2.50				
BZX61 8V2	0.20	BD115	0.50	TAA630S	2.50				
BZX61 9V1	0.20	BD124	1.80	TAA630S	2.50				
BZX61 10V	0.20	BD131	0.70	TAA630S	2.50				
BZX61 11V	0.20	BD132	0.60	TAA630S	2.50				
BZX61 12V	0.20	BD133	0.70	TAA630S	2.50				
BZX61 13V	0.20	BD134	0.70	TAA630S	2.50				
BZX61 15V	0.20	BD144	2.50	TAA630S	2.50				
BZX61 16V	0.20	BD159	0.80	TAA630S	2.50				
BZX61 18V	0.20	BD238	0.50	TAA630S	2.50				
BZX61 20V	0.20	BD380	0.70	TAA630S	2.50				
BZX61 22V	0.20	BD441	0.70	TAA630S	2.50				
BZX61 24V	0.20	BD537	0.70	TAA630S	2.50				
BZX61 27V	0.20	BD538	0.70	TAA630S	2.50				
BZX61 30V	0.20	BD507	0.70	TAA630S	2.50				
BZX61 33V	0.20	BD508	0.70	TAA630S	2.50				
BZX61 36V	0.20	16181	1.20	TAA630S	2.50				
BZX61 39V	0.20	16182	1.20	TAA630S	2.50				
BZX61 47V	0.20	BD709	1.00	TAA630S	2.50				
BZX61 72V	0.20	BD710	1.00	TAA630S	2.50				
AC107	0.35	BD442	0.70	TAA630S	2.50				
AC127	0.50	BD379	0.50	TAA630S	2.50				
AC127/01	0.60	BF115	0.60	TAA630S	2.50				
AC128	0.60	BF118	0.60	TAA630S	2.50				
AC128/01	0.60	BF152	0.40	TAA630S	2.50				
AC141	0.50	BF154	0.20	TAA630S	2.50				
AC141K	0.60	BF157	0.70	TAA630S	2.50				
AC142	0.40	BF158	0.70	TAA630S	2.50				
AC142K	0.60	BF160	0.80	TAA630S	2.50				
AC176	0.60	BF163	0.60	TAA630S	2.50				
AC176/01	0.60	BF167	0.50	TAA630S	2.50				
AC186	0.40	BF173	0.50	TAA630S	2.50				
AC187	0.40	BF177	0.50	TAA630S	2.50				
AC187K	0.60	BF179	0.50	TAA630S	2.50				
AC188	0.40	BF180	0.50	TAA630S	2.50				
AC188K	0.60	BF181	0.60	TAA630S	2.50				
AD140	1.50	BF182	0.50	TAA630S	2.50				
AD142	1.50	BF183	1.50	TAA630S	2.50				
AD143	1.50	BF184	0.50	TAA630S	2.50				
AD145	1.50	BF185	0.50	TAA630S	2.50				
AD149	1.00	BF194	0.20	TAA630S	2.50				
AD161/2	1.50	BF195	0.20	TAA630S	2.50				
AD162	0.70	BF196	0.20	TAA630S	2.50				
AD262	1.50	BF197	0.20	TAA630S	2.50				
AF121	0.60	BF198	0.15	TAA630S	2.50				
AF124	0.60	BF199	0.15	TAA630S	2.50				
AF125	0.60	BF200	0.15	TAA630S	2.50				
AF126	0.60	BF201	0.15	TAA630S	2.50				
AF127	0.60	BF240	0.45	TAA630S	2.50				
AF139	0.60	BF241	0.45	TAA630S	2.50				
AF239	1.00	BF256LC	0.50	TAA630S	2.50				
AL102	3.00	BF257	0.50	TAA630S	2.50				
AU107	3.00	BF258	0.50	TAA630S	2.50				
AU110	3.00	BF271	0.60	TAA630S	2.50				
				BF273	0.20	TBA396Q	2.00		
				BF274	0.25	TDA440	2.50		
				BF336	0.50	SN76001N	1.50		
				BF337	0.50	TBA520	2.00		
				BF338	0.50	TBA120S	1.00		
				BF355	0.80	TBA396	2.00		
				BF458	1.00	TCA270SQ	2.00		
				BF459	1.00	TDA2030	8.00		
				BF473	0.50	TDA2140	6.00		
				BFX29	0.50	TDA2150	6.00		
				BFX84	0.50	TDA2160	6.00		
				BFX88	0.50	TDA1230	3.00		
				BFY50	0.50	TDA3089	2.00		
				BFY52	0.50	TDA1054M	2.00		
				BFY90	0.50	MC1349P	1.50		
				BF381	0.50	SAA661	0.60		
				BF389	0.50	SAS560S	2.00		
				BF393	0.40	SAS570S	2.00		

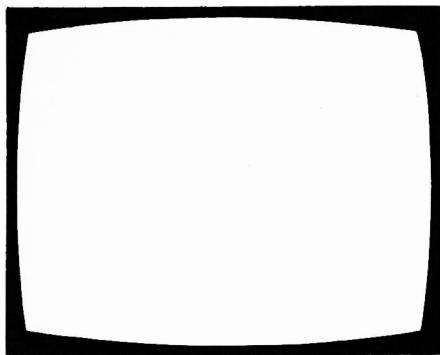

TELEVISION

January
1981

Vol. 31, No. 3
Issue 363

COPYRIGHT

©IPC Magazines Limited, 1981. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

SUBSCRIPTIONS

An annual subscription costs £10 in the UK, £11 overseas (\$24.20 Canada or USA). Send orders with payment to IPC Services, Oakfield House, Perymount Road, Haywards Heath, Sussex.

BINDERS AND INDEXES

Binders (£4.40) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 75p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

- 121 **Leader**
- 122 **Teletopics**
News, comment and developments.
- 124 **Teletext Decoder Corrections**
- 127 **The Hitachi GP4 Colour Camera**
by David K. Matthewson, B.Sc., Ph.D.
Colour video cameras are becoming remarkably cheap. The Hitachi GP4 has been selected as an interesting example. Its features are described, its use by both an experienced operator and a novice reported upon, and a look is taken at the electronics employed.
- 130 **VCR Clinic**
by Steve Beeching, T.Eng.(C.E.I.)
More knowhow on what can go wrong with VCRs, plus comments on some recent introductions on the market.
- 132 **Long-distance Television**
by Roger Bunney
Reports on DX reception and conditions, and news from abroad. Of particular interest recently have been the extraordinary F2 conditions, giving reception over vast distances.
- 135 **Getting Organised for Field Servicing**
by Harold B. Berkley, T.Eng.(C.E.I.)
A lot of time and effort can be wasted in field servicing unless careful attention is paid to selecting and arranging a kit of tools and spares for maximum efficiency.
- 136 **The Exorcism of Fred**
by Les Lawry-Johns
Well it is Christmas time, just about. So what's wrong with a ghost story? In addition to ghosts there've been problems with a Marantz stereo cassette deck, some TV sets, and those who won't keep their electronics' problems out of more important business (card games).
- 138 **VHS Tracking Meter**
by L. Sadarangani
It's simple enough to make this meter, which can give improved performance and other benefits to users of VHS machines.
- 139 **Letters**
- 140 **Aerial Phaser Unit**
by Roger Bunney
The idea of clearing an interfering signal from a section of the band so as to be able to receive another signal at the same frequency may seem improbable, yet that's what this unit does.
- 142 **Practical TV Servicing:
Making the Most of your Meter**
by S. Simon
Your multimeter can tell you almost everything – provided you know how to use it and interpret its readings. Simon says how, especially when testing transistors.
- 144 **Video in/out Conversion for the G11**
by A. R. Rumbelow
The Philips G11 colour chassis may not initially seem the ideal candidate for this treatment. It can be done without too much difficulty however, and being a reliable chassis it's worth adapting.
- 145 **Next Month in Television**
- 146 **Video Camera, Part 4**
by Malcolm Burrell
Constructional, setting up and component details, plus the last two boards designed for the project.
- 151 **Small-screen Monitor, Part 2**
by Luke Theodossiou
Component details, layout and print pattern for the board, and notes on construction.
- 152 **Readers' PCB Service**
- 154 **Service Bureau**
- 156 **Test Case 217**

OUR NEXT ISSUE DATED FEBRUARY WILL
BE PUBLISHED ON JANUARY 21

CAMPBELL ELECTRONICS Limited

Unit 5/6, Heath Hill Estate,
Dawley, Telford,
Shropshire. TF4 2RH
Tel. Telford (0952) 502422/502447

Telegrams. CAMELEC
Telex. CHAMCOM 35191

DISTRIBUTORS OF SPECIALIST SPARES TO RADIO & TELEVISION SERVICE DEPTS; NATIONWIDE


Your source to better components

ITEMS SHOWN WITH * INDICATES THESE ARE SOLD IN PACKS OF 5

TRANSISTORS																							
*Increase sold in packs of 5					*Increase sold in packs of 5																		
AC127	54	AF239	1.00	BC119	49	BC173	19*	BC547	14*	BD1508	1.29	BF123	29	BF222	29	BF450	52	BU111Y	3.18	R1038	2.72	TIP126	78
AC128	58	AF279S	1.15	BC125	20*	BC178	20*	BC548	14*	BD150C	1.09	BF154	25*	BF224	35*	BF458	52	BU126	2.10	R1039	2.74	TIP127	1.49
AC141	68	AL102	2.90	BC126	20*	BC179	28	BC549	19*	BD163	97	BF156	55	BF240	29*	BF459	62	BU204	1.79	R2008	2.89	TIP205S	85
AC142	68	AL113	2.90	BC135	23*	BC182L	14*	BCX31	30	BD166	61	BF158	39*	BF241	29*	BF459	62	BU205	2.53	R2009	2.52	TIP205S	85
AC153	57	AU103	2.80	BC137	20*	BC182L	14*	BCX32	29*	BD181	1.03	BF160	59	BF255	34*	BF459	62	BU206	2.76	R2010	2.89	TIP205S	85
AC176	59	AU106	3.58	BC137	20*	BC182L	14*	BCX33	29*	BD182	80	BF167	48	BF256	32	BF459	62	BU208	2.88	R2029	2.45	TIP205S	85
AC187	68	AU107	2.74	BC139	39*	BC186	38	BCX34	35	BD183	80	BF173	50	BF257	49	BF459	62	BU208/02	2.98	R2030	2.55	TIP205S	85
AC188	68	AU108	2.74	BC140	39	BC187	33*	BCX35	35	BD187	80	BF177	60	BF258	49	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AD149	1.64	AU110	2.90	BC141	38	BC212L	15*	BCY70	25*	BD201	78	BF178	35*	BF259	49	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AD161	75	AU111	2.90	BC142	39	BC213L	16*	BCY71	34*	BD222	46	BF179	49	BF262	64	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AD162	1.03	AU112	2.90	BC143	39	BC214L	16*	BCY72	25*	BD225	57	BF180	49	BF263	68	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AF115	1.04	AU113	3.05	BC147	15*	BC237	19*	BD115	81	BD232	83	BF181	59	BF271	49	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AF116	1.04	AU110	1.71	BC148	11*	BC238	17*	BD116	96	BD233	83	BF182	50	BF273	20*	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AF117	1.04	BC107	18*	BC149	15*	BC239	15*	BD131	60	BD234	80	BF183	50	BF274	27*	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AF118	1.38	BC108	18*	BC150	15*	BC307	19*	BD132	72	BD237	76	BF184	49	BF324	57	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AF125	59	BC109	18*	BC151	20*	BC327	22*	BD133	69	BD238	67	BF185	49	BF336	49	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AF126	61	BC113	20*	BC152	16*	BC337	17*	BD135	58	BD245	103	BF194	19*	BF337	49	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AF127	1.04	BC114	18*	BC153	15*	BC338	17*	BD136	58	BD247	75	BF195	15*	BF338	49	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AF139	88	BC115	23*	BC154	20*	BC341C	29	BD140	58	BD509	77	BF198	19*	BF355	80	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AF178	2.04	BC116	20*	BC155	16*	BC41E	35	BD144	2.49	BD510	65	BF197	19*	BF362	62	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AF180	2.12	BC117	19*	BC156	16*	BC462	75	BD150A	94	BDX32	2.86	BF198	28*	BF363	62	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
AF181	2.14	BC118	33*	BC171	17*	BC463	76	BD150A	94	BDX32	2.86	BF199	25*	BF422	62	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85
				BC172	19*	BC463	76	BD150A	94	BDX32	2.86	BF200	38	BF423	62	BF459	62	BU209	2.88	R2030	2.55	TIP205S	85

THYRISTORS, SILICON SWITCHES, DIACS

BFT43	51	BT109	1.58	BT110	1.70	BT119	4.43	BT120	4.45	BT122	8.88	BT106	1.31	TIC46	54*
BR100	29*	BR101	42*	BR102	42*	BR103	42*	BR104	42*	BR105	42*	BR106	42*	BR107	42*
BR108	42*	BR109	42*	BR110	42*	BR111	42*	BR112	42*	BR113	42*	BR114	42*	BR115	42*
BR116	42*	BR117	42*	BR118	42*	BR119	42*	BR120	42*	BR121	42*	BR122	42*	BR123	42*
BR124	42*	BR125	42*	BR126	42*	BR127	42*	BR128	42*	BR129	42*	BR130	42*	BR131	42*
BR132	42*	BR133	42*	BR134	42*	BR135	42*	BR136	42*	BR137	42*	BR138	42*	BR139	42*
BR140	42*	BR141	42*	BR142	42*	BR143	42*	BR144	42*	BR145	42*	BR146	42*	BR147	42*
BR148	42*	BR149	42*	BR150	42*	BR151	42*	BR152	42*	BR153	42*	BR154	42*	BR155	42*
BR156	42*	BR157	42*	BR158	42*	BR159	42*	BR160	42*	BR161	42*	BR162	42*	BR163	42*
BR164	42*	BR165	42*	BR166	42*	BR167	42*	BR168	42*	BR169	42*	BR170	42*	BR171	42*
BR172	42*	BR173	42*	BR174	42*	BR175	42*	BR176	42*	BR177	42*	BR178	42*	BR179	42*
BR180	42*	BR181	42*	BR182	42*	BR183	42*	BR184	42*	BR185	42*	BR186	42*	BR187	42*
BR188	42*	BR189	42*	BR190	42*	BR191	42*	BR192	42*	BR193	42*	BR194	42*	BR195	42*
BR196	42*	BR197	42*	BR198	42*	BR199	42*	BR200	42*	BR201	42*	BR202	42*	BR203	42*
BR204	42*	BR205	42*	BR206	42*	BR207	42*	BR208	42*	BR209	42*	BR210	42*	BR211	42*
BR212	42*	BR213	42*	BR214	42*	BR215	42*	BR216	42*	BR217	42*	BR218	42*	BR219	42*
BR220	42*	BR221	42*	BR222	42*	BR223	42*	BR224	42*	BR225	42*	BR226	42*	BR227	42*
BR228	42*	BR229	42*	BR230	42*	BR231	42*	BR232	42*	BR233	42*	BR234	42*	BR235	42*
BR236	42*	BR237	42*	BR238	42*	BR239	42*	BR240	42*	BR241	42*	BR242	42*	BR243	42*
BR244	42*	BR245	42*	BR246	42*	BR247	42*	BR248	42*	BR249	42*	BR250	42*	BR251	42*
BR252	42*	BR253	42*	BR254	42*	BR255	42*	BR256	42*	BR257	42*	BR258	42*	BR259	42*
BR260	42*	BR261	42*	BR262	42*	BR263	42*	BR264	42*	BR265	42*	BR266	42*	BR267	42*
BR268	42*	BR269	42*	BR270	42*	BR271	42*	BR272	42*	BR273	42*	BR274	42*	BR275	42*
BR276	42*	BR277	42*	BR278	42*	BR279	42*	BR280	42*	BR281	42*	BR282	42*	BR283	42*
BR284	42*	BR285	42*	BR286	42*	BR287	42*	BR288	42*	BR289	42*	BR290	42*	BR291	42*
BR292	42*	BR293	42*	BR294	42*	BR295	42*	BR296	42*	BR297	42*	BR298	42*	BR299	42*
BR300	42*	BR301	42*	BR302	42*	BR303	42*	BR304	42*	BR305	42*	BR306	42*	BR307	42*
BR308	42*	BR309	42*	BR310	42*	BR311	42*	BR312	42*	BR313	42*	BR314	42*	BR315	42*
BR316	42*	BR317	42*	BR318	42*	BR319	42*	BR320	42*	BR321	42*	BR322	42*	BR323	42*
BR324	42*	BR325	42*	BR326	42*	BR327	42*	BR328	42*	BR329	42*	BR330	42*	BR331	42*
BR332	42*	BR333	42*	BR334	42*	BR335	42*	BR336	42*	BR337	42*	BR338	42*	BR339	42*
BR340	42*	BR341	42*	BR342	42*	BR343	42*	BR344	42*	BR345	42*	BR346	42*	BR347	42*
BR348	42*	BR349	42*	BR350	42*	BR351	42*	BR352	42*	BR353	42*	BR354	42*	BR355	42*
BR356	42*	BR357	42*	BR358	42*	BR359	42*	BR360	42*	BR361	42*	BR362	42*	BR363	42*
BR364	42*	BR365	42*	BR366	42*	BR367	42*	BR368	42*	BR369	42*	BR370	42*	BR371	42*
BR372	42*	BR373	42*	BR374	42*	BR375	42*	BR376	42*	BR377	42*	BR378	42*	BR379	42*
BR380	42*	BR381	42*	BR382	42*	BR383	42*	BR384	42*	BR385	42*	BR386	42*	BR387	42*
BR388	42*	BR389	42*	BR390	42*	BR391	42*	BR392	42*	BR393	42*	BR394	42*	BR395	42*
BR396	42*	BR397	42*	BR398	42*	BR399	42*	BR400	42*	BR401	42*	BR402	42*	BR403	42*
BR404	42*	BR405	42*	BR406	42*	BR407	42*	BR408	42*	BR409	42*	BR410	42*	BR411	42*
BR412	42*	BR413	42*	BR414	42*	BR415	42*	BR416	42*	BR417	42*	BR418	42*	BR419	42*
BR420	42*	BR421	42*	BR422	42*	BR423	42*	BR424	42*	BR425	42*	BR426	42*	BR427	42*
BR428	42*	BR429	42*	BR430	42*	BR431	42*	BR432	42*	BR433	42*	BR434	42*	BR435	42*
BR436	42*	BR437	42*	BR438	42*	BR439	42*	BR440	42*	BR441	42*	BR442	42*	BR443	42*
BR444	42*	BR445	42*	BR446	42*	BR447	42*	BR448	42*	BR449	42*	BR450	42*	BR451	42*
BR452	42*	BR453	42*	BR454	42*	BR455	42*	BR456	42*	BR457	42*	BR458	42*	BR459	42*
BR460	42*	BR461	42*	BR462	42*	BR463	42*	BR464	42*	BR465	42*	BR466	42*	BR467	42*
BR468	42*	BR469	42*	BR470	42*	BR471	42*	BR472	42*	BR473	42*	BR474	42*	BR475	42*
BR476	42*	BR477	42*	BR478	42*	BR479	42*	BR480	42*	BR481	42*	BR482	42*	BR483	42*
BR484	42*	BR485	42*	BR486	42*	BR487	42*	BR488	42*	BR489	42*	BR490	42*	BR491	42*
BR492	42*	BR493	42*	BR494	42*	BR495	42*	BR496	42*	BR497	42*	BR498	42*	BR499	42*
BR500	42*	BR501	42*	BR502	42*	BR503	42*	BR504	42*	BR505	42*	BR506	42*	BR507	42*

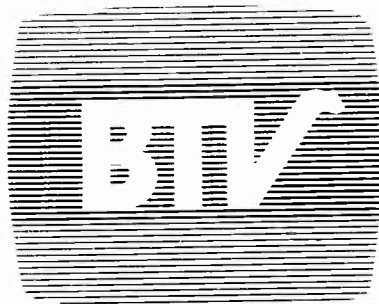

Can you afford NOT to switch to the fantastic BRIARWOOD TV trade offer?

**100's of colour TVs
100% complete - as they arrive - in batches of ten
ONLY £13.00 per set**

**COLOUR TVs WITH TESTED TUBES
GUARANTEED 100% COMPLETE**

	IN 10's	In 20's	GOOD WORKING in 10's
PYE 691	£18.00 each	£15.00	£33.00
PYE 697	£21.00 each	£18.00	£38.00
GEC 2040	£18.00 each	£15.00	£33.00
BUSH 184	£23.00 each	£20.00	£38.00
THORN 3000 19"	£28.00 each	£25.00	£43.00
THORN 3000 25"	£23.00 each	£20.00	£38.00
THORN 3500 26"	£28.50 each	£25.00	£43.00
DECCA BFD - 30's	£28.00 each	£25.00	£43.00
KORTING	£25.00 each	£22.00	£45.00
TELPRO	£23.00 each	£20.00	£38.00

Please note there is 15% VAT on all the above prices.

Foreign makes of TV's i.e. Skantic/Luxors, ASA's, Mitsubishi, Teleton, Grundigs, Saba's etc., in batches of 10's @ £40.00 each


Later types of sets i.e. G8, Thorn 3500 Varicap, ITT/KB, Thorn 8500, GEC 2100 etc., in batches of 10's @ £50.00 each.

OPENING TIMES MON-FRI 9.00-12.00/1.00-5.45 (CLOSE 4.30 SAT)

**CASH & CARRY SPECIAL SERVICE TO THE TRADE
OR ASK ABOUT SPECIAL DELIVERIES ON LARGE QUANTITIES**

BRIARWOOD TELEVISION
Briarwood House, Preston Street
BRADFORD, West Yorkshire ND7 1LU
Tel: (0274) 306018

BRIARWOOD TELEVISION LIMITED

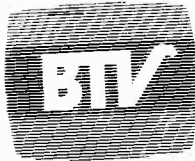

BRIARWOOD

QUALITY SELECTED EX EQUIPMENT SPARES

MISC S/Output Trans. £1
+ VAT + P&P
F/Output Trans.
£1.25 + BAT + £1 P&P
Scancoils £1.50 + VAT
£1 PIP. Other spares
available, please write or
phone for details.

MONO TUNERS
6 button integrated all at
£4.00
U.H.F. P/Button D/S
£3.50, U.H.F. P/Button
S/S **£4.00**, Rotary **£3.00** +
£1 P&P

MONO TUBES
(tested)
19" Rimguard £3.00
23" Rimguard £4.00
20" Rimguard £5.00
24" Rimguard £6.00
- £5.00 P & P

MONO LOPTS
All D/Standard Lopts at
£4.00 + £1 P&P.
All S/Standard at **£4.00** +
£1 P&P.

MONO PANELS
i.e. Philips, Bush, etc.
£3.50 + £1 P&P.
Quotations for complete
S/hand chassis if
required. (Diff. prices)

PLEASE ADD 15% V.A.T.
TO ALL ITEMS AND
OVERSEAS AT COST.
CASH WITH ALL ORDERS.

VALVES (MONO & COLOUR)

PCL82	0.10	30C1	0.10	PCC189	0.10	EF183	0.10	PL504	0.25	ECL80	0.10
PCL83	0.25	30C17	0.10	30C15	0.10	EF184	0.10	6/30L2	0.10	PL509	1.00
PCL84	0.10	PCF802	0.10	30C18	0.25	6BW7	0.10	30PL1	0.25	PY500	1.00
PCL85	0.10	PCF805	0.25	PC97	0.20	EH90	0.10	30PL13/4	0.10	GY501	1.00
PCL86	0.10	PCF806	0.10	PC900	0.10	DY802	0.10	30FL1/2	0.25	PL508	0.50
PFL200	0.10	PCF808	0.25	EF80	0.10	PY800/1	0.10	ECC82	0.10	PCF200	0.50
PCF801	0.10	PCF80	0.10	EF85	0.10	PL36	0.25	ECC81	0.10	EY51	0.15

Please note there is 25p Postage and Packing per order.

**WE DO NOT SELL
RUBBISH AT
BRIARWOOD TV**

D/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	EHT	REG	CON	S/OUPUT	POWER	L/TB	F/TB
Bush/Murphy	5.00	5.00	6.50	—	—	5.00	1.50	5.00	—	—
GEC/Sobell	5.00	5.50	—	—	—	5.00	—	—	—	—
Philips	5.00	7.00	—	—	—	5.00	—	—	—	—
Decaa	5.00	9.00	9.00	—	—	5.00	2.00 (19" only)	6.00	—	7.50
Thorn 2000	5.00	5.00	5.00	6.50	6.50	7.00	—	—	—	5.00
Pye	7.00	6.00	7.00	—	—	5.00	—	—	—	5.00
Baird	6.50	8.50	7.00	—	—	5.00	—	6.50	10.00	5.00
								—	—	5.00
								—	—	5.00

Postage & Packing £1.25

S/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	VIDEO	CON	POWER	L/TB	F/TB
Bush 184	9.50	—	12.00	—	6.00	6.00	12.00	—
GEC Hybrid	6.00	6.50	9.00	—	5.00	—	—	12.00
Philips G6 S/S	9.50	—	10.00	—	5.00	—	—	6.00
Thorn 3000	6.00	6.00	6.00	—	5.00	20.00	20.00	6.00
Pye 691/693	6.00	6.00	8.00	—	5.00	—	15.00	5.00
Thorn 3500	6.00	6.00	6.00	6.50	12.00	20.00	20.50	6.00

Kotring and other foreign panels available on request.

Postage & Packing £1.25

COLOUR TUBES

17"	£15.00
18"	£15.00
19"	£15.00
19" A49/192	£18.00
20"	£18.00
22"	£20.00
25"	£15.00
26"	£22.00

Plus P&P **£6.00**
New rebuilt tubes
available on request.

COLOUR TUNERS

Bush	£5.00
GEC	£5.00
Philips G6 S/S	£5.00
Pye 691	£5.00
Thorn 3000	£5.00

Some new tuners in
stock, can supply on
request. Many Foreign
Tuners also available on
request. Plus P&P £1.

COLOUR LOPTS

Most Lopts available
from £5.00. Both
British & Foreign
makers. Please ring
or write.
P&P per Lopt £1.00

MISC.


S/Output transformer
from £1.50.
F/Output from £1.25.
Scancoils from £5.00.
P&P £1.00
Other spares available on
request.

THORN 1500 TUNERS
NEW SPECIAL OFFER
AT £8.00

Postage & Packing £1.00

NEW PRODUCTS!

£2.50 each
£1.00 p&p

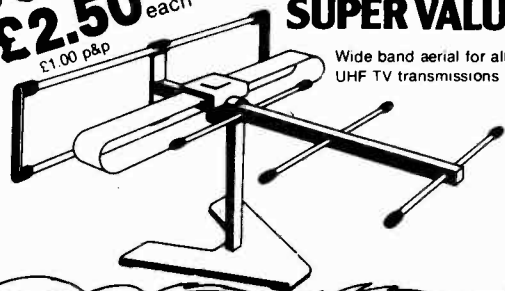


Wide band aerial for all
UHF TV transmissions

SUPER VALUE - SUPER QUALITY

£5.95 each
£1.75 p&p

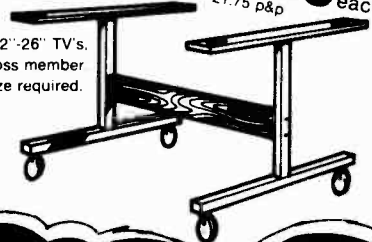Fits 22"-26" TV's.
wood finished cross member
State size required.



TV scores with quality

WHY NOT TRY OUR EXPRESS MAIL ORDER ON ANY OF THE ITEMS LISTED

NEW SPARE SELECTION

TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £
AC107	0.24	AF170	0.92	BC173	0.12	BD132	0.36	BF199	0.14	OC25	1.00	2N2219	0.40
AC113	0.22	AF172	1.00	BC177	0.12	BD133	0.37	BF200	0.28	OC26	1.00	2N2646	0.40
AC115	0.23	AF178	1.00	BC178	0.12	BD135	0.30	BF216	0.12	OC28	1.30	2N2926	0.15
AC117	0.30	AF180	1.00	BC178A	0.12	BD136	0.30	BF217	0.12	OC35	1.00	2N3053	0.21
AC125	0.23	AF181	1.00	BC179	0.12	BD137	0.30	BF218	0.12	OC36	0.90	2N3054	0.60
AC126	0.23	AF186	0.90	BC182L	0.09	BD138	0.31	BF219	0.12	OC38	0.90	2N3055	0.60
AC127	0.22	AF239	0.46	BC183L	0.09	BD139	0.40	BF220	0.12	OC42	0.45	2N3442	1.00
AC128	0.22	AU113	1.40	BC183LA	0.10	BD140	0.37	BF221	0.21	OC44	0.60	2N3702	0.15
AC131	0.13	BA130	0.08	BC183LB	0.10	BD144	1.39	BF222	0.12	OC45	0.50	2N3703	0.12
AC141	0.24	BA145	0.14	BC184L	0.09	BD145	0.50	BF224	0.18	OC46	0.39	2N3704	0.18
AC142	0.24	BA148	0.21	BC186	0.21	BD177	0.50	BF256	0.37	OC70	0.39	2N3705	0.18
AC141K	0.31	BA155	0.08	BC187	0.21	BD178	0.50	BF258	0.30	OC71	0.39	2N3706	0.14
AC142K	0.31	BAX13	0.05	BC209	0.11	BD203	0.40	BF259	0.30	OC72	0.39	2N3707	0.14
AC151	0.21	BAX16	0.08	BC212	0.09	BD204	0.70	BF260	0.25	OC74	0.39	2N3708	0.14
AC165	0.21	BC107	0.11	BC212L	0.09	BD222	0.73	BF262	0.28	OC75	0.39	2N3772	2.00
AC166	0.21	BC108	0.11	BC213L	0.09	BD233	0.36	BF263	0.25	OC76	0.39	2N3773	2.50
AC168	0.22	BC109	0.11	BC214L	0.09	BD234	0.34	BF271	0.27	OC77	0.50	2N3819	0.30
AC176	0.22	BC113	0.11	BC237	0.09	BD237	0.44	BF272	0.27	OC78	0.23		
AC176K	0.28	BC114	0.11	BC238	0.09	BD238	0.44	BF273	0.16	OC81	0.26		
AC178	0.23	BC115	0.11	BC240	0.31	BDX22	0.73	BF336	0.30	OC810	0.14		
AC186	0.26	BC116	0.11	BC249	0.35	BDX32	1.98	BF337	0.29	OC82	0.26	DY87	0.52
AC187	0.23	BC117	0.12	BC251	0.22	BDY18	0.80	BF338	0.29	OC820	0.20	DY802	0.64
AC188	0.23	BC119	0.24	BC257	0.20	BDY60	0.80	BF479	—	OC83	0.30	ECC82	0.52
AC187K	0.30	BC125	0.15	BC262	0.18	BF115	0.30	BFT	0.27	OC84	0.30	EF80	0.50
AC188K	0.30	BC126	0.15	BC263B	0.20	BF121	0.29	BFT	0.27	OC85	0.28	EF183	0.70
AD130	0.58	BC136	0.15	BC267	0.19	BF154	0.12	BFX84	0.27	OC123	0.25	EF184	0.70
AD140	0.68	BC137	0.17	BC281	0.24	BF158	0.19	BFX85	0.27	OC169	1.20	EH90	0.75
AD142	0.80	BC137	0.23	BC300	0.27	BF159	0.24	BFX	0.30	OC170	1.20	PC86	0.85
AD143	0.70	BC139	0.23	BC301	0.27	BF160	0.23	BFY37	0.22	OA91	0.07	PC88	0.85
AD145	0.70	BC140	0.24	BC302	0.30	BF163	0.30	BFY50	0.21	BRC4443	0.65	PCC89	0.65
AD149	0.64	BC141	0.27	BC303	0.27	BF164	0.30	BFY51	0.21	R2008B	1.50	PCC189	0.70
AD161	0.42	BC142	0.27	BC307	0.11	BF167	0.30	BFY52	0.21	R2009	1.30	PCF80	0.80
AD162	0.42	BC143	0.27	BC307A	0.11	BF173	0.30	BFY53	0.27	R2010B	1.50	PCF86	0.72
AD161		BC147	0.10	BC308A	0.12	BF177	0.26	BFY55	0.33	R2265	1.50	PCF801	0.70
AD162	1.00	BC148	0.10	BC309	0.14	BF178	0.24	BFX	—	R2305	0.38	PCF802	0.78
AF106	0.42	BC149	0.10	BC337	0.12	BF179	0.28	BHA0002	1.90	R2305	0.38	PCL82	0.70
AF114	0.37	BC153	0.12	BC338	0.15	BF180	0.30	BSX20	0.23	BD222	0.37	PCL84	0.75
AF115	0.37	BC154	0.12	BC487	0.20	BF181	0.34	BSX76	0.23	R2540	2.50	PCL86	0.81
AF116	0.37	BC157	0.12	BC547	0.10	BF182	0.30	BSY84	0.36	S2802	—	PCL805	0.82
AF117	0.40	BC158	0.12	BC548	0.11	BF183	0.29	BU105	1.00	SCR957	0.65	PLF200	1.00
AF118	0.45	BC159	0.12	BC549	0.11	BF184	0.27	BU105 02	1.50	TIP31A	0.38	PL36	0.90
AF121	0.37	BC160	0.26	BC557	0.12	BF185	0.29	BU105 04	2.00	TIP32A	0.36	PL84	0.74
AF124	0.83	BC161	0.26	BCX33	0.10	BF186	0.32	BU126	1.40	TIP32A	0.36	PL504	1.15
AF125	0.30	BC167	0.11	BD112	0.39	BF192	—	BU205	1.20	TIP3055	0.53	PL508	1.50
AF126	0.30	BC168	0.11	BD113	0.65	BF194	0.15	BU206	1.60	TIP31B	0.39	PL509	2.45
AF127	0.30	BC169	0.11	BD115	0.32	BF195	0.13	BU208	1.60	TIS90	0.23	PL802	2.55
AF139	0.40	BC171	0.10	BD116	0.47	BF196	0.13	OC22	1.10	TIS91	0.25	Py88	0.75
AF150	0.27	BC171A	0.10	BD124	1.30	BF197	0.13	OC23	1.30	TV106	1.09	PY500A	1.60
AF151	0.30	BC172	0.10	BD131	0.36	BF198	0.12	OC24	1.30	MJE340	0.50	PY81.800	0.65
										MJE520	0.45		

E.H.T. Trays

TYPE	PRICE £
Pye 691 693 4.50	
Pye 715/731/735 5.50	
Pye 737 5.40	
Decca (Large Screen) CS2030/2232/2630/2632/2230/2233/2631 5.00	
Decca 80 5.30	
Decca 100 5.30	
Philips G8 5.30	
Philips G9 5.50	
Philips 550 5.30	
GEC C2110 5.50	
GEC Hybrid CTV 5.10	
Thorn 3000/3500 5.00	
Thorn 800 2.42	
Thorn 8500 4.75	
Thorn 9000 5.50	
GEC TVM25 2.50	
ITT KB CVC 5/7/8/9 5.10	
ITT KB CVC 20/25 5.50	
Bush CTB25 MK3 8.00	
Quadrupler Bush X179 4.50	
RRi (RBM) A823 5.00	
Bang & Olufsen 4/5000 Grundig 5010/5011/5012/6011/6012/7200/2052/2210/2252R Tandberg (radionette) 6.60	
Autovox Grundig 3000/3010 Saba 2705/3715	
Telefunken 709/710/717/2000 6.80	
Korting 6.80	

VALVES

TYPE	PRICE £
DY87 0.52	
DY802 0.64	
ECC82 0.52	
EF80 0.50	
EF183 0.70	
EF184 0.70	
EH90 0.75	
PC86 0.85	
PC88 0.85	
PCC89 0.65	
PCC189 0.70	
PCF80 0.80	
PCF86 0.72	
PCF801 0.70	
PCF802 0.78	
PCL82 0.70	
PCL84 0.75	
PCL86 0.81	
PCL805 0.82	
PLF200 1.00	
PL36 0.90	
PL84 0.74	
PL504 1.15	
PL508 1.50	
PL509 2.45	
PL802 2.55	
Py88 0.75	
PY500A 1.60	
PY81.800 0.65	

All transistors, IC's offered are new and branded. Manufactured by Mullard, I.T.T., Texas, Motorola etc. Please add 15% VAT to all items and overseas at cost. P & P U.K. 50p per order, overseas allow for package and postage. Cash with all orders. All prices subject to alteration without notice.

MAIL ORDER TV BARGAINS

PYE 691	22" @ £55.00
PYE 691	26" @ £55.00
PYE 697	22" @ £65.00
PYE 697	26" @ £65.00
BUSH 184	19" @ £70.00
BUSH 184	22" @ £70.00
BUSH 184	26" @ £70.00
GEC 2040	19" @ £55.00
GEC2040	22" @ £55.00
GEC 2040	25" @ £55.00
GEC 2040	26" @ £65.00
KORTING	22" @ £70.00
KORTING	26" @ £80.00
THORN 3000	19" @ £70.00
THORN 3000	25" @ £60.00
Good working mono's Pye, GEC, Bush etc.	
20" & 24" S/S	£15.00
20" & 24" D/S	£14.00
19" & 23" D/S P/Button	£12.00
19" & 23" D/S Rotary	£ 8.00

Cheques, P.O. or Cash with orders Please. Please note there is 15% VAT on all the above prices. Plus £10.00 p & p for colour TV, £5.00 for mono. ENGLAND, WALES and SCOTLAND. Inland N & S IRELAND £15.00 for colour. £7.00 for mono.

TYPE PRICE £

IC's

BTT6018	1.00
CA3605	1.20
MC7/c	
MC14016	0.50
SN76003N	1.40
SN76013N	1.20
SN76013ND	1.00
SN76023N	1.20
SN76023ND	1.00
SN76110N	1.00
SN76226DN	1.50
SN76227N	1.20
SN76532N	1.30
SN76550N	0.30
SN76666N	0.70
TAA570	1.38
TBA120AS	1.00
TBA120S	0.75
TBA120SQ	0.75
TBA395	2.20
TBA341	0.97
TBA520	1.40
TBA520Q	1.10
TBA530Q	1.10
TBA540	1.30
TBA540Q	1.45

TBA550Q	1.40	BAX13	0.08
TBA560C	1.50	BAX16	0.10
TBA560CQ	1.50	BY126	0.10
TBA570	1.00	BY127	0.10
TBA570Q	1.00	BY164	0.40
TBA800	1.00	BY179	0.57
TBA810	1.50	BY226	—
TBA920	2.00	BY227	0.12
TBA920Q	1.50	BYF206	0.14
TBA990Q	1.50	1N4001	0.04
TCA270SQ	1.45	1N4002	0.05
TCA270SA	1.45	1N4003	0.06
TCA270Q	—	1N4004	0.07
TCA1327B	1.00	1N4005	0.07
TCA800	2.00	1N4006	0.08
TDA1010	—	1N4007	0.08
TDA1327B	1.00	1N4148	0.05
SBA750	1.75	1N4751	0.14
SC9503P	1.20	1N5401	0.12
SC9504P	1.20	1N5403	0.12
SL901B	3.50	1N5404	0.14
SL917B	5.00	1N5405	0.14
DIODES & THYRISTORS		1N5406	0.14
OA47	0.06	1N5408	0.25
OA81	0.06	BR100	0.22
OA90	0.06	BR101	0.28
OA91	0.07	BT106	1.19
BA130	0.10	BT108	1.23
BA145	0.16	BT109	1.09
BA148	0.18	BT116	1.60
BA154	0.18	BT120	1.60
BA155	0.10	2N4444	0.90

E.H.T. TRAYS MONO

950 MK2	
1400	2.50
1500 18" 19"	
stick	2.75
1500 24" 5	
stick	2.85
Single Stick Thorn TV	
11, 16K 70V	0.75
TV 20 2 MT	0.75
TV 2016K	
18V	0.75
BUSH 718	1.30

EXPORT COLOUR & MONO TV's AVAILABLE READY FOR USE OVERSEAS

BRIARWOOD TELEVISION LTD

Briarwood House, Preston Street, Bradford West Yorkshire BD7 1LU
Tel: (0274) 306018

Manufacturers Surplus Components FIT THE RIGHT PART

300 mixed $\frac{1}{2}$ and $\frac{1}{4}$ watt resistors £1.95
 150 mixed 1 and 2 watt resistors £1.95
 300 mixed **Capacitors**, improved pack, most types £3.95
 100 mixed **Electrolytics** £2.95
 300 mixed **Printed Circuit** mounting **Components** for various TVs, resistors, caps etc £1.95
 300 printed circuit **Resistors** $\frac{1}{4}$ to 4 watt £1.45
 100 **High Wattage** TV resistors, **Wirewound** etc. £2.95
 100 mixed miniature Ceramic and Plate Caps £1.50
 100 mixed polystyrene capacitors £2.20
 25 mixed **Pots and Presets** £1.20
 25 mixed **TV Presets** £1.00
 20 assorted **TV VDRs** and **Thermistors** £1.20
 10 assorted **TV Convergence Pots** £1.00
 20 assorted **TV knobs**, includes push button, chrome, control types etc. Mostly Thorn and ITT £1.00
 10 assorted **Valve Bases**, B9A, ceramic, EHT, etc. £1.00
 20 assorted **Sync Diodes** blocks for various TVs £1.00
 10 **Spark Gaps** £1.00
 20 assorted **Zener Diodes** 1 watt and 400mW £1.50
 100 **Mixed Diodes**, includes zener, power, bridge, varicap, germanium, silicon etc. All full spec. £4.95
 12 assorted **I.C. Sockets** £1.00
 20 Gen. purp. **Germ. Diodes** £1.00

GRUNDIG

UHF/VHF Varicap Tuners.
 Fit 1500 GB, 3010 GB.
 Brand new £12.50

PUSH BUTTON KNOBS

Type 1 15mm long x 11mm diam. Brushed Aluminium Finish
 10 for £1

Type 2 10mm long x 10mm diam. Chrome Finish
 10 for £1

Both types fit standard $3\frac{1}{2}$ mm square shafts as used on most music centres etc. **100 for £7**
1000 for £50

SPECIAL SCOOP PURCHASE OF MULLARD CAPACITORS

Spillages, Floor Sweepings, Cosmetic Imperfects etc. All mixed up. Factory clearance.

UNREPEATABLE OFFER

Polyester C280's (Liquorice Allsorts) **100 mixed £2. 1000 mixed £12**
Miniature Electrolytics (Blue Type) **150 mixed £2. 1000 mixed £10**

De Luxe Fibre Glass Printed Circuit Etching kits

Includes 150 sq. ins. copper clad F/G. board. 1 lb ferric chloride 1 dalo etch resist pen. Abrasive cleaner. Etch tray plus instructions.

Special Price £4.95.

1 lb F.E. C1 To mil. spec. **£1.25**

5 lb F.E. C1. To mil. spec. **£5.00**

150 sq. in. **Single sided** board **£2.00**

150 sq. in. **Double sided** board **£3.00**

Why Buy Expensive Triplers!

Repair your old 5 and 3 sticks at a **Fraction of the Cost.**
10 Replacement Rectifier Sticks (Thorn). **£1.00**

Special TV Bargain Parcels

Lots of useful parts including damaged panels, tuners, components etc. 10lb for £7.50

Hardware Pack

Includes BA nuts and bolts, nylon, posidrive, self-tapping "P" clips, cable markers, clamps, fuse holders etc. **£1 per lb.**

ITT CTV. SCAN COILS complete with conv. yoke. Plessey type. **£4.95**

TRANSISTOR MOUNTING KITS

TO3 (BU208 etc) **8 for 60p**

TO220 (TIP 33 etc) **10 for 60p**

TO77 (BD131 etc) **12 for 60p**

Pack of each **£1.50**

All include **Mica insulators** and **relevant washers.**

I.C. SOCKETS

DIL 14 pin **10 for £1**

Quil 16 pin. **12 for £1**

Dil to Quil 16 pin **10 for £1**

CASSETTE MAINS LEAD

7' lead with Fig. 8 Plug. **75p, 3 for £2**

ITT BLUE LATERAL

Assembly (single knob type) **60p**
3 for £1.50

ITT Spun Aluminium Control Knobs. $\frac{1}{4}$ " diam. $\frac{1}{4}$ " shaft **5 for £1**

SAVE THAT TUBE.

Fit our **C.R.T. Isolating Transformer.** Ideal for HTR./Cath. Shorts. 200-220-240 inputs. 750-900 MA outputs with thermal cutout. Made for **Thorn 4000 C.T.V.** but works O.K. on other sets. **£3.00 each** **2 for £5.00**

Pye 697 Line + Power Panels. Damaged with some components missing but ideal for spares. Good value. **£2.20 each**
3 for £6

SPECIAL

Thyristors, **SS106.** Like **BT106.**
60p each **3 for £1.50**
10 for £4.00

3A 100V Diodes **8 for £1.00**

2A 800V Metal Diodes
12 for £1.00

Degaussing V.D.R.'s (Red, Orange, Black), fit most sets. **5 for £1.**

Bush CTV 25 Quadrupler Remo type **Q25B.** equiv. to ITT. TU25 30K. with mounting brackets. **£2 each.**
3 for £5

GEC single standard, hybrid chassis. convergence panel. Brand new, complete with plugs and leads **£2.50**

G.E.C. S/S Hybrid Focus Assembly with lead **£1.50**

SPECIAL OFFER

GEC transistor rotary tuners with slow drive, AE Skt. and leads **2010 Series** **£1.50**

Line linearity coils. **50p each, 3 for £1**

4 Knobs black with chrome caps to fit ITT, Thorn, GEC and most small diam. shafts **60p per set**

ITT CVC5 power panel. New but five resistors never fitted **£1.50**

4 P/B UHF TUNER suitable for **VC200** and some Pye and Philips sets. 3 hole fixing. **£2.75**

Pye mono mains droppers with voltage link. **50p 3 for £1.00**

147 Ω + 260 Ω **50p 3 for £1.00**

69 Ω + 161 Ω **50p 3 for £1.00**

R2010B

£1 each

Portable TV EHT Sticks

"Siemens TV 18 KV". Fit most portables **50p each 3 for £1.00**

Pye 18" CT200 V. Cap P/B Assembly with leads and plug **£3.90**

Also:- **Miniature Mains Transformers** 4.5V-0-4.5V at 250Ma **90p each.**
3 for £2.50

2N3055H **60p each 3 for £1.50**

FOCUS RODS ($2\frac{1}{2}$ " V.D.R.) **75p each**
3 for £2

BB105B U.H.F. Varicap Diodes **20 for £1**

BF195 BF199

BC171 BC546

BC338 BC548

BC183L BC549

BC108 BC559

BC154 BC212L

AF289 BF245

BCX45 BFY57

BF506 BCY43

12 of any one Type £1.00

Thorn 1500 Bias Caps. 160uF 25v **20 for £1.50**

ZENERS

400mW. 2.7V, 4.3V, 4.7, 5.6, 6.2V, 6.8, 7.5, 27V, 30V
 10 of one type 80p. 10 of each type **£6.00**
 10 of each type **£5.50**

1.3W. 12V, 13V, 18V,
 10 of one type **£1.00**
 10 of each type **£2.50**

DIACS

TAA550

IN4000

IN4002

BR100

STABILIZERS

GEN. PURPOSE DIODES

30 for £1.00

25 for £1.00

BA158

6 for £1.00

4 for £1.00

20 for £1.00

20 for £1.00

10 for £1.00

TRANSISTOR PACKS

Our Transistor Packs are even better than before! **100 NEW AND MARKED TRANSISTORS** including BC238, ME0412, BF274, BC148, BC182L, BC338 and, or other similar types. A random analysis of these packs yielded between 98 and 106 transistors of 17 to 20 different types with an average total retail value of £14 - £16. **OUR PRICE ONLY £4.95**

200 transistors as above but including BD131, 2N3055, AC128, BFY50, BC154, BF394, BC184L, etc.

ONLY £9.95

Send **60p P. & P.** on all above items; send Cheque or P.O. with order to:-

SENTINEL SUPPLY DEPT. TV

149a Brookmill Rd., Deptford, London SE8

(Mail Order address only. Callers by appointment)
 Trade enquiries for quantity welcome.

Surplus stocks purchased for cash.

TRANSDUCTORS 90° fit **G8** etc. **£1.20 each 3 for £3**
RBM/ITT. Capacitor **220uf 400v** **£1 each 3 for £2.50**
THORN 900, 950 Triplers. **£1 each 3 for £2.50**


L.O.P.T. for **R.B.M. 823A** Chassis **£4.50 each 3 for £10**

BD131 **4 for £1**
BD132 **4 for £1**

MANOR SUPPLIES

PAL COLOUR BAR GENERATOR

plus CROSS HATCH KIT (Mk. 4)

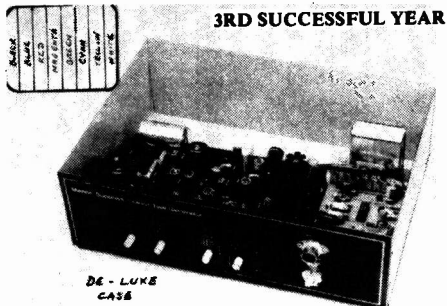

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s. on colour bar P.C.B.

PRICE OF MK4 COLOUR BAR & CROSS HATCH KIT £40.25 + £1.40 P/Packing. DE-LUXE CASE £5.95. ALUMINIUM CASE £3.30, BATT HOLDERS £1.70, ALTERNATIVE STAB. MAINS SUPPLY KIT £5.55.

ALSO THE MK3 COLOUR BAR GENERATOR KIT FOR ADDITION TO MANOR SUPPLIES CROSS HATCH UNITS. £28.75 + £1.40 p.p. CASE EXTRA £2.00. BATT. HOLDERS £1.70.

- ★★ Kits include drilled P.C. board, with full circuit data, assembly and setting up instructions.
- ★★ All special parts such as coils and modulator supplied complete and tested, ready for use.
- ★★ Designed to professional standards.
- ★★ Demonstration models at 172 West End Lane, NW6.
- ★★ Every kit fully guaranteed. Technical back-up service.

MK4 DE LUXE (BATTERY) BUILT & TESTED £66.70 + £1.35 P&P.
 MK 4 DE LUXE (MAINS) BUILT & TESTED £80.50 + £1.50 P&P.
 VHF MODULATOR (CHI to 4) FOR OVERSEAS £4.60.
 INFORMATION ON VIDEO TAKE-OFF FOR C.C.T.V.

(ALL PRICES INCLUDE 15% VAT)


MANOR SUPPLIES

TELETEXT KIT (MK2)

(INCORPORATING MULLARD DECODER 6101VML)

BACKED BY YEARS OF EXPERIENCE

INFRA RED REMOTE CONTROL

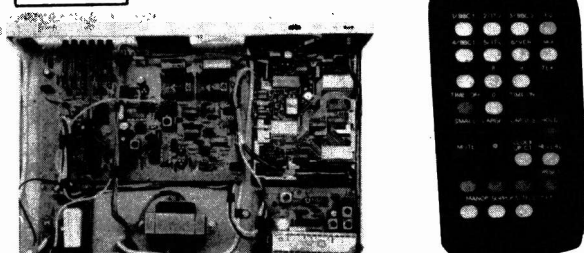

- EXTERNAL UNIT. PLUGS INTO AERIAL SOCKET OF TV RECEIVER.
- LATER SPEC (DOUBLE HEIGHT, BACKGROUND COLOUR ETC).
- INFRA-RED REMOTE CONTROL (MULLARD 5000 SYSTEM) STATION SELECTION, TEXT, MIX, TIME, DOUBLE HEIGHT, HOLD, CLOCK, REVEAL, RESET ETC, ETC.
- INCLUDES COMPLETE & TESTED 6101 VML (MULLARD) DECODER, SAW FILTER IF PANEL & 32 BUTTON REMOTE CONTROL HANDSET.
- SUITABLE FOR BBC DEAF SUB-TITLE TRANSMISSIONS. REMODULATES PICTURE.
- CONVERTS ANY UHF RECEIVER TO STATION SELECTION REMOTE CONTROL AND TELETEXT. (SIMPLIFIED KIT AVAILABLE FOR REMOTE CONTROL ONLY).
- FACILITIES FOR VIDEO OUTPUT, MONITORS, CCTV ETC.
- AUDIO OUTLET FOR EXTERNAL HI-FI AMPLIFIER.
- EVERY KIT EASY TO ASSEMBLE & FULLY GUARANTEED. TECH. BACK-UP SERVICE.
- DE-LUXE CASE MEASUREMENTS APPROX. 154 x 104 x 34.
- WORKING MODEL AT 172 WEST END LANE, N.W.6.

FURTHER DETAILS ON REQUEST

ALSO, MANOR SUPPLIES TELETEXT MK1 KIT (TEXAS) NOW WITH REMOTE CONTROL PRICE £193.20 P/P £2.80.

TELETEXT & TELEVISION SPARES

"TELEVISION" NEW PORTABLE RECEIVER PARTS AVAILABLE. WORKING MODEL & PANEL TEST SERVICE
SPECIAL OFFER TEXAS XM11 TELETEXT MODULE NEW & TESTED, LIMITED QUANTITY AT HALF PRICE £69.00 p.p. £1.40.
NEW CTV SIGNALS BOARD PARTS NOW AVAILABLE.
'TELEVISION' COLOUR RECEIVER PROJECT ALL PARTS AVAILABLE AT PRESENT. POWER, SIGNAL & TIMEBASE. SEND OR PHONE FOR LIST. WORKING MODEL ON SHOW WITH TELETEXT. (PANEL TEST SERVICE NOW AVAILABLE).
NEW SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND TESTED FOR T.V. SOUND & VISION £32.80 p.p. £1.10.
TELETEXT 5V STABILISED MAINS POWER SUPPLY (FOR TEXAS OR MULLARD DECODERS) £6.70 p.p. £1.00.
TELETEXT 23 UNIT DE-LUXE HANDSET WITH 5 YD. CABLE £11.30 p.p. £1.00. XM11 INTERFACE PANEL (THORN) £2.10 p.p. 75p.
CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET £12.65 p.p. 50p. (ALUM CASE £2.60 p.p. 80p.)
ADDITIONAL GREY SCALE KIT £3.35 p.p. 35p.
TV TEST GENERATOR UHF MODULATOR £4.60 p.p. 40p.
UHF SIGNAL STRENGTH METER KIT £20.00 (VHF VERSION £21.60). ALUM CASE £2.00 DE LUXE CASE £5.95 p.p. £1.60.
CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR & MONO £25.80 p.p. £1.80.
THORN 9000 FACIA INCL. CHANNEL SELECTOR, INDICATOR SET CONTROLS, ETC. £5.50 p.p. £1.60.
PHILIPS 210, 300 Series Frame T.B. Panels £1.15 p.p. 75p.
BUSH Z718, BC6100 SERIES SURPLUS LINE T.B. PANEL Z904, INCL. LOPT, EHT STICK, FOCUS ETC, 18" £17.25 p.p. £1.80.
BUSH A823 IF PANEL (EXPORT VERSION) £3.25 p.p. £1.00.
BUSH Z718 BC6100 SERIES IF PANEL £5.75 p.p. 80p.
BUSH A816 IF PANEL (SURPLUS) £1.90 p.p. 80p.
BUSH 161 TIMEBASE PANEL A634 £3.25 p.p. £1.40.
GEC SERIES I MONO PANELS £2.10 p.p. £1.30.
GEC 2110 DECODER, RGB PANELS £5.75 EACH p.p. £1.00.
GEC 2010 SERIES TIMEBASE PANEL £1.15 p.p. 95p.
GEC 2040 (TYPE) CDA PANEL £2.88 p.p. £1.25.
GEC 2040 CONVERGENCE PANEL £2.88 p.p. £1.30.
PYE 697 Line T.B. P.C.B. type salvaged £4.80 p.p. £1.50.
THORN 3000 LINE TB PCB £5.75 each p.p. 85p.
THORN 3000 VID, IF, DEC, Ex Rental £5.75 each p.p. £1.30.
THORN 8000/8500 IF/DECODER PANELS salvaged £5.50 p.p. £1.60.
THORN 8000/8500 POWER/SALV. SPARES £2.88 p.p. 60p.
THORN 9000 LINE T.B. (incl. LOPT etc.), SALV., SPARES £8.62 p.p. £1.60.
MULLARD AT1022 Colour Sp. Coils £6.90 p.p. £1.60, AT1023/05 Convergence Yoke £2.90 p.p. 95p, AT1025/06 Blue Lat. 90p p.p. 40p.
PHILIPS G9 Signal Board Panels for small spares £4.80 p.p. £1.00.
PHILIPS G6 Single standard convergence panels £2.90 p.p. £1.20.
G8 Decoder panels salvaged £4.25. Decoder panels for spares £2.00 p.p. £1.15.
VARICAP UHF ELC1043/06 £7.82, ELC1043/05 £6.35 p.p. 45p., G.I. type (equiv. 1043/05) £4.00 p.p. 40p. Control units, 3PSN £1.40, 4PSN £1.75, 5PSN £2.00, 6PSN £2.10, Special Offer 6PSN £1.15 p.p. 40p.
BUSH "Touch Tune" assembly, incl. circuit £5.75 p.p. 85p.
VARICAP UHF-VHF ELC 2000S £9.80. BUSH TYPE £9.00 p.p. 85p.
VARICAP VHF MULLARD ELC1042 £7.95 p.p. 45p.
UHF/625 Tuners, many different types in stock. UHF tuners transist. incl. s/m drive, £3.28. Mullard 4 position push button £2.88 p.p. £1.30.
TRANSISTORISED 625 IF for T.V., sound, tested. £7.82 p.p. 75p.
MULLARD EP9000 Audio Unit incl. LP1162 Module £4.38 p.p. 85p.
LINE OUTPUT TRANSFORMERS. New guar. p.p. £1.00.

BUSH 145 to 186SS series.....	£8.50	COLOUR LOPTS p.p. £1.25.	
BUSH, MURPHY A816 series.....	£9.80	R.B.M. A823.....	£5.60
DECCA 20/24, 1700, 2000, 2401.....	£8.50	R.B.M. Z179.....	£6.70
FERG., HMV, MARCONI, ULTRA		DECCA Bradford (state Model No.).....	£10.15
850 to 1580.....	£6.80	DECCA 80, 100.....	£9.50
GEC 2000, 2047 series, etc.....	18.50	GEC 2028.....	£7.82
INDESIT 20/24EGB.....	£8.50	GEC 2040.....	£11.30
ITT/KB VC1 to 53, 100, 200, 300.....	£8.50	GEC 2110 Series.....	£12.20
MURPHY 1910 to 2417 series.....	£8.50	ITT CVC 5 to 9.....	£10.15
PHILIPS 19TG170, 210, 300.....	£8.50	ITT CVC 30 Series.....	£10.15
PYE, INVICTA, EKCO, FERR.		PYE 691-697.....	£20.50
368, 169, 569, 769 series.....	£8.50	PYE 697 PC.....	£14.40
		PYE 731-715.....	£7.85
		PHILIPS G8, G9.....	£10.15
		PHILIPS 570.....	£7.85
		THORN 3000/3500 SCAN, EHT.....	£7.85
		THORN 8000/8500.....	£14.80

SPECIAL OFFER
 GEC 21143/FINELINE..... £5.50
 PYE 40, 67..... £5.50
 THORN 1590/1591..... £5.50
 KB VC ELEVEN (003)..... £3.25

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO F.O.P.TS.
THORN 950 3 Stick Tray £1.15 p.p. 55p. Most others available.
THORN 3000/3500, 8000, 8500, MAINS TRANSF. £10.15 p.p. £1.60.
6-3V CRT Boost Transformers £5.00 p.p. 95p.

Telephone 01-794 8751

CALLERS WELCOME AT SHOP PREMISES


THOUSANDS OF ADDITIONAL ITEMS AVAILABLE
 NOT NORMALLY ADVERTISED, ENQUIRIES INVITED

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Sta. (Jubilee) Buses 28, 159 pass door
 W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)
 W. Hampstead (Brit. Rail) access from all over Greater London.

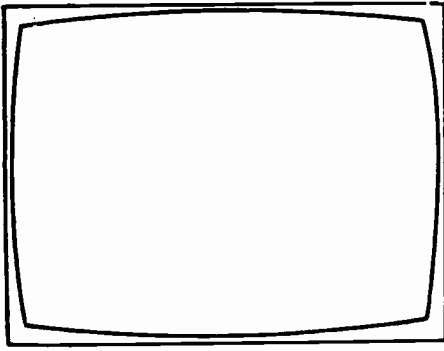Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.
 ALL PRICES INCLUDE VAT AT 15%



TELEVISION

EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Colin R. Brown
01-261 5762

PRICE INCREASE

We regret the need to increase the cover price of *Television* again, to 70p from next month's issue. The new price is not unreasonable when compared to such everyday items as a pint of beer or a packet of cigarettes, and every effort will be made to continue to provide our readers with an authoritative service on which they can rely.

CORRECTION

In our article on solid-state TV cameras (November 1980) it should have been said that the *cassette* used in the prototype Sony Cam-Corder, not the VCR itself, is 56 x 35 x 13mm.

Crystal-gazing

Crystal-gazing and futurology are by and large harmless enough exercises. In fact the only harm comes when someone actually takes notice of what the crystal gazer says. The damage then done tends to be proportional to the distance ahead that the crystal gazer claims to be able to see.

One can be reasonably sure about the likely situation six months ahead. A year hence is a fair bet too for prophesy. A couple of years ahead and the view gets more murky. Few would claim to be able to suggest in much detail exactly what lies ten years ahead. The cynic can say that things will be much the same only more so, barring catastrophes, but while this is undoubtedly true it doesn't get one very far.

For some, the thirties was a time when the future held out great hope. I seem to recall seeing at an impressionable age books and comics that provided a glowing picture of what was to come. We'd all live in skyscrapers, and apparently spend our days travelling by air or by super-speed train from one metropolis to another – in perpetual sunshine of course. The picture was usually rather lacking in detail about what people were actually up to most of the time, and the images of the hardware of the future were inclined to be somewhat unconvincing – streamlined versions of what already existed. Like the streamlined biplanes that landed on the tops of those skyscrapers!

Well, we now have quite a few skyscrapers of sorts – of sorts people have discovered they don't like living in. In fact the one profession which does seem to have been taken in rather by futuristic visions is that of architecture. Even if most of us don't have to live in high-rise buildings, we still have to live amongst buildings that may have looked exciting on the drawing board but once built look tatty and uninviting, especially on a wet day (that's the bit the architect doesn't show his client!).

There are dangers then in getting carried away by visions of the future. And the dangers can be expensive. Unwanted tower blocks have had to be demolished, and what sort of return have we got on our investment in supersonic travel? It's interesting to note that the sorts of things that tend to make the greatest difference in everyday life are not the sorts of things that visionaries dream of: they are things like refrigerators, washing machines, vacuum cleaners and typewriters.

One has the feeling that there's a moral of sorts here, for the UK at any rate. We've many splendid engineering achievements to show. But do they add up in economic terms? We spend a great deal of money on research and development, but precious little of it seems to be spent on everyday things that can be sold on the mass market. Compare this with the Japanese economy. What an uncanny knack they have for spending their resources on developing products that people actually want and can use! Maybe they have better crystal balls, or maybe they pay more attention to the short-term prospects revealed.

One crystal gazer who's reported recently is André Baumes, Grundig's managing director. Commenting on commitment to the 21st century, he sees the family "looking at a flat screen, probably around 60 inches across, and with a control panel which will control just about everything from the TV screen to the video recorder, disc, teletext, Prestel, cinefilm transfer unit" and so on. In the shorter term, he expresses "great optimism" on projection TV. "With a projection TV, you can have a marvellous atmosphere, like being in a cinema. You place your hi-fi speakers on each side of the screen, and you get the best cinefilms in the world played back via a transfer unit with really good sound."

We don't place much trust in our own crystal ball. Right now however it does suggest to us that the VCR, about which we've expressed reservations in the past, is on the point of establishing itself as a standard item of domestic electronic equipment – simply because the Japanese can provide them at such incredibly reasonable prices. They could become so well established so soon that the coming videodiscs will not get much of a look in. On the other hand if discs really do turn out to be as cheap as anticipated, the video disc and tape could coexist as audio discs and tapes do. Teletext, being cheap to provide and cheap to build into sets, looks a reasonable bet, but viewdata – well, how many people have any need to be able to plug into a vast store of computerised information (and access will never be all that cheap)? As for projection TV, one thing's certain – most of us will continue to live in cramped conditions which totally preclude "a marvellous atmosphere, like being in a cinema." Oh yes, and the crystal ball unfortunately shows all the hardware coming from afar – brought to us in a streamlined biplane against a background of the rising sun...

Teletopics

VCR CLEANING

A joint statement has been issued by the companies marketing VHS machines in the UK – Akai, Ferguson, Hitachi, JVC, Panasonic and Sharp – commenting on the increasing number of products now available for cleaning the audio and video heads in VHS VCRs. VCR users are advised that such products have neither the approval nor the recommendation of the VCR manufacturers. “In our opinion” the statement continues, “the use of such head cleaning equipment – either in cassette or kit form – is unnecessary with any VHS machine since the composition and action of the tape itself cleans the heads during use. In laboratory tests it has been found that the head cleaning products currently available are not only ineffective but may cause damage to either the video heads or the tape used in the recorder. The video heads in VHS machines should be cleaned only by qualified service engineers, after they’ve established the need for this.”

The video head cleaners currently available are of two types: first cassettes containing either mildly abrasive or chamois leather tape, and secondly kits containing chemicals and an applicator. Cassettes with abrasive tape are considered ineffective and could also be harmful, possibly causing excessive wear of the video heads and roughening the surfaces of the tape transport mechanism. Cassettes with chamois leather wipe the surfaces of the audio and video heads, the capstan and pinch wheel and the cassette loading arms, but do not deal with the cavities around the video heads. Some cassette cleaners of this type are used in conjunction with a cleaning fluid which is sprayed on to the chamois leather. The VHS companies consider this to be potentially hazardous since the fluid could harm components within the machines or, should a cassette be inserted shortly after cleaning, fluid remaining on the heads could act as an abrasive to the tape, damaging both the tape and the heads. The use of kits with chemicals and an applicator necessitates partial dismantling of the machine in order to obtain access to the head drum: it is not advisable for non-qualified users to undertake this sort of thing.

Sony agree that cleaning is not something that should be done by users. They say that if the heads are clogging the problem should be dealt with by the appropriate service department.

Network Marketing Ltd., who distribute the Allsop 3 VHS cassette cleaner, comment that this cleaner is effective and non-abrasive in its action – the alcohol cleaning fluid also acts as a lubricant to reduce the risk of abrasion, and would have evaporated during the time between unloading and reloading a cassette. They agree that it doesn’t deal with the cavities around the video heads, but say they don’t claim that it does and that no cleaning tape would effectively do this.

It would seem to us that any cleaning should be undertaken only by those who, if at all uncertain, can obtain advice direct from the VCR distributors.

WHO'S WHO

In the face of stiffening world-wide competition in the consumer electronics field, the major European manufacturers have been busy consolidating their positions. We reported last month that Philips in N. America have

taken over the GTE-Sylvania consumer electronics interests in the USA. In 1978, the last year for which figures are readily available, Philips world-wide were second only to Matsushita (Panasonic) in the league of colour receiver manufacturers. Since GTE-Sylvania were also in the top ten, this takeover considerably strengthens Philips’ position. W. Germany’s largest colour set manufacturer, Grundig, is also in the top ten and nowadays operates jointly with Philips. In a further move to consolidate their position, Philips have acquired the ownership of the Marantz trademark in all markets except N. America. This acquisition includes 100 per cent of Marantz of Europe and its subsidiaries, the whole of Marantz Australia, most of the Superscope manufacturing organisation in Taiwan and a 43 per cent interest in Marantz Japan – the latter is expected to be increased to 50 per cent.

France’s largest indigenous TV manufacturer, Thomson-Brandt, acquired the W. German setmaker Nordmende some while back and has more recently acquired Saba from GTE-Sylvania. Models fitted with the new Saba Q chassis have been introduced on the UK market recently.

In the UK, Rediffusion have reached agreement with Sharp to produce small-screen colour sets based on Sharp designs at Rediffusion’s factory in County Durham.

SECOND GENERATION PORTABLE VCR

JVC have introduced a new portable VCR, Model HR2200E, which weighs just 11½lb and uses 50% less components than their previous VCRs. A newly JVC developed high precision brushless quartz locked direct drive motor drives the head drum and transports the tape steadily while the VCR is being carried, a microprocessor providing full logic control. Advanced features include variable speed playback, edit start control which automatically aligns separately recorded segments to avoid distortion, and a shuttle search facility allowing programmes to be viewed in both the forward and reverse modes at ten times the normal speed. The machine can be powered from the mains, a car battery or its own rechargeable nickel-cadmium battery pack. It’s complemented by the TU22E unit which acts as a tuner/timer (with ten day preset capability), a.c. power adaptor and battery charger, or the AAP22E power adaptor/battery charger unit.

TV TELEPHONE

Zenith in the USA have introduced a TV set they call the “Space Phone”. It can be connected to the telephone line to receive incoming calls, the viewer answering from his arm chair by operating the “Space Command” button on his remote control handset. The receiver incorporates a microphone to pick up the user’s voice. If the set is connected via a phone unit it can also be used for making outgoing calls.

RANK-TOSHIBA

The unwinding of the Rank-Toshiba joint TV set manufacturing operation will involve Rank in buying out Toshiba’s share for a nominal sum and taking responsibility for running down the Plymouth and Redruth plants. This stage is due to end next March, when Toshiba will take over the main Ernsettle plant and continue the production of Toshiba brand sets. Production is expected to resume at the reduced rate of around 100,000 sets a year, and Toshiba are unable to say what percentage of the workforce they will be able to take on.

Rank Radio International is to continue in operation for

the time being – and in fact three new Bush Models have just been announced, the BC7205, which is fitted with a 20in. 90° tube, and two models fitted with the T26 chassis (30AX tube). The latter are the 22in. Model BC7310 and 26in. BC7410, which feature “Infracolour” remote control and a DIN socket for connecting an external tape recorder, amplifier or headphones.

Meanwhile, if anyone reads this column they may have noticed that a sidehead plus three lines of text disappeared from the bottom right-hand column on page 66 last month. The heading read “Service Notes – Rank”, and the text read to the effect that details of the latest Rank chassis have been released (the T24H and T18).

MINI VCR

Technicolour Audio-Visual are marketing in the USA a compact portable VCR that weighs only seven pounds and uses a cassette only slightly larger than a standard audio one, giving half an hour's playing time. Helical scanning is used, but the cassette is not compatible with the VHS or Beta formats. The VCR is aimed at competing with film equipment rather than other VCR systems. It's made by Funai Electric in Japan, the tape and cassette being produced by Fuji. Any home colour or monochrome video camera can be used with it.

ITT80 CHASSIS

ITT's latest chassis, the ITT80, is designed to drive the new generation of 20 and 22in. 90° PIL tubes. This means that, as in the recently introduced CVC800 chassis (for 14/16/20in. 90° tubes), no EW raster correction circuitry is required. There are two main sections, the CVC820 power supply/timebase board and the CVC850 signals board. The circuitry is basically similar to that used in the CVC800, though there are numerous detail differences, including the use of complementary-symmetry RGB output stages.

STATION OPENINGS

The following relay transmitters are now in operation:

Dentdale (Cumbria) TV4 ch. 53, BBC-1 ch. 57, Border Television ch. 60, BBC-2 ch. 63.

Ellon (Aberdeenshire) BBC-1 ch. 39, Grampian Television ch. 42, BBC-2 ch. 45, TV4 ch. 49.

Forest Row (Sussex) BBC-1 ch. 48, BBC-2 ch. 54, Thames/London Weekend Television ch. 62, TV4 ch. 66.

Hedleyhope (County Durham) BBC-1 ch. 40, Tyne Tees Television ch. 43, BBC-2 ch. 46, TV4 ch. 50. Horizontal polarisation.

Kenmore (Tayside) Grampian Television ch. 23, BBC-2 ch. 26, TV4 ch. 29, BBC-1 ch. 33.


Lydbrook (Gloucestershire) BBC-1 ch. 40, HTV-West ch. 43, BBC-2 ch. 46, TV4 ch. 50.

Slad (Gloucestershire) HTV-West ch. 23, BBC-2 ch. 26, TV4 ch. 29, BBC-1 ch. 33. Horizontal polarisation.

Polarisation is vertical unless otherwise stated.

HITACHI'S LATEST CAMERAS

At a suggested retail price of £399 including VAT, Hitachi have introduced what must be one of the cheapest colour video cameras now available – one which should appeal to both the newcomer and the established video enthusiast. The camera, Model VKC750, complements the GP4 series, which is made by and distributed via Hitachi Denchi Ltd. As in the GP4, a single tri-electrode pickup tube is used, with separate electrodes for each of the primary colours. This, together with the use of advanced i.c. circuitry, has enabled the weight to be reduced to 4lb, with a battery consumption

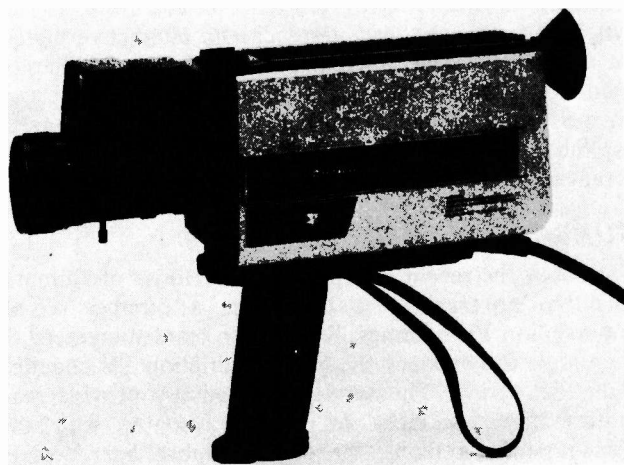

The new Hitachi Model VKC750 single-tube colour camera – the suggested retail price is only £399.

of only 5.8W. The built-in double-image optical viewfinder is linked to a 2.8:1 zoom lens with a focal length of 13.5–37.5mm. There's a colour temperature control button which operates in conjunction with a balance meter, and a high-low sensitivity switch. Pictures can be obtained under lighting conditions ranging from 100 lux to 100,000 lux. A LED indicator in the viewfinder indicates when recordings are being made, whether the light is insufficient, and low battery power.

Meanwhile Hitachi have produced, for the Japanese market initially, what's claimed to be the world's smallest home colour video camera, Model VKC1000. The secret of the reduced size and weight (2½lb including a 6× power zoom lens) is the use of a single-chip MOS image sensor i.c. instead of a pick-up tube. The initial price (in Japan) is expected to be around £690. The horizontal resolution is 260 lines, the vertical resolution 350 lines and the minimum signal:noise ratio 46dB. The use of a solid-state sensor gives quick start, the image appearing in less than half a second after switching on.

THORN SOFTWARE

A new company, Video at Home, has been set up within the Thorn TV Rentals organisation to supply the group's rental outlets with software (prerecorded video cassettes) for VHS VCRs. Besides feature films such as Jaws, The Muppet Movie, Psycho, Saturday Night Fever, Genevieve etc. there'll be a wealth of musicals and sport. The cassettes will be available to buy or rent from all Thorn TV Rentals outlets (DER, Radio Rentals, Multi Broadcast and Focus), the initial catalogue including over 80 titles. Customers will also be able to join a video club – the year's subscription will enable the member to rent or buy cassettes at a reduced rate. Thorn Rentals expect to have over 100,000 VHS subscribers by the end of the present financial year, and anticipate supplying over a million blank tapes through their 1,200 branches next year.

Thorn-EMI Video Programmes and publishers Longman have announced the development of a new system for learning foreign languages at home, using a personal computer. Languages available initially will be French, German and Spanish, with Italian to follow – these are the result of a joint project to create programmes for exclusive use on the Atari 400 and 800 personal computers. Distribution will be in the USA initially, with UK distribution to follow. Each course consists of five twin track cassettes (containing both computer programmes and audio tracks), together with a learner's manual. The audio

material is under programme control, and is thus synchronised to the text, graphics and interactive material on the screen. The machine's interactive capabilities are used to the maximum, the learner having to provide answers, check answers, make choices, play games, assemble text and check understanding. The course is arranged so that learners can progress at their own speeds.

SUBSCRIPTION TV

Following the recent statement in the House of Commons that the government is to license a number of pilot subscription TV schemes, Rediffusion have announced that they hope to introduce the first subscription TV channel in Hull this spring. The service will initially provide recent feature films – eight or nine a month, with three transmissions a night, the cost to subscribers probably being in the region of £4-5 a month. The service operates in conjunction with cable networks of course.

BRITISH VIDEOGRAM ASSOCIATION

The British Videogram Association, which has been formed to represent the interests of videogram producers in this country, has now been officially set up. There are over 30 members, including Thorn-EMI, CBS Records, BBC Home Video, Warner Bros. and Intervision. Amongst the Association's first priorities will be the formalisation of terms and conditions for the employment of creative talent, the protection of copyrights and mechanical rights, an approach to the government for a levy on the sale of blank cassettes, liaison between the videogram industry and relevant bodies from other related industries, and consideration of the commercial piracy problem. The word videogram is new to us, but seems a logical way of covering both video cassettes and discs (playable, we'll assume, on machines you don't have to wind up).

ILLEGAL VIDEO CASSETTES

JVC (UK) Ltd. report that illegal, imitation JVC E180 blank video cassettes have appeared in the UK. Though branded JVC, the tapes differ in the following respects: (1) The JVC cassette has a cellophane wrapping with a stripe to open the pack: the imitation is shrink wrapped. (2) The JVC tape's cellophane wrapping has a yellow cut tape: the imitation doesn't. (3) The JVC cassettes are contained in a ten pack carton with JVC printed on it: the imitations come in twelve pack cartons. (4) The JVC cartons are packed five to a JVC printed master carton holding fifty cassettes: the imitation cartons are packed four to a plain master carton that contains 48 tapes. (5) There's a difference in the design of the bottom shell of the cassette body. Being branded imitations, the counterfeit tapes are illegal.

NEW PORTABLES

A 14in. monochrome portable, Model 1045, has been added to the Pye range. It uses the now well established TX chassis. Two more portables have been added to the Ferguson range, Model 3857 (black case) and 3858 (white). Called the "Courier", these sets are fitted with the 1691 chassis.

Two interesting models have been added to the Hitachi range. The K2300 is described as a bedside TV, which combines a 4½in. TV set and digital clock. It has a four-way power supply option. The set works at either v.h.f. or u.h.f., and also incorporates a v.h.f./m.w./l.w. radio. The suggested price is £115. The K2400 is described as a portable entertainment centre, combining a 4½in. TV set and cassette radio. The suggested price is £175.

From Philips comes the TC2100, which combines a three waveband a.m./f.m. radio, cassette recorder/player, digital clock and 9in. monochrome TV set – the clock can be programmed to switch on the TV, radio or cassette player at any preset time. All this is housed in a remarkably compact square case. The TC2000 is a version without the cassette player.

INTERNATIONAL VIDEO WEEK

An international video week is to be held on 10-17th May, with events in London and Birmingham. Participating in the week will be *The Economist* newspaper, the British Film Institute, the British Industrial and Scientific Film Association and exhibition organisers Brintex. *The Economist* Video Conference will be held on May 11-12th at the National Film Theatre, the International Video Festival on May 13-15th at the same venue, and the Audio, Video and TV Fair on May 10-17th at the National Exhibition Centre, Birmingham. An International Video Forum will be held during the week at the National Film Theatre, London.

Teletext Decoder Corrections

THE following corrections to the *Television* teletext decoder up-date series (June-September 1979) should be noted.

(1) New mother board power supply feeds (see Fig. 3, page 540, August 1979 issue). The 70V and one of the two 12V power supply feeds to the board were shown transposed. This must be corrected as follows. Disconnect the 12V feed from pins 25/26 of the i.f. panel edge connector on the mother board, also the 70V feed from pins 23/24. Reconnect the 70V feed to pins 25/26 and the 12V feed to pins 23/24. Remove the wire link between pins 25/26 and the track to the modulator, connecting this to pins 23/24 instead.

(2) Write signal to the memory board. Refer to the mother board layout (Fig. 3, page 540, August 1979). The link between pin 7 of the input board and pins 8/9 of the memory board was not shown. For normal operation these two points should be linked together. A modification is possible however (see Fig. 1). A page hold switch can be incorporated by including a switch in series between these points. Connect a 10kΩ resistor from pins 8/9 of the memory board to the 5V rail to ensure proper operation of the memory when the switch is opened. Opening the switch freezes the page currently being displayed on the screen.

(3) Colour options board (refer to Fig. 7, page 586 and Fig. 5, page 585, September 1979 issue). Pin 2 of IC7 must be connected to the nearby track leading to pin 28 of the edge connector.

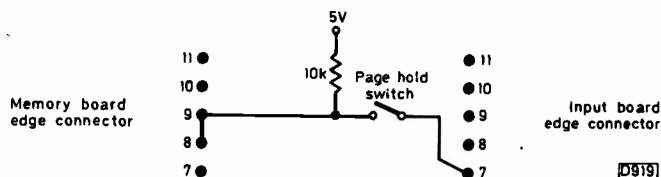


Fig. 1: Correction to the connections between the memory and input board edge connectors on the mother board – viewed from the print side. A page hold switch can be added at this point as shown above.

ARE YOU IN THE DARK?..
..ABOUT OUR



COLOUR T.V. PANEL EXCHANGE REPAIR SERVICE

FULL RANGE OF
THORN · RBM · PHILIPS
PYE · INVICTA · GEC
DECCA · TELPRO
AND MANY OTHER MAKES

90 DAY GUARANTEE ON ALL REPAIRS
SAME DAY POSTAL SERVICE

We employ a large skilled Staff, who utilise some of the most sophisticated Test equipment available, inclusive of AUTOMATIC FAULT FINDING COMPUTERS together with specially designed SERVICING JIGS which in short means to you -

HIGH QUALITY REPAIRS - AT LOW COST



ONE OFF
OR



100 OFF · NO ORDER TOO
LARGE OR SMALL

SEND FOR PRICE LIST

SEND FOR CATALOGUE
BLOCK DISCOUNTS FOR TRADE CONTRACTS

TO

Campbell Electronics Ltd.

Unit 5, Heath Hill Estate, Dawley, Telford, Shropshire TF4 2RH.
Telephone: Telford (0952) 502422. Telex 35191 Chamcon

LOOK!

Phone: LUTON
BEDS. 38716

OPPORTUNITIES TRADE SALES

ALL SETS GUARANTEED
COMPLETE

OVER SIX HUNDRED SETS

ALWAYS IN STOCK

Pye 20T, Philips G8;

Ferguson 3-3k5

Murphy, Bush, Decca, GEC

All from

£35.00 £50.00

Square Screen, Mono's from

£5.00 ALL MODELS

Sets for spares from

£2.00

All include VAT

OPPORTUNITIES

9A, Chapel Street, Luton, Beds.
LUTON 38716

9.30-6.00 p.m. Weekdays, 10.30-1.00 p.m. Sundays.

Technical Training in Radio, Television and Electronics

Start training TODAY and make sure you are qualified to take advantage of the many opportunities open to trained people. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college has helped thousands of people to move up into higher paid jobs - and they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

City and Guilds Certificates:-

Telecommunications Technicians,
Radio, TV and Electronics Technicians,
Electrical Installation Work,
Technical Communications,
Radio Amateur,
MPT General Radio Communications
Certificate.

Diploma Courses:-

Electronic Engineering,
Electrical Engineering,
Computer Engineering,
Radio, TV, Audio Engineering, Servicing and
Maintenance (inc. Colour TV)
New Self-Build Radio Courses with Free Kits.

Colour TV Servicing

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study courses which are approved by a leading manufacturer.

The ICS Guarantee

If you are studying for an examination, ICS will guarantee coaching until you are successful - at no extra cost.

POST OR PHONE TODAY FOR FREE BOOKLET.

I am interested in.....

Name.....

Address.....

..... Phone No:

ICS International Correspondence Schools,
Dept. 285C, Intertext House,
LONDON SW8 4UJ. Tel 622 9911
(all hours)

P.V. TUBES

38A WATER STREET
ACCRINGTON LANCs BB5 6PX

SUPPLIERS OF TELEVISION COMPONENTS

Telephone: Accrington (0254) 36521

TRADE COUNTER OPEN MON-FRI 9a.m.-4.30p.m.
SAT. MORN. 9.30a.m.-12 NOON.

PLEASE ADD 15% VAT TO ALL PRICES

NEW MONO TUBES

Mullard A31/510 12" 110"	£17.00
Mullard A34/510 14" 110"	£18.50
Hitachi A31/300 12" 110"	£15.00
Vega 12" 90"	£15.00
Vega A50/120 20" 110"	£13.50
Vega A61/120 24" 110"	£15.00

REBUILT COLOUR TUBES

17", 18", 19", 20"	£28.00
22"	£30.00
25", 26"	£34.00
28" 110"	£36.00

Glass for glass exchange
2 year warranty.

MULLARD COLOUREX/OR MAZOA NEW LIFE

18"	£59.50
19"	£51.00
20"	£55.00
22"	£45.00
25"	£55.00
26"	£57.00
28" 110"	£60.50

Glass for glass exchange
1 year warranty 4 year optional.

Carriage incl. VAT on carriage
MONO £5.00
COLOUR £5.00
PORTABLE £3.50

NEW VALVES

1.21 EY867	68	PCL84	81
72 EY90A	1.33	PCL85/805	79
66 E280/1	56	PCL86	81
80 GY501	1.45	P5000	2.93
68 G234	1.56	PFL200	1.35
80 KX66	6.98	PL36	1.15
80 PC66	81	PL81	94
98 PC68	81	PL82	46
135 PC92	80	PL83	1.43
80 PC97	1.14	PL84	84
88 PC90	80	PL95	1.00
104 PC684	70	PL504	1.32
113 PC685	85	PL508	2.28
84 PC688	82	PL509	2.28
77 PC689	79	PL519	2.28
84 PC8189	1.02	PL802	2.15
78 PC805	1.40	PY33	61
68 PCF80	75	PY88	81
68 PCF86	1.13	PYS00A	1.40
119 PCF200	1.23	PY800/1	69
143 PCF800	1.38	UCF80	67
163 PCF801	1.13	UCH81	1.43
102 PCF802	86	UCL82	84
163 PCF805	1.63	UCL83	94
163 PCF806	1.30	UL84	1.02
66 PCF808	1.63	U26	1.30
68 PCM200	1.45	U191	95
82 PCL82	78	EF23	85
2.22 PCL83	2.00	UY85	80

All valves are new - boxed - guaranteed.
Please add 15% VAT to ALL items.

RECTIFIER TRAYS

Thorn 950	£4.25	GEC 2110 before Jan 77	£6.95
Thorn 1500/1580	£3.85	GEC 2110 after Jan 77	£6.65
Thorn 1500 5 stick	£4.25	GEC 1028 2028, 1040	£5.64
Thorn 1600	£3.45	ITT/KB CVC5/7/8/9	£5.35
Thorn 3000/3500	£6.89	ITT/KB CVC20/25/30	£5.35
Thorn 1400	£3.85	Korting (similar to Siemens TVK1)	£5.85
Thorn 8000	£3.51	Philips 3113 550/1/3	£5.85
Thorn 8500/8800	£5.40	Philips G8	£5.85
Thorn 1400	£7.43	Philips G9	£6.33
Decca CTV 19/25	£5.35	Pye 691/3	£5.13
Decca CS1730/3 CS1830/5	£3.68	Pye 731/25	£5.40
Decca 1910 Bradford	£5.92	Rank BM AB23/2179	£5.78
2213		Rank BM AB23 A/V	£6.89
Decca 30	£5.92	Reddifusion MK1	£6.04
Decca 80	£6.28	BRC 2000	£6.60
Decca 100	£6.04	'Universal Tripler'	£5.40

TRANSFORMERS

LINE OUTPUT TRANSFORMERS	
Type	Price (p)
Bush A774	£11.75
Replacement Tripler for A774	£10.75
Decca 80	£8.58
Decca 100	£8.58
Decca 1730	£8.58
Decca 2230	£8.58
GEC 2040	£9.20
GEC 2110	£8.58
Philips G8	£10.00
Pye 691/3	£14.00
Philips G9	£10.15
Thorn 3500	£9.00
Scan AC EHT Transformer	£5.00
Thorn 8000	£9.00
Thorn 8500	£10.00

MAINS DROPPERS

Type	Price (p)
Decca 20 Decca 20 Series	£1.10
GEC 2018	70
Philips 210/5050	66
Philips GB 5081	35
Philips GB 5083	35
Pye 725	53
RBM AB23	55
RBM AB23	77
Thorn 1500	68
Thorn 3500	68
Thorn 8000	86
Thorn 8500	83

PREFERRED VALUES

RESISTORS	
WIREWOUND	
Price Each (p)	
4 watt 1 ohm-1.5kohm	13
2.2k, 3.3k	15
4.7k, 6.8k	17
10k	22
7 watt 1 ohm-4.7kohm	4
5.6k 12k	15
15k-22k	18
11 watt 1 ohm 6.8kohm	17
10k 15k	18
22k	21
17 watt 1 ohm 10kohm	24
15k, 22k	25

SEMICONDUCTORS

Type	Price (p)	Type	Price (p)
AC126	22	BC212	9
AC127	22	BC212L	9
AC128	20	BC213	9
AC128K	32	BC213B	10
AC141K	34	BC213L	9
AC142K	30	BC214	9
AC176	25	BC214L	10
AC176K	32	BC237	9
AC187	26	BC238	8
AC187K	28	BC251A	12
AC188	25	BC251B	15
AC188K	37	BC252A	12
AD140	75	BC252B	12
AD143	82	BC261A	18
AD149	79	BC261B	15
AD181/2	42	BC262A	15
AD182	42	BC300	30
AF124	34	BC301	28
AF127	32	BC303	28
AF138	42	BC307	28
AF209	45	BC307A	10
AL102	£2.00	BC327	11
AL103	£2.00	BC328	8
AL107	£2.00	BC337	11
AL113	£1.49	BC338	9
BC107	11	BC411	30
BC107A	12	BC546	7
BC107B	13	BC547	10
BC108	11	BC548	10
BC108A	12	BC549	7
BC108B	12	BC550	7
BC108C	14	BC557	7
BC109	11	BC558	7
BC109A	14	BC572	13
BC109B	13	BD115	30
BC109C	11	BD116	65
BC114	12	BD124P	60
BC116A	12	BD124-2N3054	60
BC140	32	BD131	33
BC141	26	BD132	35
BC142	21	BD135	40
BC143	24	BD135	26
BC147	9	BD136	27
BC148	9	BD137	23
BC149	9	BD138	23
BC157	11	BD139	28
BC158	9	BD140	30
BC159	10	BD144	£1.20
BC180	25	BD182	70
BC181	28	BD183	65
BC170B	10	BD201	85
BC171	9	BD202	80
BC171A	10	BD203	80
BC171B	10	BD204	84
BC172	9	BD222	47
BC172A	10	BD222	46
BC172B	10	BD232	45
BC172C	10	BD233	35
BC173B	12	BD234	31
BC174B	10	BD235	31
BC182	9	BD236	31
BC182B	10	BD237	31
BC183A	12	BD238	33
BC183LA	10	BD232	£1.50
BC184	9	BDY 20	20
BC184LA	10	BD115	35
BC204	9	BF127	26
BC208	13	BF154	12
BC209	10	BF158	18

ALL GOODS ARE BRAND NEW

SEMICONDUCTORS

Type	Price (p)	Type	Price (p)
27 BU326A	£1.42	CA3065/ETT6016	
24 BU407	£1.25	ML232B	£2.20
22 E1222	28	ETR6016/1	
26 MJE340	40	ML231B	£2.20
28 MJE520	44	MC1307	£1.00
30 BC214	9	MC1327	£1.00
36 OC79	15	MC1349	£1.20
30 R2008B	£1.80	MC1351	£1.00
30 R2010B	£1.80	MC1352	£1.00
30 R2285	£1.40	SAS5605	£1.80
30 R3222	58	SAS570S	£1.80
11 R2323	67	SL901B	£4.45
10 R2461	£1.50	SL917B	£6.25
10 R2540	£2.80	SL1310	£1.80
15 BF198	15	SL13270	£1.20
15 BF198	15	SN76003N	£1.75
15 BF199	15	SN76013N	£1.15
30 BF200	30	SN76023N	£1.45
16 TF31C	41	SN76033N	£1.53
15 TF32C	42	SN76110N	£1.30
28 TF41C	46	SN76131N	£1.30
25 TF42C	47	SN76227N	£1.50
26 TF47	70	SN7633N	£1.10
24 TP2955	90	SN76533N	£1.30
12 TP3055	63	SN76544N	£1.35
9 BF274	21	SN76544N	88
36 TIS91	21	SN76566N	70
30 TV106/02	£1.20	TAA550	28
34 ZN696	19	TAA570	£1.80
37 ZN7905	22	TAA661B	£1.20
37 ZN7905	22		
60 ZN3054	60		
33 ZN3055	60		
20 ZN3702	11		
23 ZN3703	10		
24 ZN3704	10		
35 ZN3705	10		
28 ZN3706	10		
27 ZN5294	38		
60 ZN5296	48		
30 ZN5298	38		
27 ZN5496	53		
28 ZSC643A	£1.50		
28 ZSC1172Y	£2.20		
25 CRYSTAL			
20 4.43MHZ	£1.30		

INTEGRATED CIRCUITS

Type	Price (p)	Type	Price (p)
TA4119	£1.70	TAA700	£1.70
BA102	17	TAA700B	£1.70
BA115	13	TAA700C	£1.70
BA145	17	TAA700D	£1.70
BA148	17	TAA700E	£1.70
BA154	6	TAA700F	£1.70
BA155	14	TAA700G	£1.70
BA156	15	TAA700H	£1.70
BA157	14	TAA700I	£1.70
BA158	14	TAA700J	£1.70
BA159	14	TAA700K	£1.70
BA160	14	TAA700L	£1.70
BA161	14	TAA700M	£1.70
BA162	14	TAA700N	£1.70
BA163	14	TAA700O	£1.70
BA164	14	TAA700P	£1.70
BA165	14	TAA700Q	£1.70
BA166	14	TAA700R	£1.70
BA167	14	TAA700S	£1.70
BA168	14	TAA700T	£1.70
BA169	14	TAA700U	£1.70
BA170	14	TAA700V	£1.70
BA171	14	TAA700W	£1.70
BA172	14	TAA700X	£1.70
BA173	14	TAA700Y	£1.70
BA174	14	TAA700Z	£1.70
BA175	14	TAA700A	£1.70
BA176	14	TAA700B	£1.70
BA177	14	TAA700C	£1.70
BA178	14	TAA700D	£1.70
BA179	14	TAA700E	£1.70
BA180	14	TAA700F	£1.70
BA181	14	TAA700G	£1.70
BA182	14	TAA700H	£1.70
BA183	14	TAA700I	£1.70
BA184	14	TAA700J	£1.70
BA185	14	TAA700K	£1.70
BA186	14	TAA700L	£1.70
BA187	14	TAA700M	£1.70
BA188	14	TAA700N	£1.70
BA189	14	TAA700O	£1.70
BA190	14	TAA700P	£1.70
BA191	14	TAA700Q	£1.70
BA192	14	TAA700R	£1.70
BA193	14	TAA700S	£1.70
BA194	14	TAA700T	£1.70
BA195	14	TAA700U	£1.70
BA196	14	TAA700V	£1.70
BA197	14	TAA700W	£1.70
BA198	14	TAA700X	£1.70
BA199	14	TAA700Y	£1.70
BA200	14	TAA700Z	£1.70

SOCKETS


8 pin	24
14 pin	18
16 pin	20
14 D/I/O	24

ELECTRONIC TUNERS

Type	Price (p)
AEG/NSF equivalent to ELCT043/05	£7.10
ELCT043/06	£7.10
4 way P/B for Decca etc	£5.80
6 way P/B for Decca etc	£7.00
4 way P/B for Pye 713	£3.00
6 way P/B for Pye 201	£16.00
GB Tuner	£10.50

SERVICE AIDS

The Hitachi GP4 Colour Camera

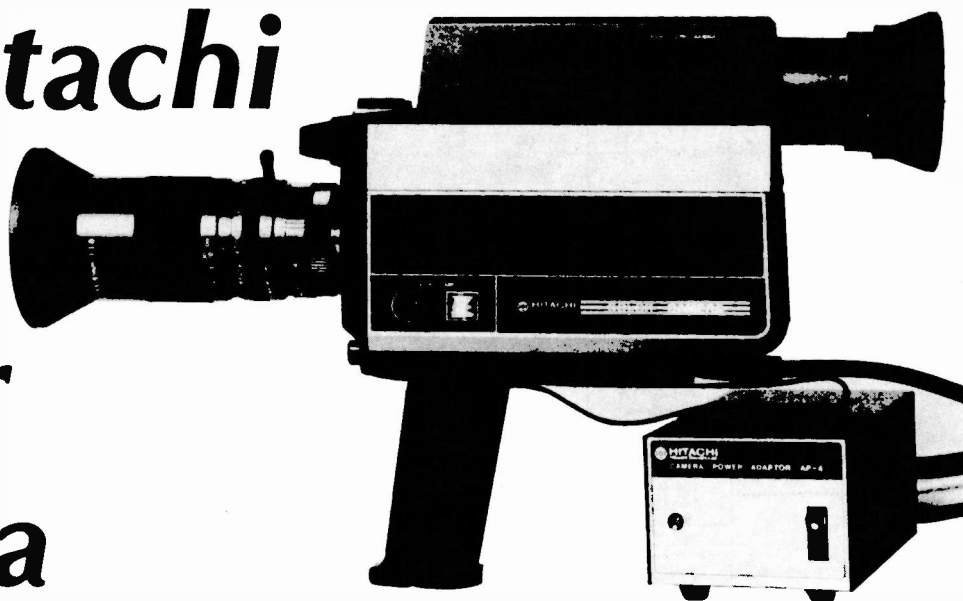

David K. Matthewson, B.Sc., Ph.D.

THE Hitachi Model GP4 is one of the latest colour cameras to be launched on the domestic video market. It's available in two versions, the GP4B and the GP4D, the former having an f2 2.8x zoom lens and an optical viewfinder whilst the latter, de luxe version has an f1.8 6x zoom lens and an electronic viewfinder which can also be used to provide instant videotape playback with a suitable VTR. The two models are otherwise identical, so we'll look at the GP4D here.

Hitachi introduced the earlier GP5 (or VKC500 as the domestic version was known) colour camera in late 1978 – regular readers will recall our review of it this time last year. It was one of the first colour cameras to be aimed at the home video market. Several lessons have clearly been learnt from that earlier model and incorporated in this latest one. The main selling feature of the GP4 however is a non-technical one – its price. The suggested retail price of the basic version is £330 and of the de luxe version £450, excluding VAT. The SRP for the de luxe GP5 is £729. These prices make the GP4 one of the cheapest colour cameras available – and that's before the discount houses get their hands on it.

Features


We'll look first at the features offered by the GP4, then at some of the technology inside it. In all honesty, there's little to choose in terms of facilities offered between several similar cameras available from a number of manufacturers. The GP4D has most of the features normally found, plus one or two special ones.

The basic camera weighs around 2.2kg and has a nice balance to it – it's rather like a large super 8mm cine camera. The 6x zoom lens covers 13.5 to 81mm and has a maximum aperture of f1.8. The iris ring on the lens can be turned to a capped position to stop light falling on the tube – this feature can also be used to fade scenes in and out. A feature not found previously on domestic cameras is the lens macro position, which allows objects between 10-30mm away to be clearly focused – useful for shots of flowers, small captions etc.

A single multicore lead connects the camera to either a portable VCR, such as the Hitachi VT7000, or a mains power supply unit which is available as an optional extra (at

a SRP of £27 plus VAT). The lead terminates in the new standard VHS 10-pin locking plug – at last the major video manufacturers have agreed to a joint standard for pin configurations and locking mechanisms. Even Sony, who employ a 14 wire lead, are producing a special 10 to 14 pin adaptor lead to enable this type of camera to be used with their Betamax VCRs such as the C7 and the SL3000 portable. A remarkable display of cooperation for once.

The electronic viewfinder can be added as an extra to the basic camera. It has a large and rather uncomfortable rubber eye-cup which encloses a plastic lens facing on to a 1in. c.r.t. This acts not only as a focusing aid but also as a playback monitor, a slide switch on the side of the viewfinder switching between playback and camera viewfinder use. There's also provision for audio monitoring via an adjacent earphone socket. Unlike some other cameras, the viewfinder lens and eye-cup cannot be focused for users who wear spectacles, nor can it be flipped back to allow several people to view videotape playbacks. There are three warning LEDs in the viewfinder. These indicate low battery power, low light and VTR running. Screwdriver adjustable presets allow the contrast and brightness of the viewfinder picture to be altered without affecting the signal from the camera to the VTR.

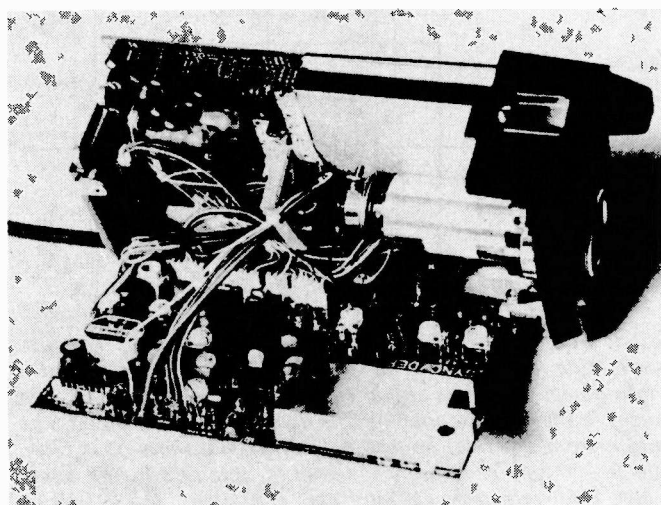

Innards of the Hitachi GP4D colour camera.

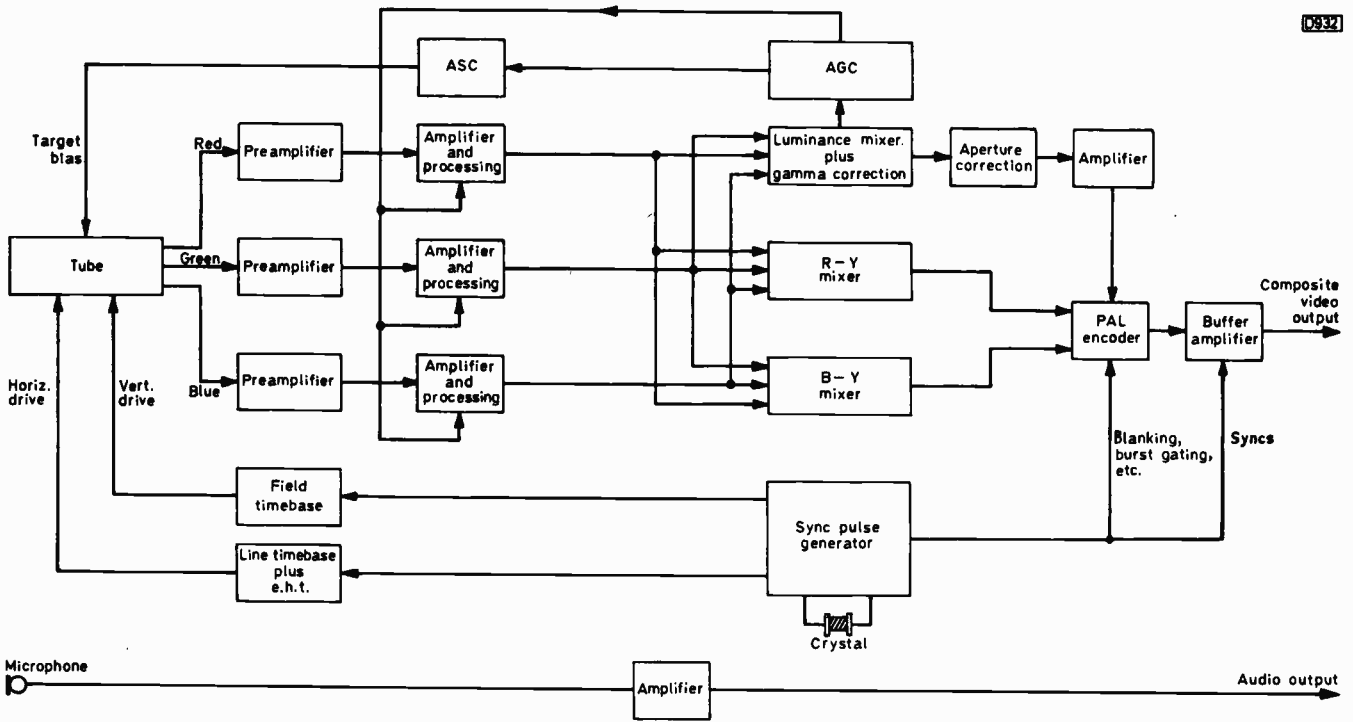


Fig. 1: Block diagram of the Hitachi GP4 colour camera.

A small, omnidirectional capacitance microphone is mounted above the lens. It can be switched off by plugging an external microphone into a socket on the right-hand side of the camera's body - any high-impedance microphone with a sensitivity of around -65dB is suitable. An accessory

shoe on the top of the camera enables suitable models to be secured.

Another switch at the rear of the camera introduces an increase in video gain of some 3dB for recording under low-light conditions. Use of this extra gain increases the noise however, so it should be employed only when essential.

The final user controls are concerned with balancing the electronics within the camera to get correct operation under different lighting conditions. With the GP5 and cameras from several other manufacturers this adjustment is carried out by watching the camera's output on a colour monitor, altering the colour temperature control until a satisfactory picture is obtained. This is not always possible under field conditions of course, and can be a problem under varying lighting conditions. The GP4 has a neat arrangement with a centre-zero meter and a single potentiometer. The camera is pointed at a white card and the control adjusted to zero the meter. This ensures that regardless of the type of lighting present, from normal daylight through overcast daylight to various types of artificial lighting, the fidelity of the output obtained from the camera remains constant.

The camera I tested was quite good without being exceptional. It did everything claimed for it, and provided generally good colour rendering. The automatic sensitivity

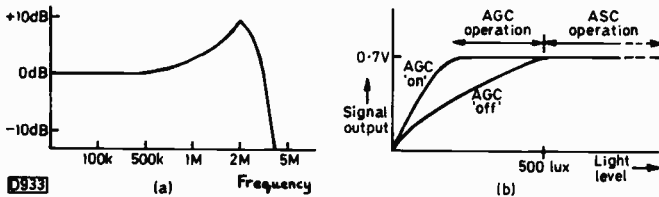


Fig. 2: (a) The frequency characteristic of the aperture correction circuit in the luminance channel - a non-linear amplifier copes with h.f. loss in the tube system, effectively improving the camera's resolution. (b) Gain/light level characteristics of the a.g.c. and a.s.c. circuits.


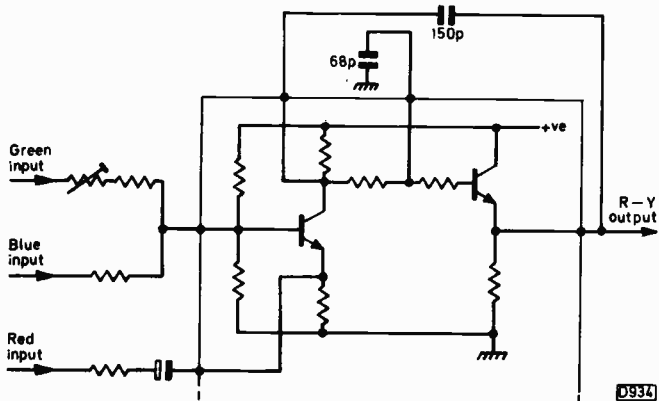


Fig. 3: Obtaining the R-Y colour-difference signal. The first stage adds the G, B and R signals in such a manner that a white object produces signal cancellation, i.e. no output. The preset in the G input enables this balance to be obtained. The output from the first stage then passes via a low-pass filter. The B-Y colour-difference signal is obtained in the same way. The relevant circuitry is contained in IC105 - type ZC0226.

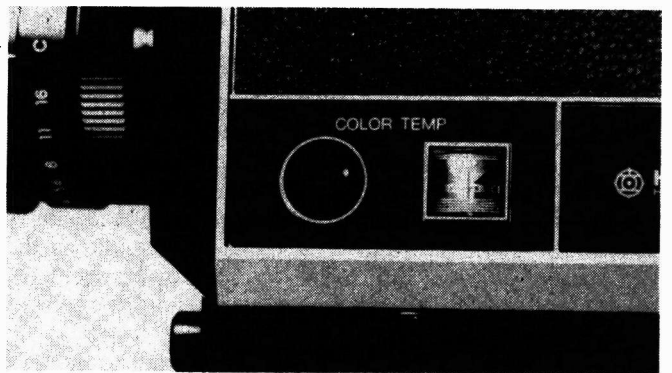

The colour temperature control and meter on the side of the camera.

circuits worked well under a range of lighting conditions, giving acceptable pictures at down to around 300 lux. Below this the results were rather muddy, but with the sensitivity control set to the high position a colour picture could be obtained at around 100 lux. For optimum results, around 2,000 lux was required at f4 – i.e. mid-morning overcast English weather. According to Hitachi the camera is designed to give optimum results at around 2,000 lux, 60 per cent reflectivity with a colour temperature of 3,000°K (i.e. tungsten lighting).

My main complaint about the picture is the apparent over enhancement of the high frequencies, presumably done to give an apparently better resolution. This tends to give rather a cardboard cutout effect. In all fairness however the camera does give very reasonable pictures, and at the price one can't complain.

The Electronics

The electronics within the camera are arranged on five printed panels. The two main ones house the sync, deflection and video circuits. The three other ones are for filters and switches. All these boards are built to the high standards one comes to expect from Japanese equipment. A block diagram of the camera is shown in Fig. 1 – the arrangement is similar to that used in the GP5, but the use of custom designed i.c.s has considerably simplified matters. The tube is a $\frac{2}{3}$ in. tri-electrode type, providing RGB output signals. This type of tube provides very good colour fidelity.

A single i.c. for each channel (red, green and blue) provides most of the amplification and the initial signal processing, including automatic level control, clipping, clamping and gamma correction. The clipping and clamping circuits fix the signal peak white and black levels respectively and don't have any special design features, while gamma correction is conventionally required to compensate for the tube's non-linear response. The automatic video signal level control is rather clever however, being built around two interrelated circuits (see Fig. 2), a.g.c. (automatic gain control) and a.s.c. (automatic sensitivity control). The a.s.c. circuit senses the level of the luminance (Y) signal, and increases the vidicon's target voltage as the video signal level falls. This in turn increases the signal current, restoring the video output level. The a.s.c. circuit operates when the light level is reasonably high. When there is less light, the a.g.c. circuit is brought into play. This circuit can cope with a difference in light level of about two lens stops, and works by altering the gain of the amplifiers in all three channels simultaneously. The high/normal sensitivity switch at the back of the camera effectively switches the a.g.c. to "on" (high) or "off" (normal).

IC105 produces the R-Y and B-Y colour-difference signals from the RGB signals. These two colour-difference signals, along with the Y signal, then go to the colour encoder where they are turned into a composite PAL (or NTSC) colour signal. Fig. 3 shows the way in which the colour-difference signals are obtained.

The sync pulse generator consists of a single CMOS chip (see Fig. 4) which is driven by a four times subcarrier frequency crystal. Division gives the 4.43361875MHz subcarrier and also the correctly phased B-Y and R-Y subcarriers. The i.c. also gives composite sync, line drive, field drive, burst flag and various blanking waveforms.

It's interesting to note that for NTSC use only six component values have to be changed and a wire link on the panel altered. But then the Japanese do design their equipment for world markets!

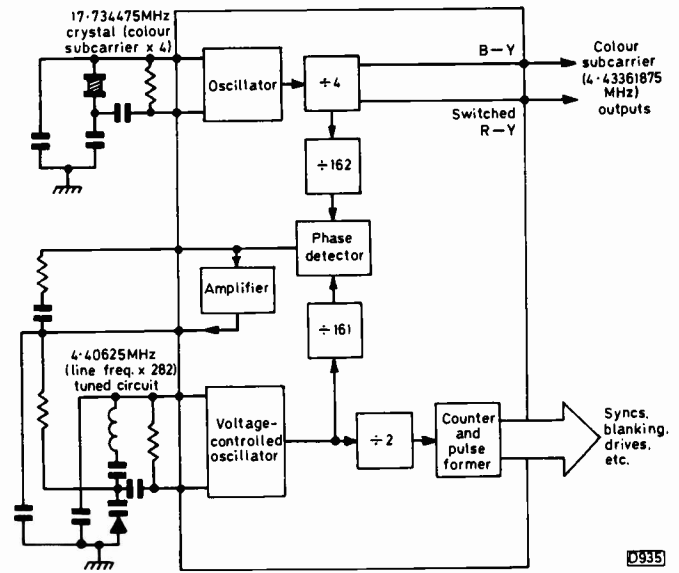


Fig. 4: Block diagram of the HD440071 sync pulse generator i.c., which is driven by a four times colour subcarrier frequency crystal.

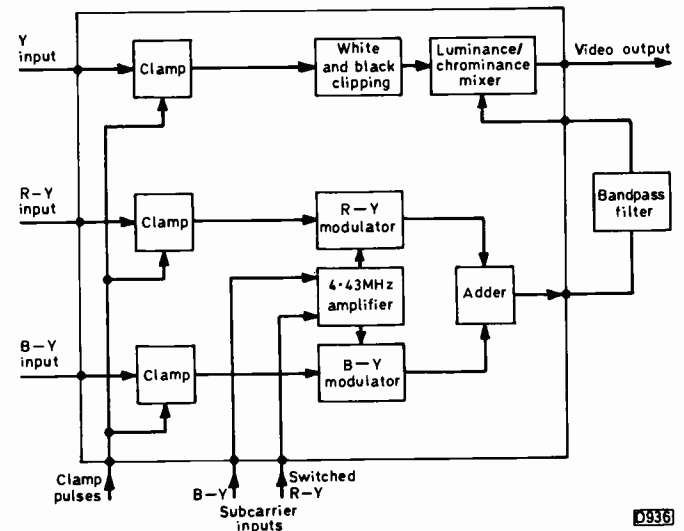


Fig. 5: Block diagram of the HA11720 colour encoder i.c.

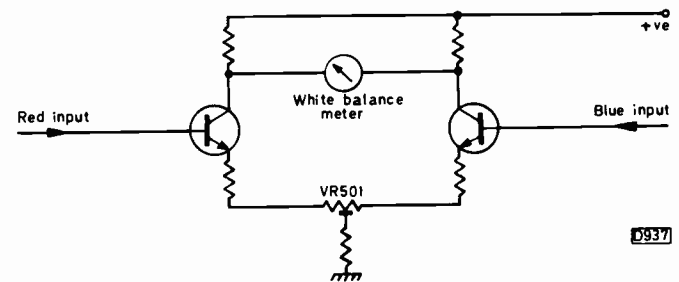


Fig. 6: Colour temperature meter circuit. VR501 is used to set the black balance with the lens capped up. When a true white signal is present the R and B signals will be equal and the meter will give a centre zero reading. The user colour temperature control at the side of the camera alters the gains of the R and B channels to achieve the correct balance.

The PAL coder is another area that's benefited from the use of i.c.s. A single CMOS i.c. is used here, type HA11720 (see Fig. 5).

The colour temperature meter circuit (Fig. 6) measures the difference between the red and blue signals. When the two are present in equal amounts, as they should be with the

meter focused on to a white card, the meter is centred. The colour temperature control provides differential adjustment of the gain in the red and blue channels, the green gain being kept constant.

The deflection and e.h.t. circuits are quite standard and operate on similar principles to those used in domestic TV sets.

Summary

In conclusion, it's a well designed camera that incorporates most of the features required for domestic use. It lacks the sophistication of say the Sony HVS200P, but you get very similar picture quality at a price of around £200 less. I'd say it's a good colour camera to start off with, for domestic use or for use in schools etc.

A Novice's Viewpoint

As an additional check, I decided to get a novice's viewpoint. Here it is – thanks Kate!

The camera is apparently designed with us non-technical, inexperienced users in mind, so I was interested to have a go. Its weight was the first factor that struck me – it's too heavy to hold comfortably for long. Immediately the camera was switched on very good pictures were obtained –

and acceptable pictures were present at very low light levels. The warning lights in the viewfinder seem a good idea – especially the low light level one. The rubber eyepiece is convenient, particularly as I wear glasses.

Manipulation of the zoom lens seemed straightforward at first, but proved difficult in practice because it couldn't be operated smoothly while wilting under the camera's weight. Focusing on maximum zoom was not too satisfactory, as the viewfinder picture is too grainy for my unpractised eye. I could have spent ages fiddling with this while any subject other than a snail passed by.

Further problems relating to the camera's weight – and I'd better mention that I am myself no little 'un – were experienced when operating the colour balance control. Keeping the camera fixed on the white card while looking at the meter at the same time presented difficulties. A needle in the viewfinder, as with a 35mm camera, would be a big improvement.

The macro lens seems to be a good idea for close ups of small objects – though I'm not too sure of what exactly. But it was not possible to hold the camera sufficiently still at close range to get a reasonably steady shot. A tripod or rest is definitely called for here.

It's a simple camera to operate, but one can't expect spectacular results in the hands of an inexperienced user. Practice and the use of a tripod are required. ■

VCR Clinic

Steve Beeching, T.Eng. (C.E.I.)

Shifting Chroma

As I've said before, the same symptoms can often be caused by various different faults. We've had three cases recently where the colour part of the picture, observed when replaying a test card, moved sideways with respect to the luminance display then back again. This fault is usually very sluggish, sometimes rhythmic and sometimes very intermittent, and I should point out straight away that the cause can sometimes be determined only by measurement using the VHS jig kit of special alignment parts (all these faults were on HR3330 and similar machines).

A very rapid shift could be seen with the first case – a pointer to the drum servo rather than the capstan servo. So the drum servo ramp and sample pulse waveform was examined. This showed that the drum was shifting. On replay this servo is locked to the signals on the control track, and is thus influenced by the tape speed and hence the capstan servo. So the check had to be carried out in the record mode.

Now the drum servo waveform is normally very stable in the record mode, the sample pulses on the ramp coming from the transmitted syncs. So if the ramp is shifting, with a wobble, the cause of the trouble is variations in the rotation of the drum. I've found that the best approach to this problem is to disconnect one of the leads to the motor and then feed it with 6V via a meter – initially on the 1A range as the motor works up to speed, then on the 100mA range. The reading thus obtained should be between 40mA and 80mA, though it's subject to a wide tolerance range. Anyway, in the case in question the motor current was varying between 60mA and 100mA instead of being stable, thus proving that the motor was at fault.

In the second case the customer sent us a tape along with the machine. On the tape there was a test card which revealed regular colour shifts – quite large errors in fact. No variation in the drum servo waveform could be detected on record, and the drum motor current was a steady 50mA. Attention was turned to the capstan servo therefore. It's no use looking at the waveform, because nothing will show up. So I checked the capstan motor current, which was found to be 65mA, varying by $\pm 1-2$ mA. Was this the cause of the trouble, or was it a red herring? Another capstan motor was tried, and this time the current was 110mA. The variation was less, but was still there.

It's at this point that the test kit starts to be useful. I put in the back tension gauge, and the measurement went off the scale. This was the problem then, too much back tension – the supply reel skidding on the tight brake band, so that there were variations in the tape tension. I'd better mention that I was using my own test tape for the checks, as the customer's one had the errors recorded on it.

On these machines there's a test point (TP8 on the audio/servo board) at the output of the drum servo sample

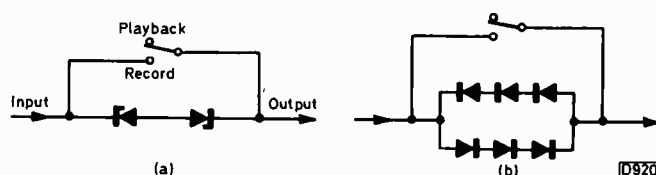


Fig. 1: The non-linear circuit (transistors X5/6/7) in the drum servo circuit used in the HR3330 is like two back-to-back zener diodes (a) or a diode string (b).

and hold circuit. This point sits at 4-4.6V d.c., and varies up and down. The variation should not be more than $\pm 0.25V$, or within 1cm on a scope set to 0.5V/cm on an a.c. range. If the variation on playback is greater, the limit set by a non-linear circuit (see Fig. 1) is exceeded and an error signal is sent to the motor drive circuits, the servo then shifting. What happens is this. If the tape speed or tension in the record mode varies, the control track pulses are recorded with a variation and the playback varies. If the playback drum servo variation is greater than normal, the excursions go outside the limits, the motor kicks and the colour shifts away from the luminance and back again. The symptoms can be erratic and intermittent, depending on whether the error level is sufficient.

The tape tension on the recorder in question was adjusted, and stability achieved. The original capstan motor was then replaced, the capstan sample pulse position was set and a test recording made. The tape transport was stable, with no noticeable colour shifts. The back tension had been well over 60gm/cm, when it should have been between 28-45gm/cm.

On the third machine the cause of the trouble was found to be the edges of the tape creasing on the tape guide next to the audio head. If the edges of the tape crinkle, the control track head-to-tape contact is erratic. This results in control track pulse timing variations, and the effects previously discussed. The only way to overcome this problem is first to check the height with equipment in the jig kit. Don't adjust the guide. It's most likely that the pinch wheel is not parallel with the capstan drive spindle: a special tool is required to adjust it.

No Colour

Two VHS machines came in recently with the no colour fault. The first one I looked at replayed a known good recording in monochrome, but with a herring bone type of patterning. This patterning cleared when the switch at the rear of the machine was moved from the colour to the monochrome position, indicating that the colour was being replayed but that there were phase errors in the colour signal processing circuitry such that the colour killer was not operating.

The way in which I tackle this sort of thing is to look at the balanced modulators and work back to the phase-locked loop and the basic voltage-controlled 2.5MHz oscillator – the circuitry was described in some detail in the May 1980 issue. As in the previous case, we found that there were no sync pulses from the servo panel (these are used in the phase-locked loop). So a check was made on the servo panel, where it was found that there was no video signal. Back to the luminance/colour panel therefore, where we had plug and socket problems on connector 83.

The trouble with the second machine was rather different. The monochrome replay was clean and was not affected by the colour/monochrome switch at the rear. Checks were made on the balanced modulators and the phase-locked loop, but everything was in order. So we traced the colour signal from the output of the second balanced modulator to the two-line delay line, where there was a distinct lack of input signal. Further tests showed that the emitter-follower transistor X204 had an open-circuit emitter.

Mostly Panasonics

We've had several Panasonic machines in recently. An NV8030 time-lapse machine required new video heads, which are not too easy to fit since they require dihedral adjustment, i.e. adjusting the video head assembly so that it's not off centre, using a gauge on the circumference as with Betamax machines. An NV3160 reel-to-reel $\frac{1}{2}$ in. tape machine had

been serviced by others and had not been right since. It required a series of adjustments to the book, then a final tweak based on experience to ensure that the replay colour picture was free from noise. I was quite pleased with this one, and so was the customer.

An NV7000, Panasonic's latest, came in with the complaint that the tape speed was varying, suspect capstan servo. I spent some time checking through the capstan servo. All very complicated – the simplified block diagram more complex than the circuit, with direct drive as well as 120° phase-shifted drives. Yours truly getting nowhere, so time for coffee. Sup, sup, slurp. Hello, what's that funny clunking noise in the top of the recorder? I'm sure the pinch roller shouldn't be moving backwards and forwards like that! Puts coffee down. Inside the top, the tape drive capstan shaft was bent. By about 30°. No wonder the capstan servo was all over the place. My next thought was of the complex task of removing the capstan direct drive motor. But no, just two plugs, three screws and out it came. Aren't these Panasonics nice to service?

More than can be said for the Sony SLC7. I've had two for evaluation. The first one refused to play my new Blondie "Eat to the Beat" cassette – there was a phase fault in the colour replay circuit. So back it went. The second one was much better till the tape rewound to the beginning. What was that bleeping sound? Why did the recorder keep trying to rewind – it was already there? If in doubt, panic! This machine had brain failure. The end of the tape alarm, which should bleep only at the end of the tape, not the beginning, was going off. After each ten second bleep, rewind would operate. But the tape was already rewound. Then the alarm sounded, and so on. At five-ten minute intervals. I decided to have a look at the microprocessor board – if I could find it. When I did I took the only corrective action possible – put the machine in the box and sent it back. Sony seem to have gone back to the dark ages with the SLC7. It's an attractive machine and performs very well when working correctly, but from the servicing point of view it's a nightmare to get at. The out of guarantee servicing costs are going to be high. Very high.

Next another Panasonic NV7000, which wouldn't record sound. A good look at the picture showed that it wasn't erasing either. A minor fault. The switching is solid-state in this machine, with a transistor used to switch the power to the erase oscillator in the record mode. The transistor has a 3V zener diode between its base and emitter to prevent reverse bias breakdown – the zener diode was short-circuit, with the result that the transistor could not switch on.

The JVC HR7700

Some information has arrived on the new JVC HR7700. Wow! Twin-loop servos, a direct drive motor for the video heads, and four more motors – for capstan, reel drives, threading and cassette lift. The most remarkable feature however is the back-space editing. When the machine is put into the record pause mode, it rewinds twenty frames. After being released back into record it plays for twelve frames to lock the servos and phase the incoming video with the control track pulses, then edits over the recording for the last eight frames. The edits take place within a frame and are beautiful.

What's the Name of that Shop?

Finally, my Newark Video Centre is now open. It's also my intention to run more frequent video courses from there for those TV service engineers who want to learn more about video. Oh yes, and to launch more receiver/monitors on to the market for video and hi-fi enthusiasts.


Long-distance Television

Roger Bunney

LAST month I expressed the hope that F2 propagation conditions would improve this winter. Fortunately the improvement has already started, producing quite dramatic signals in most parts of the UK. Signal strengths have been such that even the most modest of DX-TV installations have been rewarded with signals from afar – from as far distant as Australia! Apart from F2, Sporadic E and tropospheric openings have also provided signals, and in fact during the two decades I've been DXing I've never experienced a more eventful month than the one under review.

I'll deal with tropospheric reception first. The prevailing high pressure systems during late September/early October produced widespread reception, particularly along the south and east coasts, from France, the Low Countries and West Germany. Conditions improved during October 1st-3rd, giving reception from Switzerland, Austria and the southerly parts of West Germany. The 3rd produced quite dramatic signals via tropospheric ducting from Switzerland, throughout Bands I and III and at u.h.f. It's the first time that the Swiss channels E2, 3 and 4 have been received at high strengths in the UK via tropospheric propagation. The signals included Grunten ch. E2. Hugh Cocks in East Sussex had these signals at overloading strengths! Here at Romsey (South Hampshire) I was pleased to receive four Swiss stations not previously received, including La Chau de Fonds ch. E9 (4kW) and Niederhorn ch. E12 (5kW). Cyril Willis (Cambridge) received RTL (Luxembourg) transmitting 625-line System G signals on ch. E27 to Belgium – a rare catch.

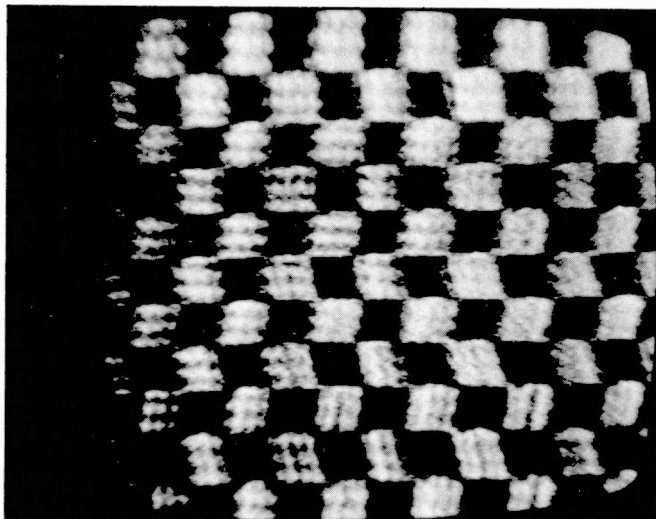The ducting area was relatively limited, with ORF (Austria) just visible here above the noise (ch. E5). Optimum reception seemed to be from around 0900 BST and throughout the morning of the 3rd. At Hugh Cocks' location reception continued into the 4th, but an approaching cold front effectively killed off further tropospheric reception during the night here at Romsey.



The Chinese checkerboard test pattern, received by Anthony Mann in Australia on ch. R1.


Hugh logged numerous West German u.h.f. stations and East German transmitters at v.h.f./u.h.f. Perhaps his most dramatic reception was of the 525-line System M signals transmitted by AFRTS (American Forces network) from Vogelweh on ch. E30 (3kW). At 1100 however the cold front arrived in East Sussex and activity ceased.

Excellent F2 Conditions

F2 conditions improved sufficiently from October 10th to give the first really distant TV signals, with TSS (USSR) present for several minutes during the morning. The intensity and variety of the signals increased during the next few days, with sightings of African transmissions and longer duration signals from the Eastern USSR. Hugh Cocks noted a suspected Kenyan signal (ch. E2) at 1600 BST on the 12th, then Russian ch. R1 and African ch. E2 signals on the 13th, trailing the first substantial opening on the 14th. From 0745 BST on this day I logged very strong Russian ch. R1 signals, both test pattern and programme, all suffering from the characteristic smearing and multiple images. Whilst talking to Hugh on the phone it became apparent that signals which were very strong in Hampshire were present though barely visible at noise level in East Sussex. This factor was noted in subsequent F2 openings, and seems to be due to increasing ionisation of the F2 layer. When the F2 opening starts, the critical frequency is such that only a very shallow v.h.f. signal can be reflected. Then as time progresses and the ionisation increases, there's a sharper angle of reflection for the same signal, the range decreasing. During this opening the signals lasted until mid-morning.

On the 18th, fortunately a Saturday, strong signals put in an appearance from 0815 BST on ch. E2 – the familiar PM5544 test pattern. This changed to a test chart with Arabic writing at 0830, then a clock (stating 1200) at 0900 followed by an Arab newscaster. Reception of this signal has been widely reported – it appears to have come from Dubai on the Gulf. During the afternoon, strong ch. E2 African signals were logged. African signals were again present on the following day – two on ch. E2, one of a football match (now known to have been from Ghana) and the other an RMA monochrome test card (suspected to have come from Nigeria).

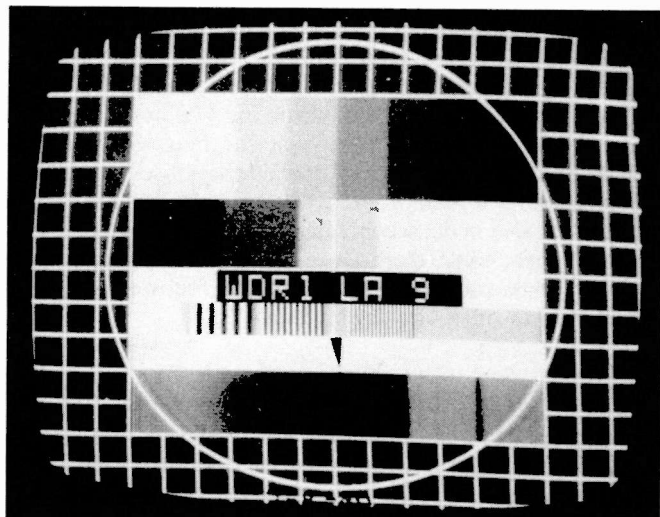The North Atlantic path has not so far provided any ch. A2 signals, though there have been highway patrol signals at up to 50MHz. African signals were present on most days following the reception mentioned above, and on the 23rd



The new WDR Fubk test pattern with identification LA9, indicating Langenberg ch. E9. Photo from Ryn Muntjewerff.

strong Dubai type programmes were present from 1330 preceded by colour bars and the PM5544 pattern. The 24th and 25th both gave incredible signals from Russia, Dubai and Africa, but perhaps the most exciting event was Hugh Cocks' reception of the Australian ch. A0 from 0935-1015. The signals were generally of poor quality and suffered from severe interference from Russian signals.

On Sunday the 26th, the USSR ch. R1 signals were relatively late in putting in an appearance – at 1031 GMT (clocks changed to winter time) – but there then followed nationwide F2 conditions. A very strong ch. E3 signal was noted during the morning, reappearing at 1350 and 1500. Several enthusiasts report that it came from Nigeria, Andrew Tett apparently seeing the NTV caption. At 1545 there was a very strong test pattern on ch. E3, while on ch. E2 sound there was a commentary on a football match between Accra and Tamale of the Ghana premier division. The accompanying vision was for most of the time at or below the noise level. Strange indeed. Finally on the 27th Russian signals with the usual ghosting/smearing appeared at 0815, then ch. A0 vision rose above the noise. Hugh Cocks observed subtitled programmes (suggesting one of the new ethnic channels) and Mark Baldwin (Rugby) received relatively strong signals.

Summary

There were SpE openings on the 12th, 16th and 17th. Strong, but less noteworthy than the international TV via F2!

Many thanks to Hugh Cocks, Mark Baldwin, Brian Fitch, Ray Davies and others who reported on their reception during the period.

From down under Anthony Mann (Perth) also reports a very good month, with Chinese and East Russian reception, also ch. B1 audio on several occasions and a new one – North Korea ch. R2 (October 14th). Malaysia ch. E2 has also provided strong signals (I'd hoped to receive this in the UK!).

Let's hope that conditions continue to improve during November.

New EBU Listings

West Germany: Power reductions – Minden chs. 26 and 57 reduced from 500kW to 300kW, Muenchen chs. 35 and 56 from 500kW to 200kW.

Finland: Two new stations transmitting YLE-2 – Pyhatunturi ch. 25 650kW, Tampere ch. 53 1,000kW, both with horizontal polarisation.

News Items

Australia: Brisbane TV BTQ7 has commenced a full teletext service – called "Seventel"!

Canada: CBC is proposing to start a second programme which will be distributed via the Anik A3 satellite, at 4GHz, and relayed to viewers via cable operators. The tentative on-air start is September 1981.

South Africa: The SABC is to start a second network by January 1982, catering for those languages not covered by TV-1. A TV-3 network is also proposed.

Japan: The Yuri satellite, which was intended to provide direct TV broadcasting to viewers, has been taken out of service due to problems with the travelling-wave tubes. Tests are being carried out with a new satellite.

Italy: RAI have obtained court approval in Florence to resume full power transmissions. Apparently pressure from commercial broadcasters had earlier led the court to order a

GOLDEN ANODISED AERIALS: SUPERB ECONOMY AMPLIFIERS: ALL PRICES INCLUDE VAT.

Masthead Amps	Type	Gain	Price
Astrax 1456	A:B:C/D (TV)	10dB	£8.88
Astrax 1450 LN	Bands 4&5 (TV)	28dB	£15.49
Astrax 1455	Bands 1&3 (TV)	25dB	£16.81
Astrax 1470	Band 2 (FM)	25dB	£11.89
Astrax 1520	power unit for above amps		£9.15
i.e. An Astrax 1456 needs an Astrax 1520 =			£18.03


IMPORTANT Quote TVM

For highly graphic lists and Brochure Send 52p. Refund of 30p on 1st purchase over £5.

AGENTS FOR FUBA & MARGON

Stockists of the finest aerials available in Britain:

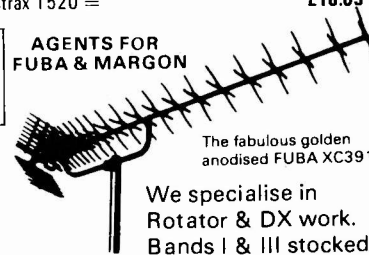STOLLE FM aerials (W.Ger.)
FUBA TV & FM aerials (W.Ger.)
MARGON TV aerials (Hol.)
UKW FM aerials (E.Ger.)
ANTIFERRENCE TV & FM aerials (U.K.)



The fabulous golden anodised FUBA XC391

We specialise in Rotator & DX work. Bands I & III stocked.

ASTRA (GOLDEN D.I.Y.) AERIALS

A friendly family firm. Our 25th. Jubilee Year.

SOME OF OUR SUPERB TV & FM AERIALS.

Name	Group:W/Band	Gain dB	Price	Discounted
Margon 103 (TV)	both	19.5/21.5	£61.41	£52.19
Margon 91 (TV)	both	18.5/20.5	£44.16	£37.53
Fuba 91 (TV)	both	18.5/20.5	£48.61	£43.75
Optimax 14 (FM)	Band 11 W/B	14	£57.50	£48.88
Optimax 8 (FM)	Band 11 W/B	9.5/10.5	£32.54	£29.29
Fuba 8 (FM)	Band 11 W/B	10.5	£40.85	£36.77

Over 3,000 aerials stocked, all transmitters; poles; flashings; rotators; clamps; wall brackets; amplifiers; diplexers; triplexers; notch filters; coax white or brown

Many of our customers come from recommendation.



53 WHITEHORSE ROAD, CROYDON, SURREY.

Nr. Spurgeons Bridge Tel: 01-684 4300
Open 9.00-5.30 TUE-SAT. 01-684 5262
Closed 12.30-1.30 Closed All Day Mon. 24 hr. answering service

FM & TV AERIALS AND ROTATORS ON DISPLAY


South West Aerial Systems

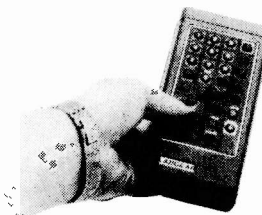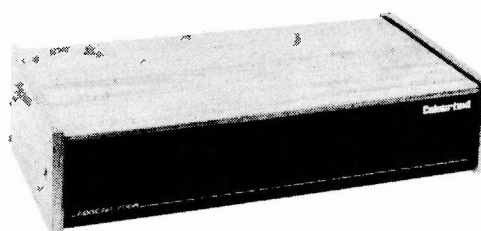10 OLD BOUNDARY ROAD,
SHAFTESBURY, DORSET.
SP7 8ND tel.0747 4370



The remarkable new Teletext adaptor from Labgear (model 7056) is available now from South West Aerial Systems. With one single connection to the receiver aerial socket, the adaptor

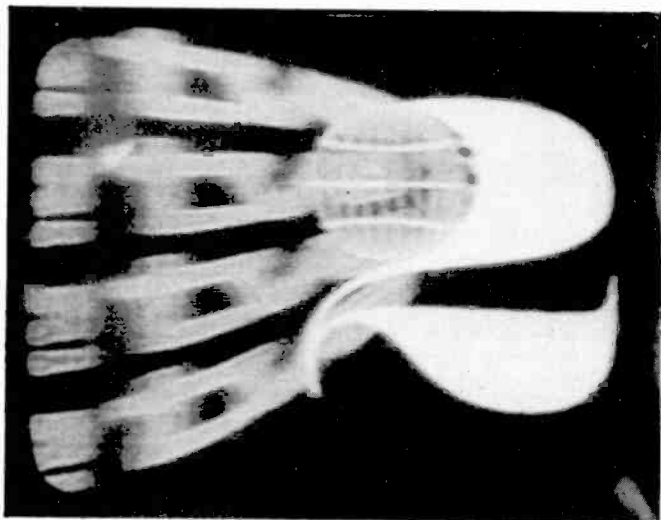provides full Oracle/Ceefax capability, cordless infra red remote control unit, double height characters, hi-fi sound feed and many more exclusive features. Send now for a fully descriptive leaflet (SAE). Our 1981 catalogue details an extensive range of aerials, amplifiers and accessories for all TV/FM installations (local, fringe and DXing) and costs 40p. Include SAE with all enquiries.



The RTVE-2 (Spain) identification slide, received by Ryn Muntjewerff (Holland) on ch. E2.

power reduction. When RAI's audience dropped to 44 per cent, RAI threatened to cease transmissions and the court reversed its earlier decision.

In brief: South Korea is to use the NTSC colour system . . . Chinese authorities in the Canton area have banned the viewing of Hong Kong TV – outdoor v.h.f./u.h.f. aerials are no longer allowed . . . The BFBS Rheindahlen, W. German TV studio has now been opened.

New Propagation Records

Roger Thorn (G3CHN) of Kingsbridge, South Devon had a two-way 144MHz contact via tropospheric ducting

with an amateur in the Canary Islands. The distance is 2,600km. On August 12th, amateur contact was made between Hartland, North Devon and Saint John, Newfoundland, again at 144MHz. The signals were weak but positive identification was established.

From our Correspondents . . .

Robert Copeman and Wenlock Burton report that the Australian ethnic TV service has now started – it's known as multicultural TV, with the call sign MTV. Test transmissions commenced on October 10th, with the start of programmes on October 24th. The PM5544 test pattern is used, with the identification "ch.0-28" at the top and "A World of TV" in the lower segment in Sydney and "ch.0-28"/"Melbourne" in the Melbourne area. Also in Melbourne, a student run educational service has been started on ch. 34.

During the tropospheric opening on October 3rd, Dave Kenny received Austrian and Yugoslavian radio transmissions in Band II.

Alexander Wiese has started a DX-TV club for European members. Publications will be in German. For details, write to PO Box 801965, 8000 Munich 80, W. Germany.

Following my mention of 430MHz amateur TV transmissions in the November column, John Wood has written pointing out that several Japanese portables can tune down to 70cm without modification and that the ELC2060 varicap tuner can also be tuned down to 430MHz without modification. Mark Baldwin, who lives near John at Rugby, receives John's transmissions using a Wolsey Colour King aerial, an ELC2060 tuner and a domestic TV set. Further information on modifying popular tuners was included and will be featured in a future column.

The Professional

COLOUR BAR GENERATOR kit

**TRULY
PORTABLE**

ONLY
£59.50
inclusive

*Compare the specifications with any kit or manufactured Colour Bar Generator on the market. Then compare the price. See Test Report in April 1980 Issue of Television.

***SPECIFICATION**

<p>(a) Line Frequency: 15,625 Hz±0.1%</p> <p>(b) Field Frequency: 50 Hz±0.1%</p> <p>(c) Interlace: 2:1</p> <p>(d) Subcarrier Frequency: 4.43361875 MHz</p> <p>(e) Colour System: PAL</p> <p>(f) Standard 75% Saturated 100% Amplitude Colour Bars, left to right: White, Yellow, Cyan, Green, Magenta, Red, Blue, Black</p>	<p>(g) Size 8"×5½"×1½" and weighs a mere 500g</p> <p>*Push Button Selection provides:</p> <p>(i) Peak White Raster</p> <p>(ii) Linearised Grey Scale</p> <p>(iii) Crosshatch</p> <p>(iv) Colour Bars</p> <p>(v) Red Raster</p> <p>*Direct connection to Television Aerial Socket</p>
---	--

* All kits are complete with a **PROFESSIONALLY FINISHED** Case, tinned, drilled and screen-printed P.C.B., step by step assembly instructions, and a simple setting up procedure (only **TWO** adjustments)

* No extras to buy, not even Batteries. It comes complete with its own re-chargeable battery and charger (Approx. 10 hours running time per charge)

* The backing of our After Sales Service Department

* V.H.F. Modulator also available

* Ready-built, aligned and tested for only £88.25, with a full twelve months guarantee

Also available with additional 1 volt p.p. 75 ohm video output. S.A.E. for details.

Prices inclusive of V.A.T. and Postage

INTRACEPT ELECTRONICS LTD.,

203 PICTON RD, LIVERPOOL L15 4LG
Tel: 051-733 3042

Getting Organised for Field Servicing

Harold B. Berkley, T.Eng. (C.E.I.)

TELEVISION servicing in the field calls for a different approach from bench servicing in the workshop. The time available per call is limited, and very often the conditions under which the repair has to be carried out are far from ideal. Field engineers tend to be "loners", with everyone adopting an individual approach – if you look in the estate cars of different engineers from the same company you'll find no two alike. Looking further, into the toolcases carried, you'll probably find even greater divergencies. Some of us are naturally neat, others not. Nevertheless there are some guidelines that can be of benefit to all and can be adapted to suit the individual's particular needs. The ideas presented in this article represent my own approach, based on ten years' experience of field servicing.

One major mistake is to carry too many tools, often duplicates, and to overstock with components. Apart from being costly and wasteful, this makes it difficult to find particular items when they are needed. The point is that time is the most precious thing for the field engineer: it should be spent diagnosing faults and carrying out repairs, not fumbling about in the back of the case for components or running to and from the car.

Several things can more conveniently be carried in one's pockets than in the toolcase. I carry a neon screwdriver, a small screwdriver suitable for adjusting potentiometers and a small double-ended metal trimmer in my shirt front pocket, and a reversible screwdriver, one end Pozidriv 2PT and the other flat, in a trouser or jacket pocket. The latter combines two screwdrivers in one and is ideal for removing set backs, some of which are held by a combination of both types of screw. The vast majority of European TV sets use Pozidriv screws, usually 2PT but also some 1PT. The Phillips crosspoint screwdriver is not a good fit, a point overlooked by those responsible for selecting the contents of some expensive toolcases. It can be difficult finding a reversible screwdriver with a Pozidriv rather than a Phillips section: I use one manufactured by Footprint of Sheffield, and find it just right for the job.

The number of small tools you need to carry in the toolcase is less than might be thought. I started field servicing in an area which included many high-rise blocks of flats – and it's no joke going from the twentieth floor several times for bits and pieces. This in fact is what got me interested in being well organised. The toolcase should enable you to deal with most situations, yet be easy to carry about. I carry one each of the following items in my case:


- Stanley Pozidriv screwdrivers, 1PT and 2PT.
- Pair of medium sidecutters.
- Pair of snip-nose pliers.
- Box spanners, 4BA and 6BA.
- Hexagonal nylon trimmer.
- Pair of tweezers.
- Dentist's mirror (very useful).
- I.C. extraction tool.
- Rechargeable soldering iron.
- Solder sucker.
- Small mains-operated soldering gun.
- Small rechargeable torch.
- And of course a multimeter.

The medium sized sidecutters can be used for fine work and should be strong enough for heavier cutting, e.g. chopping the lugs off smoothing capacitors. I find expensive small pliers and cutters unnecessary for field servicing, but others may have different opinions on this.

I've been using rechargeable soldering irons since they first came on the market. They are ideal for field servicing – no looking for mains sockets and extension leads, or waiting for the iron to heat up and cool down. I carry two in fact, one in the toolcase and the other charging from an adaptor in the car. There are several makes on the market. The Wahl iron I use has rather fragile bits, but the ones sold by Tandy for their irons can be used instead and are very robust. One iron of particular interest is the "Scope" one made in Australia and imported by Toolrange Ltd. It uses a patented "carbon arc" principle, but I've yet to try one. Rechargeable irons can be used only for light soldering of course, so as a standby a soldering gun is useful. The Ersa Sprint is small enough to fit in the tool case yet still gives 150W.

If you're starting from scratch, why not take the plunge and invest in a digital meter with LCD display? Tandy have one that retails for £49.95: it's an excellent meter with an Ohms range that goes up to 20MΩ. What no one tells you about digital multimeters however is that they are pretty useless for making cold checks on semiconductor devices – the old forward and reverse resistance checks on diodes and transistor junctions. You just get confused. So you will also need a small, cheap and nasty meter with an Ohms range for testing semiconductor devices.

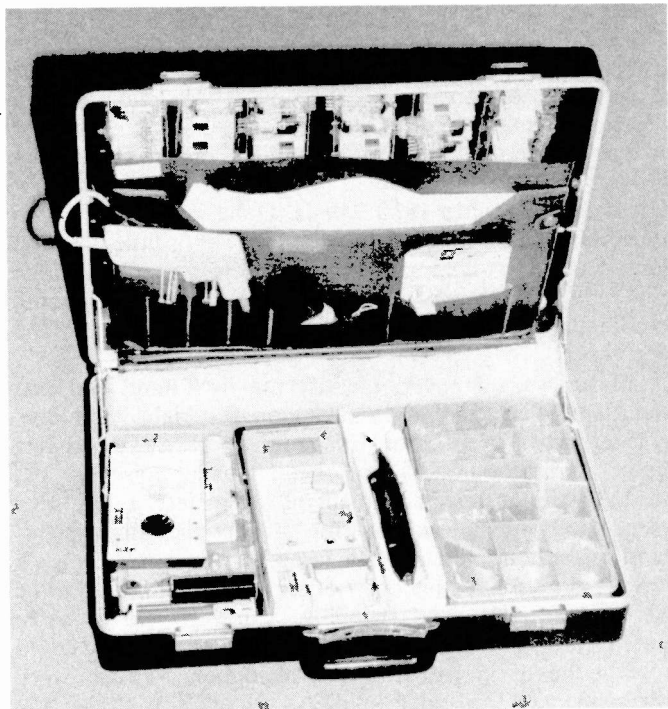Another gadget worth carrying is a simple battery tester (try Tandy). This is a recent addition to my kit, being handy



Everything you need to take with you – conveniently arranged in a Custom executive briefcase.

for use with sets featuring remote control – it's worth testing the batteries in the transmitter unit before getting involved in fault-finding in the remote-control circuitry.

So much for tools. What about components? Contrary to the belief in some quarters, the valve is very much alive so far as the field service engineer is concerned – a fact that Philips seem to have overlooked in their latest toolcase. I bought one of their cases some years ago. It had special plastic clips to hold valves and was an excellent case, though after several years of heavy use the outer case fell apart. So I bought an executive briefcase made by Custom – they do a deep one, 19 × 14 × 16in., which is ideal – and glued the valve clips in the lid (see photo). The folder provided is useful for circuits, and the little pockets intended for pens can be used for trimmers, tweezers, etc. It's obviously not feasible to carry a full set of manuals, but the

circuits for the popular chassis you're likely to meet should fit in the folder.

At the rear of the case I've made a small compartment about 2½in. wide and the full width of the case. This takes all the small tools. In front of this I have four Raaco plastic boxes (10½ × 6 × 1½in.) for components. These can be stacked two high. It's prudent to have a stout rubber band round each. There's still room for the multimeters I carry, the soldering iron and gun and one or two other items. A piece of plastic foam about ½in. thick covers the lower compartment and doubles as a kneeling mat. As mentioned before, don't overstock with components. Throw the used ones in a box, and replenish daily.

In addition to making life a lot easier, the toolcase impresses the customer, giving him confidence in your technical ability. ■

The Exorcism of Fred

Les Lawry-Johns

WHEN I heard all the shouting and cursing coming from the bathroom I had an uneasy feeling that something was wrong. Only that morning the gas fitter had been to repair the multipoint so that honey bunch could have her bath and splash around happily. Now it seemed that she wasn't splashing around, and it appeared that a bath was out of the question as the gas was again not flowing. It was all my fault of course.

I did my best. I took an electric kettle up and plugged it in for her so that she could splash around in the sink, but she still wasn't happy. So the next day I phoned the gas board and told them that as far as gas goes, it had gone again.

Another and much nicer chap came and said that the faulty unit couldn't be repaired and that he would bring a new one as soon as possible. The next day brought two messages from the gas board: one was a bill for the repair of the old unit, the other was a note to say that a new unit would be fitted in two days' time.

Smack on time the new unit arrived, and was fitted by the fitter who had brought his stereo cassette deck with him to be repaired. Apparently, all the time it was playing there was an intermittent crack from one speaker, accompanied by a distinct jump on the right-hand VU meter. The left did not appear to be affected.

It was a Marantz 1820 Mk II. Quite a nice job if you understand these things, but normally I'm a little shy and confess to a total ignorance of them. If he was good enough to get my honey bunny into hot water however, I was going to sort this thing out however much I suffered. And suffer I did.

Off screws, off cover. Identify the right-hand and left-hand amplifiers and concentrate on the right-hand one. Without a cassette in, but with the thing playing away like mad, there shouldn't have been much noise in the headphones nor any movement of the meters. Every now and again however there was this distinct click in the right-hand headphone and a small jump on the meter.

So I shorted the base and emitter of what appeared to be the final amplifier and the noise vanished. Good, we're making progress. Ignore the fact that a slight click could now be heard in the left-hand headphone, about every fifteen seconds.

Proceed down the right-hand channel to the input, shorting the base to emitter of each transistor in turn, and at

no point did the click reappear on that side. It reappeared only when the amplifier was left working normally – and then far louder on the right-hand side. So we listened for the background hiss, and this too was louder on the right-hand side. When the two sides were equalised, the clicks sounded the same and both meters responded to them. I sat there encased in my headphones and pondered.

The regularity of the clicks suggested that the cause was nothing irregular. Therefore it was something building up a static charge due to regular movement.

"You're the only moving thing" I said to the cassette motor, prodding it with my meter and leaving it there. What a masterstroke! What genius resides here! Removing the prod and allowing fifteen seconds on my dad's old watch brought back the clicks. The cassette motor is cushioned on rubber grommets, and has no bond to earth. It has now. The gas man was awfully pleased. Then I gave him the bill.

Enter Mr. Slaughter

Mr. Slaughter's a jolly fellow. Must be something to do with his living. I don't mean the *fact* that he's living, I mean what he does for a living. He's a butcher of course. What a way to get rid of your inhibitions! Chop up a leg here or there. Nice piece of breast madam? – certainly. Slice, slice. Anyway, I helped Mr. Slaughter in with his Bush CTV1122 (Rank A823A chassis). "Picture's sort of faded. As though the entrails have been taken out, ha, ha." "O.K. Mr. Slaughter, call back this afternoon. I may have managed to stuff them back by then."

When Mr. Slaughter had departed I was alone again. As all geniuses who can earth the casing of a Marantz cassette motor must be. I would again try my diagnostic ability.

The picture certainly lacked entrails – we don't say guts in this magazine, we leave that sort of thing to *Wireless World*. Plenty of foreground but no background. Our diagnosis was immediate. Faulty SL901 demodulator/matrixing chip. Just to be sure, I clipped in the test panel. Lovely picture. "When the chips are down, you know who the men are" I muttered. With two deft sweeps of the desoldering braid the SL901 was free. Pop in the new one and Bob's your auntie.

In went the new chip and back went the panel, not forgetting to put the black plug back in the power unit.

When I switched on I noticed a flash from the surge-limiting thermistor, and resolved to change it before completing the job.

The picture was still the same and all my cheer departed. The sound was o.k. and the colour was there, so I made another guess. The luminance emitter-follower transistor – where was it? I grabbed the circuit and took off my glasses so that I could see it. There it was, 3VT3 (BC148). Coupled to the luminance delay line via that electrolytic . . . that electrolytic (3C43). Then I remembered. I always do when I've wasted quite a bit of time.

The capacitor is of the type (you know the ones) that when frightened by the meter reads about 500k Ω and steady. The circuit said 6.5 μ F, the faulty one was 10 μ F, so I put in an 8 μ F type because one was looking at me out of the box. In it went (round the right way for a change) and harmony was restored – until I switched on and the surge-limiting thermistor flashed and fell to bits. Why didn't I change it the first time I noticed?

The Card Game

We labour for six days without complaint. Almost without complaint. On Sunday morning we tidy up a bit, sort out the books etc., and at twelve o'clock get ready for the big event of the week. At one o'clock the card game starts at "The Call Girl" which, if you remember, is a pub in Harper St. where Ernie presides over the taking of our hard earned cash.

All week long honey bunch and I are on the best of terms. Most of the time. But at one o'clock on Sundays we are bitter enemies, no quarter asked or given. She's Sean's partner, and I have either Mick or Dick depending upon who's helping Ernie behind the bar.

The game is whist, and therefore partners are not always on the best of terms, or let's say don't always see eye to eye, though I must say that honey bunch and Sean rarely fall out and are most polite to each other. This is in distinct contrast to my partner and I, who scream and shout abuse at each other at the slightest suggestion of one trumping the other's trick. Despite this we are usually handomely in the lead after a hard fought battle, and honey bunch has many theories as to why this should be, none of which holds water as far as I'm concerned.

If there's one topic I hate during all this it's TV sets, and if anyone broaches the subject to me at Sunday lunch time they usually get short shrift. When Sean was dealing this week however (he deals hearts as trumps) he started telling me about his TV set that had gone wrong the previous day. I didn't hear a word of it because I've got a lot of wax in the ear nearest to him. The fact that I didn't hear what he said upset honey bunch who immediately accused me of not taking any notice of what Sean was saying.

"I can't hear through this ear" I explained. I'd just about got the gist of it however. ITV keeps dropping out, but the other two channels are fine. "The grease in the tuner unit wants cleaning out" I said. This seemed to me a perfectly valid explanation, since the set was a Thorn 1500. Sean muttered something like the grease in his tuner being about as troublesome as the wax in my ear.

But we got back to playing cards, and Dick and I won the hand by two tricks. It was then Dick's turn to deal and he deals clubs. "My set's playing about as well. Keeps going green it does." His set was a Thorn 9000, which we'd sold him some four years earlier. I was busy collecting all my trumps and putting them in order when Sean stirred it up.

"He doesn't hear out of that there, but I can tell you what's wrong. You've got wax in your tuner unit."

I shot Sean a baleful look. "He hasn't got grease in his tuner, but you have and when I clean it out tomorrow the ITV will be as good as the other two, however daft that seems, and what's more I doubt whether you'll get one trick in this hand."

That concentrated everyone's attention on their cards wonderfully. Honey bunch whispered "I bet he's got a handfull of trumps."

"Too true I have" I sneered, and then realised that I'd heard her whisper very well. "I haven't any wax in this ear, so there."

A Ghost Story

I suppose that at this time of the year a ghost story's in order. This one I've known about for some time, so it's not a tale that someone has just made up. Maybe there's an explanation, but I can't see it.

Our local newsagent and his wife and family live in a house at the top of the road, adjacent to an old church that was pulled down some years ago, the site being grassed over and preserved. Some years ago they realised that some peculiar things were happening, like rings vanishing from the dressing table in the bedroom and appearing on top of the TV set. Silly things, but irritating when you put a thing down in one place and then find it somewhere else. Hardly a ghost however. Then one day on arriving home in the evening they found a quaint looking old man in a funny hat sitting in a chair in the lounge. When they came in he got up and walked through the wall (the people next door also see him passing through apparently). He didn't seem to harm anyone, so they accepted him as an occasional visitor and called him Fred.

They saw a lot of him after that, coming and going at odd times, and he seemed to have a liking for that particular chair. Their teenage daughter was not so keen however, since she swears that he laid on her bed one night and wouldn't get off for some considerable time, during which she was unable to move. They also have two sons who were well acquainted with Fred, and a black and white spaniel by the name of Toby who was scared stiff of him. On one occasion when Fred appeared and walked toward Toby, the poor dog became almost hysterical and backed up the stairs with every hair on his body standing on end. In short therefore everyone in the house had seen him.

When I heard about all this I was convinced that one of the younger members of the family was responsible for the manifestation, as young people often are without being aware of this peculiar ability. As they get older they seem to lose the ability, and many a good ghost has gone west merely because the children have grown up. In this case however the children were not particularly young, and the one most affected by Fred appeared to be the dog.

As I say all this was well established and caused little concern. Some time later however the family acquired another dog, this time a golden spaniel by the name of Copper. Now Copper is one of the most extraverted and joyous dogs I've ever known. Always chasing around and barking for the sheer fun of it.

Copper hadn't met Fred who popped in only from time to time. One evening however Fred appeared in the lounge just as Copper came hurtling through the front door and into the lounge. Copper saw Fred and made straight for him. Fred took one look at the barking dog and promptly vanished. He hasn't been seen since. Or so I'm told.

So now you know what to do if you want to exorcise a ghost. Any ideas about the different effects on the two dogs?

VHS Tracking Monitor

L. Sadarangani

IN VHS videocassette recorders the video signal is recorded on the tape using frequency modulation between the limits 3.8-4.8MHz. During playback the paths traced by the video heads across the tape must match the pattern recorded on the tape for the maximum f.m. signal output to be obtained, i.e. the maximum signal-to-noise ratio. There are two aspects to obtaining this condition. First, the user adjusts the tracking control on the front panel to obtain a clear picture on the TV set. This adjustment operates through the head drum servo system. Secondly the servo system compares the head drum speed and the control signals recorded on the tape and corrects the drum speed via feedback action.

The tracking control can be adjusted manually or can be set to the "auto" position. The latter is not always the best setting however, particularly when a prerecorded cassette from a different machine is being played back. The auto position also fails to give optimum results if the machine hasn't been set up correctly. It's generally best therefore to adjust the control manually whilst watching the screen.

An alternative approach to setting up the tracking is described in this article – the use of an external metering unit which indicates the amplitude of the off-tape f.m. signal on a scale marked 0 to 10. This method has a number of useful advantages that are not immediately apparent – as follows.

First, adjusting the tracking control for a maximum reading on the meter provides a definite way of achieving the best possible picture not only when viewing but also when making a recording. This is because when making a recording it's essential to adjust for maximum f.m. signal, i.e. signal-to-noise ratio, which corresponds to a picture with minimum noise (fuzziness).

Secondly, if the meter reading obtained with a particular prerecorded tape is noted it's possible to keep an eye on the machine and the cassettes. If the meter reading falls at a later date, this indicates that maintenance is required – the video heads may be dirty or the control head out of alignment. This also gives an idea of the condition/quality of the tape.

Thirdly, the meter provides a check on the auto position of the tracking control. Note the meter reading in the auto position, then see what is the best reading that can be

obtained using the tracking control manually. If the difference between these readings is greater than 1dB, the position of the audio/control head requires adjustment.

Circuit Details

The most convenient point for monitoring the playback f.m. level in the JVC machines is at TP7 (playback f.m. output) on the preamplifier/record amplifier board, which is mounted on the left-hand side of the machine. The maximum f.m. level at this point is usually around 300mV. The signal then goes off to the chroma and luminance circuits for processing.

The meter circuit must interface as simply as possible therefore at this point, and be capable of amplifying and rectifying the signal thus obtained in order to drive the level meter. The circuit used must also be sensitive to the small variations in the playback f.m. signal level obtained as the tracking control is adjusted.

Several circuits were tried, but the one shown in Fig. 1 was found to offer the best solution in terms of performance and the minimum number of components. It's based on the Plessey SL612C integrated circuit, a low-noise amplifier which is usually found in i.f. applications. The i.c. provides a voltage gain of 34dB, with a maximum signal handling capability of 210mV r.m.s. It operates with supply voltages in the range 5V to 12V, drawing 5mA at 5V. Supply line decoupling is included within the i.c.

The signal from TP7 in the VCR is connected to the i.c.'s input via the input attenuator control RV1. This control is used to set up the meter's f.s.d. TP7 is connected to a d.c. blocking capacitor within the machine, so no input blocking capacitor is required. C1 is required at the output from the i.c. however. D1 removes the negative-going f.m. signal transitions, with the result that the meter indicates the average signal level on its scale. This simple circuit was found to work satisfactorily – improvements were made during the design but were found to be unnecessary.

The regulator IC1 maintains the supply voltage at 5V. Since the complete circuit draws 10mA, a PP3 battery is used as the power source.

The meter used is scaled from 0 to 10, and with the circuit shown the change in f.m. signal level from one scale mark to the next represents a ratio of approximately 1:1, i.e. 1dB.

Construction and Calibration

The instrument is calibrated by recording a signal on the

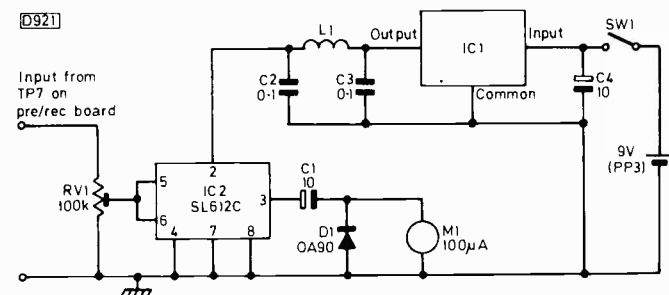


Fig. 1: Circuit of the VHS tracking monitor.

★ components list

- IC1 78L05 100mA, 5V regulator
- IC2 SL612C Plessey i.f. amplifier
- C1 10μF, 16V electrolytic
- C2 0.1μF ceramic
- C3 0.1μF ceramic
- C4 10μF, 16V electrolytic
- L1 1A v.h.f. choke-RS Components type 238-255
- M1 100μA f.s.d. RS Components meter type 259-561, Scaled 0-10
- D1 0A90 diode
- RV1 100kΩ preset

IC2 is available from:
Semiconductor Specialists (UK) Ltd.,
Falling Lane,
Yiewsley,
West Drayton.

VCR and then playing it back with the tracking control in the auto position. Adjust RV1 until the meter reads 10. Next check with the tracking control used manually. If the machine is correctly set up internally, a reading of between 9 and 10 will be obtained. If the reading is greater than 10, adjust RV1 to reduce it to 10. Full-scale deflection corresponds to an input of 20mV at pins 5/6 of IC2 and an output of 1V at pin 3.

The circuit is so simple that a layout doesn't seem necessary. The prototype was built on a piece of Veroboard 2x1in., and was then incorporated in a plastic box along with an on/off switch, the meter and a PP3 battery. The

input connection from the VCR to RV1 can be routed via the recorder's ventilation area or the lead can be pushed through a small hole drilled in the machine's back panel. Screened wire is strongly recommended.

Performance

The instrument has been found to perform satisfactorily, observation showing that the maximum meter reading corresponds with the best picture. It was interesting to see the different signal levels obtained with different cassettes – a difference as great as 6dB was noted. ■

Letters

ANOTHER SONY SAGA

The article in your June issue on the Sony set that blew gate-controlled switches brought to mind a recent, similar problem I encountered. The set was a Sony KV192SA, which is similar to the KV1810, and came in with its chopper and line output GCSs short-circuit. We replaced these and checked that the start-up circuit was operational with the set powered via a variac. Everything seemed to be o.k., so the set was connected to the mains. Bang went the chopper and mains fuse. In the hope of avoiding an expensive recurrence of the trouble we fitted a new start-up GCS and replaced the line output stage tuning capacitor (C542), then renewed the chopper. Start up on the variac was o.k., and the set was put back into service. Ten days later the set failed whilst in use, blowing the chopper GCS and the fuse again.

Since the set was in operation when it failed, the start-up circuit was obviously in order. A new chopper was fitted and the set came back to life – for three hours. This time the chopper again failed (for the fourth time), taking with it the 10Ω, 7W series resistor R607. The fuses were intact however. We went through the official Sony troubleshooting procedure, but nothing much came to light. A check with the scope revealed the presence of line drive right up to the gate of the line output GCS. Fortunately this time we'd another, working set of the same type available, so we were able to compare waveforms.

What we discovered was that the waveform at the collector of the line driver transistor (Q509) in the faulty set had a distinctly damped appearance, the leading positive-going edge not rising as rapidly as it should. Obviously the line driver transformer T502 had shorted turns, which was confirmed by replacement.

So what had been happening? The incorrect drive waveform had sporadically failed to turn on the line output GCS, thereby removing the chopper drive (no 19V rail). If this left the chopper on, it would go short-circuit.

*Martin Pomeroy,
Johannesburg, S. Africa.*

IC FAILURE

The problem I had with a colour set fitted with the Thorn 8500 chassis was occasional failure of the SN76227N decoder i.c. Assuming that this was due to some sort of flashover trouble, I made a careful check of the components on the c.r.t. base panel. The result was that W601 in the beam limiter circuit was found to be short-circuit, its failure in this way reducing the effectiveness of the beam limiting

action. Replacing it seems to have cured the trouble, and as this problem could be expensive it seems worth mentioning it for the benefit of other readers.

*S. W. Wakelam,
Birmingham.*

SERVICE COMMENTS

I was interested to read the article on ASA hybrid colour receivers in the September issue – particularly the description of the unusual beam limiter/spot suppression circuit which operates on the tube's cathodes. You see we had one of these sets in not so long since, due to poor sound and a faulty on/off switch. The sound problem was simply a worn PCL86 valve, but the on/off switch puzzled us at the time because of the single-pole, two-way switch ganged to it. This was found to be wedged in an intermediate position, so that the pole was making both ways. The wedge was removed, and both switches were found to be making and breaking correctly. Sound and e.h.t. were present, but there was now no raster. Check tube base voltages and find the first anode supplies missing due to the feed resistor R336 having gone open-circuit. It seems that wedging the switch in the intermediate position had resulted in the tube being kept in the switch-off spot suppression mode, with the cathodes sufficiently negative to give a picture (the RGB drives are applied to the grids). An unusual set of circumstances to say the least!

Concerning the Decca 30 series set with very bad flutter (*Service Bureau*, October), this could well be due to the beam limiting voltage smoothing electrolytic C69 as you suggest. When this component deteriorates it causes such faults as brightness changes from one side of the picture to the other, weak contrast, weak colour and complete loss of field sync (since it provides the video emitter-follower transistor's base bias). This last fault can lead one to a frustrating search in the sync separator/field timebase departments. C69 seems to suffer (not immediately) after failure of the PL509's cathode resistor R467. I find that when R467 has failed, C434, R36 and R37 are usually replaced but not C69. This results in the faults previously listed eventually putting in an appearance.

*A. M. Sheppard,
Swansea.*

A CORRECTION

In my letter on resistors in the September issue the subject of noise with carbon composition resistors was mentioned. Unfortunately someone changed "excess noise" to "excessive noise". Excess, or voltage-dependent, noise is the accepted technical expression, and I'd appreciate it if you would print this correction.

*E. F. Good,
Darlington, Co. Durham.*

Aerial Phaser Unit

Roger Bunney

ONE of the main problems one experiences with DX-TV reception in Band I is that of interference. Adjacent channel problems will arise from the use of a wideband i.f. strip, while electrical and industrial electronic equipment, motor car ignition systems and local BBC 405-line signals all add their quota. The unit described here was initially constructed in an attempt to reduce the effects of interference caused by a VDU installation. It was subsequently realised however that the device can be used to remove or reduce interference from a variety of sources. It can actually remove an unwanted signal, leaving the spectrum clear for receiving another weaker signal at the same frequency!

Early efforts to reduce the effects of the interference from the VDU installation revolved around the use of stacked aerial arrays. An improvement was obtained by using separate feeders from the stacked arrays, combining the signals indoors with additional lengths of feeder used to give a 180° phase shift so as to get cancellation of the interference picked up by the two arrays. I feel that there's scope for experimentation here, using delay lines instead of lengths of coaxial cable. Another approach tried was to use a simple circuit to get cancellation of the unwanted signal by adding a reference signal in anti-phase. The results obtained were doubtful however, and I fell back on the use of notch filters.

Subsequently I noticed in the RSGB publication *Radio Communication* an advertisement for the G3JFK "AVP4 Antenna Vector Processor". This claimed that it could dramatically reduce interference when used in the h.f. communications band. I got in touch with the manufacturers, Radmic Systems Ltd., at Crawley, and received a very enthusiastic reply from the designer of the unit, Ken Franklin. The AVP4 was designed for use up to 30MHz, but enough information was given in the handbook to get me to go back to the earlier experiments using a reference signal to get cancellation of unwanted interference. There are two inputs to the AVP4, one from an h.f. dipole and the second from a modified reflector element. The idea is that when the phase and amplitude of the input from the reflector are adjusted suitably and this signal is then added to the input from the dipole, interference (particularly from the rear) can be reduced by 40dB upwards. So I set out to produce a Band I version.

Circuit

The circuit that eventually emerged is shown in Fig. 1. It's simply a means of comparing a wanted signal input, with interference, and a reference signal that contains a high level of interference only. The idea is to adjust the phase of the reference input so that it's 180° out of phase with the interference in the wanted signal input. Then, by adjusting the amplitude of the reference signal and adding it to the wanted signal input, the interference should theoretically cancel out. Note that the interference reference source must be of higher amplitude than the interference accompanying the wanted signal for this to work, i.e. the reference signal has to be phased and reduced to match the interference you are trying to cancel.

The reference signal input is passed via a TDA1061 integrated pin diode attenuator network to the 180° phase

splitter D1/D2/L1. SW1 forward biases either D1 or D2 depending on the position it's switched to, so that the input passes via either D1 or D2. Coils L1 and L2 are wound on a ferrite toroid (type T37-12 from Ambit), using 26 or 28 s.w.g. enamelled wire. L2 consists of nine turns wound over two thirds of the toroid, while L1 consists of four turns, centre tapped, wound between the central turns of L2. Seal the windings on the core with clear varnish. This gives tight signal coupling. L2 is tuned by CT1 and CT2, with CT1 used to set the l.f. resonance when CT2 is at maximum capacitance. The field-effect transistors Tr2 and Tr3 provide a buffer between L2/CT2 and the low-impedance input of the SH120 (or SH124) hybrid wideband amplifier. The output from the wideband amplifier passes through a second pin diode attenuator network, which is used for amplitude adjustment, to the mixing network R32/VC. Pin diode D3 is included to enable the input from the DX aerial to be removed (with SW2 in the chassis position). This enables L2/CT2 to be tuned to approximately the correct setting without the wanted signal being present or masking the peaking action.

Use

Two aerials are required of course. One will be the normal DX array, the other being orientated to give maximum pick-up of the interference signal (reference signal input). To operate the unit, use SW2 to remove the DX input and tune L2 for maximum interference. Then switch SW2 to the other position so that the two signals mix. Set VR1 for minimum attenuation, using VR2 to attenuate the reference signal. Provided the reference input is at a higher level than the interference present with the DX input, it will be possible to reduce the setting of VR2 until the reference signal is seen to equal the interference accompanying the DX signal input. If reducing the setting of VR2 (increasing the attenuation) suddenly produces an increase in interference, SW1 is in the correct phase position and careful adjustment of CT2 and VR2 will give an interference null. If reducing the setting of VR2 (increasing the attenuation of the reference signal) reduces the interference in the display, so that only the interference present in the DX input appears, reverse the position of SW1. VR1 is included to prevent overloading.

Once CT2 has been peaked and the situation where the interference reduction is seen to be working has been reached, a further slight adjustment of CT2 will produce a phase shift and in combination with the settings of VR2 and SW1 interference cancellation should be achieved. The operation may seem to be rather complicated, but with experience the correct setting of the phaser unit is both easy and quick.

Results

The circuit certainly works with the two main problems present at my location, i.e. the presence of the BBC ch. B3 and radiation from the VDU room at night. The latter comes from a single source. Unfortunately during the day there are six VDUs in operation, in different positions and each radiating individual information. Thus one or more of the VDUs can be phased out, but not all of them.

By using the main Band I DX aerial at 53ft and another

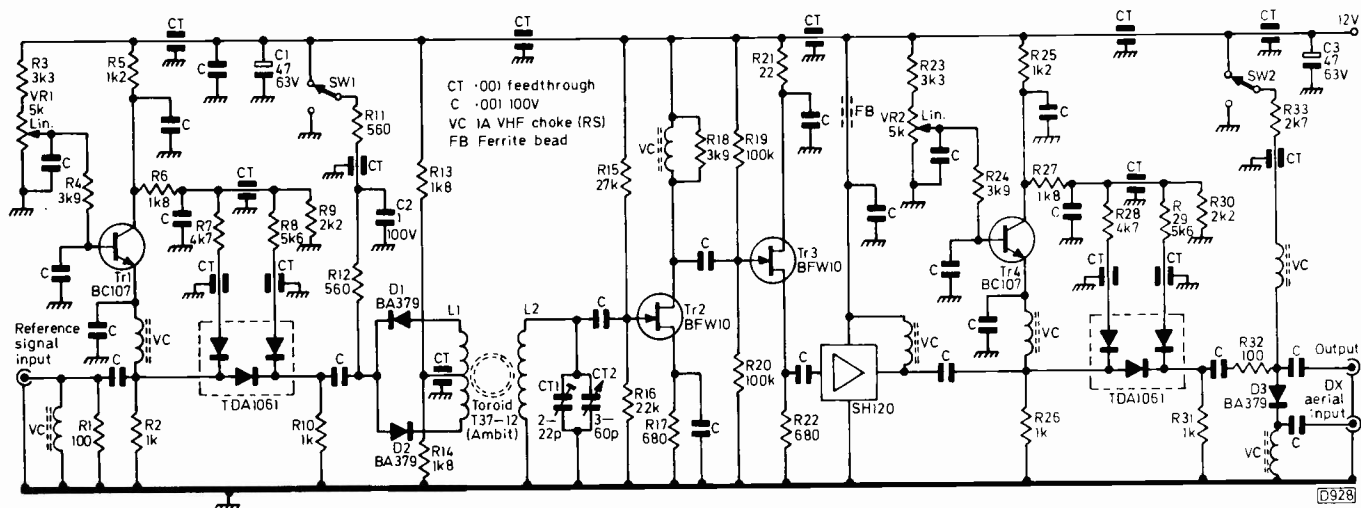


Fig. 1: Circuit diagram of the aerial phaser unit. CT1 is a miniature preset trimmer and CT2 a Jackson aerial trimmer. The pin diodes can be type BA479. The SH120 is an SGS device. SW1/2 are s.p.d.t. sub-miniature switches. House the unit in an Eddystone diecast box. Three coaxial sockets (Belling-Lee type) are required.

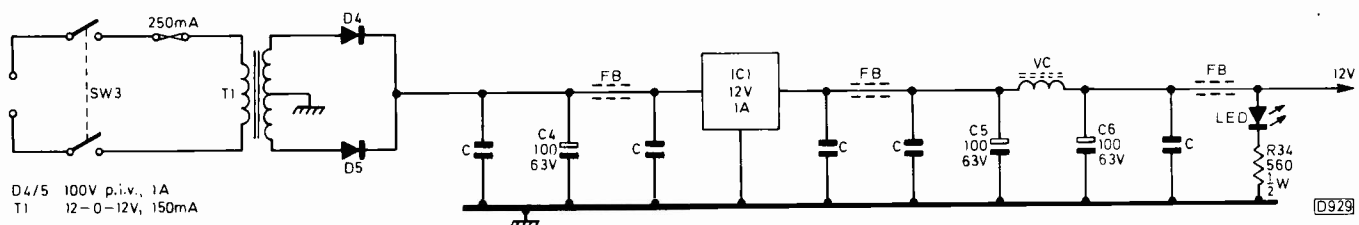


Fig. 2: Power supply circuit.

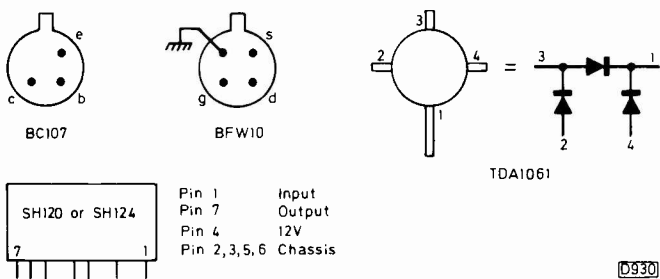


Fig. 3: Pin connections.

the wanted DX information if this is also present on the reference input.

The value of the unit should now be apparent. The DXer living in an area with a ch. B2 (48.25MHz sound carrier) local signal will not be able to use a notch filter if he wants to receive a ch. E2 (48.25MHz vision carrier) signal clearly. The phaser unit however will enable him to remove the ch. B2 sound so that the frequency is clear for ch. E2 vision reception. Rotating the aerial will affect the conditions of course, necessitating readjustment of the unit.

A modification I'm considering is to add a circuit prior to the first pin diode network to give a delay of at least 360°. This could be done using either a few turns wound on a toroid (see Fig. 4) or simply a coil.

Note that the reason for using VR2 as the main attenuator adjustment is to minimise the amount of noise from the wideband amplifier and the rest of the circuit mixed with the DX signal.

Despite the unit being a first attempt, the performance figures achieved were most encouraging. At maximum the reference channel has a gain of 8.5dB, so the loss in this channel is relatively high. Attenuation of the DX signal fed via D3 is 1.9dB, rising to 30dB when SW2 is switched to the chassis position. Attenuation of the unwanted signal varies with setting accuracy, but will be at least 30dB and typically above 40dB. If an additional delay circuit, as mentioned above, is added to give a wide time delay range, it should be possible to get extremely good performance figures with any input source.

Acknowledgement

Finally my thanks to Ken Franklin of Radmic Systems Ltd., 10 Weald Drive, Crawley, Sussex RH10 6JU for his help and encouragement with the project. The integrated pin diode networks were obtained from Ambit International. ■

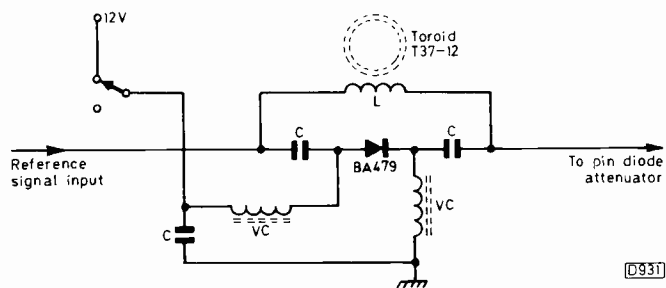


Fig. 4: Contemplated modification. L consists of approximately five turns on the toroid. Alternatively the coil could be wound on a 1/4 in. coil former, with a dust core to enable the time delay to be preset.

Band I array at 35ft on the same mast, it's possible to phase out completely either the local ch. B3 sound carrier or the vision carrier, leaving just noise. This represents an attenuation of 40dB upwards, the action being not unlike that of a notch filter though leaving the frequency clear for any other signal present on the DX array only.

The reference signal aerial should be the lower of the two and orientated for maximum interference reception. If it's mounted too high you may well get a degree of cancellation of

Practical TV Servicing: Making the most of your meter

S. Simon

OUR postbag suggests that a large number of readers, including those who followed the beginners' TV servicing series, still don't know how to use their meters to the maximum advantage and misunderstand some of the readings they obtain.

Testing Transistors

One of the handiest checks that can be made with an ohmmeter is to prove whether or not a transistor is capable of conducting. This is surely so well known that it hardly bears repetition. Yet the strange thing is that some of the facts one sees stated are simply not true. What are we on about this time?

It's often stated that to test an npn transistor you apply the black probe to its base and the red probe to either the collector or emitter. If you get low readings conduction has been proved. True. It's also stated that if you get a low reading when making the check between the transistor's emitter and collector the transistor is faulty due to leakage. This is not necessarily so however, and has resulted in many a good transistor being consigned to the waste bin.

A Game of Simon Says

What Simon says is that, using an AVO Model 8 or similar meter, you should first switch it to the lowest ohms range and then look at the transistor to be tested. If it's of the straightforward amplifier variety, say a BC148, it's perfectly true that if you get a reading between its emitter and collector the transistor should be consigned to the waste bin. If however the transistor is designed for use in a gain-controlled stage, for example a BF196, there must be a reading of around 50Ω between the emitter and collector, with the black probe to the emitter and the red probe to the

collector, if the transistor is to function correctly. The reading you obtain may vary up to around 100Ω , but the fact is that you should obtain such a reading. A reading should not be obtained when the probes are reversed, i.e. red to the emitter and black to the collector, and this is where the confusion arises.

So when you're checking a transistor designed to work with forward a.g.c., you should expect a reading of about 30Ω between the base and collector and the base and the emitter, with the black probe to the base for an npn device: you should also get a reading almost as low when reading between the collector and the emitter, with the red probe connected to the collector. No readings when the leads are reversed. O.K.?

With the meter switched to its low ohms range most transistors can be checked in situ. With the meter switched to the $\times 100$ range the external circuitry may cause confusing readings – depending on the resistor values used.

What we've said does not apply to straight amplifier transistors of the BF337 type for example, where readings should be obtained between the base and the other two electrodes only.

Voltage Checks

Next to voltage measurements. Switch the set on and the meter to the voltage range appropriate to the measurement to be made. The first fact that should be appreciated here is that connecting up the meter will have an effect upon the circuit being checked. This is so because the circuit has to provide the energy to deflect the meter's movement. Some cheaper meters require a considerable current flow to deflect the pointer, and this current flow will alter the circuit's operation, with the result that you get a misleading reading.

If the voltage measured is divided by the current required to deflect the meter, a figure in ohms will be obtained. A good meter should have a sensitivity of $20k\Omega/V$ or more, which means that using a $20k\Omega/V$ meter will impose little current drain on the average circuit. If the circuit employs high-value resistors – some focus networks for example use resistor values of hundreds of megohms – the application of a moving-coil meter will affect the circuit considerably. In this case there's no point in trying to take a reading unless you know the sort of reading you should expect with the sort of meter you're using.

Having got that much off our chest we can get down to the job in hand, checking circuit operating conditions.

A typical IF Circuit

Let's consider a typical i.f. amplifier (see Fig. 1) consisting of two gain-controlled stages (VT1/2) and one straight amplifier (VT3). We'll assume that it uses two BF196 transistors and a BF197. Simon says that such a circuit can give rise to some confusion, so that if possible the circuit diagram should be to hand.

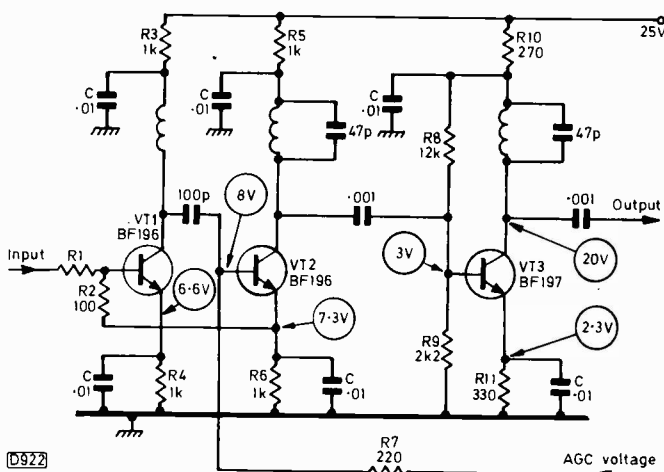


Fig. 1: A typical three-stage i.f. amplifier circuit, with the a.g.c. voltage applied to the base of the second transistor VT2 and to the base of the first transistor VT1 from the emitter of the second transistor via R2. The capacitors marked C provide decoupling in the emitter and collector circuits.

The reason for this confusion is that the a.g.c. is often, as shown, applied to the base of the second transistor rather than to the base of the first one. If so, making the base of the second transistor more positive with increased signal strength (an npn transistor with forward a.g.c. applied) will increase the transistor's emitter voltage (across R6). This increased emitter voltage can be used to bias the base of the first transistor (feedback via R2). Thus the gain of both transistors is being controlled. This mode of a.g.c. operation is the opposite to that employed with controlled valves, of the EF183 variety for example. In this case increased signal strength would result in an increased negative voltage being applied to the valve's control grid, thus reducing the valve's conduction. Unfortunately applying a negative-going control voltage to the base of a transistor will result in it cutting off sharply, with little or no control range. So we go about things differently, applying forward a.g.c. as it's called.

So with a circuit such as that shown in Fig. 1, the first obvious voltage check to make is at the emitter of the second transistor. Why? Because VT2's base voltage is derived from the a.g.c. line, while the voltages around VT1 are set by VT2. The voltage across R6 is the result of the current flow caused by VT2 conducting. If the transistor is operative, there will be a voltage difference of 0.7V between its base and its emitter. Say the base voltage is 8V. The emitter should be at 7.3V. This is the standard voltage drop developed across a forward biased silicon pn junction.

So if we find that VT2's base and emitter voltages are about right, with a voltage difference of roughly 0.7V between them, we can assume that VT2 is operational and turn our attention to the first transistor – to see whether it too is doing its job. Since the base of this transistor is biased from the emitter of the second one, a voltage of 7.3 – 0.7V is to be expected at the emitter of the first transistor, i.e. a voltage of around 6.6V. If this is found to be the case, it would appear that VT1 and VT2 are in order. Having made these quick – but not conclusive – checks, we would turn our attention to the third transistor.

A.G.C. is not applied to this one, and its base voltage will be much lower, say 3V. So the emitter should be at about 2.3V, and assuming that the supply line is 25V the collector voltage should be about 20V. This 5V difference indicates that the transistor is passing current, and is another quick check that indicates whether or not the stage is operating normally.

If on the other hand the base voltage is found to be somewhat higher, with precious little voltage at the emitter and the collector voltage at say 25V, we know immediately that VT3 is not passing current and that its base-emitter junction is probably open-circuit. This situation is not unusual with the transistor used in the final i.f. stage. Switch the set off and the meter to ohms to check the transistor's base-emitter junction.

Pitfalls

All this is easy enough, but there are pitfalls. The transistors may be working, but the i.f. strip may not be working. We quoted 8V as the initial a.g.c. line voltage. This is perhaps a trifle on the high side, and something around 6V is perhaps more what to expect. If the a.g.c. voltage is incorrect, it would obviously be appropriate to look at the a.g.c. circuit. A very low a.g.c. voltage would suggest that a leaky electrolytic capacitor in the a.g.c. circuit is pulling the voltage down. If the voltage is high however we would be more inclined to suspect lack of decoupling, leading to instability. In this event shunting each decoupling capacitor

in the i.f./a.g.c. circuits with a known good one could be a productive exercise.

It's far more often the case that an a.g.c. amplifier transistor is at fault however. So this transistor (or these transistors) should receive a close look, bearing in mind that one or more of them could be of the pnp variety, which means that polarities are reversed – the red probe has to be connected to the base and the black one to the emitter and collector for the initial conductivity checks. These transistors should be of the straight amplifier type, so there should be no low reading in one direction when checking between the emitter and collector.

This is not meant to be a fault tracing exercise on i.f. strips however, merely a guide to checking transistors in situ.

We said that 0.7V represents the basic turn-on bias for the base-emitter junction of a silicon transistor. If this voltage difference is not present, the transistor will not conduct. It takes no great effort to identify a transistor's base and emitter leads, and even less to short them together with a screwdriver blade or test probe. We prefer to use a screwdriver because this leaves the probes free for making voltage measurements. Say at the transistor's collector. If no change in voltage is recorded here when the transistor's base and emitter are short-circuited, the transistor was clearly not conducting in the first place – either because it's incapable of doing so (check it with your ohmmeter) or because the associated circuitry is preventing it from doing so.

Before taking voltage readings you should have a good idea of what to expect. Take a sync separator stage for example. The transistor used for this purpose is usually arranged so that it spends most of the time cut off. Occasionally things may be arranged the other way round, the transistor being fully on between pulses, then fully off when the sync pulse arrives. Voltage checks are not very conclusive under these conditions therefore, and a scope check is more useful.

Audio Circuits

Let's venture into the audio side of a TV set however. The detected audio signal is pretty weak, and whilst it may be able to drive a high-impedance headphone it certainly won't drive a loudspeaker. So it's fed first to a preamplifier stage, which may well contain high-value resistors in its base circuit. This takes us back to the meter's loading effect: if there's any doubt about the validity of the voltage reading obtained at the base of the transistor, it would be better to check the emitter voltage or, if the emitter is connected direct to chassis, the transistor's collector voltage. With the meter recording the collector voltage, short the transistor's base and emitter leads. The collector reading should then rise to the supply line voltage. In practice touching a screwdriver blade on the base will produce a loud hum from the speaker if the whole audio circuit is operating, so this is obviously the first check to make, going on to make voltage and cold ohmmeter checks if there's no hum or the fault being investigated is distortion. The point is that some preamplifier stages employ high-value resistors which render base voltage checks invalid or even inadvisable (since the d.c. conditions will be changed by the meter).

Very noisy sound (loud crackling or rustling) should also direct attention to the audio preamplifier stage. The first check this time is to short-circuit the base and emitter to see whether this stops the noise. If so, one is faced with several possibilities: a faulty transistor (most likely), a leaky

coupling capacitor (usually in the base circuit), or a defective resistor. This latter possibility is one that's usually ignored, but is a distinct likelihood if the transistor and the capacitors all prove innocent. Failure to take the resistors into consideration has caused many a good man to go prematurely grey.

Dry-joints

The other cause of defective transistor circuit operation is dry-joints, which seem to abound on some printed panels. If in doubt, resolder all suspect connections, but bear in mind that the application of the heat from the soldering iron might well remake a poor connection not at the joint but within a capacitor or a transistor, particularly the latter, with the result that the cessation of noise (say) is only temporary. When you appear to have cleared the fault, switch the set off, pretend to wrap it up – then check it again from cold. It pays to carry out this recheck.

This applies to all sections of the receiver – particularly the three colour drive (video output) stages, which normally

run fairly warm and are thus hotbeds of discontent you could say.

Summing up

We hope that this brief outline has cleared up some doubts about checking transistor circuits, particularly where forward a.g.c. is involved. We've concentrated on npn silicon transistors since these are the most common. To prove a pnp device however all that's necessary is to reverse the polarity of the meter's probes – remembering that where forward a.g.c. is concerned, a reading between the collector and emitter in one direction only may simply mean that the device is intended for use in a controlled stage. Other things to remember are that in older sets you may come across germanium transistors, that you will encounter transistors operated upside down (with the emitter to the supply line and the collector connected to chassis), and that you may find negative as well as positive supply lines. But then you'd note these things from the circuit you'd be looking at, wouldn't you?

Video in/out Conversion for the Philips G11 Chassis

A. R. Rumbelow, G3KKC

WHEN you first look at the circuitry used in the Philips G11 chassis, it may not seem to be a very suitable candidate for video input/output conversion. We've been getting excellent service from this chassis however, and required a cheap monitor. So we decided to take a closer look. The outcome is the conversion presented in this article. A couple of chassis have been modified in the manner shown, and have proved to work very successfully in daily use.

Conversion Procedure

The conversion procedure is as follows. First build up the video input/output buffer circuits shown in Fig. 1. They are quite simple and can be built on a small piece of stripboard. The next thing is where to break into the G11's circuitry? The demodulated video signals are present within the U600 vision detector module on the i.f. panel. The relevant circuitry is shown in Fig. 2. The emitter-follower T653 feeds the chrominance and luminance circuits, so to get a video output all that's necessary is to tap off the signal developed across its emitter load resistor R654. See Fig. 3. When it comes to feeding video into the G11 things get a little more complicated.

First, as a comparison of Figs. 2 and 3 shows, it's necessary to break the link between the emitter of T653 and C651 (which feeds the chrominance circuitry)/R661 (in the feed to the luminance circuitry). There's an added complication in that the G11's sync circuits are fed from a different point – from the output of pin 10 of the TCA270S i.c. within module U600. This output appears at pin 13 of the U600 module, so a further break has to be made on the i.f. board print after pin 13.

Switching between off-air reception and video input operation is carried out by means of a two-pole changeover relay (RS Components type 348-914). This has a 700 Ω coil

which is energised to change over to video input when switch SW1 is closed. The connections to the relay are shown in Fig. 3. Mount the relay on top of can U600, using Araldite.

The modification within the U600 module consists of moving the position of R654, cutting the print adjacent to the emitter of T653 and adding a couple of leads to connect to the relay. Leave the earthy end of R654 undisturbed: move the other end from its original position, soldering it directly to the emitter of T653 via a small hole drilled near to T653's emitter. Then cut through the print immediately to the left of the emitter, and add a pair of leads, one connected to the emitter of T653 and the other to the feed end of C651. Bring the leads out through the top of the can and connect them to relay pins 5 and 6.

For the sync switching, cut the print on the i.f. panel leading from pin 13 of module U600, then take a pair of leads from across the cut to pins 8 and 9 of the relay.

When the relay's coil is not energised, the set is in the off-air condition and the video output is also available. Note

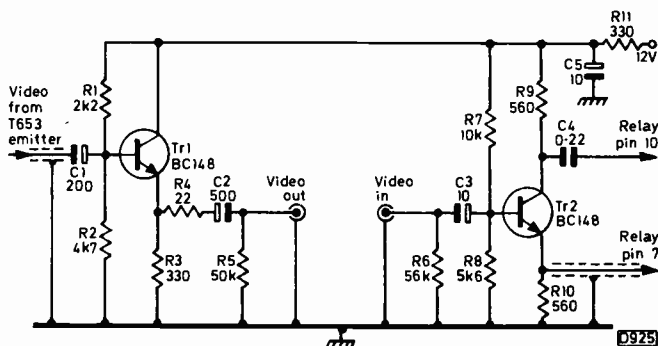


Fig. 1: Video in/out buffer circuits. Terminate the video output socket with a 75 Ω resistor when not in use.

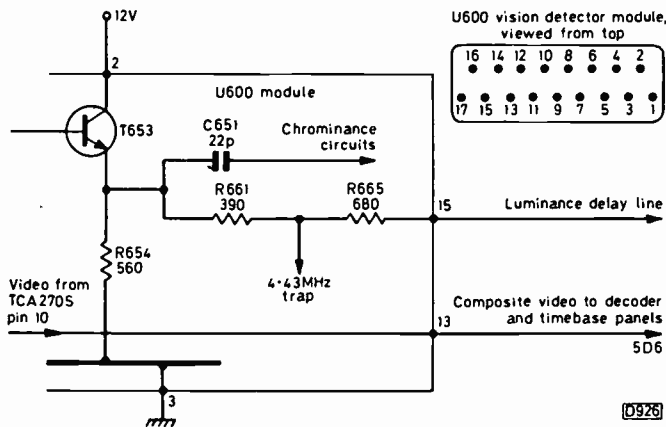


Fig. 2: Conversion is carried out in the emitter circuit of transistor T653 in the U600 vision detector module and in the printed track leading from pin 13 of the module.

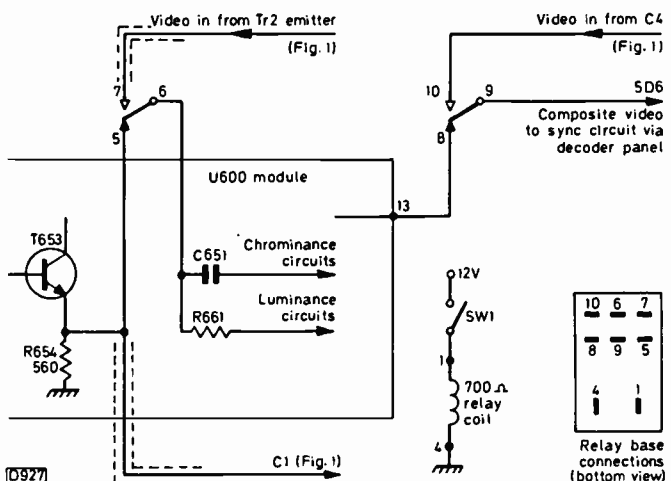


Fig. 3: Details of the conversion, using an RS relay type 348-914 for video in/out switching.

that the video output socket should be terminated with a 75 Ω resistor when not in use. The video input/output buffer circuits and the relay are powered from the G11's 12V LT2 rail, which is conveniently available at pin 2 of module U600. Pin 3 of the module can be used as the earth connection.

To mount the switch and the input/output sockets, first remove the Philips nameplate panel – this can be done by using a soldering iron to melt the plastic clips inside the cabinet. Cut a suitably sized piece of 20 s.w.g. aluminium to fit the space thus made available, and fix it with Araldite within the cabinet. Drill out and mount two BNC 75 Ω sockets and a small single-pole changeover toggle switch. The piece of aluminium serves to strengthen the mounting of the sockets and switch. The video input/output board can be conveniently mounted below the loudspeaker, using self-tapping screws. There are two vacant plastic pillars into which these can be screwed.

Mains Isolating Transformer

Finally, note that it's essential to use an external 500VA mains isolating transformer – the chassis sits at around half mains potential. We use an RS Components type 207-481, which is in an insulated case, modified so that the plug and socket are not compatible with standard 13A mains connectors.

The suggested conversion can easily be removed and the set restored to "standard" operation. ■

next month in

TELEVISION

● STUDIO 80 PROJECT: MIXER

Having completed the basic video camera, the next item in this series is a video mixer. Once again the aim has been to design a simple system that can be used by the video enthusiast with limited finances. A-B channel mixing is used, a single fader control selecting the signals from video switch banks A or B.

One great advantage of having a mixer is that given two or more video sources more interesting video recordings can be made – lively programmes, lectures and so on.

An effects unit has been designed to complement the mixer, and can be housed in the same cabinet. Later articles will deal with this.

A common sync pulse source is necessary when dealing with more than one video signal, and for this purpose a ZNA134 sync pulse generator i.c. is incorporated in the mixer.

● SERVICING FEATURES

Amongst the servicing features next month are notes on the Siemens Model FC365, from Mike Dutton, and information from Derek Snelling on troublesome Tandbergs and EW modulator faults on the Philips G11 chassis. Sol Simon's subject is defective capacitors.

● MINI PROJECTS

Two mini projects deal with interference of one sort or another. For Keith Cummins, the problem was noise (due to harmonics) when tape recording TV sound signals. The solution was found to be the use of an active filter. For Hugh Cocks the problem was intermodulation effects when using a bipolar transistor wideband amplifier in Band III. A mosfet amplifier overcame the problem.

● TEST REPORT

Eugene Trundle tests the Thandar/Sinclair PFM200 digital frequency counter and comments on the uses he found for it.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO
(Name of Newsagent)

Please reserve/deliver the February issue of TELEVISION (70p), on sale January 21st, and continue every month until further notice.

NAME

ADDRESS

Video Camera

Part 4

Malcolm Burrell

IN the past three issues the camera's circuitry has been described and two of the four PCBs have been shown. We can now show the remaining two boards and provide constructional, setting up, and component details.

Construction

Constructional details of the camera are shown in Fig. 12. Drill four holes in the lower shell (assuming that a 203 Verobox is used) to support the deflection coils, which are mounted on 6BA screws. These should be approximately $\frac{1}{2}$ in. long to allow for the final positioning of the coils relative to the lens mount. The holes should be countersunk since the lens mount must rest flush on the front of the case, with the boss protruding through the aperture. Three fixing holes are needed for the mount, which has countersunk fixings. The screws for the mount could be of the 6BA round-head type, about $\frac{1}{2}$ in. long. Don't drill the holes for the mount until you've obtained one – the external dimensions vary slightly.

Make all seven holes and the lens aperture before assembly. Insert the countersunk yoke fixing screws first, with a dab of quick setting glue in the hole. Fit the lens mount, then fit 6BA nuts to the protruding countersunk screws, with washers to support the deflection yoke, which is mounted next. Fit washers and nuts to secure the yoke.

A C mount (16mm) lens should be used. Fortunately this enables the tube to be inserted and removed without having to remove the lens mount. Though a D mount lens could be employed, such a lens could cause shading at the picture edges.

The black lead from the deflection coils (EMI type KV12S) is the internal screen. This should be connected to the common earth tag on the power supply.

The pinning of the EMI 9831 vidicon is as follows: pin 1 cathode, pin 2 mesh, pins 3 and 4 heater, pin 5 grid, pin 6 first anode, pin 7 wall/focus anode.

We suggest constructing the video/field timebase board first. Use the components specified – this is important – and position them close to the board as shown in Fig. 11 last month. The resistors stand on end, and the leadout wires should be neatly bent using pointed-nosed pliers. The value

of Tr2's emitter resistor R4 is critical and needs careful adjustment – otherwise no output will be obtained. It's best to use a 500 Ω potentiometer initially, mounted on the posts, replacing this with a fixed value resistor after testing.

After building the board, inspect it carefully, connect a 12V supply and, with a scope connected to the video output pin 5, observe the output: touching pin 1 (input from the vidicon's target) will produce a great deal of noise when the potentiometer in the R4 position has been adjusted correctly.

Instability may be a problem, and it may be necessary to connect an earth lead temporarily to pin 2 as well as pin 10.

Next check that the field timebase is working by connecting the scope to pin 11. A relatively large, rounded sawtooth will be seen if all's well, and connecting the field scan coils temporarily will produce approximately the waveform shown in Fig. 17. Check that adjusting the setting of VR1 varies the frequency while adjusting VR2 adjusts the amplitude. The linearity control VR3 has only a slight effect on the scope's trace – care is needed not to induce field judder with this adjustment. Check that a field frequency waveform is present at pin 3.

Without a scope some guesswork is needed. The use of an earpiece or headphones should enable the low-pitched buzz of field pulses to be heard however.

The sync pulse generator panel is much easier to build and get operational. Note however that the correct waveforms will not be present everywhere until the board is connected to the video/field timebase board from which the field pulse input is obtained. Once this connection has been made and everything powered up, the waveforms can be checked (see Fig. 17) or, alternatively, a monitor connected to the video board (terminate the output with a 75 Ω resistor if necessary) should show a raster with sync pulses. Adjust VR1 for vertical lock and VR4 for horizontal lock. Touching the video input pin 1 on the video board should produce noise etc. without undue loss of sync.

The video/field timebase and sync boards are mounted side by side on a panel of copper-clad board, which is slotted into the Verobox. Each panel must have a separate earth lead to the common earth point (see Fig. 18). Use screened leads for the target input, video output and



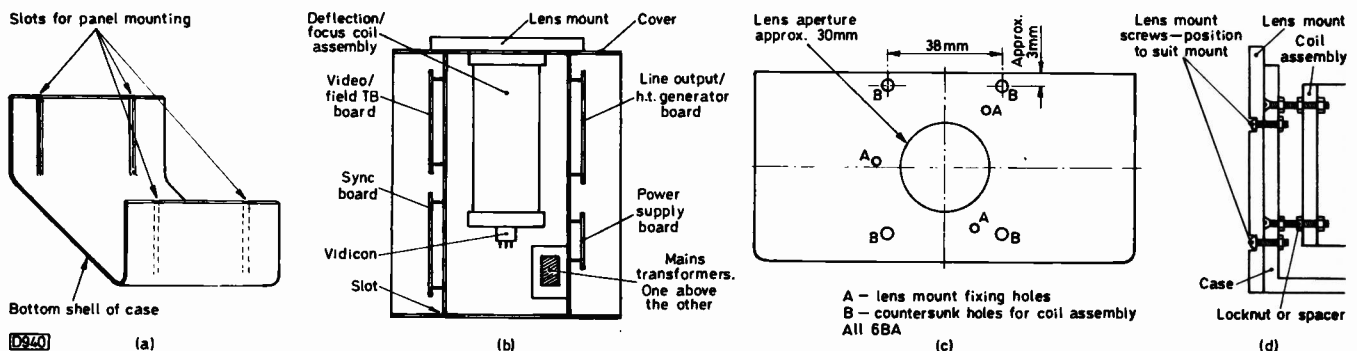


Fig. 12: Constructional details, using a Verobox type 203. We suggest mounting the boards with spacers on sheets of plain copper-clad board as shown in (b), with the copper side towards the deflection/focus coil assembly. Suggestions for fitting the EMI coil assembly and a C lens mount are shown in (c) and (d).

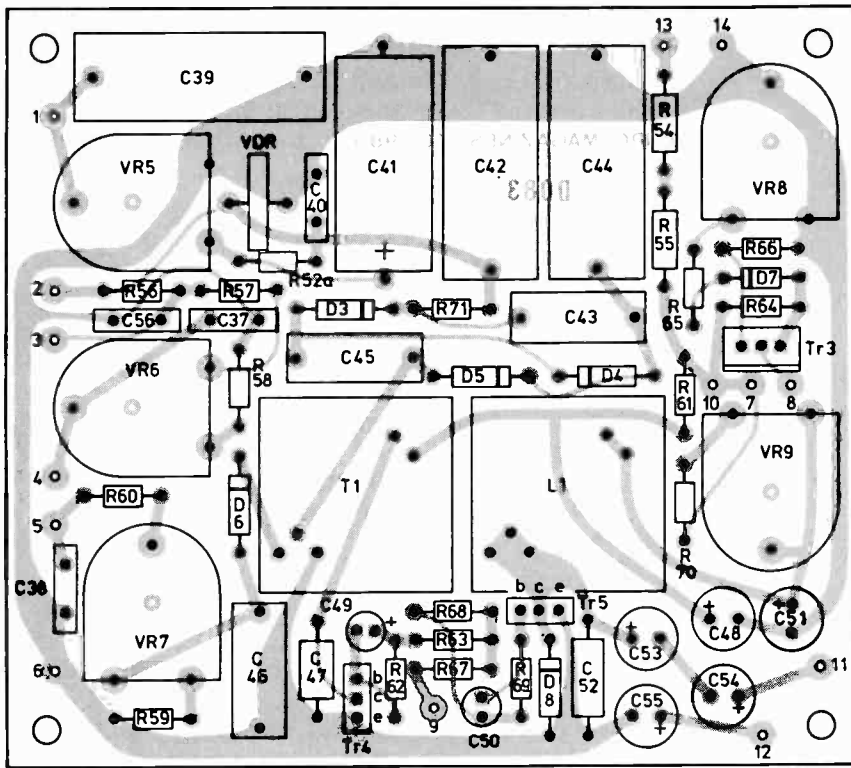

TMG622

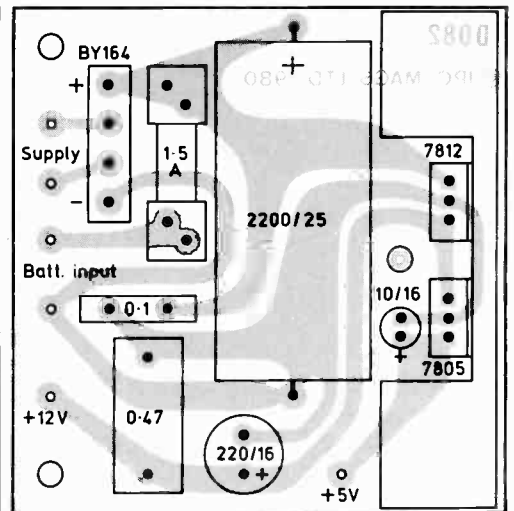

TMG621

Fig. 13 (above): Power supply board component layout. Fit a tag to the bolt securing the 7812 regulator, and use this as the common earth point for the entire camera. Fig. 14 (left): Line timebase/h.t. generator board layout. R61 and R70 should be spaced off the board.

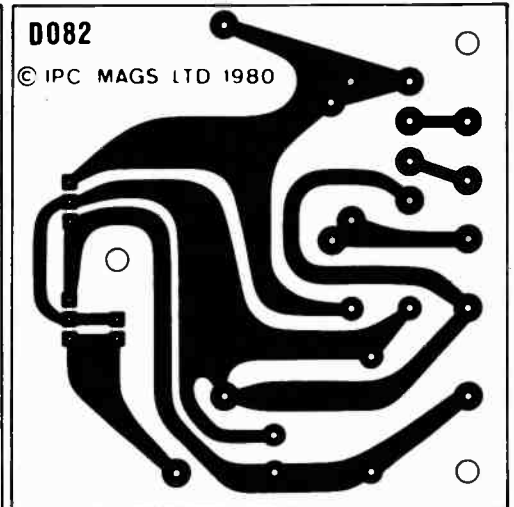
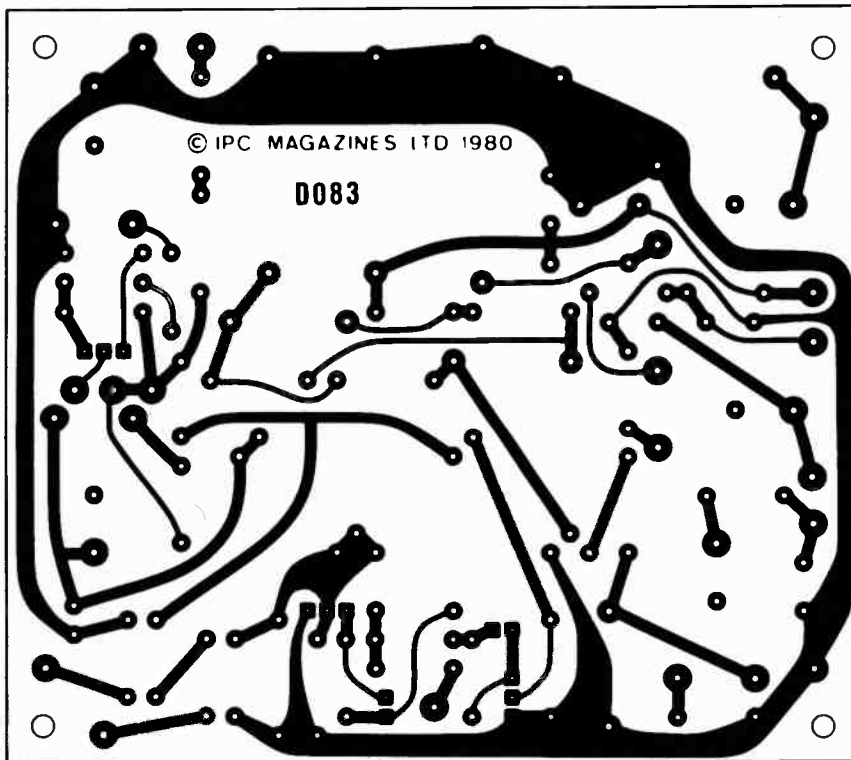


Fig. 15 (above): Power supply board print pattern.

Fig. 16 (left): Line timebase/h.t. generator board print pattern.

external sync input – microphone cable is suitable. Only the target lead braid is connected to the video earth at pin 2. At the target end, the braid is connected to the outer foil of the deflection yoke, close to the target connector. A short length of braid is also used to connect this point to a tag in contact with the lens mount. Without this, stray r.f. would cause patterning on the picture, particularly when adjusting the lens. Connect the inner of the cable and R53 to the target connector, taking the other end of R53 back to pin 1 of the line timebase/h.t. board. Keep the video cable as short as possible.

On the original prototype, the electrostatic focus (VR6) and target bias (VR5) controls were mounted on a control

panel for user operation. Provision has been made to mount them on the line output/h.t. generator panel however as internal presets. They can be mounted for external use with leads to the panel as required. I'd recommend leaving the electrostatic focus control as an internal preset – the focus drifts a bit as the camera warms up, but can be left at an optimum setting – with the target bias as an externally adjustable control.

Keep the leads tidy – binding them together to form a loom improves the appearance and reduces instability. If any video instability remains, adding a separate earth return to pin 2 on the video board should improve matters. Remember that, as pointed out in Part 1, all earth returns

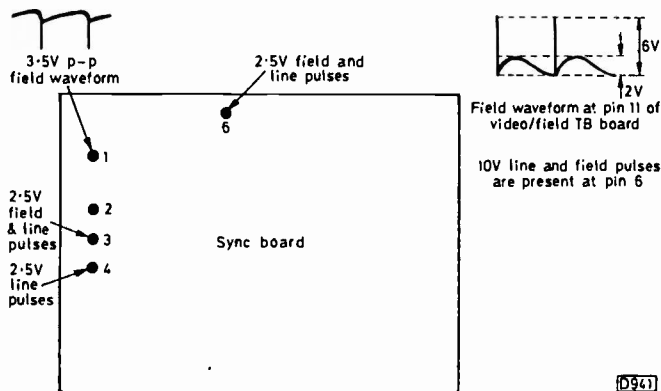


Fig. 17: Waveforms. A pulse of about 100V should be present at the collector of Tr4, with a pulse of 50-80V at the collector of Tr5.

should be taken to a tag bolted to the 7812 regulator on the power supply panel.

Setting Up

Having built the boards and made all relevant connections, set up the camera as follows. Don't insert the vidicon tube at the start – there's no protection to prevent target damage, which will be permanent if the tube is operated at high beam current with either of the scans absent – the result will be a prominent vertical or horizontal white line on the picture.

Temporarily connect a 68Ω, 1W resistor between points 13/14 on the line output/h.t. generator board, apply power and check that the vidicon's 6V heater voltage is present and correct. Using a scope, check that a 6V sawtooth is present at the input to the field scan coils (green lead on KV12S assembly), and that a flyback pulse is present at point 11 on the line output/h.t. generator board. With a meter, check that approximately -120V is present at the junction of D6/C46 and that 250V or so is present at the junction C40/R56. Remove the 68Ω resistor and switch off.

We'll assume that the video/field timebase and sync boards have already been checked as described above and the hold controls adjusted. Fit the tube, set the beam control VR7 to the maximum negative voltage end, the width (VR9) and height (VR2) controls to maximum, and all other controls to midway. Connect the video output to a monitor, terminated as necessary, switch the camera on and adjust VR7 towards the chassis end, at the same time gradually increasing the setting of the target bias control VR5. The monitor screen should brighten, with at least one of the curved edges of the target visible. Adjust the focus controls (VR8 and VR6) for the sharpest display, then try to move the target image to an approximately central position, using the centring (alignment) rings on the deflection yoke.

Fit the lens and focus on a nearby, well lit object. Adjust the lens aperture in conjunction with the target bias control VR5, reducing the beam current (VR7) as necessary, until a vaguely recognisable image is seen. Roughly set the lens focus for a better display, then reduce the scan amplitudes in order to *increase* the image size on the monitor.

Measure the distance from the object to the front of the lens, set the lens so that its markings correspond with this, then adjust the position of the deflection yoke on its mountings for the sharpest display. Secure the yoke.

Set up a test card at a reasonable distance from the camera and increase the scan amplitudes slightly to ensure that its corners just touch the edges of the target. Reduce

the scan amplitudes until the test card fills the screen, and trim the focus controls for the sharpest display. The magnetic and electrostatic focusing (VR8 and VR6) are interdependent, so you may at first find it confusing trying to get the optimum focusing in conjunction with adjustment of the lens.

Use

Generally, the brighter the scene, the smaller the lens "stop" and the smaller the target bias – too much beam current produces picture blurring and defocusing. Set the target bias just short of this point. Operation in poor light conditions requires a larger lens aperture and increased target bias. The depth of field will be impaired, so will the focus, and there'll be a tendency for images to "stick" as objects move. With experience, optimum results will be obtained.

Faults and Problems

The semiconductor devices used are surprisingly robust – the ones in the prototypes were subjected to a certain amount of misuse . . . Most constructional problems will be caused by incorrectly positioned components (especially on the video/field timebase board, where the compact circuitry can cause confusion), dry-joints or open-circuit 10Ω decoupling resistors. The latter have a very short life when subjected to inadvertent short-circuits whilst testing. The CA3046 i.c. needs to be treated with care – in the event of a suspected fault it's possible, after disconnecting the relevant pins, to wire in a BC107 transistor as a check. The section used for vidicon blanking is rather vulnerable – tell-tale sloping black lines (flyback lines), fairly widely spaced, are usually due to the i.c. being at fault.

Noise from the video amplifier is rare. If a random herringbone pattern is present, try screening the points where the target lead is connected to either the video board or the deflection yoke. If the noise resembles that of cross-modulation with an aerial system, i.e. random lines missing from the picture, monitor the field scan waveform at pin 11 and note whether there's noise on the scope trace. If so, temporarily bridge C23 with an 0.01μF capacitor and if the fault clears change R39 to 56kΩ and C23 to 0.0033μF.

If, even with neat wiring and the screening can fitted, there's instability – usually vertical lines which spread across the screen as the target bias is increased – disconnect C5 and note the effect. If the fault clears, leaving a very poor image, add a 270Ω resistor in series with C5 (see Fig. 19), and add a 10kΩ resistor between the collector and base of TR2 (soldered on the print side of the panel). It may be necessary to increase the value of R4 when this is done.

After final testing, you may find that the definition is improved by increasing the value of C4 to about 0.0047μF.

On some monitors you may notice a line flyback pulse near the centre of the screen, i.e. a vertical white line whose position changes as the horizontal frequency control is adjusted. This pulse can be removed by taking a separate earth wire to the common earth point from the negative plate of C55. R52a can be reduced to 4.7MΩ if necessary should a greater target bias range be required. If the picture is dim, with excessive width, reduce the value of R70 and increase the value of VR9 to get a greater control range. This may increase the dissipation in the potentiometer, so that a more robust type spaced off the board may be required. Since line collapse with voltages still present on the

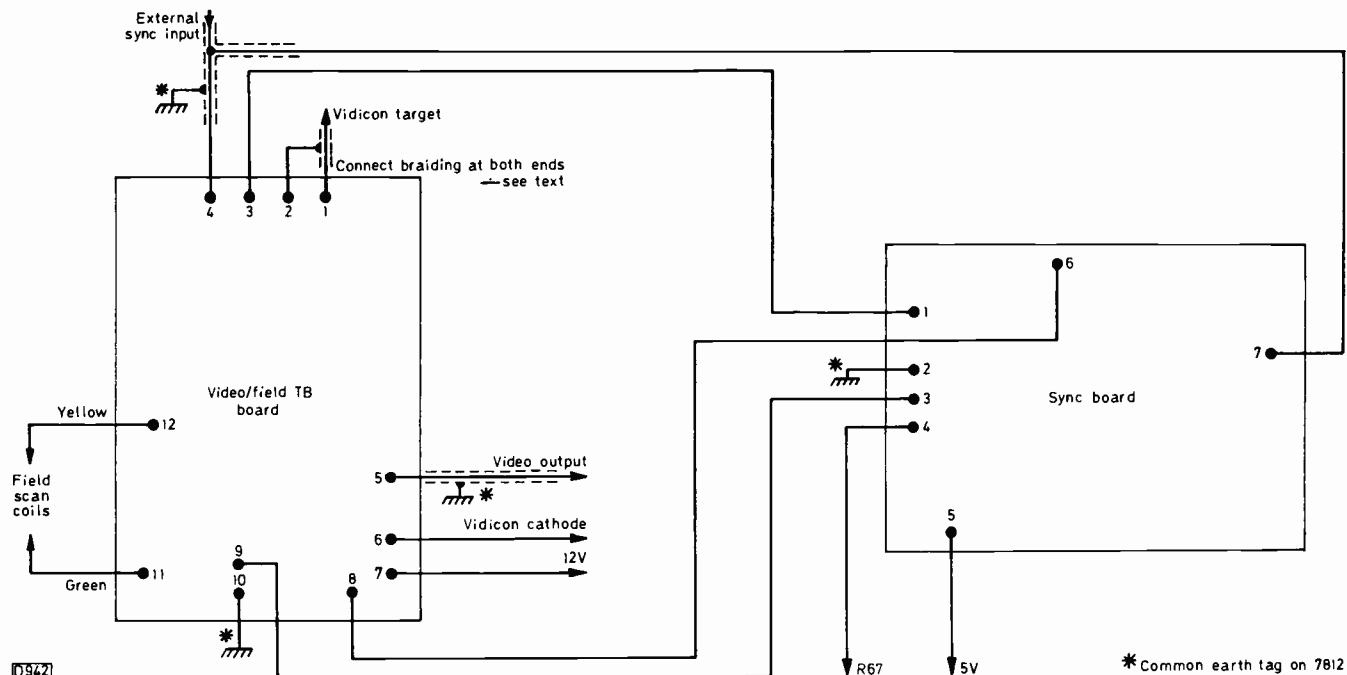


Fig. 18: Connections to the video/field timebase and sync pulse generator boards.

tube could cause permanent damage, it would be a wise precaution to add a 560Ω $\frac{1}{2}W$ resistor in parallel with R70 and VR9 to preserve some horizontal deflection in the event of failure of either of these components.

Precautions in Use

Don't point the camera at extremely bright lights or the sun. Avoid keeping the camera pointed at a scene for too long with a high target bias setting, otherwise you'll get a semi-permanent image. Avoid very contrasty scenes except for effect. Keep the lens capped, or at the very least at minimum aperture, when not in use. Keep the lens and target clean and free from condensation.

Inadvertent exposure to a bright light which causes an image burn-in can often be cleared by operating the camera pointed at a light card for a while. Unless the damage is severe, the marks will disappear after prolonged use.

Lens

Use a reasonably good quality lens. Those from 35mm etc. still cameras will generally give disappointing results and a severely reduced field of view. Unless you fit a zoom lens, a wide-angle lens will be adequate for indoor use. A telephoto lens may work well, but you'll have to keep well

back. This will give quite good close-ups at several yards range. The lens shown on our October cover is not suitable – it just happened to be the only one around when the cover photograph was taken.

Notes on Vidicons

Note that a vidicon works badly if under scanned – in fact its output can be undetectable. Apart from this, the target may retain an image of the raster, so that when the full scan is obtained this image will mar the picture. The secret of setting up is start with maximum scan amplitudes, which with some cameras will enable the whole target to be seen as a bright ball on the monitor. Then reduce the scans to normal. As the scans are reduced, the image intensity decreases and the picture size *increases*.

Vidicon tubes are cheaper than most other pickup devices. They nevertheless give good pictures under reasonable lighting conditions. The aims of the present camera design have been cheapness and simplicity. It has its limitations therefore. It can resolve 3-4MHz under good conditions however, the definition limitations lying mainly with the quality of the lens used and the operating conditions rather than the design of the video amplifier.

Vidicon Supply

The original prototypes were fitted with EMI vidicons. If difficulty is experienced in obtaining these, note that a vidicon of Japanese manufacture, type 8844, is available from Complete Video Systems, 49 Malden Way, New Malden, Surrey KT3 6EA.

Miscellaneous Points

The Verobox mentioned was used because it's one of the few cheap off-the-shelf cases that's suitable. One way of avoiding many of the screening problems associated with the video amplifier, and at the same time avoiding the need to use a lens mount, is to use a purpose-built metal case. A manufacturer of cases for security cameras has suggested that he would be prepared to supply cases for the project –

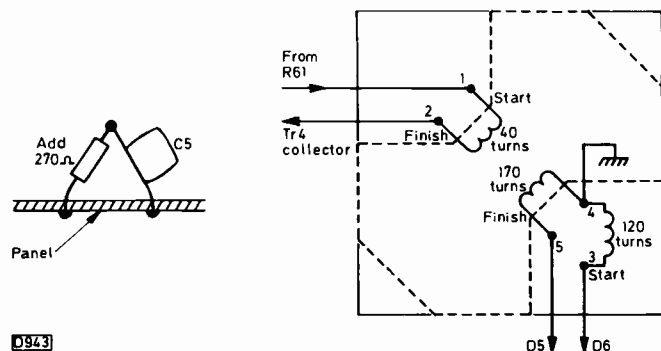


Fig. 19 (left): Adding a 270Ω resistor in series with C5.
Fig. 20 (right): Method of winding T1.

contact Mr. Wright, Robawn Engineering Ltd., Unit 1, Stobart Street, Sheepfold Industrial Estate, Monkwearmouth, Sunderland, Tyne and Wear.

In Part 1 it was stated that only the 7812 regulator needs

to be mounted on a heatsink. It was found to be advisable to reduce the current in the 7805 regulator however. In the event, it was finally decided that the simplest solution was to mount both regulators on a common heatsink. ■

★ Video camera components list

Resistors:

R1	1M	R57	5M6
R2	2k2	R58	2M2
R3	2k7	R59	1M
R4	270*	R60	220k
R5	2k2	R61	82 2.5W w.w.†
R6	10	R62	47
R7	1k5	R63	10
R8	100	R64	820
R9	1k5	R65	560
R10	10k	R66	47
R11	10k	R67	47
R12	1k	R68	10
R13	2k2	R69	47
R14	3k3	R70	270 2.5W w.w.
R15	560	R71	100k†
R16	820		0.25W, 5% carbon film
R17	1k2		unless otherwise stated.
R18	560		*See text.
R19	100		
R20	4k7		
R21	15k		
R22	270		
R23	470		
R24	1k5		
R25	47k		
R26	4k7		
R27	330		
R28	100k		
R29	47		
R30	22k		
R31	560		
R32	1k		
R33	150k		
R34	560k		
R35	470k		
R36	22k		
R37	10		
R38	47k		
R39	220k		
R40	100k		
R40a	3R3		
R41	4R7		
R42	22k		
R43	100k		
R44	1M		
R45	5k6		
R46	10k		
R47	1k		
R48	6k8		
R49	560		
R50	6k8		
R51	3k3		
R52	12k		
R52a	5M6		
R53	1M		
R54	33½W		
R55	33½W		
R56	33k†		

Presets:

VR1	100k miniature
VR2	1M miniature
VR3	100k miniature
VR4	4k7 miniature
VR5	2M2 see text
VR6	2M2 standard
VR7	2M2 standard
VR8	470 standard
VR9	100 standard
	All vertical mounting.

Capacitors:

C1	470p ceramic plate
C2	10µF 16V radial electrolytic
C3	4n7 ceramic plate
C4	680p ceramic plate
C5	4n7 ceramic plate
C6	22µF 16V radial electrolytic
C7	33n Siemens polyester
C9	10µF 16V radial electrolytic
C10	4µ7 35V radial electrolytic
C11	4µ7 35V radial electrolytic
C12	100µF 16V radial electrolytic
C13	22n Siemens polyester
C14	47n Siemens polyester
C15	100n Siemens polyester
C16	100n Siemens polyester
C17	150n Siemens polyester
C18	100n Siemens polyester
C19	100n Siemens polyester
C20	10µF 16V radial electrolytic
C21	100µF 16V radial electrolytic
C22	22µF 16V radial electrolytic
C23	33p ceramic plate
C25	100n Siemens polyester
C26	100µF 16V radial electrolytic

C27	1n ceramic plate
C28	680n Siemens polyester
C29	680n Siemens polyester
C30	470p ceramic plate
C31	10n 1% polystyrene
C32	2n2 ceramic plate
C33	1n ceramic plate
C34	1n ceramic plate
C35	100n ceramic disc
C36	470µF 16V radial electrolytic
C37	1n 750V ceramic disc
C38	1n 750V ceramic disc
C39	470n 630V polyester
C40	1n 750V ceramic disc
C41	1µF 450V axial electrolytic
C42	1µF 400V polyester
C43	100n 630V polyester
C44	470n 630V polyester
C45	100n 630V polyester
C46	100n 250V polyester
C47	2n2 500V polyester
C48	47µF 16V radial electrolytic
C49	4µ7 50V radial electrolytic
C50	4µ7 50V radial electrolytic
C51	47µF 16V radial electrolytic
C52	4n7 500V polyester
C53	47µF 16V radial electrolytic †
C54	47µF 16V radial electrolytic †
C55	47µF 16V radial electrolytic †
C56	1n 750V ceramic disc

Semiconductors:

D1	1N4148
D2	1N4148
D3	BY207
D4	BY207
D5	BY207
D6	BY207
D7	1N4148
D8	BY207
Tr1	BFW10
Tr2	BC214L
Tr3	TIP31
Tr4	BD131
Tr5	BD131
IC1	TBA500P
IC2	CA3046
IC3	TDA1170
IC4	555
IC5	74121
IC6	74123
IC7	74123
IC8	7400
IC9	7400

Power Supply:

2200µF 25V electrolytic
100n ceramic disc
220µF 16V radial electrolytic
470n Siemens polyester
10µF 16V radial electrolytic
BY164 bridge rectifier
7812 regulator
7805 regulator
1.5A fast fuse with p.c.b. fuse clips
15mm length of RS heatsink type 401-497
PCB

Miscellaneous:

Lens and C lens mount. See text
Verobox type 203 or alternative. See text
Mains on/off toggle switch
500mA anti-surge fuse and fuseholder
½in. vidicon EMI type 9831/AM or alternative. See text
Vidicon scan coil/focus coil assembly. EMI type KV12S or alternative to suit tube
VDR, Mullard type E299DD/P354
L1 and T1, wound on Mullard LA4543 core assembly with single-section bobbin and two retaining clips (Maplin Type 3 – order as HX09K, HX10L, HX11M). For winding details see Fig. 20.
Two 0-15V/0-15V 200mA 6VA mains transformers, Maplin order no. WB15R (two off)
Sockets for vidicon base, video output, external sync input and battery input.

†Value or rating change since circuit published.

Small-screen Monitor

Part 2

Luke Theodossiou

THE only circuit section not covered in last month's article is the power supply. A 5V regulator i.c. (IC4) is used, with its output voltage made variable from around +9.5V to +12V. This is achieved by placing a 4.7V zener (D9) and a 1k Ω preset in series with the common lead to the regulator. This has the effect of increasing the d.c. closed-loop gain, with a subsequent increase in output voltage. In order to maintain a high ripple rejection ratio, C32 decouples the common lead, thus reducing the a.c. gain to its original value. The output from the i.c. is used to drive the series pass transistor Tr5.

Construction

The single board design makes construction extremely easy, and constructors should not encounter any difficulties with this. We suggest starting off by inserting all the smaller components (e.g. resistors and diodes) and progressing on to the larger items. We strongly recommend that the components used are as in the components list, since the board is specifically designed for these.

A screened lead is required for the video input, with its screen going to connector A1. All other leads need not be screened. The input impedance exhibited by the TDA2150 is fairly high, and if required a 75 ohm resistor may be wired directly across the video input circuit for line termination. It may of course be made switchable. The contrast and brightness controls are both 10k Ω linear rotary or slider controls, with their tracks connected between +10.5V and earth and the wipers connected to the appropriate points.

The mains transformer should be a 15V 3A type with its secondary connected to connectors D2 and D3. If a d.c. supply is used, such as a car battery, this should be connected to D4 and D1, ensuring correct polarity.

The tube base board is the same as that used in the monochrome portable (reference no. D076), the exception being that the c.r.t. grid is now connected to +10.5V, which is available at the c.r.t. heater connector. It's a simple matter therefore to arrange for connector A to be bridged to connector B.

The circuit and component layout details for the c.r.t.

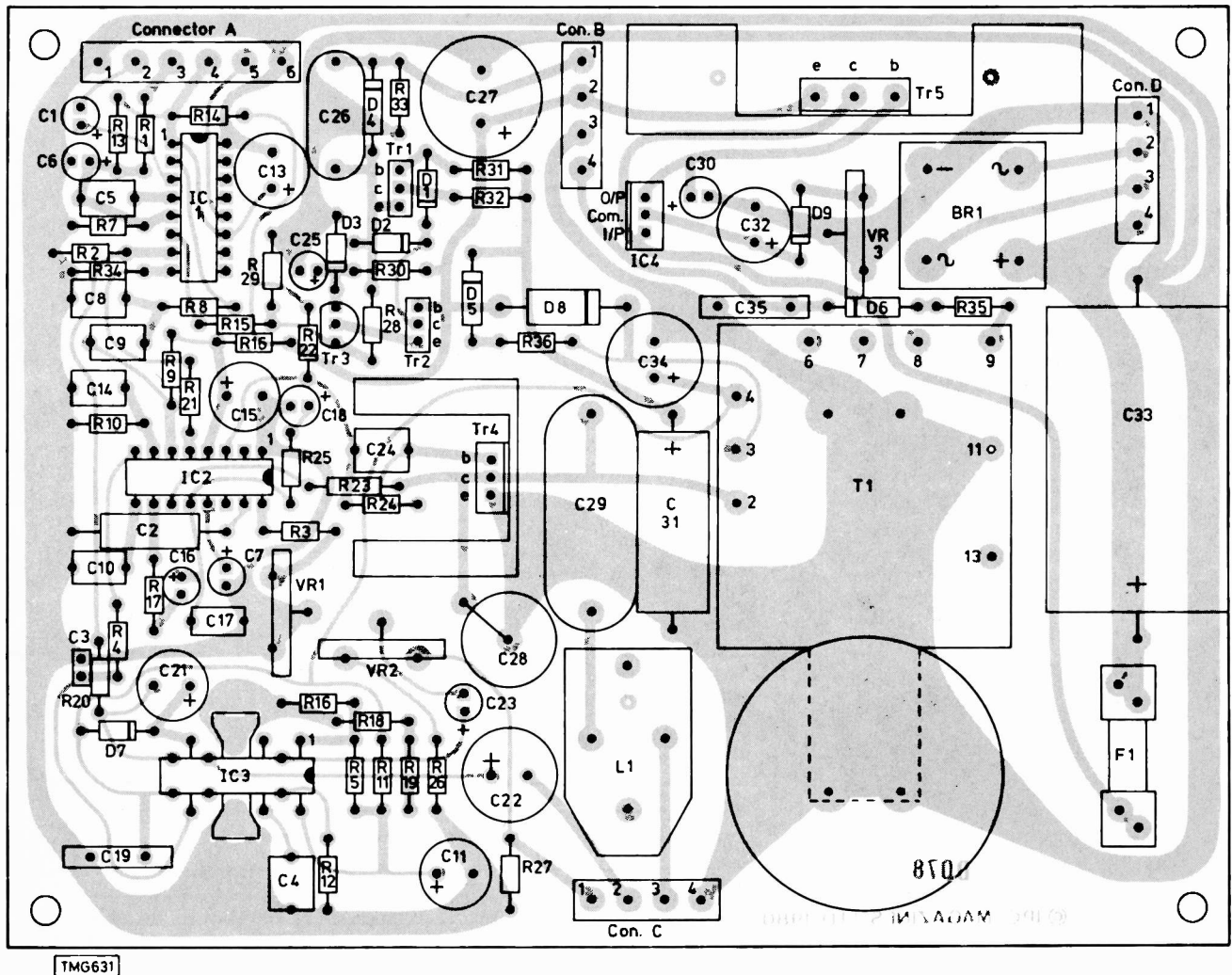


Fig. 3: Component layout on the printed board.

★ Monitor Components List

Capacitors:

C1	10 μ F 16V radial electrolytic
C2	10n 2.5% polystyrene
C3	10n ceramic plate
C4	150n Siemens polyester
C5	150n Siemens polyester
C6	10 μ F 16V radial electrolytic
C7	1 μ F 63V radial electrolytic
C8	150p ceramic plate
C9	330n Siemens polyester
C10	100n Siemens polyester
C11	100 μ F 16V radial electrolytic
C13	100 μ F 16V radial electrolytic
C14	330n Siemens polyester
C15	100 μ F 16V radial electrolytic
C16	22 μ F 16V radial electrolytic
C17	100n Siemens polyester
C18	4 μ 7 50V radial electrolytic
C19	100n Siemens polyester
C21	100 μ F 25V radial electrolytic
C22	470 μ F 16V radial electrolytic
C23	10 μ F 16V radial electrolytic

C24	330n Siemens polyester	R10	1k2
C25	10 μ F 16V radial electrolytic	R11	1k8
C26	220n 250V polyester	R12	180k
C27	1000 μ F 16V radial electrolytic	R13	68k
C28	33n 1000V mixed dielectric	R14	10
C29	2 μ 2 250V polyester	R15	1k
C30	10 μ F 16V radial electrolytic	R16	10
C31	10 μ F 250V axial electrolytic	R17	470
C32	220 μ F 16V radial electrolytic	R18	12k
C33	4700 μ F 25V axial electrolytic	R19	18k
C34	220 μ F 50V radial electrolytic	R20	100
C35	10n 750V ceramic disc	R21	1k

Resistors:

R1	39k
R2	100
R3	4k7
R4	3k3
R5	47k
R6	33k
R7	27k
R8	2k2
R9	1M



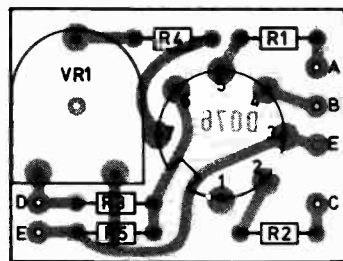
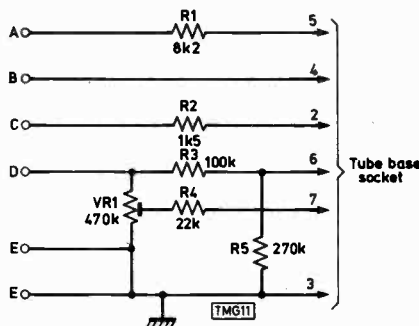


Fig. 4: Circuit and component layout, c.r.t. base board.

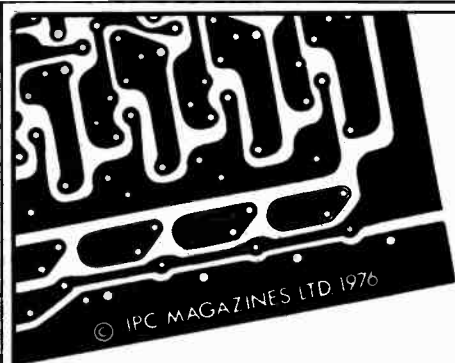

All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned.

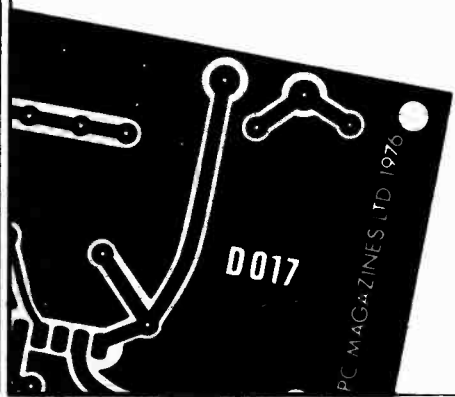Any correspondence concerning this service must be addressed to READERS' PCB SERVICES LTD, and not to the Editorial offices.



TELEVISION READERS PCB SERVICE

Issue	Project	Ref. no.	Price
November 1976	Ultrasonic Remote Control	D007/D008	£3.85 per set
March 1977	Teletext Decoder Power Supply	D022	£3.75
May 1977	Teletext Decoder Input Logic	D011	£12.50
June 1977	Wideband Signal Injector	D031	£1.00
June 1977	Teletext Decoder Memory	D012	£10.50
July/Aug 1977	Teletext Decoder Display	D013	£11.00
September 1977	Teletext Decoder Switch Board	D021	£1.75
April/May 1978	CRT Rejuvenator	D046	£3.00
October 1978	Colour Receiver PSU Board	D052	£4.00
January 1979	Colour Receiver Signals Board	D053	£10.75
February 1979	Commander-8 Remote Control System	D054/5	£6.00 per set
March 1979	Colour Receiver Timebase Board	D049	£17.13
July 1979	Colour Pattern Generator	D062	£14.50
		D063	£9.15
September 1979	Teletext Decoder Options Board	D064	£8.50
August 1979	Teletext Decoder New Mother Board	D065	£6.00
August 1979	Simple Sync Pulse Generator	D067	£4.00
September 1979	New Teletext Signal Panel	11331	£8.00
October 1979	Teletext Keyboard	D057	£3.50
October 1979	Teletext Interface Board	D058	£5.00
November 1979	Colour Receiver Remote Control	D066	£5.00
January 1980	Remote Control Preamplifier	D061	£3.75
February 1980	Teletext/Remote Control Interface	D070	£9.50
February 1980	LED Channel Display	D071	£4.00
March 1980	Improved Sound Channel	D072	£3.25
May 1980	Monochrome Portable Signals Board	D074	£6.25
June 1980	Monochrome Portable Timebase Board	D075	£7.75
July 1980	Monochrome Portable CRT Base Board	D076	£1.00
Sept/Oct 1980	New CTV Signals Panel	D077	£9.50
January 1981	Small-screen Monitor Board	D078	£8.50
December 1980	Video Camera Pulse Generator Board	D079	£4.50
December 1980	Video Camera Video/Field Timebase Board	D080	£5.50
January 1981	Video Camera Power Supply Board	D082	£2.00
January 1981	Video Camera Line Timebase/H.T. Board	D083	£4.00

To:— Readers' PCB Services Ltd. (TV), Fleet House, Welbeck St., Whitwell, Worksop, Notts.

Please supply p.c.b.(s) as indicated below:

Issue	Project	Ref.	Price

Prices include VAT and post and packing. Remittance with order please.

NAME _____

ADDRESS _____

Post Code _____

R22	330	Semiconductors	D1	1N4148
R23	100k, ½W		D2	1N4148
R24	680		D3	BZY88 C3V6
R25	1k2		D4	BY206
R26	100		D5	BY206
R27	2R2		D6	BY207
R28	47k 2% thick film		D7	1N4001
R29	2k2		D8	BY298
R30	2k2		Tr1	BF458
R31	22k 2% thick film		Tr2	BF458
R32	1k		Tr3	BC182L
R33	330k		Tr4	BU807
R34	1k		Tr5	TIP33
R35	330		BR1	RS Components 262-078
R36	10		IC1	TDA2150
0.25W, ± 5% carbon film			IC2	TDA9513
unless otherwise shown			IC3	TDA1044
			IC4	7805

Miscellaneous:

- P.c.b. ref. no D078
- Heatsink for Tr4: RS Components 401-964
- Heatsink for Tr5: RS Components 401-497 (50mm)
- L1, T1, scan coils: Set of wound components available from Manor Supplies
- Mains transformer: Secondary 15V, 3A
- Mains on-off switch
- Mains fuse (500mA A/S) with holder
- F1 2A A/S
- Contrast control 10k lin.
- Brightness control 10k lin.
- C.r.t. base board ref. D076
- Base board components (see Fig. 4)
- Video input socket (e.g. 75Ω BNC)

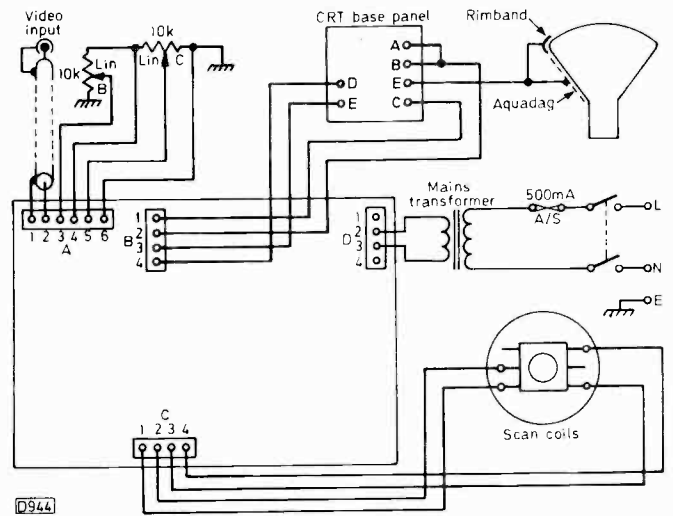


Fig. 5: Interconnection diagram.

base board are shown in Fig. 4. We recommend the use of 0.5W carbon composition resistors on this panel. Figs. 3 and 6 show the main panel details.

Connecting Up

An interconnection diagram is shown in Fig. 5 and is self-explanatory. We understand that Manor Supplies will provide a connection diagram for the specific scan coils which will be supplied – those shown on the diagram are a guide only. ■

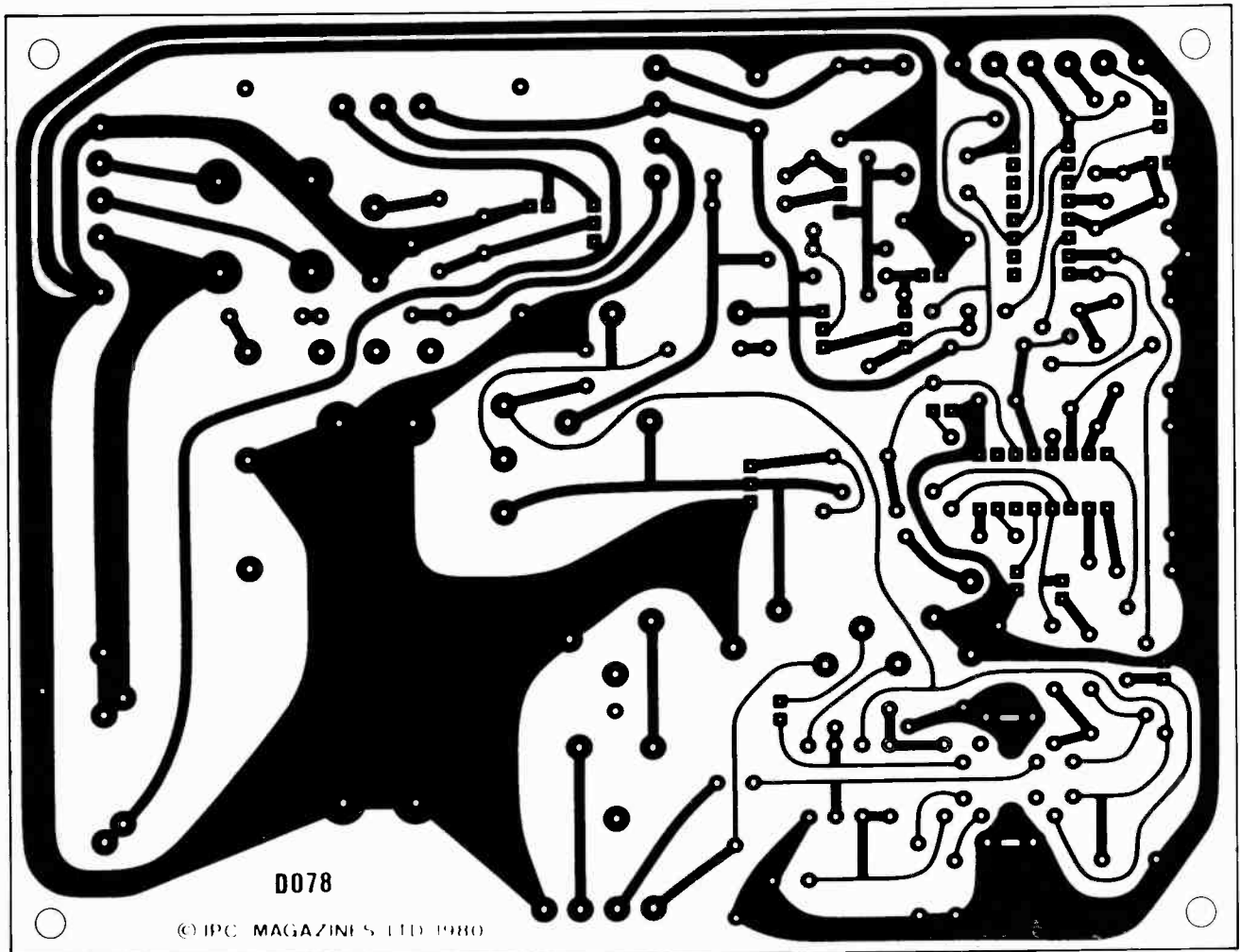


Fig. 6: Printed board print pattern.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a 75p postal order (made out to IPC Magazines Ltd.), the query coupon from page 156 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

GEC 2040

The trouble is sibilance after the set's been on for about three-four hours. Since the fault seems to be temperature dependent I tried running the set with the back removed. This made no difference. The quadrature detector coil has been adjusted, but again this didn't help. The trouble is worse when the volume is set to a low level. A new audio output valve has been fitted, and the voltages around it are all about right.

Sometimes the loudspeaker cone warps when the set has warmed up, giving this effect. Fit a new speaker, then trim the quadrature coil for best results – Angela Rippon's speech is ideal for this purpose!

BEOVISION 3400 CHASSIS

There's ample e.h.t. but no raster, with the c.r.t.'s cathodes at around 220V. Disconnecting the luminance output valve's anode load resistor and operating the service switch produces a horizontal line across the screen, but this is the only result I can obtain.

We take it that the c.r.t. heaters are alright – if not, the 6A feed fuse will have failed. Otherwise it seems that the tube is incorrectly biased. The voltage at the cathodes is about right, so check for 100V at the grids (if low, check the voltages around the tracking circuit transistor 3TR3), for 350-650V at the first anodes (if missing check 8D9/8C32), and for 4-5kV at the focus pin 9.

PYE 697 CHASSIS

This set was bought as a non-worker, but after replacing the e.h.t. tripler and the field output transistors I found that it was in good shape. The main problem is poor interlace, which tends to spoil the fine picture detail.

Interlace can be tricky on this chassis. The sync separator transistor VT7 is on the i.f. panel, and we suggest checking around the integrating circuit R36/C41 and the interlace diode D4. Our guess is that C41 (0.0047 μ F) has changed value.

THORN 1500 CHASSIS

The initial fault was no e.h.t. This was traced to defective scan coils which damped the line output stage. On connecting an aerial, a broken up, negative picture was obtained. The contrast control had no effect, but adjusting the r.f. gain control produced a normal, synchronised but very noisy picture. I then discovered the preset contrast control, and by juggling with this and the r.f. gain control obtained a noise free picture, though lacking in punch as far as the contrast is concerned and with the whites apparently

clipped. The setting of the preset contrast control is very critical – all or nothing or complete lack of sync.

Since the main contrast control has no effect, we'd start by checking the electrolytic coupling capacitor C37 which is connected in series with it. The preset contrast control sets the level of signal tapped off to the a.g.c. circuit, so it's possible that there's a fault here. If the a.g.c. department is in order, the voltage across C11 should be about 6.7V. Suspects in the a.g.c. circuit are the electrolytics C3 and C6 and the transistor VT3. If these checks fail to reveal the cause of the trouble, it's likely that one of the 0.01 μ F ceramic decouplers in the i.f. strip is leaky. Check C8, C13 and C25. A low emitter voltage reading will reveal the defective stage.

GEC C2110 SERIES

The trouble with this set is that the field hold is very poor – very delicate adjustment of the field hold is necessary, and on some days the rolling cannot be stopped. When the defect is worst, the picture loses half an inch at the top and bottom. An improvement has been obtained by reducing the setting of the height control.

The cause of the trouble could be in the field timebase or the power supply. The usual cause of field hold problems on the field timebase panel is the electrolytic C452 (4.7 μ F) which decouples the emitter of the field sync pulse amplifier transistor TR451. If the trouble is due to a power supply fault, the suspects are the BT106 regulator thyristor and its BR100 trigger diac.

RANK A823 CHASSIS

There's a perfectly good monochrome picture, and sound, but no sign of colour. The 18V supply to the decoder board is present, and disabling the colour-killer makes no difference. The voltages around the SL901 i.c. are correct, but the voltages around the transistors in the burst/reference oscillator section are haywire. The transistors themselves have been checked and found to be in order.

The first thing to establish is whether the chroma signal is reaching the decoder – most of the chroma amplification is carried out on the i.f. panel in this chassis. The chroma comes into the decoder panel at plug 3Z1-9 – check at test point 3TP3. If the chroma signal is arriving at the decoder panel, it's possible that the pulses from the line output stage aren't. They should be present at 3TP1. If they are, they may still not be getting anywhere much if diode 3D3 in the feed to the burst gate pulse generator tuned circuit is open-circuit. It would be worth checking 3C43 (100 μ F) in the crystal oscillator circuit.

HITACHI CNP190

The user brightness control now has to be at maximum to get a reasonable picture. Is there a preset brightness control, and if so how should it be set?

The internal brightness control R310 is labelled sub-brightness and is in the corner of the signal panel opposite the cut-out corner. The drill is to set the user brightness control to midway, then adjust R310 for the correct brightness level, i.e. keep the black but allow full brightness. One wonders why the brightness level has changed however? Check the tube's first anode voltages (pins 4, 5 and 13), which should be at about 400V. If this voltage cannot be achieved, check back to the supply resistor R722 (120k Ω) on the deflection panel – there should be about 560V at connector L1. If all's well here, it would be an idea to check the 10 μ F electrolytic (C312) in the brightness control circuit.

BEOVISION 2600/3200 CHASSIS

A faint vertical stripe is present on the left-hand side of the screen, about 2½ in. from the edge. The stripe is about half an inch wide and is red on the left, green on the right. It's present on colour and monochrome programmes, and with no signal, though it only shows up against a dark background – if the screen is brightly illuminated on the left-hand side, the stripe is not visible. The video valves (12HG7 and ECL84) and the clamp diodes (EAA91s) have all been replaced. Another problem with the set is that the field hold is at times very touchy – i.e. it needs careful adjustment, works correctly for a while, then loses lock again. A new ECC81 field oscillator valve has been fitted.

To deal first with the field sync problem, fit a new PL508, then adjust the adjacent d.c. balance potentiometer 501 for zero voltage at the valve's control grid (TPg3). If the fault persists, check the BC110 field sync amplifier transistor. The colour striation is often caused by leaky diodes in the pulse feeds to the signal circuits. Check D513 (OA81) in the feed to the cathode of the 12HG7, and the BA148 diodes D578/580 in the feeds to the EAA91 clamp diodes. Also check the anode load resistor (R202, 4.7kΩ) in the ECL84 blanker circuit.

EKCO T554

The trouble with this Japanese made monochrome portable is a faulty regulator transistor. I'm having difficulty getting a replacement however. Any suggestions?

The l.t. regulator transistor used in this model is type 2SA473Y. It's a silicon pnp device rated at 3A. A BD204 would be a suitable replacement, or a 2N6126.

TV GAME

My Pye colour set (697 hybrid chassis) provides perfectly normal off-air reception, but I can't get locked colour with a TV game that was bought. The game has been tried on a Sony colour set and gives correct colour. No fault can be found on the Pye set, which will handle games in monochrome, with correct sound and sync. Adjusting the fine tuner on a colour game produces broken colour without sound, but the colour fades away very quickly when the tuning is corrected.

It could be that the colour game's burst timing is non-standard and that the Sony set doesn't object to this. In the Pye hybrid colour chassis the burst gate pulse is derived from the sync pulse in the incoming signal, with the delay set by the tuned circuit L28/C126. It would be an idea to see whether slight adjustment of L28 helps matters.

COMBI COLOUR

The trouble with this set is that the e.h.t. overwinding on the line output transformer keeps burning out. The GY501 e.h.t. rectifier has been replaced, but the problem persists. One replacement transformer lasted for only three weeks, while another lasted just three days. And they're not cheap!

The line output stage in these sets often runs hot, with the result that everything gets overheated. Some of them were not adapted for 240V operation, being originally designed for 200V operation on the Continent. To get the heater voltage down, fit an additional 50Ω resistor in the heater chain (assuming that the set uses a conventional diode plus resistor dropper circuit – some of them used a paper capacitor). Doing this will considerably reduce the heat in the line output stage. Check that the e.h.t. is not too high, resetting if necessary with the horizontal amplitude control R517 – adjust for normal picture width. Also check C501 (180pF) in the line drive waveform shaping circuit. The set

will still work if this goes open-circuit or low in value, but the drive to the PL509 will be excessive and R517 may have been offset to compensate. The early transformers used on these sets were notorious, but the Mk. 2 version is more reliable. Converting to tripler operation would help keep down the cost of the repair.

RANK A774 CHASSIS

The trouble with this set is that the picture pulls to the right (viewed from the front). BBC-2 is perfect, the problem being on BBC-1 and ITV. On a BBC-1 test card the circle tends to have ripped edges and there's picture pulling, approximately two inches, across the top, the rest of the picture being perfect.

First ensure that the contrast control is not advanced farther than is necessary to produce a reasonable picture, as this fault is usually due to the video output stage being overloaded. Check the settings of the preset controls on the left-hand side of the chassis, particularly the video bias control 2RV1. If the fault persists on certain channels only, check the aerial.

DECCA 80 CHASSIS

The TBA920 sync/line oscillator i.c. was replaced to cure intermittent field rolling and slow upwards jumping of the field, and the TDA1170 field timebase i.c. has been replaced to cure distortion at the top of the raster. The only problem now is that once or twice during an evening's viewing the picture will jump vertically – only one field. Could this be due to the camera at the transmission end, or is there another fault in the set?

This effect sometimes occurs on ITV as the local station comes on or off the network. If it occurs on BBC as well, R301 (2.2MΩ) which biases the sync input pin of the TBA920 is suspect.

SABA H CHASSIS

After a while any vertical lines in the bottom half of the picture appear wavy. This is accompanied by trapezium distortion. Also the brightness control is at maximum and although the picture is normally quite good the screen appears to be blank on dark scenes.

The preset controls P701 (EW phase) and P702 (EW amplitude) often overheat after the set has been running for a time. They then go open-circuit, producing the bent verticals and distortion described. Try slight readjustment of each control in turn when the fault condition occurs – this often re-establishes continuity, the bent verticals jumping back to a straight position. Readjusting the preset brightness control P357 at the centre bottom of the signals board usually provides an acceptable picture brightness level.

THORN 1500 CHASSIS

There's a sharp, clear raster but no picture. The sound is perfect, and when the set is switched off the picture appears momentarily and then fades out. I've checked around the video circuit without finding anything amiss.

This sounds like a classic case of a.g.c. trouble – confirm by checking the voltages around the a.g.c. amplifier transistor VT3. If the voltages here are wrong, check VT3, the a.g.c. detector diode W1 and the a.g.c. reservoir/smoothing electrolytics C3/6. D.C. voltage checks are the clue to this trouble. We've also had trouble with C8 and C13 leaking. These 0.01μF capacitors decouple the emitters of the two gain-controlled i.f. transistors, thus affecting the voltages in the first two i.f. stages.

SANYO MODEL CTP5101

The initial symptom with this set was that the height collapsed to about four inches. The set was left for a couple of days, and on switching on gave a normal picture for the first evening. On the second evening the picture started to come up from the bottom, and now seems to be quite stable with the picture about an inch short at the bottom. Voltage checks reveal that the voltage at the collector of the discharge transistor Q423 (type 2SC536 or 2SC945) is substantially down at 1.8V instead of 8.5V. Any ideas for a suitable replacement for this transistor?

The field timebase circuitry used in these sets is usually extremely reliable, so we've little experience of faults in this area. The low voltage you mention could be due to leakage in the discharge transistor Q423 or in the field charging capacitors C429/C430, to a changed value resistor in the charging circuit or incorrect drive to Q423 from the preceding oscillator stage. The transistor and the capacitors are the most likely suspects – a BC107 can be used in the Q423 position.

BEOVISION 3200

The trouble is no line sync with weak field sync. On detuning a poor picture with reasonable sync is obtained, but with correct tuning the line won't lock and the picture appears to be over-contrasted, though the control does provide some variation. The fault is not in the tuner or the i.f. panel, as with good replacements fitted the fault is still present. The only other thing I can tell you is that there was a burn up in the line output stage, as a result of which a new line output transformer had to be fitted and some capacitors replaced.

If the output transformer that had to be replaced was the scan one (8014108) rather than the e.h.t. one, make sure that you correctly phased the pulse winding feeding the a.g.c. gate via pins 8/9 of plug 3. This is the small sleeved winding on the spare transformer limb and is easily connected back-to-front. Check also the 12V zener diode 112 and the screened leads that carry the sync signals around the main chassis – these have a habit of going short-circuit. Finally, ensure that the N +30V line is in order.

TEST CASE

217

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

With all types of sets tuning drift is these days a major headache for the serviceman. Far from solving the problems of tuning drift and poor resetting, the introduction of varicap tuners and, in some cases, the fiendishly complex circuits used for tuning and remote control channel selection have meant an increase in the workshop load. Gone are the mechanical dark ages when a squirt of jungle juice sufficed to clear such problems!

A recent case in point was a Tandberg colour set which arrived in the workshop for attention due to a tuning drift problem – it was one of the sets fitted with the CTV2-2 chassis. As a first step, the voltage on the varicap tuning line was monitored. This remained stable, so the diagnosis reached was that the tuner unit itself was responsible. It's the familiar ELC1043/05 type, so the decision was made to fit a replacement. The unit used was a pin-compatible one made by Elpro.

On switching on and tuning in, the long-suffering technician was confronted with a very snowy, barely-locked picture. This prompted him to check the connections to the panel and the aerial connections to the tuner. These were all in order, so as the latest fault seemed to have been introduced by the new tuner another one, of the same make, was fitted. The results were exactly the same.

With the prospects of any profit from the job rapidly receding, the original tuner unit was replaced in the set. The

result was a noise-free picture, but with the original drift problem still present. The cause of the problem was eventually traced – it turned out to be a rather obscure one – and the set was then sent off in good working order. Now for a hint: for those not familiar with these sets, there are two tuners, an ELC1042 for v.h.f. reception and the ELC1043/05 for u.h.f. reception. This is relevant to the unusual fault!

SOLUTION TO TEST CASE 216

– page 98 last month –

The paradoxical symptoms with last month's Rank A823 receiver were an overheating h.t. filter resistor (8R15) though there was no excessive d.c. flowing through it – in fact the d.c. was quite low. The next test made, the one that provided the vital clue, was to measure the a.c. flowing through the resistor. This revealed the presence of a very heavy ripple current. Everything then clicked into place! The h.t. reservoir capacitor 8C9 had gone virtually open-circuit, with the result that the h.t. smoothing capacitor 8C10 was being asked to perform both roles. In consequence, the average d.c. voltage across 8C10 was low – hence the low h.t. output – while the ripple current flowing through 8R15 and 8C10 was sufficient to heavily overload the resistor.

The circuit used in this power supply is relatively simple, and it's easy to be blasé about fault diagnosis. As this example shows, there are still traps for the unwary!

QUERY COUPON

Available until 21st January, 1981. One coupon, plus a 75p (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 154.

TELEVISION JAN. 1981

Published on approximately the 22nd of each month by IPC Magazines, Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by Carlisle Web Offset, Newtown Trading Estate, Carlisle. Distributed by IPC Business Press (Sales and Distribution) Ltd., 40 Bowling Green Lane, London EC1R 0NE. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £10, Overseas £11 per annum payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

★ NEW ★ COLOUR BAR GENERATOR

U.H.F. AERIAL INPUT PATTERN GENERATOR CPG6-RF

All Facilities of our PG6RF



PLUS COLOUR BARS.

Produces 7 invaluable patterns.

**Robust, Battery Powered, Pocket Sized Unit,
Plugs Straight into Aerial Socket.**

W H I T E	Y E L L O W	C Y A N	G R E E N	M A G E N T A	R E D	B L U E	B L A C K
-----------------------	----------------------------	------------------	-----------------------	---------------------------------	-------------	------------------	-----------------------

FEATURES:

- ★ CROSSHATCH GRID
- ★ DOT MATRIX
- ★ VERTICALS
- ★ PLUS PAL COLOUR BARS;
ONLY 3 SIMPLE ADJUSTMENTS.
- ★ PG6RF OWNERS; Buy Add-On 'C6' Unit!
- ★ HORIZONTALS
- ★ WHITE RASTER
- ★ GREYSCALE

ORDER NOW!

PG6RF KIT £25.87 BUILT £33.35 – As per TV Review, Jan. 1979

C6 KIT £18.98 BUILT £26.45 – Add-on Colour to PG6RF

CPG6RF KIT £42.55 BUILT £63.25 – Both above combined.


These prices INCLUDE P & P and 15% VAT. Export VHF versions available.

In response to demand we have produced an add-on Colour Bar unit C6 to upgrade the PG6RF to PAL COLOUR. A MUST for TV construction or servicing! Available as a KIT or BUILT & TESTED. Kit includes all components and ready built modulator etc. Hundreds sold, reliable design.

Full 12 month guarantee on built units.

MAIL ORDER ONLY

Quantity Discount
on application

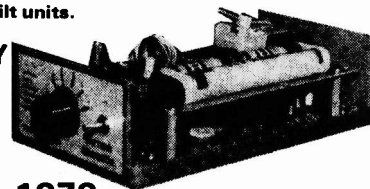

ACCESS
ORDERS
WELCOME

PLEASE NOTE OUR NEW ADDRESS. ORDER FROM:—
TECHNALOGICS LIMITED (DEPT. TV)
WINDMILL WORKS, STATION ROAD,
SWINTON, MANCHESTER M27 2BU.

TELEPHONE: 061-793 5293

TV LINE OUTPUT TRANSFORMERS

by FAST RETURN OF POST SERVICE
PRICES INCLUDE P. & P. & 15% VAT

COLOUR TRANSFORMERS

DECCA	CS1730, 1733, 1830, 1835	} £10 RETAIL £9 TRADE (Trade Orders only)
DECCA	30 series Bradford Chassis	
DECCA	80, 100 series	
ITT	CVC 5 to CVC 9	
ITT	CVC20, CVC30, CVC 32	
PHILIPS	G8, G9 Chassis	
PHILIPS	K80 (Rewind only – old unit required – £12)	

WINDINGS

BUSH	Colour Hybrid quadrupler type	£6.00
RANK	T20A chassis	£6.00
PHILIPS	G6 EHT Overwind (exchange basis only)	£7.00
PHILIPS	G6 Primary	£5.00
PYE	691 to 697 EHT Overwind ★	£3.00
PYE	691 to 697 Primary Winding ★	£4.00
EMO	90 degrees	£7.00

★ please state which

MONO LOPTS

Most British & Foreign
makes supplied.
£9 RETAIL £8 TRADE
Separate windings
also available.

REWINDS
Rewind Service Available
Mono or Colour
SAE all enquiries.

Open Mon. – Fri. 9 to 5.30 pm Callers Welcome.

All lopts and windings are new and guaranteed for 6 months.

**PAPWORTH
TRANSFORMERS**
80 Merton High Street
London SW19 1BE

Barclaycard and
Access welcome



01-540 3955

ARE YOU

USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling **used colour televisions from home** in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial CASH INCOME with a starting capital of less than £20. Our new unique publication "**How to Deal Successfully in Used Colour Televisions**" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have 'pooled' their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can **succeed immediately**.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure **certain success**. Indexed information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail – for both televisions **and** new/used spares. Monochrome sets are also covered, as are "invisible" cabinet repairs. **Plus FREE on-going advice and FREE regular updating service.**

You can start tomorrow – but you'll need our guide. The latest big illustrated edition is out now, and costs just **£4.95** – a small price to pay for financial independence!

ORDER TODAY FROM:

GLOBUS INDUSTRIES LTD., UNIT 18, DARLEY ABBEY MILLS, DERBY.

To: Globus Industries Ltd., Unit 18, Darley Abbey Mills, Derby.

Please send by return post "How to Deal Successfully in Used Colour Televisions".

I enclose cheque/p.o. for **£4.95**.


NAME

ADDRESS


TOP QUALITY REBUILT TV TUBES

Rebuilt on the most modern equipment to original manufacturers specification

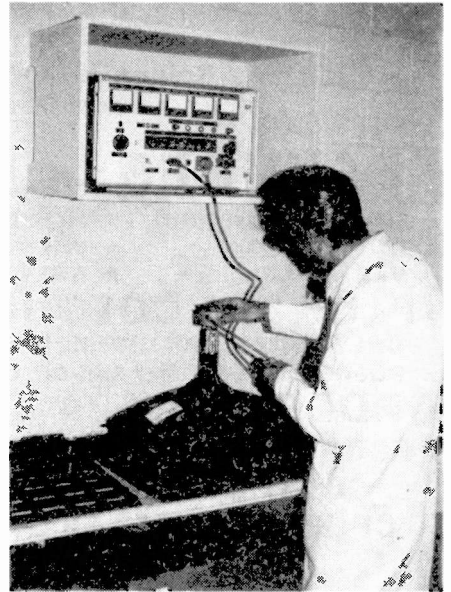- ★ HIGH FOCUS
- ★ LONG LIFE
- ★ FULLY TESTED
- ★ FULLY GUARANTEED



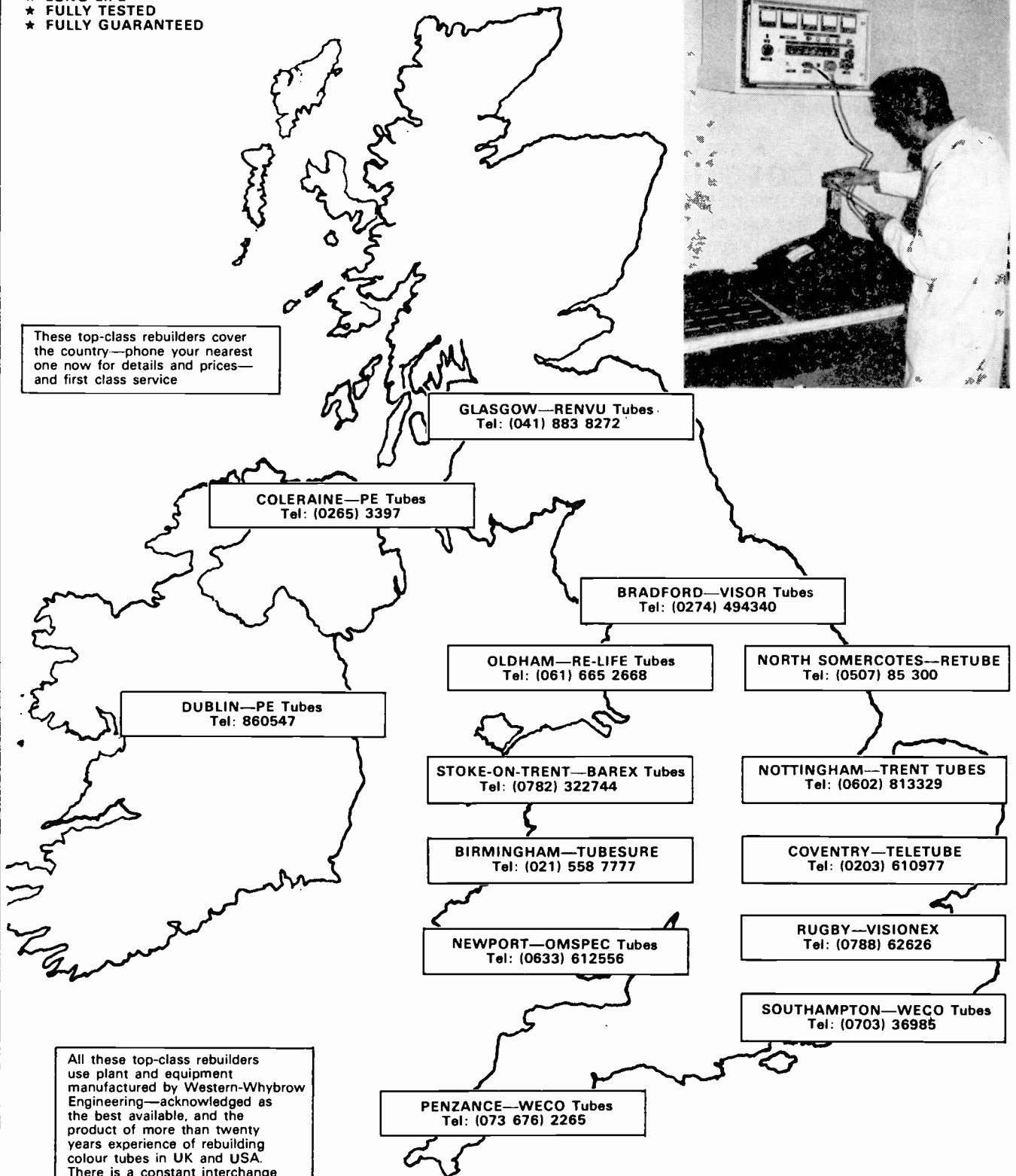These top-class rebuilders cover the country—phone your nearest one now for details and prices—and first class service



All these top-class rebuilders use plant and equipment manufactured by Western-Whybrow Engineering—acknowledged as the best available, and the product of more than twenty years experience of rebuilding colour tubes in UK and USA. There is a constant interchange of information to ensure the highest standard of rebuilt tube.

WMTV LTD. – THE TV PROFESSIONALS



THE BEST DEAL IN TV's

- ★ Britain's most reliable source of Quality T.V.'s.
- ★ Hundreds of working polished T.V.'s.
- ★ Full customer testing facilities.
- ★ Thousands of untested S/S Colour T.V.'s from **£10**.
- ★ Quantity deliveries arranged anywhere in Britain or the World.

Special Deals

- ★ Mixed 25" 4 for **£30**
 - ★ GEC 19" 10 for **£100**
 - ★ BRC 26" 10 for **£250**
 - ★ Pye 691 22" **£12** each
 - ★ Continental Mix 5 for **£100**
 - ★ PYE 205 22" 10 for **£199**
- All above prices are plus 15% V.A.T.*

RING 021-444 6464 FOR DETAILS OF QUANTITY DISCOUNTS

MAIL ORDER TV's – Working Colour TVs supplied by Mail Order and fully tested before despatch.

- ★ GEC 2100 22" **£45** ★ PYE 205 22" **£60**
- ★ BRC 22"/26" **£70** ★ BUSH 184 22" **£40**
- ★ BRC 8000 17" **£65** ★ BUSH A823 22"/26" **£60**

Above MAIL ORDER prices include V.A.T. but please add £12 p & p/T.V. Set.

- ★ New T.V. Stands.
- ★ Fully adjustable.
- ★ **£6.25** plus £1.75 p & p.
- ★ Quantity discounts.
- ★ Price inc. V.A.T.



EXPRESS MAIL ORDER SPARES

★ Ex-equipment Panels

	Con	Power	Line	Decoder	Video	IF	Frame	Tripler	LOPTX
RBM 823	7.00	6.00	14.00	14.00	—	6.00	9.00	3.00	3.00
BRC 3000	6.00	12.00	12.00	6.00	6.00	6.00	6.00	4.00	6.00
BRC 3500	9.00	12.00	12.00	6.00	6.00	6.00	6.00	4.00	6.00
GEC 2100	6.00	—	—	8.00	6.00	6.00	10.00	5.00	5.00
PYE 205	6.00	—	12.00	8.00	7.00	6.00	5.00	5.00	7.00

Postage & packing **£1.25** Panels **50p** Triplers

Ex-Equipment Valves

	Tested	Untested
ECC82	20	10
PCF80	20	10
PCF802	18	9
PCL82	20	10
PCL84	20	10
PCL85/805	18	9
PCL86	20	10
PFL200	20	10
PL36	23	10
PL504	23	10
PL508	35	18
PL509	90	30
PL519	£1.00	40
PL802	£1.35	—
PY500	45	20
PY800/81	20	10
PY801/88	20	10
30FL1/2	30	20

- ★ p & p paid but minimum order of £3.00 please.
- ★ Deduct 10% discount on orders over £20.00.

Ex-Equipment Colour Tubes

All fully tested

17" (A44-271X)	£18.00
18" (A47-342X)	£18.00
18" (A47-343X)	£18.00
19" (A49-191X)	£18.00
20" (A51-120X)	£25.00
22" (A56-120X)	£17.00
25" (A63-200X)	£10.00
26" (A66-120X)	£20.00
26" (A67-120X)	£17.00

Please add £5.00 p & p per C.R.T.

Equipment Spares

*Always available

- ★ Colour and Mono Scan Coils **£1.50** + £1.00 p & p.
- ★ Tuners for all makes of Colour and Mono **£4.00** + £1.00 p & p.
- ★ Mono tubes fully tested. All Sizes – please state size on order **£3.00** + £4.00 p & p.
- ★ Reconditioned 50p meters **£92.00/Box of 10** incl. p & p.
- ★ PLESSEY SL918 colour ICs with ● circuit for substitution of SL917 **£2.00** + 25p p & p.
- ★ NEW VHF/UHF Varicap Tuners with circuit and full data **£1.25** + 75p p & p.

WE ARE OPEN MON-SAT 9.30-5.45

PLEASE NOTE – ALL THE ABOVE MAIL ORDER PRICES INCLUDE 15% V.A.T.

**WMTV LTD. 92 HIGH ST (A435) KINGS HEATH B'HAM B14 7JZ TEL. 021-444 6464
021-444 2575**

THE FAMOUS BI-PRE-PAK

CROSS HATCH GENERATOR

THOUSANDS SOLD!



More than ever these days, a cross hatch generator is absolutely essential to TV engineers, etc. It is the only accurate way to align all three guns in colour TV. The proven reliability, small size, easy operation and stability of this truly famed instrument is such that we are offering it once again, but this time, when stocks have been sold, it is not likely that supplies will be available again at anywhere near present prices. With improvements incorporated – plug-in I.Cs for example – it is going to be wanted more than ever. Many thousands are in regular use by TV renters and suppliers, etc. As this Generator is a VIDEO FEED UNIT and NOT R.F., it can be used anywhere overseas without having to worry about frequency matching. Operates from its own self-contained standard batteries.

DESIGNED SPECIALLY FOR COLOUR T.V. CONVERGANCE

● **EASY BUILD KIT** with instructions **£14.50**

● **READY BUILT AND TESTED** (Less Batteries) **£16.75**

Prices include V.A.T. and postage in U.K.


● **LIMITED STOCKS SO PLEASE ORDER PROMPTLY.**

- ★ VERTICAL/HORIZONTAL/DOT/CROSS HATCH PATTERNS
- ★ FOUR POSITION PATTERN SELECTOR SWITCH
- ★ TOUGH FIBRE GLASS CASE 5½" x 3" x 3"
- ★ OPERATES FROM SELF-CONTAINED BATTERIES
- ★ VERY EASY TO CARRY AROUND – REQUIRES NO EXTERNAL POWER SOURCE
- ★ PLUG-IN I.Cs AND SENSITIVE SYNC PICK-UP CIRCUIT
- ★ FUNCTIONS TO FULL PROFESSIONAL AND COMMERCIAL REQUIREMENTS
- ★ FOR PROMPT, NO DELAY DELIVERY
- ★ IN KIT FORM OR READY-BUILT, TESTED AND GUARANTEED

ORDER DIRECT FROM **BI-PRE-PAK LTD.** 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF
Telephone (0702) 351048 – Shop Hours 9.30 am–6.00 pm.

TELEPART

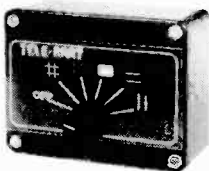13 WORCESTER ST.,
WOLVERHAMPTON,
WV2 4LJ
Tel: (0902) 773122
Telex: 336810



Telepart Pattern Generator

- Exceptionally light and durable
- Pocket size for outside service
- PP3 battery power source
- Five different test patterns for colour and mono TV
- Cross hatch grid
- Dot matrix
- White raster
- Horizontals
- Verticles

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customers home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

PRICE £14.95 (Subject to V.A.T.)

Telepart Colour Bar Generator

- Exceptionally light & durable
- Compact 13 x 17.5 x 5.5 cms
- Battery powered for mobility
- Cross hatch grid
- White raster
- Grey scale
- Colour bars
- Sound

A Versatile Generator for Servicing or aligning mono or colour TV receivers. Lightweight and very compact for outside service. Features sound facility often not found on more costly generators.

PRICE £49.95 (Subject to V.A.T.)

Power Supply

A Power Supply can be supplied for the Telepart COLOUR BAR GENERATOR. This compact unit mounts by 2 screws into the Battery compartment and converts the unit to a bench instrument.

PRICE £5.50 (Subject to V.A.T.)

QUALITY TV'S ALWAYS AVAILABLE

GOOD STOCKS OF MODERN COLOUR
PLENTY OF SINGLE STANDARD MONO
VERY COMPETITIVE PRICES
COME TO THE BEST IN THE WEST

TELETRADERS

ST. LEONARDS WAREHOUSE
ST. LEONARDS ROAD, NEWTON ABBOT, DEVON
Telephone: (0626) 60154

APOLLO

HIGH TEMPERATURE PUMPED COLOUR TUBES
Orders accepted by phone, same day delivery. Manchester area £3.50. Mail Order anywhere by request, fitting while you wait £15 extra.

18"	A47 – 342 x 343 x	£33.00
19"	A49 – 120 x /192 x	£33.00
20"	A51 – 220 x /110 x	£33.00
22"	A56 – 120 x /123 x	£36.00
25"	A63 – 120 x	£39.00
26"	A66 – 120 x A67 – 120 x	£39.00

These tubes replace many Toshiba types.

Callers welcome, please phone first.

061 799 0854

Reg Office:

43 Clarke Cres, Little Hulton,
Nr. Manchester M28 6XM.

While stocks last – 3 hour conversion kits for Philips 1500 Video's £99 inc. P. & P.

T.V. ELECTROLYTIC CAPACITORS

600mfd 250v.	G8	£1.30
600mfd 300v.	G8	£1.50
600mfd 300v. (PC)	G9	£1.40
600mfd 300v.	A823	£1.40
400mfd 350v.	8500	£1.40
400mfd 400v. (PC)	9500	£1.76
470mfd 250v. (PC)	G11	£1.30
800mfd 250v. (PC)	G9	£1.50
200 + 300mfd 350v.	691	£1.80
400 + 400mfd 350v.	Decca	£2.30
150 + 150 + 100mfd	1500	£1.40
175 + 100 + 100mfd	3500	£1.75
200 + 200 + 75 + 25mfd	CVC5	£1.70
200 + 200 + 150 + 50mfd	2047	£1.70
200 + 200 + 100 + 32mfd	169	£2.20
300 + 300 + 150 + 100 + 50mfd	2040	£2.60
1000mfd 63v.	3500	80p.
2200mfd 63v. (PC)	G9	50p.
1250mfd 50v.	691	45p.
4700mfd 25v. (PC)	1590	60p.
2500 + 2500mfd 30v. (PC)	A823	90p.

PLASTIC FILM CAPACITORS

Mains Filter Capacitors 250v. AC working			
0.047mfd	26p.	0.22mfd	42p.
0.1mfd	36p.	0.33mfd	48p.
1.0mfd (Three wire type) 45p.			
1000v. DC range			
0.047mfd	22p.	0.22mfd	42p.
0.1mfd	28p.	0.47mfd	54p.
2kV Flyback suppression type			
4700pF	28p.		
5200pF	35p.		
11,000pF	48p.		
Scan correction type			
0.91mfd G11.	44p.		

P. E. WHITE

22 York Road, Camberley,
Surrey GU15 4HR.

CASH WITH ORDER PLEASE

All the above prices are for single items.
PLEASE ADD 30P. PER ORDER
TO COVER POSTAGE AND PACKING.
ADD VAT AT 15%



Tenrec Electronic Engineers Ltd
502 Bearwood Road
Warley, West Midlands
021 429 8150

LIMITED VIDEO OFFER

J.V.C. V.H.S. system. Portable Colour Recorder.
Mains/Batt. Model HR4100. Colour Camera
GX33. Zoon lens. Batt. op. Complete Ready to go

£999

includes VAT, P&P & insurance.

*A31-410, 12" Mono Tube New. Special Price for Current
"Television" Feature; £19. P&P-£2.

**Plenty of used colour panels working. S.A.E. for
list. 50p p. & p.**

Trade enquiries welcome

(All prices include VAT)

(T.I.)

AERIAL SPLITTERS

Two way in white box with three
black insulated co-ax sockets.
Completely made up with two spare
co-ax plugs.
Price only £1.70 EACH.

CALLERS WELCOME

Large stock of capacitor, resistors,
P.C.B. etching compound, TV valves,
loft aerial and co-ax cable.
Open for Callers: Tuesday, Thursday,
Friday and Saturday morning.

SIGNAL INJECTORS with (pre-set) variable AF, which emits RF harmonics into
the UHF band. Protected up to 300 volts dc. Complete with leads **£5.70 each.**
All prices include VAT at 15%. P&P per order 30p. S.A.E. for leaflets. Access cards.

ELECTRONIC MAILORDER LTD,

62 Bridge Street, Ramsbottom,
Via Bury, Lancs. BL0 9AGT. Tel. Ramsbottom (070 682) 3036.

AERIAL AMPLIFIERS

Aerial amplifiers can produce
remarkable improvement on the picture
and sound in fringe or difficult
areas.

B45 - for mono or colour this is
tunable over complete UHF television
band.

B11 - for stereo or standard VHF/FM
radio.

B12 - for VHF television band 1 & 3.
**All amplifiers are complete
and ready to use.**

Battery type PP3 or 8v to 18v dc, next
to the set type fitting. Prices **£6.70
each.**

TV LINE OUTPUT TRANSFORMERS (ALL NEW AND FULLY GUARANTEED)

(Prices include VAT at 15%)

Discount to Trade Post and Packing 85p

RANK BUSH MURPHY

Z146 A640 dual std mono	8.50
Bush A792, A793 single std mono	8.50
A774 single std mono	8.50
A816 solid state mono	9.60
Z712 T16a T16b mono portable	9.60
A823 A823b A823av colour	11.35
Z179 Z722 series colour	18.06
Z718 18" series	24.57
Z718 20" 22" 26" series	24.57
T20a T22 series colour	14.43

PYE

169 173 569 573 769 series	8.50
RV293B 368 series	8.50
691 692 693 697 series colour	
Two types see below	
Printed circuit version	21.41
Wired in version	15.26
713 715 570 series colour	12.32
731 735 737 741 colour	9.51
725 colour	9.51

DECCA

MS2000 MS2400 mono	6.80
MS1700 2001 2020 2401 mono	8.50
MS2404 2420 2424 mono	8.50
1210 1211 1511 portable	10.24
GYPSY portable	10.24
CS1730 1733 colour	9.51
CS1830 1835 colour	9.51
'30' series BRADFORD colour	9.51
80 series colour	9.51
100 series colour	9.51

G.E.C.

2000 to 2064 dual std mono	8.50
2047 to 2105 3112 to 3135	8.50
"GAIETY" FINELINE	8.50
2114 portable mono	9.50
3133 3135 M1501H portable mono	9.50
DUAL STD hybrid colour	11.59
SINGLE STD hybrid colour	11.59
SINGLE STD solid state 90° or 110°	9.51

INDESIT

20EGB 24EGB mono	9.51
------------------	------

PHILIPS

170 series dual std mono	8.50
210 300 series mono	8.50
320 series solid state mono	10.00
G6 single std colour	19.88
G8 series colour	9.51
G9 series colour	9.51
G11 series colour	17.36

KB-ITT

VC2 to VC10 VC12 to VC100	9.00
VC200 VC205 VC207 mono	8.50
VC300 VC301 VC302 portable	8.50
CVC1 CVC2 colour	9.51
CVC5 CVC7 CVC8 CVC9 colour	10.00
CVC20 series colour	10.53
CVC30 CVC32 series colour	9.51
CVC40 series	15.90

GRUNDIG

HYBRID 717 1500 3010 colour	12.57
5010 6010 5011 6011 6022	
2222	12.57
1510 2210 2252 5012 colour	12.57

FERGUSON HMV MARCONI ULTRA THORN

950 mk2 1400 mono	8.50
1500 20" 1500 24" 1580 mono	8.50
1590 1591 1592 1593 mono	8.50
1612 1613 1712 mono	8.50
1600 1690 1691 mono	11.85
1615 series mono	14.64
3000 3500 EHT or SCAN	8.50
8000 8000a series colour	12.14
8500 8800 series colour	12.14
9000 series colour	12.14
9800 series colour	23.85

TELPRO all models	9.51
TANDBURG CTV 2-2 colour	9.51
NDROMENDE solid state	9.51
TELEFUNKEN 637 647	9.51

WINDINGS

Post & Packing 40p

RANK BUSH MURPHY

Colour hybrid quadrupler type	5.60
T20a T22 Z719 Z722 Pry & Sec	6.83
Z718 series primary	5.60
Z718 series EHT overwind	7.20

PHILIPS

G6 eht overwind	7.20
G6 primary	4.60
KORTING hybrid series	7.60
WALTHAM 125 EHT overwind	3.00

PYE

691 to 697 EHT overwind*	3.07
691 to 697 primary*	4.60
*Please state printed circuit or wired version	

FERGUSON HMV MARCONI

ULTRA THORN	
8000 8000a primary	4.50
8500 8800 primary	4.50
8500 8800 EHT overwind	6.00

Contact your nearest depot for service by return.
Callers welcome. Please phone before calling.

Tidman Mail Order Ltd.,

236 Sandycombe Road,

Richmond, Surrey.

Approx 1 mile from Kew Bridge.

Phone: 01-948 3702

Mon-Fri 9 am to 12.30 pm.
1.30 to 4.30 pm.
Sat 10 am to 12 pm.

Hamond Components

(Midland) Ltd.,

416, Moseley Road,

Birmingham B12 9AX.

Phone: 021-440 6144.

Mon-Fri 9 am to 1 pm.
2 pm to 5.30 pm.



THIS MONTH'S

SPECIAL OFFERS
ONLY

AVAILABLE AT THE SPECIFIED BRANCH

**5
DOUBLE
CHIP
BUSH OR
5
THORN
8000
FOR £200
+ VAT**

CONTACT:
SAM WILSON
NORTHERN
Thornbury
Roundabout,
Leeds Road,
Bradford 3
Tel: (0274) 665670

**26"
THORN
3500
WORKING
SETS
4 FOR
£100
+ VAT**

CONTACT:
JOHN PALMER
SOUTHERN
Watling Street
Hockcliffe,
North Dunstable
(on A5)
Leighton Buzzard
Tel: (0525) 210768

CALL AND
SEE THE
DIFFERENCE.
BEST BUYS
IN LONDON
COLOUR TV's
WORKING AND
NON WORKING
400/500
GOOD CLEAN
FRESH STOCK

CONTACT:
GRAHAM AYRES
LONDON

Cedar House
Nobel Road,
Eley Estate,
Edmonton,
LONDON N 18
Tel: (01) 807 4090

**OUR
CLEARING
HOUSE AT
CLEARING
PRICES
BUY SIX
COLOUR
SETS OFF
OUR PILE
OF 300
FOR
£75 + VAT**

CONTACT:
ROGER DOLMAN
MIDLAND
48/52 Pershore Street,
Birmingham 5
Tel: (021) 622 1023

**5
THORN
8000
FOR
£200
+ VAT**

CONTACT:
DAVID THOMAS
WEST
Unit 4a, Bulwark
Industrial Estate,
Chepstow,
Nr. Bristol.
Tel: Chepstow
(02912) 6652

MAIL ORDER PROTECTION SCHEME

INTRODUCTION

The Office of Fair Trading have agreed that the notice of the Mail Order Protection Scheme to appear in periodicals carrying mail order advertising should appear as follows:—

"MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfill orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded."

REBUILT CATHODE RAY TUBES IN

SOUTH WALES

NEWPORT

CARDIFF

NEATH

C.R.T. SERVICES

274 Chepstow Road, Newport, Gwent.
Tel Newport 272008.

TUBES ALSO AVAILABLE FROM OUR STOCKISTS IN

CARDIFF

NEATH

Dependable TV, 9 Crwys Rd.
Tel. Cardiff 44006

Sureview, 89 Windsor Rd.
Tel. Neath 57676

CURRENT PRICE LIST

A44-271X, A47-342X/343X	£30	470ERB22, 470FTB22	£40
A49-120X, A51-110X	£30	A51-161	£40
A56-120X, A56-140X	£33	A56-500X, 560HB22	£43
A63-120X, A66-120X	£36	A66-500X	£46
A66-140X, A67-120X/150X	£36	Add 15% VAT to all prices.	

Prices are based on a type for type exchange tube suitable for reprocessing.

TWO YEAR GUARANTEE ON ALL TUBES

CELTEL

WARNERS MILL
SOUTH STREET
BRAINTREE
ESSEX
(0376) 26384

UNIT 5A,
KEMPS SHIPYARD,
QUAYSIDE ROAD,
BITTERNE,
SOUTHAMPTON
0703 331899

COLOUR & MONO TV's
WORKERS & NON-WORKERS,
EX EQUIPMENT TUBES & PANELS
RE-BUILT COLOUR TUBES

Now at Bridgwater!

WELLVIEW

SERVES THE WEST

Exchange Colour

	our price	+VAT	15% total price
A44/270X-271X	£27.00	£4.05	£31.05
A47/342X-343X	£27.00	£4.05	£31.05
A49/120X	£27.00	£4.05	£31.05
A51/110X	£27.00	£4.05	£31.05
A55/14X	£32.00	£4.80	£36.80
A56/120X	£32.00	£4.80	£36.80
A63/120X	£36.00	£5.40	£41.40
A66/120X	£36.00	£5.40	£41.40
A67/120X	£36.00	£5.40	£41.40
A67/200X	£36.00	£5.40	£41.40

New Mono

	our price	+VAT	15% total price
A31-120-300	£15.00	£2.25	£17.25
A50-120	£14.74	£2.21	£16.95
A61-120	£15.96	£2.39	£18.35

18 month full guarantee (Established ten years).

Send cash or cheque together with old tube with your order.

Carriage=£4.50 including VAT

ALSO YOUR VALVE SUPPLIER
NEW AND BOXED
(inclusive of VAT)

DY802=74p	ECC82=64p	EF183=78p
EF184=64p	PCC89=72p	PCF802=98p
PCL82=78p	PCL84=92p	PCL805=97p
PFL200=£1.15	PCL86=97p	PL504=£1.38
PL509=£2.82	PL519=£2.92	PY88=70p
PY800=70p		PY500A=£1.52

Postage and Packing 10p per valve. All orders over £10 Free of charge.

Special News Flash

"TUBE REPLACEMENTS"

53A Exeter Road,
Exmouth. Tel: 6210

ARE OUR AGENTS FOR
AVON - DEVON - SOMERSET
THEY OFFER FREE DELIVERY PLUS
MOST OTHER TV SPARES
FREE CATALOGUE ON REQUEST

Colour Sets.

600 ex-rental TVs
Good sets good prices
Call and see

All mail order and
enquiries to
Head Office and
Factory

WELLVIEW TUBES LTD

Unit No1, Monmouth St,
Bridgwater, Somerset.
Tel. 0278 425690-722816

DISPLAY ELECTRONICS

REGUNNED COLOUR TUBES 2 YEAR GUARANTEE

Up to 19".....	£29.50
20".....	£31.50
22".....	£33.50
25".....	£35.50
26".....	£37.50

The above prices are for standard 38mm Delta Gun Types. Prices on application for P.I.L. Tubes etc. Some types available without pre-supply of glass at extra cost.

Carriage/Packing £5 up to 75 miles from works. £6.50 over. Please add 15% VAT

REGUNNED MONO TUBES 2 YEAR GUARANTEE

20".....	£11.00
24".....	£13.00

Carriage/Packing £4.00 up to 75 miles from works. £5.00 over. Please add 15% VAT.

BUDGET CORNER

Buy any 5 mixed types Cash 'n Collect - Take 20% discount.

OR

Buy any 5 Mono mixed sizes Cash 'n Collect at **£8.50** (20") and **£10** (24").
PLEASE ADD 15% VAT.

CALLERS WELCOME

Late night Thursdays until 8pm
Saturdays until midday.

N.B. Customers intending to collect orders are requested to telephone in advance:— even popular types may be out of stock for short periods.

V.D.U./RADAR TUBES

We have supplied British and Foreign Airlines with rebuilt V.D.U. Tubes for several years and also have Radar Display Tubes operating on British Airfields.

Home and export enquiries for Radar Display Tubes manufactured from new (with phosphors to specification) are invited.

WHOLESALE STOCKISTS

Following recent expansion of our production capability we are seeking wholesale stockists who have the facilities to hold stocks of tubes and who will give our customers the same service that they have come to rely upon at the factory.

**WATERLOO ROAD,
UXBRIDGE,
MIDDLESEX**

Telephone: Uxbridge 55800

TELEVISION TUBE SHOP

NEW TUBES AT CUT PRICES

EUROPEAN TYPE Nos.

	Price £	VAT £
A28-14W.....	21.95	3.29
A31-19W/20W.....	19.95	2.99
A31-120W/300W.....	17.95	2.69
A31-410W/510W.....	17.95	2.69
A34-100W.....	18.50	2.77
A38-160W.....	17.50	2.63
A44-120W.....	27.00	4.05
A50-120W.....	17.95	2.69
A59-23W.....	21.50	3.22
A61-120W.....	19.95	2.99

U.S.A./JAP. TYPE Nos.

9AGP4.....	21.82	3.27
190AB4/C4.....	23.00	3.45
230ADB4.....	28.50	4.28
230DB4/CT468.....	26.60	3.99
240AB4A.....	17.95	2.69
CT507 equiv.....	18.95	2.84
CT512.....	27.50	4.12
310DGB4/DMB4.....	23.00	3.45
310EUB4.....	19.95	2.99
310EYB4.....	18.75	2.81
310FDB4.....	23.50	3.52
310FXB4.....	17.50	2.62
310GNB4A.....	23.50	3.52
310HCB4.....	23.50	3.52
340AB4.....	22.50	3.38
340AYB4.....	30.00	4.50
340RB4/CB4.....	26.00	3.90
340AHB4.....	26.00	3.90

**Some Rebuilt Japanese
& European Types
Available from
£14.00 + VAT £2.10**

COLOUR TUBES

New and Mullard Colourex*

12VARP22.....	62.50	9.37
330AB22.....	73.50	11.03
470FUB22B.....	97.50	14.63
A44-271X.....	65.00	9.75
A47-342X.....	69.50	10.42
A47-343X.....	69.50	10.42
A49-191X.....	59.50	8.92
A51-161X.....	67.00	10.05
A51-220X.....	64.00	9.60
A56-120X.....	58.50	8.77
A63-120X.....	69.50	10.42
A66-120X.....	65.00	9.75
A66-140X/410X.....	70.50	10.57
A67-120X.....	65.00	9.75
A67-140X/200X.....	69.50	10.42
A67-150X.....	75.00	11.25

Old Bulb Required for Colourex
ALL TUBES TESTED BEFORE
DESPATCH & GUARANTEED
FOR 12 MONTHS. 4 YEAR
GUARANTEES AVAILABLE ON
MOST TYPES


CARRIAGE

Mono £3.00 Colour £5.00

Mainland only. Overseas Rates on Application.

TELEVISION TUBE SHOP LTD.
52 BATTERSEA BRIDGE RD.,
LONDON, SW11.

Tel. 228 6859/223 5088

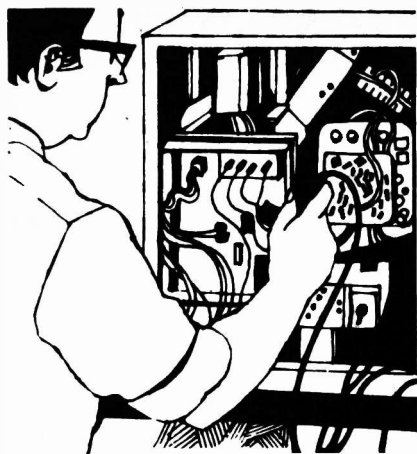

SETS & COMPONENTS

TV PANELS & MODULES

Designed and manufactured by **LED Co.** Used by the leading TV rental and maintenance companies.

PHILIPS G8 SERIES

NEW!! Convergence Panel (Rear Mounted) for 550

A.F.C. Module £6.50
Vision Gain Module £8.28

PHILIPS 570 – PYE 713-715-735 etc.

I.F. Filter/Gain Module £11.45
Detector Module £10.30

PYE HYBRID RECEIVER

Solid State CDA Panel £21.00
Ready Built £16.95
In kit form £16.95
Audio Module (LP1162 equiv) £6.60
All prices include VAT and 1st class postage. Quantity discounts and credit terms available. Ask for details.

LED Co London Electronic Development Co.

21-23 Clifford Rd., London SE25 5JJ
Tel. 01-656 7014

SMALL ADS

The prepaid rate for classified advertisements is 25p per word (minimum 12 words), box number 60p extra. Semi-display setting £4.80 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Television, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

IRELANDS LARGEST DISTRIBUTORS OF COLOUR AND MONO TELEVISIONS

Mono from £5, Colour from £20,

Delivery can be arranged. Working sets to order.

ALSO DISTRIBUTORS OF SERVICE EQUIPMENT, COMPONENTS AND TOOLS, AERIALS, VIDEO RECORDERS, RADIOS AND CASSETTES ETC.

TELETRONICS, SESKINORE, OMAH, CO. TYRONE. TEL: FINTONA 389 (STD 066 284)

TV PATTERN GENERATOR

UHF output, plugs straight into aerial socket, provides cross-hatch and peak white patterns, size 100 x 75 x 40mm.

£17.75

price includes battery, P&P, and VAT.

Further details of this and our other products on request.

C. L. JERVIS,
15 Mercer Grove,
Wolverhampton, WV11 3AN.
TEL (0902) 736606.

TURN YOUR SURPLUS capacitors, transistors, etc. into cash. Contact Coles-Harding & Co., 103 South Brink, Wisbech, Cambs. 0945 4188. Immediate settlement.

TELETRONIC (NORTH EAST) LIMITED.

"SEE-VU" Works,
Strangford Road,
Seaham, Co. Durham.
Tel. (0783) 812142

Competitive - Reliable
REBUILD COLOUR TUBES
Hot pumped and Reband
Two year guarantee - Four Year Available
ENQUIRIES WELCOME

Ask for our list of sixty types JAPANESE 'IN LINES' and 20AX.

The North-East's largest rebuilder.
Established 1957

Mono tubes also available.

Southern Valve Co.,

2nd Floor, 5 Potters Road, New Barnet, Herts.

Tel: 01-440 8641 for current prices & availability, all popular valves stocked. NO CALLERS, SAE Lists. Cash with order. Same Day Postal Despatch. (Lunch 12.30-2p.m.)

Valves, Tubes, Aerials etc by LEADING-MAKERS. Send SAE Lists or Phone for current prices. Counter or MAIL ORDER. NO COD. Speedy Despatch assured. No order under £1.

Philip Beaman, 6 Potters Road, New Barnet, Herts.
Tel: 01-449 1934/5 (1934 Recording Machine).
Please phone for opening hours.

QUALITY REBUILT TUBES

HIGH TEMPERATURE PUMPING

COLOUR (2 year Guarantee)

90° up to 19" £31
90° 20" - 22" £33
90° 25" - 26" £36
110° and PIL £38

MONO (including thin necks) from £12.

All prices + VAT

Delivery UK Mainland £6.

4 year Optional Guarantee

Send or phone for full list and terms.

WELTECH PICTURE TUBES
Unit 3-10 Wembley Commercial Centre,
East Lane, Wembley, Middx.
01-908-1816

IRISH TV DEALERS

Call now for a full range of colour and mono TVs. All sets sold working. Delivery can be arranged to any part of Ireland. Call write or phone:

TELESCREEN

Bellanaleck Quay, Near Enniskillen,
Co Fermanagh, N. Ireland
Tel: Florencecourt 388.

When replying to Television Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

SUFFOLK TUBES LIMITED

214 Purley Way, Croydon, Surrey.
Tel: 01-686 7951/2/3/4

SUPPLIERS OF MONO AND COLOUR TUBES TO MAJOR RENTAL COMPANIES.

ALL COLOUR TUBES HOT PUMPED AT 385c AND REBANDED TO BRITISH STANDARD. 415 1972 CLAUSE 18-2.

19" and 22" TUBES APPROVED. OTHER TYPES PENDING.

BRITAINS LARGEST INDEPENDENT REBUILDER FOR 21 YEARS.

MAINS DROPPER RESISTORS

POWER SECTIONS

Type 11	12 Watts	40p ea.
4R7, 7R5, 10R, 12R, 15R, 18R, 22R, 27R, 33R, 39R, 47R, 56R, 68R, 75R, 82R, 100R, 120R, 150R, 180R, 220R.		
Type 12	18 Watts	46p ea.
	2K5 2K85	

COMPLETE UNITS

Philips G8 2R2 + 68R	52p
Philips 210 118 + 148 + link	57p
Thorn 1500 350 + 20 + 148 + 1500 + 317	86p
Thorn 3000/3500 6 + 1 + 100	72p
Thorn 8000 56 + 1K + 47 + 12	86p
Thorn 8500 50 + 40 + 1K5	92p
GEC 2018 10 + 15 + 19 + 70 + 188	88p
RR1 A640/TV161 250 + 14 + 156	69p
PL802T SOLID STATE VALVE	£2.30

VAT inclusive. Add 15p P&P for orders below £1.00

ACORD ELECTRONICS LTD.,
45 Stoke Road, Guildford, GU1 4HT

LOOK!

THORN 3000/3500 & 9000 TRIPLERS

High Quality Silicon Replacement Units
T3500 only **£4.95** inc. P.P. Add 74p V.A.T.
T9000 only **£6.45** inc. P.P. Add 82p V.A.T.

Quotes for 50+. **1 Year Guarantee**

WING ELECTRONICS

15, Waylands, off Tudor Road, Hayes End, Middlesex.

COLOUR TUBES

Rebuilt with new electron gun, to British Standard. High temperature pumping.

Here is what you pay.		VAT
17-18-19 inch.....	£29	4.35
20 inch.....	£30	4.50
22 inch.....	£31	4.65
25 inch.....	£34	5.10
26 inch.....	£35	5.25

Guarantee 2 years.
Exchange basis.

CALLERS ONLY

TELESTAR TUBES

575c Moseley Road, Birmingham B12 9BS.
Tel: 021-440 5712.

LLOYD ELECTRONICS

63 North Parade, Grantham, Lincolnshire

PL802/T Top Quality Solid State Valve • **£2.50** each.
Solid State C.D.A. Panel for 'Pye' 203/205 series • **£19** each.
I.F. Gain module for 'Pye' 713/731-series • **£9.50** each.
Replacement 'Rank/Bush/Murphy' Power Supply Panel (A823) **£17.50**.

VAT & P/P included
QUANTITY DISCOUNTS

G6 SPARES. ELECTRONICS. SAE. Early radios. Sole, 37, Stanley Street, Ormskirk, Lancs.

TUBE REGUNNING PLANT complete with full training. Tel. 0742 583845.

TV DX.

High Quality Equipment Supplied by THE specialist in the DX field.

Some of my products:-

Band I sound/vision notch filter. Please state channel **£17.95**.

Band I/II tunable Mosfet preamplifier. 25dB gain. Very low noise/cross modulation figure. **£27.95**.

Band III tunable Mosfet preamplifier. 24dB gain. Highly suitable for use in locations near band II FM stations **£25.95**.

Tunable set side Uhf preamplifier. Highly suitable for areas where conventional preamplifiers will not work due to high level local signals. Mains **£24.95**.

Philips G8 selectivity modules. Gives extra IF selectivity to your TV **£1.10**.

FM DX! 88-108MHz tunable mosfet preamplifier **£25.95**.

TV DX receivers available. Please send sae for my product list to:

H. COCKS,

Cripps Corner,
Robertsbridge,
Sussex.
Tel 058083-317.

*The above prices include post/packing.
Callers welcome - Please telephone first.*

COLOUR TELEVISION PANELS taken from televisions untested from £1. Thorn 2000, 3000, RBM A823 many others. Sae for new list. Camber Television Centre, Lydd Road, Camber, Sussex.

STS

FOR
QUALITY
USED T.V.s

200 EX RENTAL
COLOUR AND MONO TVs
ARRIVING WEEKLY
GOOD CLEAN CABINETS

Bush ★ Decca ★ GEC
Pye ★ Philips ★ Thorn
Grundig ★ Sanyo ★ ITT Etc

TROLLEY STANDS AND
ALL SIZE REGUN TUBES.

DELIVERY IF REQUIRED

Call or phone now to:

SOUTHERN TRADE SERVICES
21 COLINDALE AVE.,
LONDON NW9
TEL 01-200-7337.

20 AX & P.I.L. TUBE

Colour Tubes.....from **£25**
20 AX all sizes.....from **£25**
Toshiba P.I.L. All Sizes.....from **£20**
Top quality Regun 90°. All sizes.....**£28**

RING: JEFFRIES 01-845 2036

COLOUR T.V.s

PHILIPS G8 COMPLETE


22" £55 26" £65

**DISCOUNT FOR
BULK BUYERS**

TEL: 965 1230 & 961 3997

**SMITH
ELECTRONICS,**

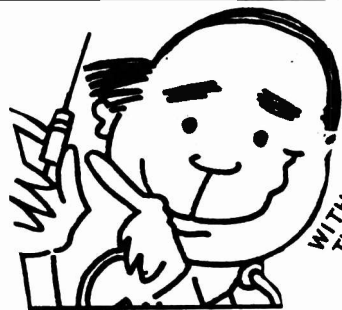**43-43A, PARK PARADE,
HARLESDEN,
LONDON N.W.10.**



**WERNETH
ELECTRONICS
LIMITED
FREEPOST.**

P.O. BOX 9, MARPLE, STOCKPORT, CHESHIRE. SK6 6YE.

WERNETH ELECTRONIC PRODUCTS · WINNINGTON RD · MARPLE · STOCKPORT · CHESHIRE

**"Just what the
doctor ordered"**

TUBE TEST INSTRUMENTS

TX 80 PROFESSIONAL **£48.85**
TX50 LOW COST SERVICE TESTER **£29.50**
TX50 COMPLETE KIT OF PARTS **£21.00**

Get to the point: fast!

IN-CIRCUIT TRANSISTOR TESTER
Designed for fault finding in Solid State circuits, this tester uses C-MOS technology to detect faulty transistors and diodes in or out of circuit.

Also identifies PNP & NPN base-emitter-collector leads.

Supplied complete with full instructions (less PP3 battery) **£15.60 inc.**

C.W.O./S.A.E. for product details.

TV WHOLESALE SUPPLIES LTD THE SPECIALISTS FOR

Good quality colour and Mono TVs. Fresh stocks in every week. Why not call and see our selection of PX, re-possession and ex rental TVs.

- ★ **COMPETITIVE PRICES**
- ★ **FULL TEST FACILITIES.**
- ★ **DELIVERY ARRANGED IF NECESSARY.**
- ★ **SPARES FOR MOST MAKES OF MODERN RECEIVERS.**
- ★ **PLUS REGUNN TUBES AT COMPETITIVE PRICES.**
- ★ **ALSO EXPORT OUR SPECIALITY.**

TV WHOLESALE SUPPLIES LTD.

**35 SHIPSTON ROAD, STRATFORD-UPON-AVON,
WARWICKS.**

TELEPHONE (0789) 4424.

Open 9.30 till 6.30 6 days a week.

On the main A34 Oxford road.

COLOUR PANEL EXCHANGE SERVICE

BRC 3000/3500, 8000/8500
GEC 2110 series
Philips G8, G9 and G11

Three months guarantee on all Exchange Panels.
Free delivery in London area.

Also Ex-Equipment Panels Thorn 3500 for sale.

All guaranteed Perfect Working Order.

Phone or send SAE for Catalogue.

KAY JAY TV SERVICE,

34, Clauson Avenue,
Northolt, Middlesex.
Phone 864-0350.

TELFURB T.V. LTD.

No. 1 in

- ★ Used colour T.V.'s
- ★ Competitive prices
- ★ Technical expertise
- ★ Fully equipped premises.
- ★ Export

Phone or Call

**51-53 HIGH STREET,
WHEATLEY, OXFORD.**

086-77-3849

VETERAN & VINTAGE

"SOUNDS VINTAGE"

The only magazine for all vintage sound enthusiasts packed with articles by top writers covering gramophones, phonographs, 78s, wireless, news, history, reviews etc.

Bi-monthly. Annual subscription £6.00 (airmail extra). Send 75p for sample copy.

28 Chestwood Close, Billericay, Essex

MISCELLANEOUS

BURGLAR ALARM EQUIPMENT. Latest Discount catalogue out now. Phone C.W.A.S. Alarm. 0274 682674.

RIGONDA AGENTS. For all spares and repairs. Fast dispatch trade service available. 01-476 1928. Star Radio, 272 Barking Road, London E.13.

WANTED

WANTED Thorn 1500 T.V.'s offers, Telephone 0202 (Bournemouth) 420229.

SERVICEABLE R.F. SIGNAL GENERATOR. F.M./A.M. facility required, write: A. Grizzle, 53 Dickinson Avenue, Low Hill, Wolverhampton.

NEW VALVES and CRT's required, PCL805, PL504, PL509, PY500A etc. Cash waiting. Bearman, 6/8 Potters Road, New Barnet, Herts. Tel: 01-449 1934/5.

CIRCUIT DIAGRAMS, plus construction notes, of Hi-Fi valve power (music) amplifiers (100W and greater) required. Write: A. A. Grizzle, 53, Dickinson Avenue, Low Hill, Wolverhampton.

T.V. SERVICE SHEETS wanted in clean condition. 25p each offered. Write Box No. 156.

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc., 10,000 models. Catalogue 24p plus SAE with orders-enquiries. Telray, 154 Brook Street, Preston, PR1 7HP.

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

JAPANESE TV service sheet specialists catalogue 25p plus S.A.E. Sandhurst Publications, 49c, Yorktown Road, Sandhurst, Camberley, Surrey.

Thousands of different full size service sheets Thousands of different manuals of all kinds in stock.
(Many of above are unique to us and obtainable nowhere else.)

Updated collection of British colour TV circuits/layouts etc. Contained in 3 huge binders - special price **£39.50.**

Updated foreign colour TV repair system for £22.50. (2 manuals, 1 binder) chassis from Grundig, Hitachi, Skantic, Luxor, Mitsubishi, Kuba, Zanussi.

Complete set of 10 unique TV repair manuals - only £49.50. Mono + colour from dual standards to latest models, McCourt & Tunbridge.

S.A.E. any quotation, also price lists, newsletter, bargain offers, details of our unique TV repair systems.

£1 + large S.A.E. any single service sheet.

Phone: 0698 883334, anytime. Callers 4-6 pm. weekdays, Saturday from 10 am.

G.T.

TECHNICAL INFORMATION SERVICE

76 CHURCH ST., LARKHALL, LANARKSHIRE ML9 1HE.

FOR SALE

EX RENTAL ETC. COLOUR T.V.'s complete from £15. Some working. Worthing (0903) 35907.

WORKSHOP CLOSEDOWN. 100+ colour panels, 1000+ valves, 3,000+ components. Chassis and sets retail value over £1,000, take £400 o.n.o. Might split. Telephone 021-472 3688.

MODERN TUBE REBUILDING PLANT. Process all T/V tubes £35.00. Can be seen in operation. 021-523-8181.

COLOUR TV PORTABLE PANELS UHF Varicap Tuner & Touchtone panel, Vis. & Sound IF, Sound output, Chroma Decoder on panel 250x200 m/m. Send Cheque/P.O. £17.50 to 'Vision On', 171 South Ealing Road, London W5.

NEW BACK ISSUES of 'Television' available 90p each post free. Cheque or uncrossed P.O. returned if not in stock. Bell's Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

**PLEASE
MENTION
TELEVISION**

**WHEN
REPLYING**

**TO
ADVERTISEMENTS**

SERVICE SHEETS. SERVICE MANUALS PRACTICAL AND TECHNICAL BOOKS

COVERING COLOUR & MONO TELEVISIONS, RADIOS,
RECORD PLAYERS, TAPE RECORDERS, ETC.

SERVICE SHEETS £1.00 PLUS S.A.E. SERVICE MANUALS ON REQUEST.

BOOKS

PRICES INCLUDE POSTAGE U.K. ONLY

TVT '79 TRANSISTOR EQUIVALENT & DATA BOOK. (A TO Z). 272 Pages	£3.50
TVT '79 TRANSISTOR EQUIVALENT & DATA BOOK. (2N. 2S. ETC.). 392 Pages....	£4.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G.J. King. Vol. 1	£9.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G.J. King. Vol. 2	£9.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G.J. King. Vol. 3	£9.75
COLOUR TELEVISION SERVICING by G.J. King. 2nd Edition	£9.80
COLOUR TELEVISION THEORY by G.H. Hutson	£7.95
LONG DISTANCE TV RECEPTION FOR THE ENTHUSIAST by R. Bunney.....	£1.70
AUDIO EQUIPMENT TESTS by G. J. King	£7.50
RADIO CIRCUITS EXPLAINED by G. J. King	£6.50
SERVICING WITH THE OSCILLOSCOPE by G. J. King. 2nd Edition	£7.20
TELEVISION SERVICING HANDBOOK by G. J. King. 3rd Edition	£7.95
BEGINNERS' GUIDE TO TELEVISION by G. J. King. 5th Edition	£3.75
BEGINNERS' GUIDE TO COLOUR TELEVISION by G. J. King. 2nd Edition	£3.75
CATHODE-RAY OSCILLOSCOPE AND ITS USES by G. N. Patchett	£4.40
TELETEXT AND VIEWDATA by S.A. Money	£6.00
TOWERS' INTERNATIONAL TRANSISTOR SELECTOR. 2nd Update	£10.35

COLOUR TV MANUALS

COVERING FOLLOWING MAKES
PLEASE SEND S.A.E. FOR QUOTATION

ALBA, BRC, BUSH, DECCA, GEC,
DEFIANT, MARCONI, EKCO, PYE,
FERGUSON, DYNATRON,
NATIONAL, HITACHI, INVICTA,
ITT/KB, RGD, GRUNDIG, SOBELL,
STELLA, SONY, MURPHY,
PHILIPS, HMV, ULTRA & OTHERS.

CIRCUIT DIAGRAM MANUALS

We supply circuit diagrams for televisions in Giant Binders,
covering most British 'Single' and 'Dual Standard' models,
consisting of 2 volumes on colour and 1 on black & white. Price
£14.50 each post free or all 3 for £40.50 post free.

WE STOCK NEW AND SECONDHAND EDITIONS OF "RADIO AND TELEVISION SERVICING" BOOKS.
FROM 1971-72 EDITION UP TO DATE. PRICES ON REQUEST.

BACK ISSUES OF FOLLOWING MAGAZINES AVAILABLE. CURRENT PRICE PLUS 25p POSTAGE PER COPY.
P. WIRELESS, P. ELECTRONICS, E. ELECTRONICS, TELEVISION, ELECTRONICS TODAY, ELEKTOR

BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, N. YORKSHIRE. TEL. HARROGATE (STD 0423) 55885

OPEN TO CALLERS DAILY 9.00 a.m. TO 5.00 p.m. (HALF DAY WEDNESDAY) PLEASE INCLUDE AN S.A.E. WITH ENQUIRIES

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

NAME

ADDRESS

.....

Send to: Classified Advertisement Manager,
TELEVISION,
GMG, Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846.
Rate
25p per word, minimum 12 words, Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

BOOKS & PUBLICATIONS

ANY SINGLE SERVICES SHEET £1. L.S.A.E. Thousands different repair/service manuals/sheets in stock. Repair data your named TV £6 (with circuits £8). S.A.E. Newsletter, price lists, quotations. AUS (T). 76 Churches, Larkhall, Lanarkshire. (0698 883334).

EDUCATIONAL

TELEVISION COMPUTER & RADAR SYSTEMS SERVICING

TWO YEAR full-time Modular Diploma course to include a high percentage of practical work.

- ELECTRONIC PRINCIPLES
- MONO TV & CCTV
- COLOUR TV & VCR
- DIGITAL TECHNIQUES
- COMPUTERS & MICROPROCESSORS
- RADAR

Each of the above Modules are 12 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Tuition fees (UK & Overseas) £400 per Module. - Computer Module £500.

Next session starts January 5th.

(Also available 2½ year course in Marine Electronics & Radar.)

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept: TT, 20 Penywern Road,
London SW5 9SU. Tel: 01-373 8721.

BETTER JOB! BETTER PAY!

GET QUALIFIED WITH ICS IN:
COLOUR & MONO TV SERVICING
COLOUR & MONO TV ENGINEERING
COLOUR & MONO TV MAINTENANCE
PLUS: Telecommunications, radio, electronics, electrical engineering, technical communications, radio communications, etc., etc.,

NEW: Self-build radio courses with free kits

Train in your own home, in your own time with ICS, the world's most experienced home study college.

**RETURN THIS COUPON TODAY
FOR FREE BROCHURE!**

ICS Int. Correspondence Schools
284C Intertext House, Stewarts Rd.
London SW8 4JJ. Tel: 01-622 9911

Name

Address

BIRMINGHAM AND DISTRICT DEALERS/ENGINEERS

NEWS FLASH

**HIGH VACUUM
QUALITY
REBUILT TELEVISION
PICTURE TUBES**

COMPETITIVE PRICES

**CONTRACT TERMS
AVAILABLE**

2 YEAR GUARANTEE

17"	18"	19"	£31.00 + VAT	£4.65
20"			£34.00 + VAT	£5.10
22"			£36.00 + VAT	£5.40
25"			£40.00 + VAT	£6.00
26"			£43.00 + VAT	£6.45

PIL Tubes our speciality.
All Prices For Tubes available on a Sound "Glass for Glass" basis otherwise £20 surcharge

**Built up to a standard
not down to a price.**

TUBESURE LTD.

Unit 111, Middlemore Industrial Estate,
Middlemore Road, Smethwick,
West Midlands. Telephone: 021-558 7777.

STANDARD T.V. TUBE

**HIGH QUALITY COLOUR AND
MONO-CHROME REPLACEMENT
TUBES AT COMPETITIVE PRICES.**

- ★ Complete New Gun fitted to every Tube.
- ★ Two year Guarantee
- ★ Every Tube Electrically Tested.
- ★ Every Tube Picture Tested.
- ★ Supplier to Major Rental Companies.

18"	19"	£25
20"	22"	£27
25"	26"	£29

All prices quoted assume the return of your old glass rebuildable condition. Old CRT cash/cheque with order. Please add VAT at 15%.

S.STANDARD TV TUBE CO.
11-29, Fashion Street,
London E1

Tel. 01-247 3097

N.G.T. COLOUR TUBES

First Independent Rebuilder with

B.S.I. CERTIFICATION

(Certificate No. 004)

2 year guarantee: 4 year option

All Colour Tubes are debanded, high temperature pumped and rebanded using new adhesives and new tension band.

19" £30, 20" £32, 22" £33, and 26" £38.

Exchange prices: add VAT at 15%

N.G.T. ELECTRONICS LTD.,
120, SELHURST ROAD., LONDON S.E.25
Phone: 01-771 3535.

20 years experience in television tube rebuilding.

**EMO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES
ETC., ETC. ● ALL SPARES READILY AVAILABLE ●**

CREDIT AVAILABLE — TRADE ONLY

Almost any TV Component supplied by return "off the shelf" e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc., etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST - RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

S.A.E. FOR FREE WALL CHART

**TELEPART (WTON) THE TELECENTRE, WORCESTER ST.,
WOLVERHAMPTON (0902) 773122**

CVC 9 ITT Control panel. **£4.00**
 CVC 20 ITT 6 push button unit & Input panel. **£5.00**
 Philips TV IF Modules 38 Mc/s 1st and 2nd IF. **£1.50**
 3500 6 push button unit for Thorn 3500. Varicap Tuning. **£1.00**

VARICAP F.M. TUNER
 Range 87.5 to 108MHz. **£2.00** (IF panel with circuit). **£2.00**
 6 position 12.5KV Resistor Unit for varicap. **50p**
 GEC IF panel (204C). **£7.50**

TV PANELS
 ELC 2000 and IF and Chroma panel TV UHF/VHF chassis. 5.5 Mc/s front end. **£15.00**
 ELC 2000M New. **£7.00**
 GEC VHF/UHF 8CH touch tune units 41C 1xSN 29862N+1xSN 16861NG+2xCBF 16848N. **£5.00**
 New circuit supplied.
 CVC panel with pots and main switches 250K, 100K, 423 500K. **£1.00**
 New (NSF/AEG) UHF/VHF Varicap tuner units.
 Cost £10. only **£4.00**
 Convergence panel for GEC 2040, 11 pots, 5 coils, 2 resistors etc. New. **£1.50**
 PYE 731 6 push button unit and 100KA pots. **£3.00**
 New circuit supplied with UHF 8ch Light action unit
 4 i/c for Varicap tuning GEC C2001/C2201. **£5.00**
 UHF Mullard 4 push button tuner unit. **£2.00**
 ITT Control Panel with Mains lead, 4 slider pots, Mains filter. **£2.50**
 Bush Rank 6 push button Unit for varicap. **£2.50**
 4 push button unit (for Varicap Tuning) 20K. **50p**
 4 pots and 6 push button unit for Varicap. Mains on/off switch + Mains filter. **£3.50**
 I.T.T. **£3.50**
 Philips T/unit UHF. **£2.00**
 Transistor UHF units with Ae socket and leads. GEC 2000 rotary type. **£2.00**
 Thorn UHF tuner unit and panel for 9000 series. **£8.00**
 Thorn 9000 frame panel. **£9.00**
 Mullard VHF Tuner V/cap V314. **£5.00**
 U321 T/unit V/cap. **£6.00**
 Thorn 3500.
 Thorn 8500 focus unit.
 Decca focus unit.
 Large or small. **£1.00** each
 4 push button unit. Thorn 1400/1500. **£3.50**
 4 push button for varicap with pots. **50p**
 Decca Bradford Tuner, 5 button (4 push). **£2.75**
 Line O/P Trans. CVC 20. **£5.00**
 12" TV tube Hitachi A31/300W. **£12.00**

SPEAKERS
 5x3 80r or 50r. **50p**
 G9 70r. **£1.00**
 5x3 35 ohm. **75p**
 6x4 15 ohm. **£1.00**
 GEC 8 ohm. **70p**

NE 2B6H 2 small neon lamps used in GEC. **3p**
 Red and Green LED, 14 mixed. **£1.00**
 TLR 102 small red LED. **5p**
 20 small red LED. **£1.00**

MAINS DROPPERS
 GEC mains dropper for models c1441H, c2001H, c2015H, c2110H, c2113H, c2118H, c2136H, c2202H, c2219, c2601H, c2611H. **20p**
 Thorn 6+1+100r. **35p**
 Pye 69+161. **40p**
 Pye 147+260r. **40p**
 (731) 3+56+27r. **50p**

CERAMIC FILTERS
 5.5 MHz. **15p**
 6MHz. **25p**
 3.5mm Jack socket. **7p**
 FT 3055. **20p**
 NPN/PNP 60v 5 amp/80w, pair. **20p**
 6 way ribbon cable, per metre. **20p**

TV XTALS
 4.433; 610 KHz. **50p**
 6 volt 23 watt soldering iron. **£2.00**
 Infra-red emitting diode, TIL30. **20p**
 750 MFD 50V. **10p**

THERMISTORS
 200+200+75+25 4 fuse holder +2BY133+resistors. I.T.T. panel. **£1.50**
 ITT PT266 3W12 (Thermistor degaussing) fits most sets. **15p**
 PTH451A or B. **20p**
 PT 37P. **25p**
 GEC 4700M/25v. **15p**
 1000M/63v ITT axle. **15p**
 22M/375v ITT. **20p**

THYRISTORS
 GEC 122M for Philips G11. **60p**
 5 amp/300v. **25p**
 52600D 7amp/400v. **30p**
 RCA 40506. **50p**
 PYE
 22N4444/OT113/BT116. **85p**
 MR 501 3amp/100v. **7p**
 MR 508 3amp/800v. **12p**
 SCR 957. **65p**
 SP 8385 Thorn. **25p**
 ELC 1043 AEG. **£4.00**

PHILIPS SNIPS:
 CUTS MOST THINGS. **£1.50**
 CO-AX plugs. **12p**
 UHF Aerial socket and leads, PYE, ITT, THORN. **35p**
 AE Isolating socket. UHF and lead, PYE, THORN, ITT. **35p**
 Plug and socket 3+6 pin printed circuit type, pair. **10p**
 Thorn Mains lead + on/off switch + control panel + slider pots. **75p**
 GEC Mains and battery switch. **30p**

FRONT END FOR MUSIC CENTRE

VHF/MW/LW size 13x3 1/2".
 4 push button unit, 7 transistors, V/condenser, 10 coils rod aerial I/C decoder CA 758E (no power supply and output stage). Circuit supplied. **£6.00**
 Output stage for music centre. **£6.00**
 Pre-amp panel 4 pots transistor etc. Plugs and sockets. **£1.00**

B9A print V/holder. **5p**
 PYE 697 long. **15p**
 TV 18 EHT. **40p**
 TV 20. **50p**
 100k 40 turn pots for V/cap tuning. **20p**
 Mains on/off rotary. **13p**
 Mains on/off push. **20p**
 D/P push button on/off. **10p**
 ITT mains on/off push button. **25p**
 IF panel. **£1.00**
 20 watt O/Put stage. **£1.00**

DE-SOLDER PUMPS. **£4.00**
 ORP 12. **40p**
 LP 1173/10 watt. **£1.00**
 LP 1170. **50p**
 AM/FM tuner unit (seconds). **50p**
 10 watt Mullard amps. NEW. **£2.00**
 AT 1025/08 Blue lateral. **15p**
 Thorn hearing aid unit + ext. loudspeaker. **£2.00**
 AD161/162, pair. **60p**
 731 PYE 600/300v, also Bush. **75p**
 EHT rectifier BY212. **10p**
 3X G770/HU37EHT. **10p**
 EHT rec 2m/a small. **20p**
 EHT rec 2m/a large. **30p**
 Both 12KV.
 EHT rec used in Thorn 1400/1500.
 Triplers x80/150. **10p**
 CSD 118xMH rec for Thorn 3500. **10p**
 GEC 8N 2/2000V. **8p**

TRIPLERS
 Thorn new type 9000. **£4.00**
 Thorn TS 25-11TDT. **£2.50**
 PYE TS25-11TBQ. **£1.50**

TS25-11TBW fits Autovox, Saba, Bang Oulfsen, Grundig Tanberg. **£3.75**
 GEC 2110 after 27.1.77. **£3.50**
 GEC G2100 TVM 25. **£2.00**
 Philips G9. **£3.75**
 Grundig 3000/3010, Seimens TVK 52. **£3.00**
 ITT LP 1174/NC. **£3.00**

MULTI CAPACITORS
 1000 + 2000/35v. **25p**
 2000 + 2000/35v. **30p**
 2500 + 2500/63v. **50p**
 470 + 470/250v. **40p**
 150 + 200 + 200/300v. **70p**
 200 + 200 + 100/325v. **60p**
 100 + 200/325v. **40p**
 200 + 200/350v. **60p**
 200 + 200 + 100 + 32/350. **70p**
 175 + 100 + 100/350v to fit 3500 Thorn. **£2.00**

THORN SPEAKERS
 1500 5 1/2 x 2 1/2 3Ω
 1590 5 x 2 1/2 12Ω
 3500 5 x 3 80Ω
 3500 7 x 3 80Ω
 9000 7 x 3 16Ω
 5 x 3 loudspeaker for GEC 15Ω **£1.00**

UHF Modulator, CCIR. **£3.00**
 Circuit supplied flush mounting socket. FM/TV **35p**
 ELC1042. **£6.50**
 ELC1043/05. **£6.00**
 Mullard. Power supply 30V 1 amp Reg. **£2.00**
 Small DX Tuner V/cap 48-88 MHz and 175-220MHz automatic changeover. **£5.00**
 Transductor AT4041/07. **£1.00**
 8 Push button switch and 1 to 8 V/Ristor unit 21-68 CH. **£2.00**
 R2540. **£1.00**
 BUY 69 (RCA1693). **£1.00**

SENDZ COMPONENTS

63 BISHOPSTEIGNTON,
 SHOEBOURNE,
 ESSEX SS3 8AF.

Reg. Office only.

Callers by appointment only.

Add 15% VAT.

Add 50p P. & P.

Add postage for all overseas parcels.

Equivalent EQ TCA 270 series	I.C.'s—cont.	Semiconductors—cont.	TIP29C	Various Mixed Packs
CA270CE 50p	SN7650N £1.00	BF181 20p	20p	10 Thermistor 50p
CA270CW 50p	SN76532 50p	BF182 20p	20p	20 Slider Pots £1.00
CA3089Q 50p	SN76533 £1.00	BF185 20p	20p	30 Presets 50p
CA3090 50p	SN76544N £1.00	BF195 7p	25p	40 Pots £1.50
I.C.'s	SN76546 £1.00	BF198 7p	25p	300 Condenser £1.50
MC476P 50p	SN76550 15p	BF200 20p	25p	300 Resistor £1.50
MC1349 50p	SN76570 50p	BF237B 7p	5p	150 Electrolytic £2.00
MC1352P 50p	SN76650N 50p	BF240 7p	5p	15 bulbs 45p
PUA758PC £1.00	SN76660N 50p	BF245A 7p	5p	100 diodes £1.00
S7246/N64100 £5.00	SN76666N 50p	BF263P 25p	5p	100 20mm fuses £2.00
SA41020 £6.00	SN76707N 50p	BF264 20p	5p	100 W/W resistors £1.50
SA41021 £5.00	*Denotes with heatsink.	BF273 7p	5p	100 ceramic and plate condensers £1.00
SA41024 £4.00		BF274 7p	5p	300 Carbon film 1/4W 1R to 2M ITT £1.50
SA41025 £5.00	Semiconductors	BF337 24p	20p	1800/4KV 5p
SAS560 £1.00	AC128 25p	BF355 30p	20p	4.7NF/5KV 10p
SAS570 £1.00	AC153K 25p	BF423 PNP 7p	7p	180PF/6KV 10p
SBA750B £1.00	AC176K 25p	BF458 NPN 12p	7p	210PF/8KV 10p
SL901 £3.00	AC187/8K pair 50p	BF458T 12p	7p	270PF/8KV 10p
SL918 £3.00	AF139 25p	BF594 7p	10p	330PF/8KV 10p
TAA320A 50p	AU113 £1.25	BSX20 5p	7p	1000PF/10KV 10p
TAA470 £2.00	BA159 7p	BSY79 7p	7p	1200PF/12KV 10p
TAA550 20p	BA182 7p	BT100 30p	7p	1000PF/12KV 10p
TAA570 £1.00	BA248 7p	BT106 50p	7p	6200PF/2000V 10p
TAA700 £2.00	BAV10 7p	BT106 special £1.00	10p	
TBA120A 40p	BB103VHF 7p	BT109 £1.00	25p	
TBA120AS 40p	BB105UHF 7p	BT116 £1.00	25p	
TBA120B 40p	BC107 7p	BT119 £1.00	10p	
TBA120C 40p	BC108 7p	BT138/10A 70p	5p	
TBA120SA 40p	BC109 7p	BT146 25p	10p	
TBA120SB 40p	BC116 7p	BT146 25p	10p	
TBA120U 40p	BC139 7p	BT151/800R 70p	10p	
TBA1441 £1.00	BC147C 7p	BTT822 £1.00	10p	
TBA396 £1.00	BC148B 7p	BTT8124 £1.00	10p	
TBA480Q £1.00	BC149C 7p	BTT8224 £1.00	15p	
TBA510 £1.00	BC154 7p	BTY80 20p	15p	
TBA520Q £1.00	BC157 7p	BU105 50p	35p	
TBA530 £1.00	BC158 7p	BU105/04 £1.00	30p	
TBA540 £1.00	BC171 7p	BU108 £1.00	5p	
TBA550Q £1.00	BC171B 7p	BU124 50p	8p	
TBA560CQ £1.00	BC173 7p	BU126 £1.00	8p	
TBA560Q £1.00	BC173C 7p	BU137 60p	50p	
TBA570 £1.00	BC174 7p	BU137 60p	10p	
TBA625 £1.00	BC182L 7p	BU204 40p	10p	
TBA641BXI £1.50	BC183 7p	BU205 £1.00	50p	
TBA651 80p	BC183LB 7p	BU208 50p	50p	
TBA673 £1.00	BC207 7p	BU208A £1.00	10p	
TBA720A £1.00	BC212LT 7p	BU208/02 £1.00	10p	
TBA750Q £1.00	BC213LA 7p	BU326 60p	10p	
TBA800 40p	BC237B 7p	BU407 50p	10p	
TBA810S £1.00	BC238 7p	BU500 £1.00	30p	
TBA890 £1.00	BC238A 7p	CA270 50p	10p	
TBA920 £1.00	BC238C 7p	CA270EW 50p	10p	
TBA920Q £1.00	BC245 7p	E1222 20p	10p	
TBA950 £1.00	BC250 7p	R2008B £1.00	10p	
TBA950Q £1.00	BC251A 7p	R2010B £1.00	10p	
TBA990Q £1.00	BC252C 7p	R2603 50p	10p	
TCA270 £1.00	BC252C 7p	OA90 7p	10p	
TCA270Q £1.00	BC257 30p	OT112 £1.00	15p	
TCA270SQ £1.00	BC300 30p	MJE51T NPN 300V 4A 25p		
TCA270SQ £1.00	BC303 30p	MJE2955/15A 50p		
TCA4500A £1.00	BC307 7p	MJE1661 25p		
TCA640 £1.00	BC308B 7p	BY127 10p		
TCA650 £1.00	BC327 7p	BY133 10p		
TCA660 £1.00	BC336 20p	BY176 type 25p		
TCA740 £1.00	BC337 7p	BY176 50p		
TCA800 £1.00	BC350 20p	BY179 35p		
TCA830S £1.00	BC365 10p	BY184 25p		
TCE82 30p	BC413C 7p	BY187/01 10p		
TCE120CQ £1.00	BC454 7p	BY190 40p		
TCE157 20p	BC455 7p	BY204/4 7p		
TCE527 20p	BC460 20p	BY206 10p		
TCEP100 £1.20	BC462 7p	BY206 10p		
TDA1170 £1.20	BC463 7p	BY210/400 7p		
TDA1190 £1.20	BC546 7p	BY210/800 10p		
TDA1327 £1.00	BC559 7p	BY226 25p		
TDA1412 50p	BD124 £1.50	BY223 5A/1500V 10p		
TDA2540 £1.00	BD131 30p	BY226 10p		
TDA2640 £1.00	BD132 30p	BY296 10p		
TDA2680 £1.00	BD136 10p	BY298 12p		
TDA2690 £1.00	BD207 30p	BY299 10p		
TDA3950B £2.00	BD221 20p	BYF3123 wire end 50p		
SN16862AN £1.00	BD228 25p	BYF3126 wire end 50p		
SN16964AN 50p	BD238 20p	BYF3214 20Kv 50p		
SN29764 £1.00	BD239 12p	BYX36/600 10p		
SN29848 50p	BD253B 35p	BYX38/600 50p		
SN75108AN £1.00	BD416 25p	BYX55/350 10p		
SN76001 £1.00	BD561/2 pair 30p	2N390 7p		
SN76003 £1.00	BD595 35p	2N2222 7p		
SN76003* £1.50	BD596 35p	2N3055 35p		
SN76008KE £1.00	BD681 25p	2N3566 7p		
SN76013* £1.50	BD807 10/a/70V 25p	2N4355 7p		
SN76018KE £1.00	NPN 9 watt 25p	2N4442 60p		
SN76023* £1.50	BF127 20p	2N4444 £1.00		
SN76033 £1.00	BF137 20p	2N6099 25p		
SN76033* £1.50	BF157 20p	2N6348 50p		
SN76115 50p	BF180 20p	2N6399A 30p		
SN76131 50p		2SK30A 7p		
SN76226 £1.00				
SN76227 50p				
SN7630P 50p				

SENDZ COMPONENTS

63 BISHOPSTEIGNTON,
SHOEBURYNNESS,
ESSEX, SS3 8AF

Reg. Office Only.

Callers by appointment only.

Add 15% VAT and 50p P. & P.

All items subject to availability.

Add postage for all overseas parcels.