

PRACTICAL


ELECTRONICS

OCTOBER 1975

35p

FREE IN THIS ISSUE! **LINEAR I.C. IDENTICHART**

PE
ENGINE
ANALYSER
FOR ECONOMY
MOTORING

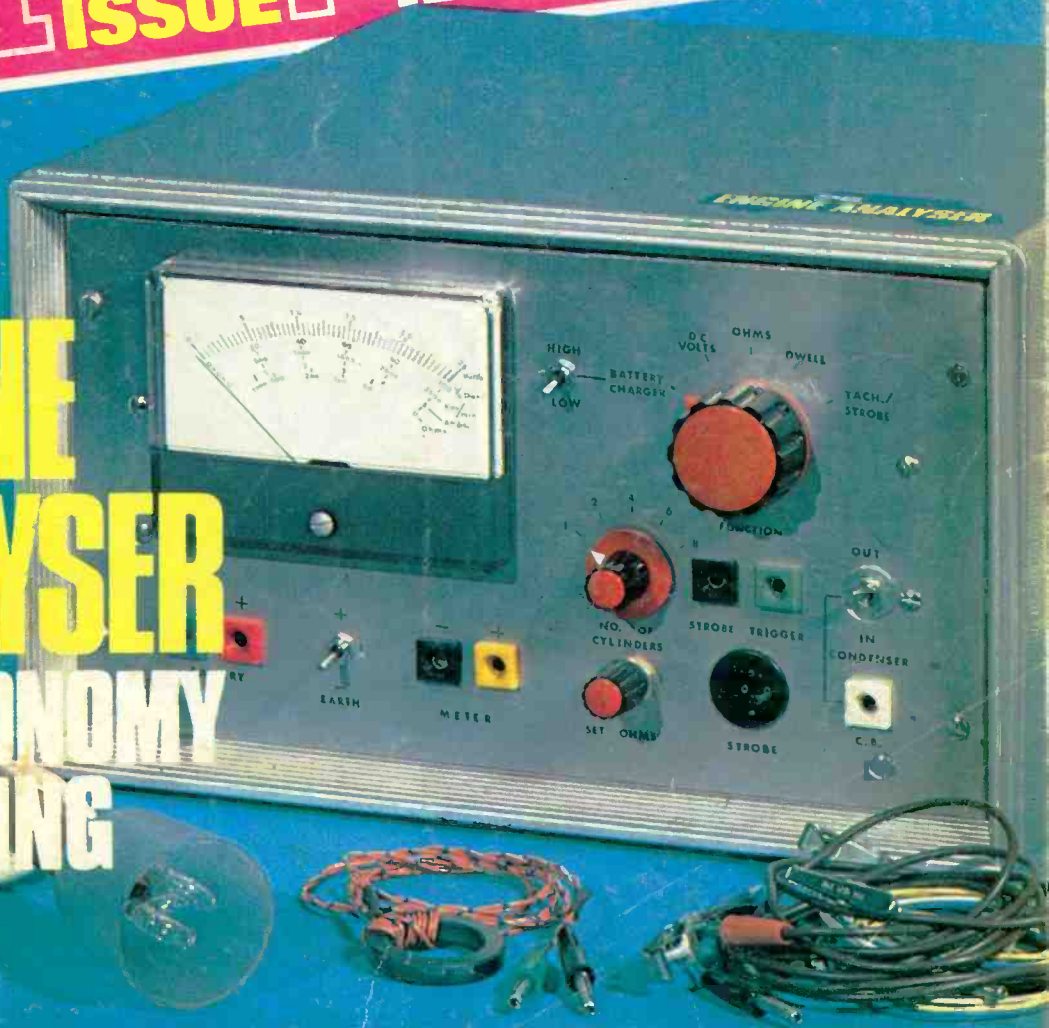

? **MICROPROCESSORS...**
the latest technology explained

PRACTICAL ELECTRONICS

VOLUME 11 No. 10 OCTOBER 1975

CONSTRUCTIONAL PROJECTS

- P.E. ENGINE ANALYSER** *by D. Haley*
Provides most of the needs for the economy minded motorist 796
- DIGITAL WRISTWATCH**
Assembling the Sabchron L.E.D. wristwatch 802
- ENVELOPE SHAPER** *by E. F. Flint*
A simple-to-build shaper with full ADSR facilities 810
- CONSTANT CURRENT LOAD**
A loading unit for power units and amplifiers 825
- LIGHT MODULATION UNIT** *by S. R. Beeching*
A two-channel sound to light effects system 828

GENERAL FEATURES

- SEMICONDUCTOR UPDATE** *by D. W. Coles*
A review of interesting devices 812
- MICROPROCESSORS—1** *by V. E. Yates*
A detailed look into this important new technology 816
- INGENUITY UNLIMITED**
Car Alarm—Simple Timer—Pulse Generator—Frequency Doubler—
VCO Circuit—Short Circuit Protection—Signal Indicator with Memory 834

NEWS AND COMMENT

- EDITORIAL**—Micro Master Minds 795
- NEWS BRIEFS**
A Stitch In Time—TV Innovations—Going Dutch—Talking to Computers—
Solar Cells—British Instrumentation 806, 843
- SPACEWATCH** *by Frank W. Hyde*
Earthquakes—Soviet Activities 809
- INTERNAVEX '75**
Some of the highlights of this years Audio/Visual show 815
- APRS '75**
A report on the Association of Professional Recording Studios exhibition 821
- BOOK REVIEWS**
Selected new books we have received 823, 832
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry 833
- PATENTS REVIEW**
Looking at Car Mirror Defrosting and a Rescue Transmitter/Receiver 841
- READOUT**
A selection of readers' letters 842

FREE ENTRY COMPETITION

- HOW INVENTIVE ARE YOU?**
Your last chance to win a Big Cash Prize 822

SPECIAL FREE DATA SHEET INSIDE THIS ISSUE

LINEAR I.C. IDENTICHART

At-a-glance functional equivalents of linear i.c.s.

Our November issue will be published on Friday, October 10, 1975
(for details of contents see page 824)

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Connoisseur

THE B.D.2 TURNTABLE ASSEMBLY

The Famous B.D.2 belt drive turntable with press button speed change has now been developed to feature a newly designed mat and brushed aluminium trim, and the perspex cover has an easy 'hinged-on, hinged-off' movement. The B.D.2 is available as a chassis unit or spring mounted on a wood plinth.



B.D.1 TURNTABLE KIT

The B.D.1 well known for its superb performance and quality is available in kit form. Construction is simplicity itself with no soldering required. Now it's so easy to own the best.

Contact your dealer for information or send a stamp for brochure.

A. R. SUGDEN & CO. (ENGINEERS) LTD

Atlas Mill Road, Brighouse HD6 1ER Telephone: Brighouse (04847) 2142. Telegrams and cables: Connoisseur, Brighouse



4½in x 3½in METER. 30µA, 50µA or 100µA, £3.85. 13p P. & P.

TAPE RECORDER LEVEL METER



500µA, 70p. 10p P. & P.



CARDIODYNAMIC MICROPHONE

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms. £7.40. 13p P. & P.

42 x 42mm meters 100µA, 500µA, 1mA, 500mA, £2.76. 11p P. & P.

60 x 45mm meters 50µA, 100µA, 500µA and 1mA VU meter, £2.92. 11p P. & P.

Edgewise meters 90mm x 34mm 1mA, £3.40. 13p P. & P.

MULTI-METER

Model ITI-2
20,000 ohm/volt, £6.90.
16½p P. & P.



3 WATT STEREO (1½ + 1½) PER CHANNEL AMPLIFIER
£4.30. 12½p P. & P.

All above prices include V.A.T. LARGE S.A.E. for List No. 11. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

ENGINEERS

FREE

YOURSELF FOR A

BETTER JOB WITH MORE PAY!

Do you want promotion a better job higher pay? 'New Opportunities' shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did!



CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

- | | | |
|---|---|--|
| <input type="checkbox"/> Practical Radio and Electronics (Technician) | <input type="checkbox"/> C. & G. Radio, TV & Electronics Mechanics | <input type="checkbox"/> C. & G. LI Installations and Wiring |
| <input type="checkbox"/> Electronic Engineering | <input type="checkbox"/> Radio Amateurs | <input type="checkbox"/> General Electrical Engineering |
| <input type="checkbox"/> Television Maintenance and Servicing | <input type="checkbox"/> Practical TV Colour Television | <input type="checkbox"/> Society of Engineers (Electrical Engineering) |
| <input type="checkbox"/> General Radio and TV Engineering | <input type="checkbox"/> Servicing | <input type="checkbox"/> Electrical Installations and Wiring |
| <input type="checkbox"/> Radio Servicing, Maintenance and Repairs | <input type="checkbox"/> Computer Electronics | <input type="checkbox"/> C. & G. Electrical Technicians (Primary) |
| | <input type="checkbox"/> C. & G. LI Radio TV Servicing cert. | <input type="checkbox"/> C. & G. Telecommunications |
| | <input type="checkbox"/> Post Master General 1st & 2nd class certs. | |
| | <input type="checkbox"/> C. & G. Electrical Engineering Practise | |

To **ALDERMASTON COLLEGE** Dept. EPE10,
Reading RG7 4PF
Also at our London Advisory Office, 4 Fore St. Avenue, Moorgate, London EC2Y 5EJ. Tel: 01-428 2721.

NAME (Block Capitals Please) _____

ADDRESS _____

POSTCODE _____

Other subjects _____

Age _____

Accredited by C.A.C.C.

Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

ORDER DIRECT FROM THE U.S. AND SAVE

SHIPMENT MADE WITHIN 3 DAYS FROM RECEIPT OF ORDER VIA AIR MAIL - POSTAGE PAID

10% Off on orders over £10
15% Off on orders over £50
20% Off on orders over £100

TTL

7400	£ 0.11 p	7448	£ 0.80 p	74150	£ 0.75 p
7401	J1	7450	12	74151	80
7402	11	7451	13	74153	71
7403	11	7453	13	74154	1.05
7404	13	7454	14	74155	95
7405	13	7450	11	74156	71
7406	22	7464	21	74157	71
7407	22	7465	21	74161	95
7408	14	7472	22	74163	1.05
7409	14	7473	26	74164	1.25
7410	11	7474	26	74165	1.25
7411	16	7475	41	74166	1.15
7413	35	7476	26	74173	95
7415	22	7483	70	74175	95
7416	22	7485	80	74176	95
7417	22	7486	26	74177	85
7420	11	7489	1.50	74180	80
7422	22	7490	45	74181	2.50
7423	22	7491	71	74182	80
7425	22	7492	44	74184	1.55
7426	23	7493	44	74185	1.45
7427	22	7494	49	74190	95
7430	12	7495	49	74191	95
7432	22	7496	55	74192	90
7437	25	74100	1.25	74193	85
7438	21	74105	60	74194	95
7440	11	74107	27	74195	80
7441	60	74112	32	74196	1.00
7422	56	74122	50	74197	75
7443	55	74123	55	74198	1.70
7444	60	74125	50	74199	1.70
7445	75	74126	50	74200	3.90
7446	85	74141	68		
7447	80	74145	75		

LOW POWER

74L00	£ 0.16 p	74L51	£ 0.16 p	74L90	£ 0.93 p
74L02	16	74L55	18	74L91	80
74L03	16	74L71	18	74L93	89
74L04	18	74L72	27	74L95	89
74L06	18	74L74	38	74L96	1.53
74L10	16	74L74	38	74L98	1.53
74L20	16	74L78	44	74L165	1.53
74L30	16	74L85	85		
74L42	89	74L86	38		

HIGH SPEED

74H00	£ 0.16 p	74H21	£ 0.16 p	74H55	£ 0.20 p
74H01	16	74H22	18	74H60	21
74H04	16	74H30	18	74H61	21
74H08	16	74H40	16	74H62	20
74H10	16	74H50	16	74H74	32
74H11	16	74H52	18		
74H20	16	74H53	20		

8000 SERIES

8091	£ 0.33 p	8214	£ 0.93 p	8811	£ 0.38 p
8092	33	8220	93	8812	60
8095	76	8230	1.42	8822	1.42
8121	49	8520	71	8830	1.42
8123	88	8551	91	8831	1.42
8130	1.20	8552	1.37	8836	27
8200	1.42	8554	1.37	8880	73
8210	1.92	8810	44		

9000 SERIES

9002	£ 0.21 p	9309	£ 0.49 p	9601	£ 0.54 p
9301	63	9312	49	9602	49

CMOS

74C00	£ 0.21 p	74C74	£ 0.63 p	74C162	£ 1.78 p
74C02	30	74C76	93	74C163	1.78
74C04	41	74C107	82	74C164	1.92
74C08	41	74C151	1.59	74C173	1.59
74C10	36	74C154	1.92	74C195	1.65
74C20	36	74C157	1.20	80C95	82
74C42	118	74C160	1.78	80C97	82
74C73	85	74C161	1.78		

9 DIGIT LED DISPLAY - FNA37

On multiplexed substrate, comm. cathode compatible with all 9 digit calculator chips, 7 segment right hand decimal, red with clear magnifying lens, .12" character, 4 to 4 MA, 1.8 V typ 2 1/2" x 1 1/2" high. **£1.95**

NINE DIGIT SPERRY GAS DISCHARGE DISPLAY

SP-425-09 1.25" x 3" overall - .25" digits - connects to 18 lead edge connector - hi voltage - prime quality. **98p**

8088 FUNCTION GENERATOR

Voltage Controlled Oscillator Sine, Square, Triangular Output 16 Pin Dip. **£2-15**

TIMERS

General purpose timer 8 pin DIP 35p
 Dual 555-DIP 61p
 Operates from unregulated +5 to 40V supply 49p

TTL

7410 DIP 8p
 7473 DIP 19p
 78175 DIP 69p

VOLTAGE REGULATORS

309K TO-3 79p
 340K TO-3 89p
 340T TO-220 69p

OCTOBER SPECIALS

POCKET CALCULATOR KIT

5 function plus constant - addressable memory with individual recall - 8 digit display plus overflow battery saver - uses standard or rechargeable batteries - all necessary parts in ready to assemble form - instructions included.



CALC. KIT WITH BATTERIES. **£10**

MEMORIES

2102-2 1024 bit x channel static RAM for use with 8008 CPU. **£2-79p**

MM5203 2048 bit static read only memory. Electrically programmable UV erasable. **£6-90**

MM5261 1024 bit fully decoded dynamic random access memory 18 pin DIP. **£1-50**

MEMORIES w/data

1101	256 bit RAM MOS	£ 0.96 p
1103	1024 bit RAM MOS	2-72
5203	2048 bit erasable PROM	13.68
5260	1024 bit RAM Low Power	2-16
7489	64 bit RAM TTL	1-50
8223	Programmable ROM	2-72

CALCULATOR & CLOCK CHIPS w/data

5001	12 DIG 4 funct fix dec	£ 1.46 p
5002	Same as 5001 exc btry pwr	1.95
5005	12 DIG 4 funct w/mem	2.42
MM5225	8 DIG 4 funct chain & dec	1-10
MM5736	18 pin 6 DIG 4 funct	2.42
MM5738	8 DIG 5 funct K & Mem	2.42
MM5739	9 DIG 4 funct (btry sur)	2.92
MM5311	28 pin BCD 6 dig mux	2.42
MM5312	24 pin 1 ops BCD 4 dig mux	1.94
MM5313	28 pin 1 pps BCD 6 dig mux	2.42
MM5314	24 pin 6 dig mux	2.42
MM5316	40 pin alarm 4 dig	2.42

LED & OPTO ISOLATOR

MV10B	Red TO 18	£ 0.14 p
MV50	Axial leads	8
MV50D2	Jumbo Vis. Red (Red Dome)	18
ME4	Infra red diff. dome	18
MAN 1	Red 7 seg. 270°	1.38
MAN 2	Red alpha num. 32"	2.72
MAN 4	Red 7 seg. 190°	1.18
MAN 5	Green 7 seg. 270°	1.62
MAN 6	6" high solid seg.	3-81
MAN 7	Red 7 seg. 270°	2.17
MAN 8	Yellow 7 seg. 270°	7.47
MAN 64	4" high solid seg.	2.45
MAN 66	6" high spaced seg	2.55
MCT2	Opto iso transistor	38

DTL

930	10 p	937	10 p	949	10 p
932	10	944	10	962	10
936	10	946	10	963	10

4000 SERIES RCA EQUIVALENT

CD4001	10 31 p	CD4013	£ 6.65 p	CD4023	£ 0.31 p
CD4009	47	CD4016	69	CD4025	31
CD4010	47	CD4017	1.62	CD4027	74
CD4011	31	CD4019	74	CD4030	52
CD4012	31	CD4022	1.50	CD4035	1.56

LINEAR CIRCUITS

300	Pos V Reg (super 723)	TO-5	£ 0.43 p
301	Hi Perf Op Amp	mDIP TO-5	18
302	Volt follower	TO 5	43
304	Neg V Reg	TO 5	49
305	Pos V Reg	TO 5	52
307	Op AMP (super 741)	mDIP TO 5	38
308	Micro Pwr Op Amp	mDIP TO 5	60
309K	5V 1A regulator	TO 3	91
310	V Follower Op Amp	TO 5-mDIP	65
311	Hi perf V Comp	mDIP TO 5	58
319	Hi Speed Dual Comp	DIP	71
320	Neg Reg 5.2, 12, 15	TO-3	74
322	Precision Timer	DIP	60
324	Quad Op Amp	DIP	1.07
339	Quad Comparator	DIP	92
340K	Pos. V reg (5, 6, 8, 12, 15, 18, 24)	TO-3	1-20
340T	Pos Volt Reg (6V, 8V, 12V, 15V, 18V, 24V)	TO-220	1-07
370	AGC/Squelch Amp	TO 5 or DIP	44
372	AF-IF Strip detector	DIP	66
376	Pos. V Reg	mDIP	33
377	2w Stereo amp	DIP	1.47
380	2w Audio Amp	DIP	81
380B	6w Audio amp	mDIP	69
381	Lo Noise Dual preamp	DIP	98
382	Lo Noise Dual preamp	DIP	98
550	Prec V Reg	DIP	54
555	Timer	mDIP	44
556	Phase Locked Loop	DIP	1.94
562	Phase Locked Loop	DIP	1.94
565	Phase Locked Loop	DIP	1.20
566	Function Gen	mDIP	1.20
567	Tone Decoder	mDIP	1.20
709	Operational AMPL	DIP	27
710	Hi Speed Volt Comp	DIP	21
711	Dual-Difference Compar	DIP	44
723	V Reg	DIP	38
738	Dual Hi Perf Op Amp	DIP	65
741	Comp Op AMP	mDIP TO-5	27
747	Dual 741 Op Amp	DIP or TO-5	44
748	Freq Adj 741	mDIP	27
1304	FM MulpX Stereo Demod	DIP	65
1307	FM MulpX Stereo Demod	DIP	65
1458	Dual Comp Op Amp	mDIP	38
LH2111	Dual LM 211 V Comp	DIP	1.07
	Audio preamp	DIP	44
3900	Quad Amplifier	DIP	33
7524	Core Mem Sense AMPL	DIP	1.04
7534	Core Mem Sense Amp	DIP	1.42
8864	9 DIG Led Cath Dvr	DIP	1.37
75451	Dual Peripheral Driver	mDIP	21
75452	Dual Peripheral Driver	mDIP	21
75453	(3S1) Dual Periph. Driver	mDIP	21
75491	Quad Seg Driver for LED	DIP	50
75492	Hex Digit Driver	DIP	55

Data included with order on request. Add 20p ea. if item is priced below 50p ea. Add 40p ea. if item is not ordered.

The prices as listed are in British pounds and pence. Send bank cheque or personal cheque with order. If international postal money order is used, send receipt with order. Minimum order £2-50p.

INTERNATIONAL ELECTRONICS UNLIMITED


P.O. BOX 1708 MONTEREY, CA. 93940 USA

PHONE (408) 659-3171

The above prices do not include any taxes leviable by a purchaser's country of residence



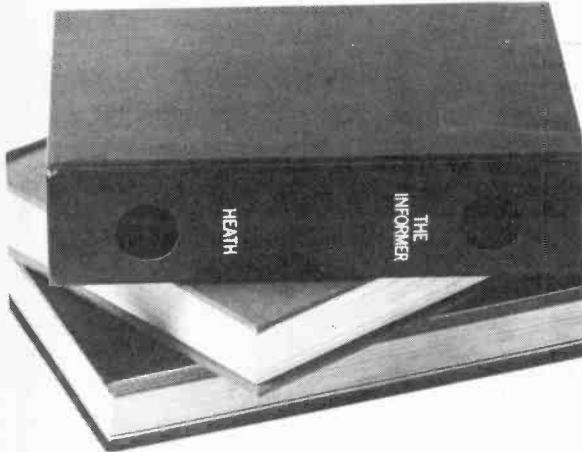Enough books are written about crime, this one stops it.



Outside it's a book. Inside it's an ingenious ultrasonic burglar alarm from Heathkit. The GD-39.


A complete kit that can be assembled in only a few enjoyable hours, with the help of a very easy to follow instruction manual.

The GD-39 works by transmitting a silent, ultrasonic signal throughout the room. And continuously monitoring it. Any movement made by an intruder in the room will then automatically produce a change in the signal. Which triggers off a lamp and, thirty seconds later, a remote buzzer, that just you hear, or a loud bell.

Enough to scare the living daylight out of a burglar. For more details, and a bookful of other ideas, just post the coupon now for your Heathkit catalogue.

Or, if you're in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

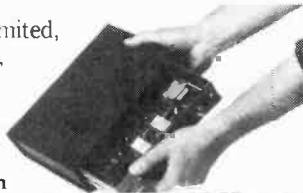Heath (Gloucester) Limited,
Dept. PE-105, Bristol Road,
Gloucester GL2 6EE.
Tel: (0452) 29451.



The GD-39 Ultrasonic Burglar Alarm

To: Heath (Gloucester) Limited, Dept. PE-105, Gloucester GL2 6EE. Please send me a Heathkit catalogue. I enclose a 10p stamp for postage.

HEATH
Schlumberger

HEATHKIT

Name _____

Address _____

Postcode _____

Monthly budget plan available

B. BAMBER ELECTRONICS

5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE

Telephone: ELY (0353) 860185 (2 lines) Tuesday-Saturday

ALL BELOW—ADD 25% VAT

TV plugs, metal type, 6 for 50p.
TV sockets, metal type, 5 for 50p.
TV line connectors (back-to-back socket), 5 for 50p.
Mixed electrolytics, large bag, £1.
OC200 transistors, 6 for 50p.
BSY95A transistors, 6 for 50p.
PNP audio type TO5 transistors, 12 for 25p.
IF cans $\frac{1}{2}$ in square, suitable for rewind, 6 for 30p.
DIN SPEAKER SOCKETS (2-pin) 4 for 30p.
HIGH QUALITY SPEAKERS, $8\frac{1}{2}$ x 6in elliptical, only 2in deep, inverse magnet, 4 ohms, rated up to 10W, £1.50 each, or 2 for £2.75 (qty discount available).

ALL BELOW—ADD 8% VAT

Black plastic knobs, $\frac{1}{2}$ in dia., $\frac{1}{2}$ in spindle, 4 for 50p.
Ring magnets, 7mm outside dia., 20 for 50p.
Large box of P.C. Boards containing transistors, I.C.'s, trim pots, resistors, capacitors, etc. (not unknown computer rubbish), £3 per box.
 $\frac{1}{2}$ in polythene chassis mounting fuseholders, 6 for 30p.
LES Lamps, 24V 1.2W, 10 for 40p.
3 Switch Push Button Units (3 x 2 pole, 2 way), min. push-push switches, $\frac{1}{2}$ in dia. buttons, mounted on one unit, 40p.
Perapex coil formers, $\frac{1}{2}$ in x $\frac{1}{2}$ in dia., 5 for 25p.
Turret tags, $\frac{1}{4}$ in dia., 25p pack.
Rotary switches, min. 4 pole 2-way, 2 for 50p.
Telephone type earpiece insert, 50p.
Reeds (for reed relays) single-pole make, 6 for 30p.
Mullard tubular ceramic trimmers, 1-18uF, 6 for 50p (as featured in Rad. Comm. Jan. p. 25).
I.C.'s, some coded, 14DIL type, untested, mixed, 20 for 25p.
Miniature slider switches, 2 pole, 2-way, 5 for 50p.

ALL BELOW—ADD 8% VAT

VARIABLE STABILISED PSU, solid-state 240V a.c. input, output 0-24V d.c. at 500mA, +32V d.c. at approx. 50mA. Voltage controlled by external 5k Ω pot. Size 7 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in (less 5k Ω pot), £5 each.
THREE-TURN WIRE-WOUND POTS, 5k Ω , for above, 75p each.
MAINS TRANSFORMERS
All 240V input, voltages quoted approx. RMS. (Please quote type no. only when ordering.)
TYPE 10.2, 10-0-10V at 2A, £1.50 each.
TYPE 18.2, 18V at 2A, £1.65 each.
TYPE 28.4, 28V at 4A + 125V at 500mA, £4.
TYPE 63.1, 6.3V at 1A, 85p each or 2 for £1.50.
TYPE 129, 400V at 20mA + 200V at 10mA + 6.3V at 500mA, £1.25.
TYPE 72703, 400V at 10mA + 200V at 5mA + 6.3V at 400mA, £1.25.
TYPE 70482, 250-0-250V at 80mA + 6.3V at 2A, £1.75.
RADIO SPARES 500W AUTO TRANSFORMERS, 100-110-130-200-220-240-250V tapped input and output, step-up or step-down facility, ex-new equip. £8.
CURLY LEADS, 4 core telephone type, 2 for 20p.
TRANSISTOR HEATSINKS, to take 2 x TO18 transistors, screw in clamps, block size 1 x $\frac{1}{2}$ x $\frac{1}{2}$ in, with holes for mounting, 3 for 50p.
LARGE DIE CAST BOXES (brand new IFT) 101 5 $\frac{1}{2}$ x 2 $\frac{1}{2}$ in, £2 each.
25-WAY ISEP PLUGS AND SOCKETS, 40p set (1 plug + 1 skt.).
Rotary switches 9-way 4-pole (separate wafers, plastic) $\frac{1}{2}$ in spindle, 40p each.
Heatsinks (Approx. 3in x 4in 2in high), 12 fins (drilled for 1 x TO3 transistor) brand new, 45p each.
PC board withdrawal handles, mixed cols., 8 for 50p.
Solder, 20SWG, 60/40 alloy, approx. 9yds, 25p.
TO3 transistor insulator sets, 10 for 50p.

TERMS OF BUSINESS: CASH WITH ORDER (minimum order £1) POST FREE (UK ONLY). PLEASE ADD VAT AS SHOWN

Export enquiries welcome. Callers welcome. Tues. to Sat. Please enclose S.A.E. with ALL enquiries.

BURNEZE


Cools soothes and heals minor burns

Burneze - unique aerosol first aid cools instantly, contains a fast-acting local anaesthetic plus antihistamine to control swelling. It deals with the lingering pain of a minor burn or scald and reduces the chance of a blister. From Boots and other chemists. S.A.E. to Potter & Clarke, Croydon CR9 3LP, for intriguing leaflet.





I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

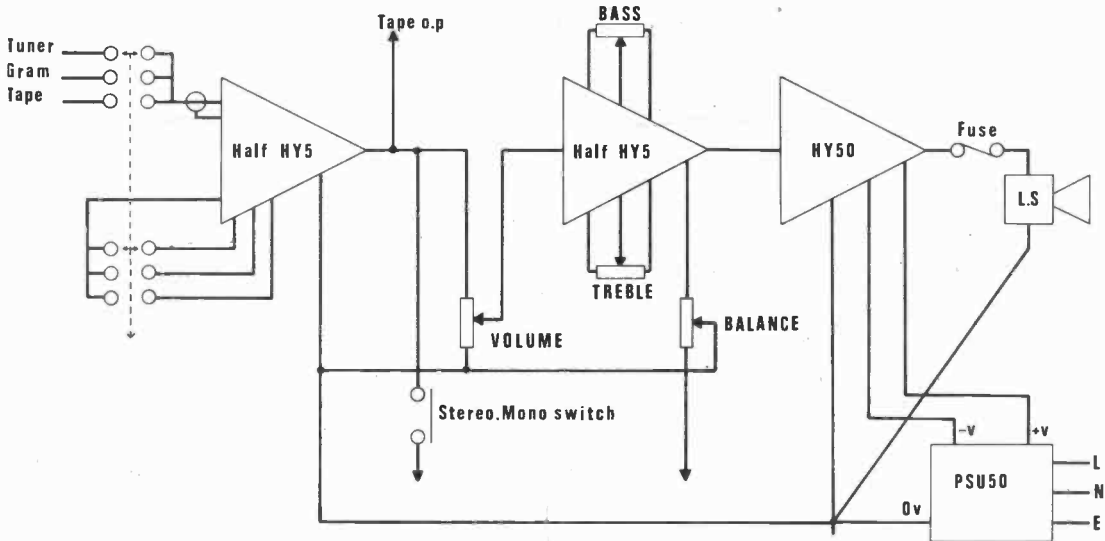

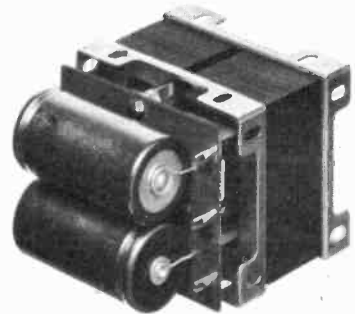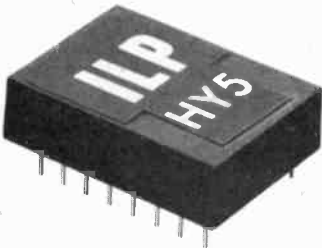MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION
Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 3–100mV; Input/impedance 47kΩ at 1kHz. Outputs: Tape 100mV; Main output 0db (0-775V RMS). Active Tone Controls: Treble ±12db at 10kHz; Bass ±12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 68db. Overload Capability: 40db on most sensitive input. Supply Voltage: ±16–25V.

The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

TECHNICAL SPECIFICATION
Output Power: 25W RMS into 8Ω. Load Impedance: 4–16Ω. Input Sensitivity: 0db (0-775V RMS). Input Impedance: 47kΩ. Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz–50kHz ±3db. Supply Voltage: ±25V. Size: 105 × 50 × 25mm.

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS
Output voltage: ±25V. Input voltage: 210–240V. Size: L 70, D 90, H 60mm.

PRICE £4.75

+£1.19 VAT
P. & P. free

PRICE £6.20

+£1.55 VAT
P. & P. free

PRICE £6.25

+£1.56 VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury,
Kent CT4 7AD.
Tel. (0227) 63218

Please Supply

Total Purchase Price

I Enclose Cheque Postal Orders Money Order


Please debit my Access account Barclaycard account

Account number

Name and Address


Signature

RADIO & TV SERVICING

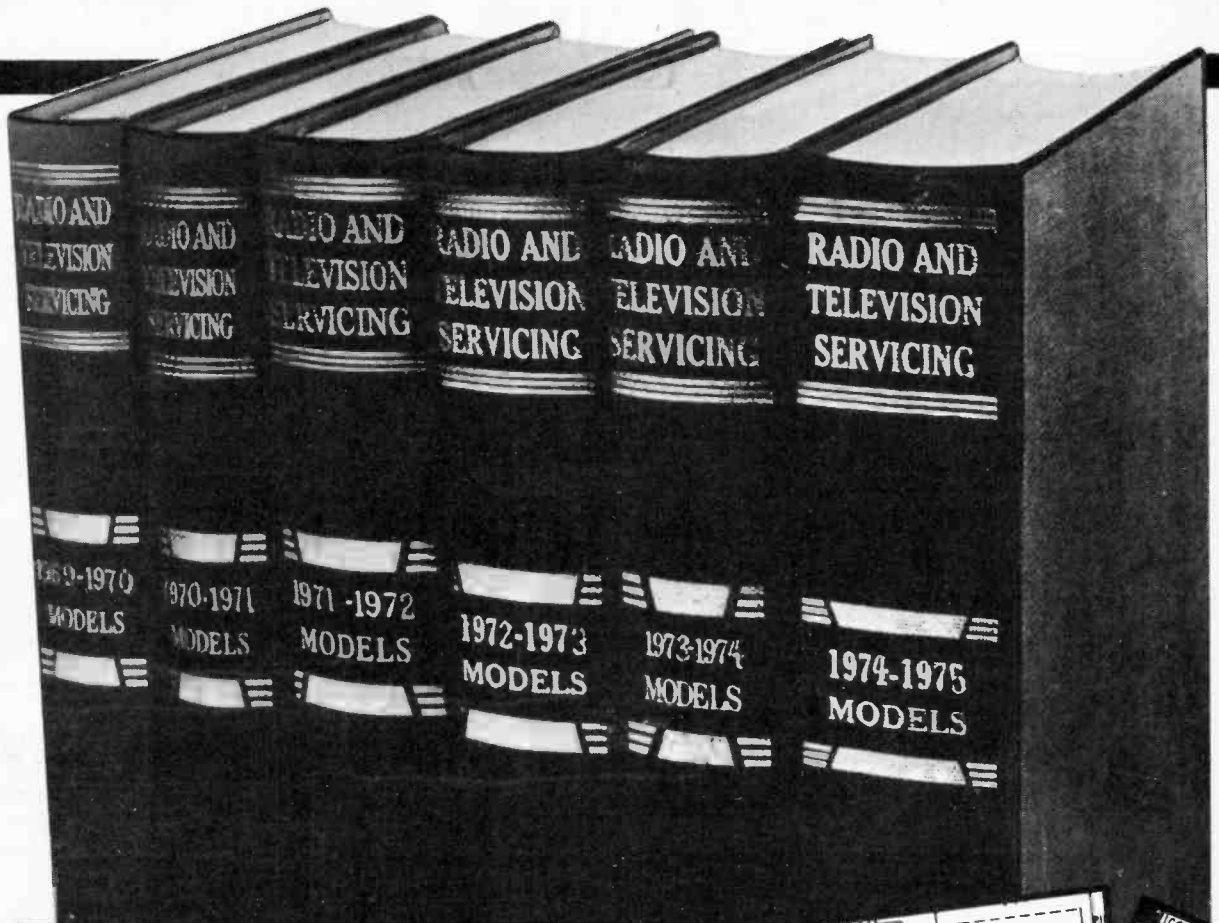

Essential data for over 1500 popular models

With this vast 6-volume library at your fingertips you have all the necessary servicing data you need covering almost every popular model from 1969 to the very latest on the market today. And not only radio and TV but stereograms, record players and tape recorders too. Much of the earlier information on this equipment is quite unobtainable elsewhere and *Radio & TV Servicing* is now the only available source of technical data. The 1975 edition, now ready, brings the library right up-to-date with abstracts from manufacturers' service bulletins issued during the past year. *Radio & TV Servicing* is the only work of its kind—a money-spinner that no service engineer should be without.

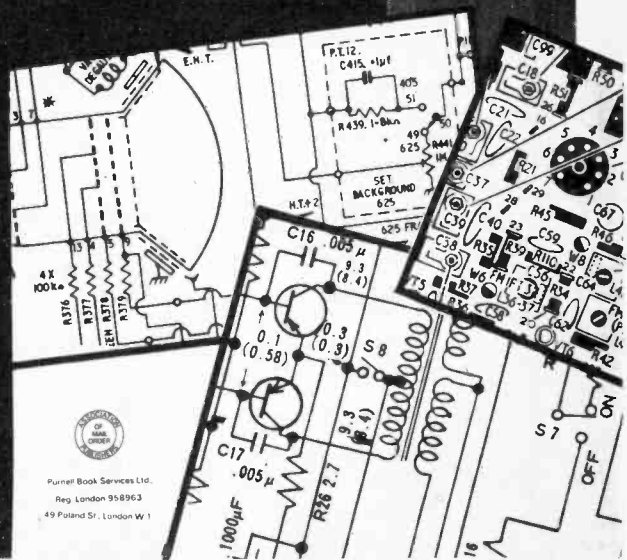

6 Volume library '69-'75 is now ready

The
only work
of its kind
anywhere


Speedier, more efficient servicing means increased turnover . . .

This library is a gold-mine of technical information. Six hard-bound volumes giving vital data on more than 1500 models of Television (colour and mono), Radios, Car Radios, Stereograms, Record Players and Tape Recorders. More than 4000 pages clearly display thousands of circuits, printed panel diagrams, component layout diagrams, waveform graphs, block diagrams, etc. Over 800 pages, devoted entirely to Colour TV, include installation instructions, new term explanations, purity adjustments, colour balance, static convergence and a wealth of invaluable information. Here, in fact, is all the data you need for efficient and speedy repair work.

Your Guarantee

Sending for these valuable books, even though you also enclose your remittance, commits you to nothing. Unless you are absolutely satisfied you are perfectly free to return the set and if you do so within 10 days of receipt your money will be refunded in full and without question.

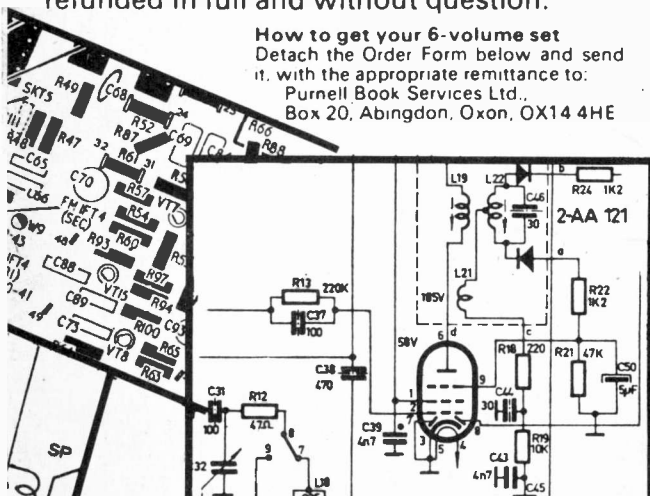How to get your 6-volume set
Detach the Order Form below and send it, with the appropriate remittance to:
Purnell Book Services Ltd.,
Box 20, Abingdon, Oxon, OX14 4HE



Makes of Colour TV include:

Alba, Baird, Bang and Olufsen, B.R.C., Bush, Decca, Dynatron, Ekco, Ferguson, Ferranti, G.E.C., Invicta, H.M.V., Marconiphone, I.T.T./K.B., Masteradio, Murphy, Philips, Pye, Sobell, Stella, Ultra, Hitachi, Thorn Consumer Electronics, Korting, R.G.D., Sony, Telefunken.

All these makes of Mono TV, Radios, Car Radios,

Stereograms, Record Players, Tape Recorders:

Aiwa, Alba, Baird, Bang and Olufsen, Beogram, Beolit, Blaupunkt, B.R.C., Bush, Cossor, Crown, Dansette, Decca, Defiant, Dulci, Dynatron, Eddystone, Ekco, Elizabethan, Ferguson, Ferranti, Fidelity, G.E.C., Grundig, Hacker, Halcyon, H.M.V., Hitachi, Invicta, I.T.T./K.B., JugoElektra, Klinger, Loewe Opta, Marconiphone, Masteradio, Monogram, Murphy, National, Nivico, Perdio, Peto Scott, Philco, Philips, Portadyne, Pye, Radiomobile, Radionette, R.G.D., Roberts' Radio, Robux, Sanyo, Sharp, Sobell, Sony, Standard, S.T.C., Stella, Stereosound, Telefunken, Teletron, Ultra, Unitra, Van Der Molen, World Radio, Thorn Consumer Electronics, Elpico, Rigonda (USSR); Waltham.

Plus such developments as:

Stereo Multiplex Transmission – Phase Locked Loop Stereo Decoding – Dynamic Noise Limiting – Adoption of Integrated Circuits in Receiver Design – Thyristor Power Supplies – Silicon Controlled Switch Timebases – Sony Trinitron Systems – Modifications to Circuitry and Fault-Finding Tips.

To: Purnell Book Services, P.O. Box 20, Abingdon, Oxon OX14 4HE

Please send me the 6-volume set of RADIO & TV SERVICING for which I enclose cheque / P.O. No. _____ crossed and made payable to Purnell Book Services Ltd. tick for the full cash price of £31.75 appropriate for £9.25 deposit to be followed by 6 successive box monthly payments of £4.00 (total £33.25)

I understand that unless I am entirely satisfied I may return the volumes in good condition within 10 days and my money will be refunded in full **BLOCK LETTERS PLEASE**

Name _____

Address _____

TRADE APPLICATION (To be accompanied by Trade Order)

Please supply _____ 6-volume set(s) of RADIO & TV SERVICING at £31.25 per set. (Credit 30 days) **BLOCK LETTERS PLEASE**

Name _____

Company _____

Signature _____

IMPORTANT: Individual volumes are available on application.

Please return entire form. Available U.K. only

057



CHINAGLIA

THE **MINOR** PROFESSIONAL QUALITY TEST EQUIPMENT

WITH

33 RANGES
20kΩ/V d.c.
4kΩ/V a.c.

- ROBUST CLASS 1.5 PRECISION MOVEMENT
- ACCURACY 2.5% D.C. AND 3.5% A.C.
- 12 MONTH GUARANTEE
- SELF-POWERED AND POCKET-SIZED
- OPTIONAL 30KV D.C. PROBE

PRICE £19.00 inc. VAT (P. & P. 80p)

PROBE £9.50



TRADE ENQUIRIES WELCOMED

For details of this and the many other exciting instruments in the Chinaglia range, including multimeters, component measuring, automotive and electronic instruments please write or telephone:

CHINAGLIA
(U.K.) LTD. 19 Mulberry Walk, London
SW3 6DZ Tel: 01-352 1897

CLOCK COMPONENTS

PE Clock Constructors see starred items*

- 6 DIGIT ALARM CLOCK KIT**—all components except for case to build clock with beep alarm, snooze function, intensity control, 0.3in LEDs £19.86
- *QUARTZ CRYSTAL TIMEBASE**—suitable for any digital clock. 32.768kHz Xtal. Xtal—high accuracy/stability for clock or watch £3.80
- *CRYSTAL TIMEBASE KIT**—will provide stable 50Hz for clock ICs giving time accurate to within a few seconds a month. contains PCB. 32.768kHz Xtal. 3CMOS ICs, trimmer, Cs, R_s, IC sockets, full instructions £8.40
- DL704E** 0.3in Red Common Cathode 7 segment LED display only 85p
- FND500** 0.5in Red CA LED £1.50 **MAN3M** 0.13in Red CC LED 48p
- *DL707** 0.3in Red CC LED £1.70 ***DL747** 0.6in Red CA LED £2.45
- MKS5253** 4 or 6 digit 12 or 24 hr format alarm clock IC with snooze £5.80
- *MM5314** 4/6 digit clock IC £4.44 **AY51224** 4 digit clock IC £4.25
- *SOLDERCON IC PIN SOCKETS**
- The sensible method for lowest cost sockets for ICs, displays, CMOS, TTL (nylon supports available if required; samples enclosed with any pin order). Strip of 100 pins for 50p; 400 for £2; 1,000 for £4; 3,000 for £10.50.
- *LSI Sockets** (Soldercon pins with nylon supports) 24, 28 and 40 pin, 30p each.

RCA CMOS PRICES ARE DOWN

Widest stock range in UK—at the new manufacturers one-off prices

£	£	£	£	£	£	£	£		
CD4000	0.17	CD4021	0.83	CD4039	7.47	CD4057	20.35	CD4082	0.18
CD4001	0.17	CD4022	0.79	CD4040	0.88	CD4059	10.84	CD4085	0.57
CD4002	0.17	CD4023	0.17	CD4041	0.89	CD4060	0.92	CD4086	0.57
CD4006	0.97	CD4024	0.84	CD4042	0.89	CD4061	16.43	CD4093	0.66
CD4007	0.17	CD4025	0.17	CD4043	0.83	CD4062	7.33	CD4095	0.86
CD4008	0.79	CD4026	1.42	CD4044	0.77	CD4063	9.90	CD4096	0.86
CD4009	0.46	CD4027	0.46	CD4045	1.15	CD4066	0.58	CD4099	1.50
CD4010	0.46	CD4028	0.74	CD4046	1.10	CD4068	0.18	CD4501	0.32
CD4011	0.17	CD4029	0.94	CD4047	0.74	CD4069	0.18	CD4502	1.02
CD4012	0.17	CD4030	0.46	CD4048	0.46	CD4070	0.18	CD4508	4.20
CD4013	0.46	CD4031	1.81	CD4049	0.46	CD4071	0.18	CD4510	1.26
CD4014	0.83	CD4032	0.88	CD4050	0.46	CD4072	0.18	CD4511	1.95
CD4015	0.83	CD4033	1.14	CD4051	0.77	CD4073	0.18	CD4518	1.03
CD4016	0.46	CD4034	7.83	CD4052	0.77	CD4075	0.18	CD4520	1.03
CD4017	0.83	CD4035	0.97	CD4053	0.77	CD4076	1.27	CD4532	1.18
CD4018	0.83	CD4036	7.47	CD4054	0.95	CD4077	0.18	CD4555	0.74
CD4019	0.46	CD4037	0.78	CD4055	1.08	CD4078	0.18	CD4585	1.45
CD4020	0.83	CD4038	0.88	CD4056	1.08	CD4081	0.18		

RCA 1975 CMOS Databook: Pin-Outs, 400 pages of data, 200 pages of circuits, applications and use, £2.30 (no VAT) plus 37p P. & P.

ADD VAT at 8% (higher rate does not apply to any of above), 15p P. & P. on orders under £3 (despatch is 1st class post BY RETURN!). Price List sent FREE with any order, or on request (a S.A.E. helps). Official orders welcomed (written or phoned)—Universities, Polytechnics, Government, Companies, etc. Export orders (no VAT), add 35p (Europe), 70p (overseas) for air mail P. & P.

SINTEL

53b Aston Street, Oxford Tel. 0865 43203

RELAY UNIT

Smart steel case 12 x 7 x 4 1/2 in with 22 PO Type relays, most with at least 3 sets c/o contacts, 4 reed relays + coils, 2 pots, resistors, capacitors, 12BH7 valve, various diodes, tag board, etc., etc. Only £3.50.

PC ETCHING KIT MK. II

Contains 1lb Ferric Chloride, 100 sq. in copper clad board, DALO etch resist pen, abrasive cleaner, etching dish and instructions. Now also includes 2 miniature drill bits. £3.50.

7b BARGAIN PARCELS

Hundreds of new components—pots, resistors, capacitors, switches + PC boards with transistors and diodes, also loads of odds and ends. Contents always changing. Only £3.

COMPUTER PANELS

Large quantity always available. 3lb asstd. £1.48; 7lb £2.85; 50lb £15. Pack with about 500 components inc. at least 50 transistors £1.

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb 80p; 3lb £1.80; 10lb £4.85; 100lb £35.

TRANSFORMERS

All mains primaries: 0-0-6V at 100mA 85p; 9-0-9V 100mA 90p; 12-0-12V 100mA 95p; 24-0-24V 500mA £1.95. 1A multitapped to give 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V, also 12-0-12 or 15-0-15 £3. 2A version £4.46. 17V 1A £1.80; 9V 1A £1.80. 1/2A £1.80. 12-0-12V at 500mA 80p. 30-0-30V 1A £3.10; 25V 1A £2.12; 12-0-12V 1A £2.05; 6-0-6V 1A £1.80.

80 metres of multi-coloured hook-up flex (40 x 2m lengths) ONLY £1.20.

Grommet mixture. Over 150 Grommets. All shapes and sizes 45p.

All prices quoted include UK post and VAT at 8% or 25% as appropriate. Surplus components and equipment wanted for cash. S.A.E. for list or enquiries.

Clearance of our store at TOWER WHARF, RAYMOND STREET, CHESTER, will begin mid-September. Over 50 tons to dispose of.

GREENWELD (PE10)

51 Shirley Park Road, Southampton, SO1 4FX. Tel. (0703) 772501. Also callers at 21 Deptford Broadway, SE8. Tel. 01-692 2009, and 38 Lower Addiscombe Road, Croydon. Tel. 01-688 2950.

BARGAIN PACKS

12 BC107	£1.20	25 1N4001	£1.20
14 BC108	£1.20	22 1N4002	£1.20
12 BC109	£1.20	20 1N4003	£1.20
15 BC148	£1.20	18 1N4004	£1.20
12 BC149	£1.20	16 1N4005	£1.20
12 BC157	£1.20	14 1N4006	£1.20
12 BC158	£1.20	12 1N4007	£1.20
12 BC159	£1.20	40 1N4148	£1.20
2 2N2646	£1.20	3 2N3055	£1.20
10 BC328	£1.20	12 BC548	£1.20
12 BF194	£1.20	12 BF195	£1.20
7 BF173	£1.20	5 BF181	£1.20

All full spec. marked components.

COMPUTER TAPE STATION

1/2 in 7 track deck and electronics in 5ft cabinet. £80 plus VAT and carr.

8 PIN DIL 741's

10 + 25p; 25 + 23p; 100 + 21p; 250 + 20p.

555 TIMERS

SPECIAL OFFER: 10 for £4.50.

75013ND 3 watt I.C. only £1.20.

RESISTORS AND CAPACITORS

400 asstd. carbon resistors £1.40. 250 Hi-stabs 1.2, 5%, 1, 1W £1.35. 100 Wirewounds, 2W to 15W £2. 200 ceramic, mica, etc. caps £1.10. 100 C280 polyesters, 0.01-0.47 £1.30. 200 min. electrolytics, but mainly unmarked, so only £1.35. 15 airpaped and compression trimmers up to 1250PF £1.10. JUMBO PACK—1 each of the above, 19.80 value for only £7.50!!

VEROBOARD

100 sq.in. about 8 pieces asstd. sizes and pitches £1.15.

MISCELLANEOUS

SPCO microswitch, 5a 12p; 15 asstd. pots 75p; plug in relay, 2500Ω 4c/o 25p; 4 x 80V 10A rects. on heat sink, ideal batt. charger £1.20; SNT6600N £1. Good range close tolerance resistors—S.A.E. list. 96kHz crystal £1.


TRANSISTOR PACKS

Large quantity of mainly unmarked out of spec. transistors in stock. Sample tests show 75% OK. Sold in mixed packs with PNP, NPN, RF, AF, plastic, metal can, small signal and power devices. At least 200 for £1.50; 500 for £3.50; 1,000 for £7. Out of spec. 2N3055 a 8 for £1.10. 25 untested BFY51 type transistors £1.10. 25 untested BC108 £1; 100 £3. 200 unmarked 1N4148 £1.

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER STEREO AND MONO

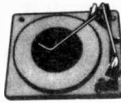Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.C. 200/250V Size 13 1/2 x 11 1/2 in.



Above motor board 3 1/2 in. Below motor board 2 1/2 in. with STEREO and MONO CARTRIDGE **£9.25** Post 75p


PORTABLE PLAYER CABINET

Modern design. Rexine covered. Vynair front grille. Chrome fittings. Size 17 x 15 x 8 in approx. **£5.25** Post 75p

Motor board cut for BSR or Garrard deck.

COMPLETE STEREO HI-FI SYSTEM

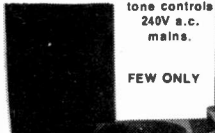Two full size loudspeakers 13 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeakers making it extremely compact, overall size only 13 1/2 x 10 x 8 1/2 in., 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls 240V a.c. mains.



FEW ONLY

Bargain Price **£25** £1 carriage

Attractive Teak finish

SPECIAL OFFER!

SMITH'S CLOCKWORK 15 AMP TIME SWITCH

0-60 MINUTES **£2.50** Post 35p

Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Brand new and fully guaranteed.



WEYRAD P50 — TRANSISTOR COILS

RAF2 Ferrite Aerial 85p Driver Trans. LFD4. 65p
I.F. P50/2CC 470 kc/s 40p Printed Circuit. PCA1 65p
3rd I.F. P50/3CC 40p J.B. Tuning Gun £1.20
Sprea Cores 50p Weyrad Booklet 10p
P50/1A 60p OPT 65p
Mullard Ferrite Rod 8 x 1/2 in., 20p. 6 x 1/2 in., 20p. 3 x 1/2 in. 10p

VOLUME CONTROLS

5kΩ to 2MΩ. LOG or LIN. L/S 20p. D.P. 35p. STEREO L/S 55p. D.P. 75p. Edge 5K. S.P. Transistor 25p

80 Ohm Coax 5p yd.

BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £2. 60 yd. £3.50. FRINGE LOSS. IDEAL 625 and colour **10p** yd

8 in. or 10 x 6 in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance, 10 watts, music power. **£4.35** Post 35p.



E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With tweeter and crossover. 10 watt. **£5.25** Post 35p
State 3, 8 or 15 ohm.

With flared tweeter cone and ceramic magnet. 10 watt. **£3.45** Post 35p
Bass res. 45-80 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm.



Bookshelf Cabinet

Teak finish 13 1/2 in x 8 in. Bass Woofer, 20 watts, £8.30 **£7.60** Post 75p

THE "INSTANT" BULK TAPE ERASER AND HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£4.35** Post 30p



BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides 8 x 4 in 55p; 8 x 6 in 85p; 10 x 7 in 80p; 12 x 8 in £1; 14 x 9 in £1.20; 16 x 9 in £1.20; 12 x 3 in 80p; 16 x 10 in £1.40. ALUMINIUM PANELS 18 s.w.g. 8 x 4 in 12p; 8 x 6 in 18p; 14 x 3 in 20p; 10 x 7 in 24p; 12 x 5 in 25p; 12 x 8 in 34p; 16 x 6 in 34p; 16 x 9 in 40p; 12 x 12 in 47p; 12 x 10 in 60p. ALI BOXES: 3 x 3 x 3 in 70p; 4 x 4 in 80p; 6 x 4 x 4 in £1; 9 x 4 x 4 in £1.25; 12 x 4 x 4 in £1.50.

ELAC 9 x 5 in HI-FI SPEAKER TYPE 59RM

This famous unit now available. 10 watts, 8 ohm.

£3.45

QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 3/4 in thick wood cabinet. Size 18 1/2 in x 16 1/2 in x 8 1/2 in. Weight 22 lbs. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6 1/2 inch Woofer £7.50 Carr. 85p
Rosewood Veneer £8.50 Carr. 85p
Baffle could be cut to take larger speaker.



RCS POWER PACK KIT

12 VOLT, 750mA. Complete with printed circuit board and assembly instructions. **£3.35** Post 30p
12 VOLT 300mA KIT, £3.15. 9 VOLT 1 AMP KIT, £3.35.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER—BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1 1/2 x 1 1/2 in. Response 25 c/s to 25 kc/s, 20 db gain. For use with valve or transistor equipment. Ideal display, teaching electro magnetism or for Post 1 metronome, strobe, etc. **£1.45** 30p

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V d.c. operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal display, teaching electro magnetism or for Post 1 metronome, strobe, etc. **95p**

BRITISH FM/VHF TUNING HEART

88 to 108 M/Cs British made. 2 Transistors ready aligned requires 1.5V d.c. Complete with 1000 component gang. Connections supplied but some technical experience essential.

Our price **£3.95** Post 25p

10-7 M/Cs I.F. strip £4.95 DECODER £4.95

MAINS TRANSFORMERS

	ALL POST 50p each
250-0-250V 70mA, 6-3V, 2A	£2.90
250-0-250 80mA, 6-3V 3-5A, 6-3V 1A or 5V 2A	£4.80
350-0-350 80mA, 6-3V 3-5A, 6-3V 1A or 5V 2A	£5.80
300-0-300V 120mA, 6-3V 4A C.T., 6-3V 2A	£7.00
MINIATURE 200V 20mA, 6-3V 1A	£1.10
MIDCUT 220V 40V, 6-3V 1A	£1.25
HEATER TRANS. 6-3V 1amp 85p, 3 amp	£1.40
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V £4.60	
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4.80	
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £7.00	
3 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8.70	
4 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £11.25	
6-6V 500mA £1. 9V 1 amp, £1. 12V 300mA £1. 12V 500mA £1. 12V 750mA £1. 10V, 30V, 40V, 2amp. £2.75, 20V, 3 amp, £2.45. 40V, 2 amp. £2.95. 22-0-22V, 4amp. d.c. £3.45. 16V, 1/2 amp. 95p. 16V, 2 amp. £2.20. 0, 5, 8, 10, 16V, 1/2 amp. £1.95. 20V 1/2 amp. £1.75. 20V 1 amp. £2.20.	
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £4.60; 500W £9.75; 150W £17.50; 1000W £23.	
BATTERY CHARGERS. Ready built with leads and clips 4 amp £4; 5 amp £4.50.	
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs, 1/2 amp 40p; 2 amp 55p; 4 amp 85p.	

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V 3A 720W insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. OUR **£13.50** Carr. 95p
Famous make. (Value £19). PRICE **£13.50** Carr. 95p
Can be used as 800W auto transformers 240-110V. IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS

2/350V	20p	250/25V	20p	50 x 50/300V	50p
4/350V	20p	500/25V	25p	900/350V	50p
8/350V	28p	100 + 100/275V85p	32 + 32/250V	200p	85p
16/350V	35p	150 + 200/275V 70p	32 + 32/450V	80p	85p
32/500V	60p	8 + 8/350V	35p	350 + 50/325V	85p
25/25V	15p	6 + 16/350V	35p	100 + 50 + 50/350V	85p
50/50V	15p	16 + 16/350V	60p	32 + 32 + 32/350V	85p
100/25V	15p	32 + 32/350V	60p	4700/63V	95p

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

MICRO SWITCHES

TRIMMERS 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p. CERAMIC, 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0-17p, 0-5 13p; 1mF 150V 15p; 2mF 150V 15p. 500V-0-001 to 0-05 5p; 0-1 10p; 0-25 13p; 0-47 25p.

SUB-MICRO SWITCHES


TWIN GANG, "0-0" 208pF + 176pF £1.20; 500pF standard 75p. 385 + 385 + 25 + 25pF. Slow motion drive 50p. 120pF TWIN GANG, 50p; 385pF TWIN GANG, 50p.

NEON PANEL INDICATORS 250V AC/AC. Amber 30p. RESISTORS. 2W, 1/4W, 1W, 20% 2p; 2W, 10%, 100 to 10M. HIGH STABILITY. 1/4W, 1W, 20% 10p; 10M, 10p.

Ditto 5%. Preferred values 10 ohms to 10 meg., 5p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 12p each. TAPE OSCILLATOR COIL Valve type 35p.

NEW MODEL "BAKER LOUDSPEAKER", 12IN 50 WATT. GROUP 50/12. 8 OR 15 OHM HIGH POWER. FULL RANGE PROFESSIONAL QUALITY. **£14.50** Post 60p

BAKER MAJOR 12" £11.50

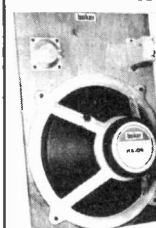

30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c/s. Rated 20W. NOTE: 3 or 8 or 15 Ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£14.50** Post 60p each
Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS 40p each

'Group 25'	'Group 35'	'Group 50/15'
12in. £8.80	12in. £10.50	15in. £19.50
25W 3 or 8 or 15 ohm	35W 3 or 8 or 15 ohm	50W 8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER AND CABINETS

For 12in or 10in dia. speaker 20 x 13 x 12in, £12.50 Post 75p
For 13 x 8in or 8in speaker 16 x 10 x 7in, £7.60 Post 60p
For 8 x 5in speaker, 16 x 8 x 8in, £5.80 Post 40p
LOUDSPEAKER CABINET WADDING 18in wide, 20p ft

GOODMANS 6 1/2 in. HI-FI SPEAKER



4 ohm or 8 ohm. 10W. Large ceramic magnet. Special Cambric cone surround. Twin cone. Frequency response, 30-15,000 c/s. Ideal P.A. Columns. HI-FI Enclosure Systems, etc. **£4.60**

NEW MODEL JUST RELEASED

R.C.S. 100 WATT VALUE AMPLIFIER

CHASSIS. 4 inputs. master volume bass and treble. Ideal P.A. Disco, or group amplifier. Professional quality, solid job. Matches all loudspeakers. **£85** carr. £2.

SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-18kc/s, 10W 8 ohm or 15 ohm £3.
De Luxe Horn Tweeters 2-18kc/s, 15W, 15 ohm £4.50
CROSSOVERS, TWO-WAY 3,000 c/s 3 or 8 or 15 ohm £1.90.
LOUDSPEAKERS P.M. 3 OHMS. 7 x 4in, £1.80; 6 1/2 in., £1.80; 6 x 5in., £1.90; 8in., £2.20.
SPECIAL OFFER: 80 ohm, 2 1/2 in, 2 1/2 in, 35 ohm, 2in, 3in, 25 ohm, 2 1/2 in. dia., 3in. dia., 5in. dia., 8 ohm, 2 1/2 in, 3in., 2 1/2 in, 15 ohm, 3 1/2 in. dia., 6 1/2 in. dia., 7x4in., 8x5in., 8x5in., 2in. dia., 2 1/2 in. dia., 5in. dia. **£1.25** each
RICHARD ALLAN TWIN CONE LOUDSPEAKERS, 8in. diameter 4W £3.50. 10in. diameter 5W £2.95; 12in. diameter 6W £3.50. 3/8/15 ohms, please state. VALVE OUTPUT TRANS. 40; MIKE TRANS. 50; 1 amp. Mike trans. mu metal 100-1 £1.25.

Loudspeaker Volume Control 15 ohms 10W with one inch long threaded bush for wood panel mounting. 1/2 in spindle. 65p each, Post 15p.

MAJOR 100 WATT ALL PURPOSE AMPLIFIER



All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8715 ohm a.c. Mains. Separate treble and bass controls. **£59** Carr. £1.00 each
Guaranteed. Details SAE.
NEW MODEL MAJOR—50 watt, 4 Input, 2 vol. Treble and bass. Ideal disco amplifier. **£49.95**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER.

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. TWO STEREO CHANNELS VERSION **£6.85**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready Built, with volume, Treble and bass controls. 18 volt d.c. Mains Power Pack £3.45

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 15p.

OUTLET BOXES, SURFACE 40p. FLUSH 60p. TWIN 85p. BALANCED TWIN RIBBON FEEDER 300 ohms. 7p yd. JACK SOCKET Std. open-circuit 18p, closed circuit 23p; Chrome Lead-Socket 45p. Phono Plugs 8p. Phono Socket 8p. JACK PLUGS Std. Chrome 30p; 3-5mm Chrome 15p. DIN SOCKETS Chassis 3-pin 10p, 5-pin 10p. DIN SOCKETS Lead 3-pin 25p, 5-pin 25p. DIN PLUGS 3-pin 18p, 5-pin 25p. VALVE HOLDERS, 10p; CERAMICS 10p; CANS 10p.

R.C.S. SOUND TO LIGHT KIT.

Kit of parts to build a 3 channel sound to light unit. 1,000 watts per channel. £12.50. Post 35p.

EMI TAPE MOTOR



EMI TAPE MOTORS, 240V a.c. 1,200 r.p.m. 4 pole 135mA. Spindle 0-187x0-75in. Size 3 1/2 x 2 1/2 x 1 1/2 in (illustrated). Post 40p. 120V Model, £1.

RADIO COMPONENT SPECIALISTS

Radio Books and Components Lists 10p. (Minimum posting charge 30p.)

337 WHITEHORSE ROAD, CROYDON
Open 9-6. Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30)
Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665

BI-PAK

TRANSISTORS

BRAND NEW FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price
AC107	0.20	BSY40	0.29	AF118	0.36	ORP61	0.41*
AC113	0.19	BSY41	0.29	AF124	0.31	P20	0.51*
AC115	0.20	BSY95	0.13	AF125	0.31	P346A	0.20
AC117K	0.30	BSY95A	0.13	AF126	0.29	P397	0.43
AC122	0.12	BU105	£2.04	AF127	0.29	ST141	0.43
AC125	0.18	C111E	0.51	AF128	0.51	ST141	0.43
AC126	0.18	C400	0.31	AF178	0.51	TIP29	0.44
AC127	0.19	C407	0.26	AF179	0.51	TIP30	0.52
AC128	0.19	C424	0.26	AF180	0.51	TIP31A	0.56
AC132	0.15	C425	0.51	AF181	0.51	TIP32A	0.68
AC134	0.15	C426	0.36	AF186	0.51	TIP41A	0.68
AC137	0.15	C428	0.20	AF239	0.38	TIP42A	0.81
AC141	0.19	C441	0.31	AL102	0.38	TIP43A	0.81
AC141K	0.30	C442	0.31	AL103	0.38	UT46	0.28*
AC142	0.19	C444	0.36	ASY26	0.26	ZN414	1.11
AC142K	0.28	C450	0.22	ASY27	0.31	ZG301	0.19
AC161	0.16	MAT100	0.19	ASY28	0.26	ZG302	0.19
AC164	0.20	MAT101	0.20	ASY29	0.26	ZG303	0.19
AC165	0.20	MAT120	0.19	ASY60	0.26	ZG304	0.25
AC166	0.20	MAT121	0.20	ASY51	0.26	ZG306	0.19
AC167	0.20	MAT122	0.20	ASY52	0.26	ZG308	0.36
AC168	0.20	MJE2955	0.88	ASY54	0.26	ZN2926 G	0.13
AC169	0.20	MJE3050	0.57	ASY55	0.26	ZN2926 Y	0.11
AC168	0.20	MJE3440	0.51	ASY56	0.26	ZN2926 O	0.10
AC168	0.25	MFF102	0.43	ASY57	0.26	ZN2926 R	0.10
AC169	0.15	MFF104	0.38	ASY58	0.26	ZN2926 B	0.10
AC176	0.20	MFF105	0.38	AS129	0.41	ZN301	0.31*
AC177	0.20	OC19	0.38	ASZ21	0.21	ZN3011	0.15
AC178	0.29	OC20	0.65	BC107	0.08	ZN3053	0.18
AC179	0.29	OC22	0.47	BC108	0.08	ZN3054	0.47
AC180	0.20	OC23	0.49	BC109	0.08	ZN3055	0.42
AC180K	0.30	OC24	0.87	BD136	0.41	ZN3319	0.15
AC181	0.20	OC25	0.39	BD137	0.41	ZN3391 A	0.17
AC182	0.30	OC26	0.30	BD138	0.51	ZN3392	0.15
AC187	0.22	OC28	0.51	BD139	0.56	ZN3393	0.15
AC187K	0.23	OC29	0.51	BD140	0.61	ZN3394	0.15
AC188	0.22	OC35	0.43	BD155	0.81	ZN3395	0.18
AC188K	0.23	OC36	0.51	BD175	0.81	ZN3402	0.21
AC1917	0.26	OC41	0.20	BD176	0.81	ZN3403	0.21
AC1918	0.20	OC42	0.25	BD177	0.87	ZN3404	0.29
AC1919	0.20	2N918	0.31	BD178	0.67	ZN3405	0.43
AC1920	0.20	2N929	0.21	BD179	0.71	ZN3414	0.16
AC1921	0.20	2N930	0.21	BD180	0.71	ZN3415	0.16
AC1922	0.17	2N1121	0.20	BD185	0.67	ZN3416	0.29
AC1927	0.19	2N1122	0.22	BD186	0.87	ZN3417	0.29
AC1928	0.19	2N1392	0.15	BD187	0.77	ZN3525	0.77*
AC1929	0.36	2N1303	0.15	BD188	0.71	ZN3614	0.69
AC1930	0.29	2N1304	0.18	BD189	0.77	ZN3615	0.76
AC1931	0.29	2N1305	0.18	BD190	0.77	ZN3616	0.76
AC1934	0.21	2N1306	0.21	BD195	0.87	ZN3646	0.09
BC173	0.15	2N1307	0.21	BD196	0.87	ZN3702	0.12
BC174	0.15	2N1308	0.24	BD197	0.92	ZN3703	0.12
BC175	0.22	2N1309	0.24	BD198	0.92	ZN3704	0.13
BC177	0.19	2N1613	0.20	BD199	0.96	ZN3705	0.12
BC178	0.19	2N1711	0.20	BD200	0.88	ZN3706	0.12
BC179	0.19	2N1899	0.32	BD205	0.81	ZN3707	0.13
BC180	0.25	2N1890	0.46	BD206	0.81	ZN3708	0.08
BC181	0.25	2N1893	0.36	BD207	0.98	ZN3709	0.09
BC182	0.15	2N2147	0.78	BD208	0.98	ZN3710	0.09
BC182L	0.15	2N2148	0.56	BD209	£1.40	ZN3711	0.09
BC183	0.15	2N2192	0.38	BF115	0.25	ZN3819	0.29
BC183L	0.15	2N2193	0.36	BF117	0.46	ZN3820	0.51
BC184	0.20	2N2194	0.36	BF118	0.71	ZN3821	0.36
BC184L	0.20	2N2217	0.22	BF119	0.71	ZN3823	0.29
BC186	0.29	2N2218	0.20	BF121	0.46	ZN3903	0.29
BC187	0.29	2N2219	0.20	BF123	0.51	ZN3904	0.31
BC197	0.19	2N2220	0.22	BF125	0.46	ZN3905	0.29
BC198	0.11	2N2221	0.20	BF127	0.51	ZN3906	0.28
BC199	0.12	2N2222	0.20	BF152	0.56	ZN4058	0.12
BC212L	0.13	2N2368	0.18	BF153	0.46	ZN4059	0.10
BC213L	0.13	2N2369	0.15	BF154	0.46	ZN4060	0.12
BC214L	0.17	2N3869A	0.15	BF155	0.71	BC113	0.10
BC225	0.26	2N2411	0.25	BF156	0.46	BC114	0.16
BC228	0.36	2N2412	0.25	BF157	0.56	BC115	0.16
BC291	0.28	2N2646	0.48	BF158	0.56	BC116	0.18
BC302	0.25	2N2711	0.21	BF159	0.61	BC117	0.19
BC303	0.31	2N2712	0.21	BF160	0.41	BC118	0.10
BC304	0.37	2N2714	0.21	BF162	0.41	BC119	0.31
BC440	0.31	2N2904	0.18	BF163	0.41	BC120	0.81
BC460	0.37	2N2904A	0.21	BF164	0.41	BC125	0.12
BCY30	0.27	2N2905	0.21	BF165	0.41	BC126	0.19
BCY31	0.27	2N2905A	0.21	OC44	0.16	BC132	0.12
BCY32	0.31	2N2906	0.16	OC45	0.13	BC134	0.19
BCY33	0.22	2N2906A	0.19	OC70	0.10	BC135	0.12
BCY34	0.26	2N2907	0.20	OC71	0.10	BC136	0.18
BCY70	0.15	2N2907A	0.22	OC72	0.15	BC137	0.18
BCY71	0.20	2N2923	0.15	OC74	0.15	BC138	0.41
BCY72	0.15	2N2924	0.15	OC75	0.16	BC140	0.31
BCZ10	0.20	2N2925	0.15	OC76	0.16	BC141	0.31
BCZ11	0.26	ACY35	0.21	OC77	0.26	BC142	0.31
BCZ12	0.26	ACY36	0.29	OC81	0.16	BC143	0.31
BD115	0.63	ACY40	0.18	OC81D	0.16	BC145	0.46
BD116	0.81	ACY41	0.18	OC71	0.16	BC147	0.47
BD123	0.67	AD123	0.36	OC82D	0.16	BC158	0.12
BD124	0.70	AD130	0.39	OC83	0.20	BC149	0.12
BD131	0.51	AD140	0.49	OC139	0.20	BC150	0.19
BD132	0.61	AD143	0.39	OC140	0.20	BC151	0.20
BD133	0.67	AD149	0.51	OC169	0.28	BC152	0.18
BD136	0.41	AD161	0.36	OC170	0.28	BC153	0.29
BFY33	0.15	AD162	0.36	OC200	0.26	BC154	0.31
BSX19	0.16	AD161 &	0.36	OC201	0.29	BC158	0.12
BSX20	0.16	AD162(MP)	0.36	OC202	0.26	BC159	0.12
BSY25	0.16	AD1740	0.51	OC203	0.28	BC160	0.46
BSY26	0.18	AF114	0.25	OC204	0.28	BC161	0.61
BSY27	0.18	AF115	0.25	OC205	0.36	BC167	0.12
BSY28	0.18	AF116	0.25	OC206	0.41	BC168	0.12
BSY29	0.18	AF117	0.25	ORP71	0.41*	BC169	0.12
BSY38	0.19	AF118	0.25	ORP12	0.41*	BC170	0.15
BSY40	0.19	AF117	0.25	ORP60	0.41*	BC171	0.15

SEMICONDUCTORS

74 SERIES T.T.L. I.C.'s

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS.

Type	Quantities	Type	Quantities	Type	Quantities
	1 25 100+		1 25 100+		1 25 100+
7400	0.14 0.13 0.12	7448	£1.02 0.99 0.97	74122	0.65 0.63 0.60
7401	0.14 0.13 0.12	7450	0.14 0.13 0.12	74123	0.69 0.68 0.65
7402	0.14 0.13 0.12	7451	0.14 0.13 0.12	74141	0.79 0.76 0.73
7403	0.14 0.13 0.12	7453	0.14 0.13 0.12	74145	£1.20 £1.16 £1.11
7404	0.14 0.13 0.12	7454	0.14 0.13 0.12	74150	£1.39 £1.30 £1.20
7405	0.14 0.13 0.12	7460	0.14 0.13 0.12	74151	£1.02 0.97 0.93
7406	0.36 0.31 0.29	7470	0.30 0.27 0.25	74153	0.93 0.88 0.83
7407	0.38 0.31 0.29	7472	0.30 0.27 0.25	74154	£1.57 £1.43 £1.48
7408	0.23 0.22 0.21	7473	0.38 0.36 0.32	74155	£1.11 £1.06 £1.02
7409	0.23 0.22 0.21	7474	0.38 0.36 0.32	74156	£1.11 £1.06 £1.02
7410	0.14 0.13 0.12	7475	0.56 0.54 0.52	74157	0.93 0.88 0.83
7411	0.23 0.22 0.21	7476	0.41 0.40 0.39	74160	£1.30 £1.25 £1.20
7412	0.26 0.25 0.24	7480	0.56 0.54 0.51	74161	£1.02 0.97 0.93
7413	0.30 0.29 0.28	7481	1.02 0.97 0.93	74162	£1.30 £1.25 £1.20
7414	0.28 0.27 0.26	7482	0.83 0.79 0.74	74163	£1.30 £1.25 £1.20
7417	0.28 0.27 0.26	7483	£1.11 £1.06 0.97	74164	£1.67 £1.62 £1.55
7420	0.14 0.13 0.12	7484	0.93 0.90 0.88	74165	£1.67 £1.62 £1.55
7422	0.28 0.27 0.26	7485	£1.48 £1.44 £1.39	74166	£1.48 £1.44 £1.39
7423	0.37 0.36 0.35	7486	0.32 0.31 0.30	74174	£1.48 £1.44 £1.39
7426	0.37 0.35 0.33	7490	0.60 0.58 0.56	74176	£1.16 £1.11 £1.06
7427	0.37 0.35 0.33	7491	£1.02 0.97 0.93	74177	£1.16 £1.11 £1.06
7428	0.42 0.39 0.37	7492	0.69 0.66 0.59	74180	£1.16 £1.11 £1.06
7430	0.14 0.13 0.12	7493	0.69 0.66 0.59	74181	£3.68 £3.56 £3.47
7432	0.37 0.35 0.33	7494	0.79 0.76 0.69	74182	£1.16 £1.11 £1.06
7433	0.39 0.37 0.35	7495	0.79 0.76 0.69	74184	£1.67 £1.62 £1.55
7437	0.32 0.30 0.28	7496	0.89 0.86 0.80	74190	£1.81 £1.76 £1.71
7438	0.32 0.30 0.28	74100	£1.39 £1.34 £1.30	74191	£1.81 £1.76 £1.71
7440	0.14 0.13 0.12	74104	0.56 0.54 0.51	74192	£1.81 £1.76 £1.71
7441	0.69 0.66 0.59	74105	0.56 0.54 0.51	74193	£1.81 £1.76 £1.71
7442	0.69 0.66 0.59	74107	0.41 0.39 0.37	74194	£1.20 £1.16 £1.11
7443	£1.11 £1.06 £1.02	74110	0.56 0.51 0.46	74195	£1.02 0.97 0.93
7444	£1.11 £1.06 £1.02	74111	0.32 0.31 0.29	74196	£1.11 £1.06 £1.02
7445	£1.47 £1.44 £1.39	74118	0.93 0.88 0.83	74197	£1.11 £1.06 £1.02
7446	£1.11 £1.06 £1.02	74119	£1.39 £1.30 £1.20	74199	£2.56 £2.50 £2.45
7447	£1.02 0.99 0.97	74121	0.46 0.40 0.41	74199	£2.31 £2.21 £2.11

Devices may be mixed to qualify for quantity price. (TTL 74 series only) data is available for the above series of I.C.'s in booklet form. PRICE 35p.

PO BOX 6 WARE HERTS

SUPER UNTESTED PAKS

Pak No.	Description	Price
U 1	120 Glass Sub-min. General purpose Germ. diodes	0-60
U 2	50 Mixed Germanium transistors AF/RF	0-60
U 3	75 Germanium gold bonded sub-min. like OA5, OA47	0-60
U 4	30 Germanium transistors like OC81, AC128	0-60
U 5	60 200mA sub-min. silicon diodes	0-60
U 6	30 Sil. Planar trans. NPN like BSY95A, 2N706	0-60
U 7	16 Sil. rect. TOP-HAT 750mA VLTG. RANGE up to 100	0-60
U 8	50 Sil. planar diodes DO-7 glass 250mA like OA200/202	0-60
U 9	20 Mixed voltages, 1 Watt Zener Diodes	0-60
U10	20 BAY50 charge storage diodes DO-7 glass	0-60
U11	20 PNP Sil. planar trans. TO-5 like 2N1132, 2N2904	0-60
U13	30 PNP-NPN Sil. transistors OC200 & 2S104	0-60
U14	150 Mixed silicon and germanium diodes	0-60
U15	20 NPN Sil. planar trans. TO-5 like 2N696, 2N697	0-60
U16	10 3Amp sil. rectifiers stud type up to 1000 PIV	0-60
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0-60
U18	8 6 Amp sil. rectifiers BYZ13 type up to 600 PIV	0-60
U19	20 Silicon NPN transistors like BC 108	0-60
U20	12 1-5 Amp sil. rectifiers top hat up to 1000 PIV	0-60
U21	30 AF. Germ. alloy transistors 2Q300 series & OC71	0-60
U23	25 MGMT's like MHz series PNP transistors	0-60
U24	20 (Germ.) 1 Amp rectifiers GJM series up to 300 PIV	0-60
U25	25 300 MHz NPN silicon transistors 2N708, BSY27	0-60
U26	30 Fast switching silicon diodes like IN914 Micro-Min	0-60
U29	10 1 Amp SCR's TO-5 can. up to 600 PIV CR8125-800	£1-20*
U32	25 Zener diodes 400 mW DO-7 case 3-33 volts mixed	0-60
U33	15 Plastic case 1 Amp sil. rectifiers IN4000 series	0-60
U34	30 Silicon PNP alloy trans. TO-5 BCY26 28302/4	0-60
U35	25 Silicon planar transistors PNP TO-18 2N2906	0-60
U36	20 Silicon planar NPN transistors TO-5 BFY50/51/52	0-60
U37	30 Silicon alloy transistors SO-2 PNP OC200, 82322	0-60
U39	20 Fast switching silicon trans. NPN 400 MHz 2N3011	0-60
U40	10 Dual transistors 6 lead TO-5 2N2060	0-60
U43	25 Silicon trans. plastic TO-18 A.P. BC113/114	0-60
U44	20 Silicon trans. plastic TO-5 BC115	0-60
U45	7 3A SCR. TO66 up to 600 PIV	£1-20*
U46	20 Unijunction transistors similar to T1843	0-60*
U47	10 TO220AB plastic triacs 50V 6A	£1-20*
U48	9 NPN Sil. power transistors like 2N3055	£1-20*
U49	12 NPN Sil. plastic power trans. 60W like 2N5294/5296	£1-20

Code No's mentioned above are given as a guide, to the type of device in the pak. The devices themselves are normally unmarked.

QUALITY TESTED PAKS

Pak No.	Quality Tested Paks	Price
Q 1	20 Red spot transistors PNP	0-60
Q 2	16 White spot R.F. transistors PNP	0-60
Q 3	4 OC 77 type transistors	0-60
Q 4	6 Matched transistors OC44/45/81/81 D	0-60
Q 5	4 OC 75 transistors	0-60
Q 6	5 OC 72 transistors	0-60
Q 7	4 AC 128 transistors PNP high gain	0-60
Q 8	4 AC 126 transistors PNP	0-60
Q 9	7 OC 81 type transistors	0-60
Q10	7 OC 71 type transistors	0-60
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0-60
Q12	3 AF 116 type transistors	0-60
Q13	3 AF 117 type transistors	0-60
Q14	3 OC 171 H.F. type transistors	0-60
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0-60
Q17	5 NPN 2 x ST.141. & 3 x ST.140	0-60
Q18	4 MADT'S 2 x MAT 100 & 2 x MAT 120	0-60
Q19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0-60
Q20	4 OC 44 Germanium transistors A.F.	0-60
Q21	4 AC 127 NPN Germanium transistors	0-60
Q22	20 NKT transistors A.F. R.F. coded	0-60
Q23	10 OA 202 Silicon diodes sub-min	0-60
Q24	8 OA 81 diodes	0-60
Q25	15 IN 914 Silicon diodes 75PIV 75mA	0-60
Q26	8 OA95 Germanium diodes sub-min-1N69	0-60
Q27	2 10A 600 PIV Silicon rectifiers 18425B	0-60*
Q28	2 Silicon power rectifiers BYZ 13	0-60*
Q29	4 Sil. transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0-60
Q30	7 Silicon switch transistors 2N706 NPN	0-60
Q31	6 Silicon switch transistors 2N708 NPN	0-60
Q32	3 PNP Sil. trans. 2 x 2N1131, 1 x 2N1132	0-60
Q33	3 Silicon NPN transistors 2N1711	0-60
Q34	7 Sil. NPN trans. 2N2869, 500MHz (code P397)	0-60
Q35	3 Silicon PNP TO-5 2 x 2N2904 & 1 x 2N2905	0-60
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0-60
Q37	3 2N3053 NPN Silicon transistors	0-60
Q38	5 PNP transistors 3 x 2N3703, 2 x 2N3702	0-60
Q39	5 NPN transistors 3 x 2N3704, 2 x 2N3705	0-60
Q40	5 NPN transistors 3 x 2N3707, 2 x 2N3708	0-60
Q41	3 Plastic NPN TO18 2N3904	0-60
Q43	5 BC 107 NPN transistors	0-60
Q44	5 NPN transistors 3 x BC 108, 2 x BC 109	0-60
Q45	3 BC 113 NPN TO-18 transistors	0-60
Q46	3 BC 115 NPN TO-5 transistors	0-60
Q47	4 NPN high gain transistors 2 x BC 157, 2 x BC 168	0-60
Q48	3 BCY 70 PNP transistors TO-18	0-60
Q49	3 NPN transistors 2 x BFY 51, 1 x BFY 52	0-60
Q50	7 BSY 28 NPN switch transistors TO-18	0-60
Q51	7 BSY 95A NPN transistors 300MHz	0-60
Q52	8 BY 100 type silicon rectifiers	£1-20
Q53	25 Sil. & Germ. trans. mixed all marked new	£1-50
Q54	6 TIL 209 Red LED	£1-20*

MAMMOTH I.C. PAK

APPROX. 200 PIECES
Assorted full-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices but some unmarked—you to identify.
OUR SPECIAL PRICE £1.20p

WORLD SCOOP

JUMBO SEMICONDUCTOR PAK
Transistors—Germ. and Silicon. Rectifiers—Diodes Triacs—Thyristors—I.C.'s and Zeners. ALL NEW AND CODED
APPROX 100 PIECES
Offering the amateur a fantastic bargain PAK and an enormous saving—identification and data sheet in every pak.
ONLY £1.85p

UNTESTED LIN PAKS

Manufacturers "Fall Outs" which include Functional and part Functional Units. These are classed as "out-of-spec" from the makers' very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price
ULIC709	= 10 x 709	0-60
ULIC710	= 7 x 710	0-60
ULIC741	= 7 x 741	0-60
ULIC747	= 5 x 747	0-60
ULIC748	= 7 x 748	0-60

C280 CAPACITOR PAK

Containing 75 of the C280 range of capacitors assorted in values ranging from .01nF to 2.2uF. Complete with identification chart.
FANTASTIC VALUE
ONLY £1.20p.

SIL. G.P. DIODES

300 mW 40 PIV (min) SUB-MIN FULLY TESTED
Ideal for Organ builders
30 for 50p, 100 for £1.50, 500 for £5, 1000 for £9.

G.P. SWITCHING TRANS

TO18 SIM. TO 2N706/8 BSY27/28/95A
All usable devices. No open and shorts. ALSO AVAILABLE IN PNP similar to 2N2905, BCY 70 20 for 50p, 50 for £1.100 for £1.80, 500 for £3, 1000 for £14.
When ordering please state NPN or PNP

G.P. 100

30 WATT GERMANIUM TO3 METAL CASE
Vbeo 80V, Vceo 50V, IC 10A, Hfe 30-170 replaces the majority of Germanium power Transistors in the OC, AD NKT range.

	1-24	25-99	100+
	44p	41p	37p

G.P. 300

115 WATT SILICON TO3 METAL CASE
Vbeo 100V, Vceo 60V, IC 15A, Hfe. 20-100 suitable replacement for 2N3055, BDY11 or BDY20

	1-24	25-99	100+
	50p	48p	46p

INDICATORS

3015F Minitron 7 Segment Indicator £1.11p*
MAN 3M L.E.D. 7 SEGMENT DISPLAY O.127" High Characters £1.76p*

ZENER DIODES

FULL RANGE IN STOCK
VOLTAGE RANGE 2-33V

	400 mw 8p	1-5 w 17p	10 w* 80p
--	-----------	-----------	-----------

EXCLUDE VAT
AT 25% TO ALL
***ADD 8%**
NO VAT
add 20p overseas
Minimum order 75p

VOLTAGE REGULATORS

TO3 Plastic Encapsulation

	5V	5V	12V	12V	15V	15V	18V
MA.7805/L199	5V	(Equip. to MVR5V)	£1-25p				
MA.7812/L130	12V	(Equip. to MVR12V)	£1-25p				
MA.7815/L131	15V	(Equip. to MVR15V)	£1-25p				
MA.7818	18V	(Equip. to MVR18V)	£1-25p				

THYRISTORS

PIV	0-6A	0-8A	1A	3A	5A	5A	7A	10A	16A	30A
	TO18	TO92	TO5	TO66	TO66	TO64	T448	TO49	TO48	TO48
10	0-18	0-15	—	—	—	—	—	—	—	—
20	0-15	0-18	—	—	—	—	—	—	—	—
30	0-19	0-22	—	—	—	—	—	—	—	—
50	0-22	0-28	0-20	0-25	0-36	0-36	0-48	0-51	0-54	£1-18
100	0-25	0-30	0-25	0-25	0-48	0-48	0-51	0-57	0-58	£1-43
150	0-31	0-38	—	—	—	—	—	—	—	—
200	0-38	0-44	0-25	0-30	0-50	0-50	0-57	0-62	0-62	£1-68
400	—	—	0-30	0-39	0-55	0-57	0-62	0-71	0-77	£1-79
600	—	—	0-39	0-48	0-69	0-69	0-78	0-99	0-90	—
800	—	—	0-58	0-65	0-81	0-81	0-92	£1-22	£1-39	£4-07

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA119	0-08	BY101	0-12	BYZ16	0-41	OA85	0-09
AA120	0-08	BY105	0-18	BYZ17	0-38	OA90	0-07
AA129	0-08	BY114	0-12	BYZ18	0-36	OA91	0-07
AA Y30	0-09	BY124	0-12	BYZ19	0-28	OA95	0-07
AAZ13	0-10	BY126	0-15	CG62	—	OA200	0-07
BA100	0-10	BY127	0-18	(OA91Eq) 0-06	—	OA202	0-07
BA116	0-21	BYZ11	0-31	CG651 (OA70)	—	8D19	0-06
BA126	0-22	BY130	0-17	OA79	0-07	IN34	0-07
BA148	0-15	BY133	0-21	OA5 Short	—	IN34	0-07
BA154	0-12	BY164	0-51	Leads	0-81	IN34A	0-07
BA165	0-15	BY X38/300-43	—	OA10	0-14	IN914	0-06
BA156	0-14	BYZ10	0-36	OA47	0-07	1N916	0-06
BA173	0-15	BYZ11	0-31	OA70	0-07	1N448	0-06
BB104	0-15	BYZ12	0-31	OA79	0-07	1S021	0-10
BY100	0-16	BYZ13	0-26	OA81	0-07	1S051	0-70

UNTESTED T.L. PAKS

Manufacturers "Fall Outs" which include Functional and part Functional Units. These are classed as "out-of-spec" from the makers' very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price
UIC07	= 12 x 7400	0-60	UIC72	= 8 x 7472	0-60
UIC07	= 12 x 7401	0-60	UIC73	= 8 x 7473	0-60
UIC02	= 12 x 7402	0-60	UIC74	= 8 x 7474	0-60
UIC03	= 12 x 7403	0-60	UIC75	= 8 x 7475	0-60
UIC04	= 12 x 7404	0-60	UIC76	= 8 x 7476	0-60
UIC05	= 12 x 7405	0-60	UIC80	= 5 x 7480	0-60
UIC06	= 8 x 7406	0-60	UIC81	= 5 x 7481	0-60
UIC07	= 8 x 7407	0-60	UIC82	= 5 x 7482	0-60
UIC10	= 12 x 7410	0-60	UIC83	= 5 x 7483	0-60
UIC13	= 8 x 7413	0-60	UIC86	= 5 x 7486	0-60
UIC20	= 12 x 7420	0-60	UIC90	= 5 x 7490	0-60
UIC30	= 12 x 7430	0-60	UIC91	= 5 x 7491	0-60
UIC40	= 12 x 7440	0-60	UIC92	= 5 x 7492	0-60
UIC41	= 5 x 7441	0-60	UIC98	= 5 x 7498	0-60
UIC42	= 8 x 7442	0-60	UIC94	= 5 x 7494	0-60
UIC43	= 5 x 7443	0-60	UIC95	= 5 x 7495	0-60
UIC44	= 5 x 7444	0-60	UIC96	= 5 x 7496	0-60
UIC45	= 5 x 7445	0-60	UIC100	= 5 x 74100	0-60
UIC46	= 5 x 7446	0-60	UIC121	= 5 x 74121	0-60
UIC47	= 5 x 7447	0-60	UIC141	= 5 x 74141	0-60
UIC48	= 5 x 7448	0-60	UIC151	= 5 x 74151	0-60
UIC50	= 12 x 7450	0-60	UIC154	= 5 x 74154	0-60
UIC51	= 12 x 7451	0-60	UIC193	= 5 x 74193	0-60
UIC53	= 12 x 7453	0-60	UIC199	= 5 x 74199	0-60
UIC54	= 12 x 7454	0-60	UIC X1 25 Assorted 74's	£1-50	
UIC80	= 12 x 7480	0-60			
UIC70	= 8 x 7470	0-60			

IDEAL FOR DISCOS

Sound to Light Master Unit



600 WATTS PER CHANNEL
Connects to your loudspeaker or loudspeaker socket. The unit can be connected to your existing spotlight fittings or to our type A or B fittings.

£30.95

including channel output plugs and mains input socket.

ALL PRICES INCLUDE V.A.T. and POST & PACKING (These prices apply to the United Kingdom only)

Twin Bank 6 LIGHT UNIT



(less lamps)
B.C. FITTING £9.55 (each)
Length 14½ inches
E.S. FITTING £10.35 (each)


Type A



(less lamp)
B.C. FITTING £1.95 (each)
E.S. FITTING £2.12 (each)


100 WATT SPOT LAMPS
Red, pink, yellow, green, blue, clear. £1-18 each
Only **£1** B.C. or E.S. Fitting
Minimum 3 lamps **£3.54**

Type B 3 BANK UNIT

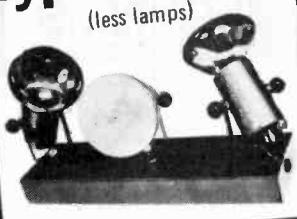

(less lamps)
B.C. FITTING £6.90 (each)
E.S. FITTING £7.26 (each)

Twin Bank 12 LIGHT UNIT

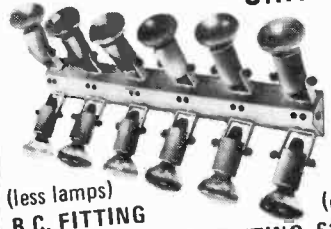

(less lamps)
B.C. FITTING £15.60 (each)
Length 31½ inches
E.S. FITTING £17.00 (each)

Send 20p for illustrated leaflet & price list.
TRAFALGAR SUPPLIES
Dept.H.T., STANDISH STREET, BURNLEY, LANCs.

OSMABET LTD

We make transformers amongst other things

AUTO TRANSFORMERS 110-200/220/240V
30W. £2-10. 50W. £2-70. 75W. £3-45. 100W. £4-50. 500W. £12-75. 1000W. £20-35, etc.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 5V 1A, 60p; 6.3V 1.5A, £1-45; 3A, £1-80; 6A, £3-60; 12V 1.5A, £1-80; 3A, £3-30; 6A CT, £4-50; 18V 1.5A CT, £3-30; 24V 1.5A CT, £3-30; 3A CT, £4-50; 5A, £6-75; 8A, £8-70; 12A, £12-40; 40V 3A CT, £6-50; 6A CT, £15-75; 25V 2A + 25V 2A, £8-40; 12V 4A + 12V 4A, £8-40.

LT TRANSFORMERS TAPPED SEC. Prim 200/240V
0-10-12-14-16-18V 2A, £3-30; 4A, £4-50.
0-12-15-20-24-30V 2A, £4-20; 4A, £8.
0-5-20-30-40-60V 1A, £4-20; 2A, £8.
0-40-50-60-80-90-100-110V 1A, £8-40.

MIDGEE RECTIFIER TRANSFORMERS
For FW rect., 200/240V a.c. 6-0-6V 1.5A or 9-0-9V 1A £1-85 each; 12-0-12V 1A or 20-0-20V 0.75A or 9-0-9V 0.3A or 12-0-12V 0.25A or 20-0-20V 0.15A or 6V 0.5A + 6V 0.5A or 9V 0.35A + 9V 0.35A or 12V 0.25A + 12V 0.25A or 20V 0.15A + 20V 1.5A, all at £1-90 each.

MAINS TRANSFORMERS
Prim. 200/240V a.c. TX6 sec., 425-0-425V 500 MA, 6.3V CT 6A, 6.3V CT 6A, 0-5-6.3V 3A £18-75; TX1 425-0-425V 250 MA, 6.3V CT 4A, 6.3V CT 4A, 0-5-6.3V 3A, £11-25; MT3 Prim. 0-110-240V, sec., 250V 100 MA, 6.3V 2A, £15-75.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec., tapped 3-6-15 ohms, A-A 6.6K/30W £8-75; A-A 3k/50W £10-15; 100W (EL34 KT88, etc.), £17-25.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30W to 400W 35p.

HI-FI SPEAKERS
5in 8Ω, £1-15; Goodman 10W full throw 8Ω, £4-25; 8in 4Ω, £1-50; EMI 13 x 8in 8Ω, 450 £4-25; 8in twin cone 8Ω, £2; 8 x 5in 3, 8, 15 or 80Ω, £1-75.

LOUDSPEAKERS
2½in 8 or 75Ω, 2½in 8 or 25Ω, 3in 3, 8 or 35Ω, 3½in 8Ω, 15Ω or 80Ω, 95p each; 5in 3, 8 or 25Ω, 5 x 3in 3, 8, 15, 25 or 35Ω, 95p each; 7 x 4in 3, 15 or 25Ω, 10 x 6in 3Ω, £1-50, 9 x 8in HI-FI C.M. 8Ω, £2-50.

SPEAKER AUTO MATCHING TRANSFORMER
12W 3 to 8 or 15Ω up or down, £1-50.

PAPER TUBULAR CONDENSERS W.E.
4 7mf, 160V, 30 x 20mm, 20p; 100 for £10.

"INSTANT" BULK TAPE/CASSETTE ERASER
Instant erasure, any diameter tape spools, cassettes, magnetised tape heads, 200/240V a.c., £3-75.

SYNCHRONOUS GEARED MOTORS, 200/240V a.c.
Brand new, Smiths, Built-in gearbox, 2r.p.h., 75p each. Carriage and VAT extra on all orders.
S.A.E. ENQUIRIES, LISTS, MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 8YQ
Tel. 01-958 9314

DIGITAL CLOCK KITS

MHI—A modular approach to digital clock building. An MHI Kit clock uses an MHI clock kit plus an MHI display kit. Any of the clock kits will interface with any of the display kits or with any other common-anode LED display. Each clock kit contains basic components plus a PCB—all you have to supply is a few resistors, transistors, etc.

MHI-5378—This kit has full car/boat clock facilities, quartz time source, brightness control, etc. Display is switchable with ignition for power saving.

Kit: MM5378, socket, CA3081, 2MHz, Xtal and trimmers, PCB £15-10

MHI-5024—The MHI-5024 kit will act as a 6 or 4 digit stopwatch chip with readouts down to 1/10 sec. Clock will count up or down and can (with additional components) also act as a calculator.

Kit: MK50204, socket, CA3081, PCB £14-00

MHI-5314—Six digit basic clock, 12/24 hour, MM5314 chip £6-60

MHI-5025—Six digit alarm clock, Snooze, MK50250 chip £9-35

MHI-7001—Six digit time/date/alarm/timer, can be used as electronic time-switch in addition to other functions £10-00

MHI-D707—Four or six digit display kit, 0.3in digits. Supplied with PCB 4 digit—£6-60, 6 digit—£9-50

MHI-D727—Four or six digits, 0.5in high digits. Supplied with 6 digit PCB 4 digit—£8-50, 6 digit—£12-00

MHI-D747—Four or six digits, 0.6in high digits. Supplied with PCB for 6 digits. 4 digit—£9-80, 6 digit—£14-70

Terms: CWO. Access, Barclaycard (simply quote your number and sign). Credit facilities to accredited account holders.
VAT—All prices exclude VAT (8%). P. & P. 15p
BYWOOD
181 Ebbwens Road, Hemel Hempstead Herts. HP3 9RD
Tel. 0442 62757

4-STATION INTERCOM



£15-95
+ VAT £19-24

Solve your communication problems with this 4-Station Transistor Intercom system: 1 master and 3 Subs, in robust plastic cabinets for desk or wall mounting. Call/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 60ft and other accessories. P. & P. 65p.

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price **£29-98** per pair. P. & P. 65p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £11-95
+ VAT 96p.

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates on/off switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. Volume. Direct tape recording model at £13-50 + VAT £1-08. P. & P. 65p. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PF10)
189 KENSINGTON HIGH STREET, LONDON, W.8

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col. (1) Coil ohms	1	2	3	4
Col. (2)	52	4-8	2 c/o	70p*
Working	85	5-9	6 c/o	80p*
d.c. volts	230	8-12	6M	80p*
Col. 3	430	15-24	2 c/o HD	80p*
Contacts	700	12-24	2 c/o	80p*
Col. (4)	700	16-24	4 c/o	80p*
Price	1,250	18-36	2 c/o	60p*
	2,500	31-43	2 c/o HD	60p*
HD =	2,500	36-45	6M	60p*
Heavy duty	9,000	40-70	2 c/o	60p*
	15k	85-110	6M	60p*

*Incl. Base. All prices incl. P. & P.

OPEN TYPE RELAYS

6 VOLT D.C. 1 make contacts 35p. Post 15p.
9 VOLT D.C. RELAY TYPE RPT641 G8
3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 15p.
12 VOLT D.C. RELAY

3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 15p.
24 VOLT D.C. 3 c/o 75p. Post 15p.

ENCLOSED TYPE RELAYS

24 VOLT D.C. 3 c/o 75p. Post 15p. Base 15p extra.
24 VOLT A.C. Mfg. by ITT. 3 h.d. c/o contacts.
55p. Post 15p. Base 15p.

55 VOLT A.C. RELAY
3 h.d. c/o contacts. Price 55p. Post 15p. Base 15p.
100 VOLT A.C. 3 c/o sealed type. 75p. Post 15p.
Base 15p.

240 VOLT RELAY

3 h.d. c/o contacts. Price 75p. Post 15p. Octal
plug in base. Post 15p.

230/240 VOLT A.C. RELAY. Mfg. by Arrow 2 h.d.
15 amp c/o contacts. Amp connectors. Price £1.
Post 15p.

220/240 VOLT A.C. RELAY

3 c/o 5 amp contacts. Sealed. Mfg. ISKRA.
£1. Post 15p. Base 15p extra.

CLARE-ELLIPTICAL TYPE RPT641 G8
Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o.
70p post paid.

110V. 2 c/o. 20 amp contacts. £1.25. Post 10p.
Many others from stock—phone for details.

C/O MICRO SWITCH

VERY SPECIAL OFFER. Mfg. by
C.E.M. 3 amp 250 volt. 10 amp 25
volt. 50 for £3. Post 25p. 100 for £5.
Post 50p. 1,000 for £45. Post paid.
Bulk purchase means LOW! LOW! prices.

SUB-MINIATURE REED

RELAY 3-9V d.c. 250 ohm Coil
Single make, size 1 1/2" x 1/2" x 1/2"
Outstanding Value only
£1 for six, £1-50 for ten. Post 15p. (Min. order
six.)

LATCHING RELAY

Twin latching relay. "flip-flop" 2 c/o
each relay. Mains contacts. 115V
A.C. or 50V D.C. operation. 240V
A.C. with 2.5K resistor. 85p. Post 15p.

TRIAC

Raytheon Tag symmetrical Triac. Type TAG.
250/500V, 10 amp, 500 p.i.v. Glass passivated plastic
triac. Swiss precision product for long term
reliability £1-00. Post 10p. (Inclusive of Data and
application sheet.) Suitable Diac 18p.

230/250 VOLT A.C. SOLENOID

Approximately 1 1/2 inch pull. Size of feet 1 1/2" x 1 1/2"
Price £1-00. Post 15p.

HEAVY DUTY TYPE. APPROX. 14 lb. pull. £2-50.
Post 30p.

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25lb
pull 1 inch travel. Two approx. 1lb pull 1/2 inch
travel. 6 approx. 4oz. pull 1/4 inch travel. One
24 volt d.c., 1 heavy duty single make relay. Price
£2-50. Post 75p. ABSOLUTE BARGAIN.

COIN MECHANISM (Ex London Transport)

Unit containing, selector mechanism for 1p, 2p and
5p coins. Micro switches, relays, solenoid operated
hooper. 24 volt D.C. Precision built to high stand-
ard. Incredible VALUE only £2-50. Post 70p.
VAT 25%.

CENTRIFUGAL BLOWER

Mfg. by Smiths Industries. 230/240V
a.c. Miniature Model. Series SE/200.
Size 95mm x 82mm x 82mm.
Aperture 38mm x 31mm. 12
c.f.m.. £2-75. Post 25p.

Mfg. by Airflow Developments Ltd.
Precision made, continuously rated, smooth running.
230/240V a.c. motor, 80 c.f.m. As illustrated but
with round aperture. £6-50. Post 50p.

Mfg. by Woods.
Extremely powerful. 220/250V a.c. 0-3A 2,700 r.p.m.
continuously rated. Capacitor start. Cast construction.
Aperture 66mm x 50mm, O/A 200mm. £12.
Post £1.

All Mail Orders—Callers—Ample Parking
Dept. PE10, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT

VARIABLE 0-260V All Types

SHROUDED TYPE

200 watt (1 amp) £10-00
0.5 KVA (2 1/2 amp) (MAX) £11-50
1 KVA (5 amp) (MAX) £15-00
2 KVA (10 amp) (MAX) £27-50
3 KVA (15 amp) (MAX) £30-00
4 KVA (20 amp) (MAX) £60-00
37.5 amp (MAX) £102-50



CARRIAGE AND PACKING EXTRA

OPEN TYPE 1 amp (panel mount) £10-00

L.T. TRANSFORMERS

0, 6, 12 Volt at 10 amp. £5-60. Post 70p.
0, 10, 17, 18 Volt at 10 amp. £7-90. Post 70p.
0, 4, 6, 24, 32 Volt at 12 amp. £9-90. Post 70p.
0, 6, 12 Volt at 20 amp. £9. Post 70p.
0, 12, 24 Volt at 10 amp. £9-20. Post 70p.
0, 6, 12, 17, 18, 20 Volt at 20 amp. £10-40. Post 70p.

Other types to order at short notice—Phone your
enquiries.

'STC' 6" RED ALARM BELL

24/48 volt DC. Brand New.

Price £4. Post 50p. VAT 25%.



'GENTS' 6" ALARM BELL

200/250V AC/DC. Brand New. Price £5. Post 75p.

VAT 25%.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon
white light flash tube. Solid state timing and
triggering circuit. 230/250V a.c. operation.

HY-LYGHST STROBE MK III

For use in large rooms, halls and utilises a silica
tube, printed circuit. Speed adjustable 0-20 f.p.s.
Light output greater than many (so called 4
Joule) strobes £14. Post 50p.

RANGE OF THREE OTHER STROBE
KITS FROM STOCK. FROM £6-30 to £21.
S.A.E. (Footscap) for details.

BIG BLACK LIGHT

400 Watt. Mercury vapour ultra violet lamp.
Powerful source of u.v. P.F. ballast is essential.
Price of matched ballast and bulb £21.
Post £1. Spare bulb £8. Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES

4ft 40 watt, £5-50 (callers only).
2ft 20 watt, £4-25. Post 40p. (For use in
standard bi-pin. MINI, 12in 8 watt, £1-60.
Post 25p. 9in 6 watt, £1-30. Post 25p.
Complete ballast unit and holders for 9in and
12in tube, £1-70. Post 25p. (9in and 12in
measures approx.)

SQUAD LIGHT

A new conception in
light control. Four
channels each capable
of handling 750 watts
of spot lights, flood lights or dozens of small
mains lamps. Seven programs all speed
controlled plus flash modulation, effectively
giving 14 different displays. Makes sound-to-
light obsolete. Completely electrically and
mechanically noise free. Can be used on same
circuit as radio mikes or sensitive amplifiers.
A whole new range of lighting effects possible
with astounding results. Already in use in
London's foremost theatres, night clubs and
discos. Conforms to all R.F.I. tests, including
Common Market regulations. Supplied in
tough, well designed case with embossed
front panel. Price only £60. Post 60p. S.A.E.
(Footscap) for further details.



POWER RHEOSTATS !!!

Superior Quality Precision Made

NEW POWER RHEOSTATS

New ceramic construction, vitreous
enamel embedded winding, heavy
duty brush assembly, continuously
rated

25 WATT 1/25/50/100/150/250/500/1k/1.5k/2.5k
ohm. £1-70. Post 15p.

50 WATT 1/15/10/25/50/100/250/500/1k ohm
£2-10. Post 20p.

100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/
3.5k/5k ohm £3-30. Post 25p.

Black Silver, Skirted knob calibrated in Nos. 1-9
1 1/2 in. dia. brass bush. Ideal for above 22p each.

VAT

VAT AT 8% MUST BE ADDED TO
ALL ORDERS FOR THE TOTAL VALUE
OF GOODS INCLUDING POSTAGE
UNLESS OTHERWISE STATED.

**SERVICE
TRADING CO.**

METERS NEW

90mm diameter

Type 65C5, 2A D.C. M/C; 5A D.C. M/C
10A D.C. M/C; 20A D.C. M/C; 50A D.C. M/C.
Type 62T2, 1A A.C. M/I; 20A A.C. M/I; 300V A.C.
M/I; ALL ABOVE £2-50. Post 20p.
Type 65L5, 300V A.C. R/M/C; £7-75. Post 20p.



REVERSIBLE MOTOR

General Electric, 230V a.c. 1,600
r.p.m. 0.25A. Complete with anti-
vibration mounting bracket and
capacitor. O/A size 110mm x 95mm.
Spindle 3/8 in. dia. 20mm long. Ex.
equipment tested. £3. Post 50p.



230/240 VOLT A.C. MINIATURE MOTOR.

20 R.P.M. Price £1. Post 15p.

BODINE TYPE N.C.I.

GEARED MOTOR

(Type J) 71 r.p.m. torque 10 lb. in.
Reversible 1/70th h.p. cycle 0-38
amp. (Type 2) 28 r.p.m. torque 20
lb. in. Reversible 1/80th h.p. 50 cycle 0-28 amp.
The above two precision made U.S.A. motors are
offered in 'as new' condition. Input voltage of motor
115V A.C. Supplied complete with transformer for
230/240V A.C. input.
Price, either type £6-25. Post 65p or less trans-
former £3-75. Post 50p.



'CARTER' 230 VOLT A.C.

GEARED MOTOR

230/240V A.C., smooth, powerful,
continuously rated. Two types: 32
r.p.m. or 10 r.p.m. Either type
£4-50. Post 50p.



ROTARY VACUUM AIR PUMP AND

COMPRESSOR

Carbon vane, oilless, 100/115V a.c.,
1 1/2 h.p. motor, 50/60 cycle, 2875/3450
r.p.m., 20 in vacuum, comp. 1-25
c.f.m., 10 p.s.i. (approx. figures).
New unused surplus stock. Supplied
with electrical connection data. FRACTION OF
MAKERS' PRICE £12. Post 50p. Suitable 110/240V,
150 watt auto transformer £3-50. Post 50p. (Both
items together Post 75p.)



PROGRAMME TIMERS


230/240V a.c. 15 r.p.m. Motors.
Each cam operates a c/o micro
switch. Ideal for lighting effects,
animated displays, etc. Ex equipment
tested.

4 cam model. 15 r.p.m. £2-00 post 35p.
4 cam model. 15 r.p.m. £2-50 post 35p.
8 cam model. 20 r.p.m. £4-75 post 40p.
8 cam model, each cam fully adjustable. 6 r.p.m.
M.f.g. by Magnetic Devices. £7-50. Post 35p.



A.C. MAINS TIMER UNIT

Based on an electric clock, with
25 amp. single pole switch,
which can be preset for any
period up to 12 hrs. ahead
to switch on for any length
of time, from 10 mins. to
6 hrs. then switch off. An
additional 60 min. audible
timer is also incorporated. Ideal
for Tape Recorders, Lights,
Electric Blankets, etc. Attractive satin copper finish.
Size 135mm x 130mm x 60mm. Price £2. Post
40p. (Total incl. VAT and Post £2-59).

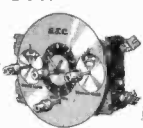

TIME SWITCH

'Horstmann' Type V Mk II Time
switch. 200/250V a.c. Two on/two
off every 24 hours, at any manually pre-
set time. 30 amp contacts. 36 hour
spring reserve in case of power failure.
Day omitting device. Fitted in heavy
high impact case, with glass observa-
tion window. Built to highest Electricity
Board Spec. individually tested. Price
£7-75. Post 50p. (Total inc. VAT £8-91)



600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers.
Will control up to 600W of lighting
except fluorescent at mains voltage.
Complete with simple instructions.
£2-75. Post 25p.

1,000 watt model, £4. Post 25p.
2,000 watt model, £8. Post 30p.

INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal
construction, suitable for bench or
field work, constant speed clutch.
Size L.8in, W.4in, H.6in, weight 6lb.
500V/500 megohms, £30. Post 80p.
1,000V, 1,000 M.Ω, £36. Post 80p.



Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

BARCLAY ELECTRONICS

NOW OFFER YOU A FULL RANGE OF ORDINARY AND SCIENTIFIC CALCULATORS



- FULLY GUARANTEED
- AT THE BEST POSSIBLE PRICES!

4 FUNCTION £
 CBM 774D 7 digit, slim pocket* 5-80
 SINCLAIR CAMBRIDGE 8 digit, slim pocket, constant 10-70
 SINCLAIR OXFORD 100 8 digit, constant* 10-70

4 FUNCTION % CONSTANT
 DECIMO VATMAN SP7 8 digit, slim pocket* 11-80
 DECIMO VATMAN 8 digit, green display 12-40
 CBM 385R 8 digit, rechargeable 10-40
 CBM 986R 8 digit, green display, rechargeable 14-80

4 FUNCTION, STORE MEMORY, %
 CBM 776MD 7 digit, pocket slim* 6-80
 CBM GL976MR 7 digit, green display, rechargeable 13-25

4 FUNCTION, FULL MEMORY, CONSTANT
 SINCLAIR CAMBRIDGE MEMORY 8 digit, pocket slim 14-55
 SINCLAIR OXFORD 200 8 digit, %* 16-25
 CBM 887D 8 digit, factor exchange, %* 11-50
 CBM2GL987R 8 digit, % factor exchange, green display, rechargeable 17-60
 DECIMO VATMAN MEMORY 8 digit, green display, % factor exchange 20-50

SEMI-SCIENTIFIC FULL MEMORY
 DECIMO SUPER VATMAN 8 digit, green display, \sqrt{x} , x^2 , factor exchange, % 21-50
 CBM 989 8 digit, green display \sqrt{x} , x^2 , factor exchange, % reciprocals, rechargeable 23-50

SCIENTIFICS, ALGEBRAIC LOGIC, DUAL FUNCTION KEYS
 SINCLAIR SCIENTIFIC 5 digit, 2 exponents, trig, log, slim pocket 16-40
 SINCLAIR OXFORD 300 5 digit, 2 exponents, trig, log, π , \sqrt{x} , reciprocals, x^2 , memory* 26-50
 DECIMO 2001 8 digit, trig, log, π , \sqrt{x} reciprocals, memory, y^x , e^x , x^2 , $x-y$, pocket slim* 31-00
 DECIMO VATMAN SCIENTIFIC as 2001, but large green display 31-00
 DECIMO SCIENTIFIC SUPERMAN 8 digit, 2 exponents, log, 1 memory, 1 memory store, y^x , e^x , reciprocals, \sqrt{x} , x^2 , pocket slim* 29-50
 CBM SR120R 8 digit, 2 exponents, trig, log, π , \sqrt{x} , reciprocals, e^x , x^2 , $x-y$, (parenthesis), exponent shift, mean and standard deviation, polar rectangular, co-ordinates, rechargeable, 2 memory stores 34-50

ROCKWELL 31R }
 ROCKWELL 51R } PLEASE SEND S.A.E. FOR NEW LOW PRICES
 ROCKWELL 61R }
 ROCKWELL 63R }

SCIENTIFICS ALGEBRAIC LOGIC, SINGLE FUNCTION KEYS
 DECIMO 2001E 10 digit, 2 exponents, trig, log, π , \sqrt{x} , reciprocals, memory, y^x , x^2 , $x-y$, memory exchange, hyperbolics, pocket slim* 40-60
 CBM SR148R same as SR120R but in addition has 10 digits, 2 exponents, 2 store memory, and single function keys 44-50

TEXAS INSTRUMENTS
 SR11 }
 SR16 } PLEASE SEND S.A.E. FOR NEW LOW PRICES
 SR50 }
 SR51 }

SCIENTIFICS, REVERSE POLISH LOGIC—SINGLE FUNCTION KEYS
 NOVUS (BY NATIONAL SEMI-CONDUCTORS)
 6010 8 digit, trig, log, x^2 , \sqrt{x} , π , $x-y$, reciprocals, memory 29-95
 4510 37-50
 4515 102 step programmable 79-95
 6020 49-95
 6030 49-95

HEWLETT PACKARD
 HP21 }
 HP35 } PLEASE SEND S.A.E. FOR NEW LOW PRICES
 HP45 }
 HP55 }
 HP65 }

*These models employ ordinary batteries but mains adaptors are available, as an optional extra.
 DECIMO ADAPTOR £3-00
 SINCLAIR OXFORD ADAPTOR £2-95
 CBM ADAPTOR £2-70
 Please add the correct amount to total if adaptor is required.
 NOTE—All rechargeable machines supplied complete with nicad batteries and chargers for the stated price.
 All prices include V.A.T. at 8% and although correct at time of going to press, may be subject to alteration without notice.

PHONE CALLS AND PERSONAL CALLERS WELCOME
 MONDAY-THURSDAY BETWEEN 2 and 5 p.m.

To BARCLAY ELECTRONICS, 1115 Finchley Rd., London, N.W.11
 Please send me of model(s)
 with/without optional mains adaptor. I enclose cheque/money order
 total value £..... which includes 50p insured post and
 packing charge.

NAME

ADDRESS

12in LONG PERSISTENCE CRT. Full spec. Price £6-50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2Hz to 8MHz. Hook up to a 9 volt battery and connect to your scope and have two traces for ONLY £6-25, P. & P. 25p. (Not cased, not calibrated.)

WIDE RANGE WOBBULATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V a.c. and use within minutes of receiving. All this for ONLY £6-75, P. & P. 35p. (Not cased, not calibrated.)

20Hz to 200kHz WB, SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £8-85 each. SINE WAVE only £6-85 each. P. & P. 35p. (Not cased, not calibrated.)

GRATICULES 12cm x 14cm high quality plastic 15p each, P. & P. 8p.

Large quantity of good quality components—NO PASSING TRADE—so we offer 3lb of **ELECTRONIC GOODIES** for £1-70. Post paid.

METER PACK—3 different meters for £2. P. & P. 55p.

MIN TRANSFORMER. 240V input, 3V 1A output. Brand new 65p each P. & P. 20p.

P.C.B. PACKS. S & D. Quantity 2 sq. ft.—no tiny pieces. 50p, P. & P. 37p.

CAPACITOR PACK—50 brand new components. only 50p, P. & P. 37p.

TRIMMER PACK. 2 twin 50/200pF ceramic, 2 twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 15p.

PHOTOCELL equ. OCP71, 13p each. MULLARD OCP70, 10p each.

DELIVERED TO YOUR DOOR, 1cwt of Electronic Scrap chassis, boards, etc. No rubbish. FOR ONLY £4.

MODERN TELEPHONES. Type 706: two-tone grey or black, £3-75 each. Type 7006: two-tone grey or green, £3-75 each. Style similar to Type 746: grey, or black, £3 each. As above but discoloured, grey only, £2 each, P. & P. all types 45p each.

CRYSTALS. 4-43MHz. Brand new, £1-25 each, P. & P. 15p.

RESETTABLE COUNTERS—4 digit by Sodeco/Stonbridge, 1,000 ohm coil, £2 each, P. & P. 35p.

HANDSETS. Complete with 2 inserts and lead, 75p each, P. & P. 37p.

DIALS. ONLY 75p each, P. & P. 25p.

HIGH VALUE—PRINTED BOARD PACK. Hundreds of components, transistors, etc.—No 2 boards the same. No short leaded transistor computer boards. £1-75, post paid.

BEEHIVE TRIMMER 3/30 pF. Brand new. Qty 1-9 13p each, P. & P. 15p; 10-99 10p each, P. & P. 25p; 100-999 7p each, P. & P. free.

HE CRYSTAL DRIVE UNIT. 19in rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) £5 each, Carr. £2.

1,000pF FEED THRU CAPACITORS. Only sold in packs of 10, 30p, P. & P. 15p.

SOME OSCILLOSCOPES ALWAYS AVAILABLE. S.A.E. stating specification and price range.

PLEASE ADD V.A.T. AT 8%
 OPEN 9 a.m. to 6 p.m. ANY DAY

CHILTMead LTD
 7/9 ARTHUR ROAD, READING, BERKS.
 (rear Tech. College) Tel. Reading 582605.

Use Access here

ELECTROVALUE

The best of all!

CATALOGUE 7 ISSUE 3

With 25p refund voucher

Up-dated Price and Product Information

112 pages plus cover. As comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 25p for spending on orders list value £5 or more SEND NOW FOR YOUR COPY BY RETURN **30p** post it's an investment in practical money-saving and reliability!

PRICES—Electrovalue policy is to review prices every three months rather than try to keep up with day by day changes as they occur. We have, in fact, held our prices for two such periods (Jan. 1st-July 1st) and our next price review is due October 1st.

DISCOUNTS apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14-99; 10% on orders list value £15 or more.

FREE POST AND PACKING in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under there is an additional handling charge of 10p.

QUALITY GUARANTEE. All goods are sold on the understanding that they conform to maker's specification. No rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Section 2/5, 28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603, Telex 264475. Shop hours: 9-5.30 daily, 9-1 pm Sats.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours: Daily 9-5.30 pm; 9-1 pm Sats.

BI-PRE-PAK

The people for component bargains



Makers of
Stirling Sound
audio equipment

ORIGINATORS OF PRE-PACKED COMPONENTS IN BRITAIN—AND STILL LEADING!

AUDIO MODULES — today's most challenging values!

POWER AMPS

SS103

Compact I.C. amp 3 watts R.M.S. Single channel (mono). On P.C.B. size 3½in x 2in. Needs 10-20V supply. **£1.75**



SS103-3

Stereo version of above (two I.C.s) **£3.25**



NEW! SS105 Mk. 2

A compact all-purpose power amp. Can be run from 12V car battery. Size 3½in x 2in. Useful 5W output (mono) into 3Ω using 12V. Excellent value. **£2.25**



SS110 Mk. 2

Similar in size to SS105 but will give 10W output into 4Ω using 24V (mono). Two in stereo give first-class results, suitable for many domestic applications. **£2.75**



SS140

Beautifully designed. Will give up to 40W R.M.S. into 4Ω. Excellent S.N.R. and transient response. Fine for P.A. disco use, etc. Operates from 45V d.c. Two in bridge formation will give 80W R.M.S. into 8Ω. **£3.60***

PRE-AMP/CONTROL MODULES

SS100

Active tone control unit to provide bass and treble facilities (stereo). **£1.60**

SS101

Pre-amp for stereo ceramic cartridges, radio and tape. **£1.60**

SS102

Pre-amp for low-output stereo magnetic cartridges, radio and tape. **£2.25**

BUILD A STEREO F.M. TUNER with these modules

SS201

Front End assembly. Ganged tuning with well engineered slow-motion geared drive in robust housing. A.F.C. facility. Requires 6-16V. Excellent sensitivity. 88-108MHz. **£6.25**

SS202


I.F. Stage (with I.C.). Designed to use with SS201 uses 1 C. Carefully checked before despatch. **£5.25**

SS203

Stereo Decoder. Designed essentially for use with SS201 and SS202, this excellent decoder can also make a stereo tuner of almost any single channel FM tuner. Supplied ready aligned. A L.E.D. can easily be fitted. **£5.62**

SAVE £5 ON THE S/S TUNER

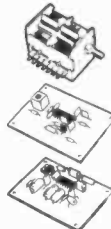By buying Units SS201, SS202 and SS203 together, the price is £12.12—a genuine saving of £5 on this very efficient tuner. **£12.12**



3 SPECIAL OFFERS

- LM 380 AUDIO I.C. (Marked SL 60745). Brand new and to spec. 3 watts R.M.S. out. With data. **£1.00***
- 2XSN 7490. Brand new I.C. to spec. decode counters. **£1.00***
- 3XSN 7400 Quad 2 input Nan gate I.C.s. **50p**

NEW RANGE TRANSISTOR AND COMPONENT PACKS

TP SELECTION

- TP5 20 Transistors, PNP Germanium. Red Spot A.F.
- TP6 20 Transistors, PNP Germanium. White spot RF.
- TP7 1 2N174 150W 80Vce Power Transistor, with mounting assembly.
- TP19 100 diodes, mixed Germanium. Gold-bonded, etc. Marked/Unmarked.
- TP23 Twenty NPN Silicon uncodet TO5. Similar to BFY50/2, 2N696, 2N1613, etc. Complementary to TP24.
- TP24 Twenty PNP Silicon, uncodet TO5. Similar to BFY64, 2N2904/5.
- TP29 8 power diodes 400V. 1 2SA Silicon FST 3/4.

UT SELECTION

- UT1 50 PNP's Germanium, AF and RF.
- UT2 150 Germanium diodes, min. glass.
- UT4 100 Silicon diodes, min. glass, similar to IN914, IN916.
- UT5 40 250mW Zener diodes OAZ24 range; average 50% good.
- UT7 30 Silicon rectifiers 750mA, mixed voltages. Top Hats, etc.
- UT9 40 NPN Silicon planers. Similar to 2N3707-11 range. Low noise amps.
- UT12 25 2N3702/3 Transistors. PNP Silicon. Plastic to 92.

CP SELECTION

- CP1 Mixed bag of capacitors—Electrolytic, Paper, Silver Mica (Approx. 150—sold by weight).
- CP2 200 (approx.) Resistors, various types, values, watts. (Sold by weight.)
- CP3 40 Wire-wound resistors, mixed.
- CP4 12 pots—pre-set, w/wound, carbon, dual, with/without switches—all mixed.
- CP7 Heat sinks, assorted. To fit SO-2 (OC72) TO-1 (AC128), etc.

ALL ABOVE PACKS—50p EACH. TP Tested and Guaranteed; UT Untested, unmarked; CP Components.

CAPACITOR DISCHARGE IGNITION KIT

Simple to assemble and fit. Improves car performance, saves on fuel. P. & P. 30p. **£7.50***

BI-PRE-PAK X-HATCH GENERATOR MK. 2

Four-pattern selector switch 3in x 5½in x 3in
Ready-built and tested in kit form **£9.93***
Please add 30p for postage and packing. **£7.93***

is invaluable to industrial and home user alike. Improved circuitry assures reliability and still better accuracy. Very compact, self-contained. Robustly built. Widely used by TV rental and other engineers. With reinforced fibreglass case. Instructions, but less batteries. (Three U2 type required.)

TV SIGNAL STRENGTH METER*

Complete kit as described in 'Television' £19.50 plus 40p for P. & P. plus VAT at current rate.

SS300 POWER SUPPLY STABILISER

Add this to your unbalanced supply to obtain a steady working voltage from 16 to 60V for your audio system, workbench, etc. Money saving and very reliable **£3.25***

PLASTIC POWER TRANSISTORS

40 WATT SILICON*		Type	Polarity	Gain	VCE	Price
40N1	NPN	15	15	20p		
40N2	NPN	40	40	30p		
40P1	PNP	15	15	20p		
40P2	PNP	40	40	30p		

90 WATT SILICON*		Type	Polarity	Gain	VCE	Price
90N1	NPN	15	15	25p		
90N2	NPN	40	40	35p		
90P1	PNP	15	15	25p		
90P2	PNP	40	40	35p		

If you prefer not to cut coupon out, please mention ETIP2 when writing.

To BI-PRE-PAK, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose inc. VAT

NAME

ADDRESS

PE9

SUNDRY

PI PAK—Approx. 170 short-lead semi-conductors and components. PNP, NPN, diodes, rectifiers, etc. on PCBs. At least 30% factory marked. Some data supplied, 50p.
UHF 625 line tuner, rotary. £2.50.
Rev Counter (for cars) (8%). £1.00.*
Books by Bernard's Publications Newnes-Butterworth's, etc.

THE FREE CATALOGUE

New edition better than ever. It's your's for free and well worth getting—only please send large S.A.E. with 10p stamp if we have to post it to you.

TERMS OF BUSINESS:

VAT at 25% must be added to total value of order, except for items marked * or (8%), when VAT is to be added at 8%. No VAT on overseas orders. POST & PACKING Add 22p for UK orders unless shown otherwise. Minimum mail order acceptable—£1. Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES Subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.

BI-PRE-PAK LTD

Co. Reg. No. B200119

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 90F.

TELEPHONE: SOUTHEND (0702) 46344.

FOUNDED IN 1959

RTVC

FOR SPEAKERS AT FANTASTIC REDUCTIONS

NEW!



LE-4 SPEAKERS

Superb performance and beautifully finished in selected teak veneers. A professional standard four-way speaker system giving 25 watts RMS power handling. Bass unit is 14" x 9" with 8" x 5" unit for mid-range and twin 3" high frequency units to give monitor type quality and performance.

Specification — Size 33" x 14" x 16" approx. Impedance 8 ohms. Power handling 25W RMS. (Peak 50 watts.) Frequency range 35 Hz—20 KHz.

Our Price £34.00 each

(normally £66.00) + £5.80 p & p.
Scotland and the Orkneys
P & P Surcharge £3.50

THE 'COMPACT'

EASY BUILD SPEAKER KIT

A compact bookshelf speaker system giving a high electro acoustic efficiency for the low powered amplifier.

The professional finish can be obtained with the minimum of tools, the infinite baffle type enclosures come ready mitred and professionally finished, simply apply glue, fold up around baffle board, and fix together with masking tape till glue dries.

The cabinet measures 12" x 9" x 5" deep approx finished in simulated teak, incorporating a quality 7" x 4" elliptical speaker, power handling 4 watts, flux density 30,000 maxwells, impedance 8-15 ohms nominal, voice coil dia 3/4" magnet size 2 3/8" approx.



£6.00
pair inclusive P & P £1.70

EASY TO BUILD SPEAKER KITS


These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMi's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3 1/2" tweeter and matching crossover.

Easily put together with just a few basic tools.

Specification (each speaker): Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20—20,000 Hz. Size 20" x 11" x 9 1/2" approx. Comparable built units (EMi LE3) sold elsewhere for over £45 pair.

£22.00 pair complete + £5.20 p & p.

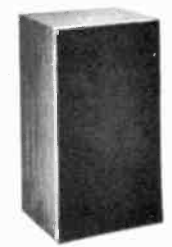Complete with crossover Components and circuit diagram



EMi 350 KIT

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

£6.50 + £1.20 p & p.

Complete with crossover Components and circuit diagram

RTVC*

NEW!

VISCOUNT IV STEREO SYSTEM

System 1a. £65.00

The new 20+20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls — volume, bass, treble, balance, mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear — for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion @ 10 watts better than 0.2%. Six switched inputs: 1. Magnetic P.U. — 3 millivolts @ 47 K ohms (R.I.A.A.); 2. Crystal/ceramic P.U. — 50 millivolts @ 50 K ohms (R.I.A.A.); 3. 4, 6. Tape Tuner/Aux. — 140 millivolts @ 50 K ohms (flat frequency response); 5. Microphone — 3 millivolts @ 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. Frequency response: 25 Hz to 25 KHz @ full rated output. Signal to noise ratio: better than -50 dB on all inputs. Tone control range: Bass ± 15 dB @ 50 Hz; Treble ± 12 dB @ 10 KHz. Power requirements: 200-250V A.C. mains @ 60 watts. Approx. size: 15 1/2" x 3" x 10".

MP60 type deck with magnetic cartridge, de luxe plinth and cover.
Two Duo Type IIa matched speakers — enclosure size approx. 19 1/2" x 10 1/2" x 7 1/2" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling. 30 watts peak.

Complete System with these speakers **£65.00** — £6.50 p & p.

System 2. £81.00

Viscount IV amplifier (As System 1a)
MP60 type deck (As System 1a)

Two Duo Type III matched speakers — Enclosure size approx. 27" x 13" x 11 1/2". Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS. 8 ohms frequency range — 20 Hz to 18,000 Hz.

Complete System with these speakers **£81.00** + £7.60 p & p.

PRICES: SYSTEM 1a
Viscount IV R103 amplifier £25.00 + £1.90 p & p.
2 Duo Type IIa speakers £30.00 + £6.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover £20.00 + £3.30 p & p.
Total if purchased separately: £75.00
Available complete for only **£65.00** + £6.50 p & p.

PRICES: SYSTEM 2
Viscount IV R103 amplifier £25.00 + £1.90 p & p.
2 Duo Type III speakers £48.00 + £7.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover £20.00 + £3.30 p & p.
Total if purchased separately: £91.00
Available complete for only **£81.00** + £7.60 p & p.



20x20 SYSTEM

Scotland and the Orkneys P & P Surcharge
System 1a £1.75 System 2 £3.50

PUSH BUTTON CAR RADIO KIT— THE TOURIST TT*



NO SOLDERING REQUIRED

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

TECHNICAL SPECIFICATION: (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide 2" high and 4 3/4" deep approx. **£9.50** + £1.05 p & p. Speaker including baffle and fixing strip **£2.00** + 45p p & p. Car Aerial Recommended — fully retractable **£1.60** + 40p p & p.

The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £8.20** + £1.05 p & p.

*STEREO 21 QUALITY SOUND FOR LESS THAN £24.00



Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white PVC and the acrylic top presents an unusually interesting variation on the modern deck plinth. Includes — BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets. Amplifier module, Ready built with control panel, speaker leads and full, easy to follow assembly instructions.


Specifications — For the technically minded: Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8–15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc., and outputs for taping discs.

Overall Dimensions. Speakers approx 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 8".

Complete only £23.20 + £3.00 p & p.

Extras if required. Optional Diamond Stylus **£1.60**. Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.80**.

*DISCO AMPLIFIER

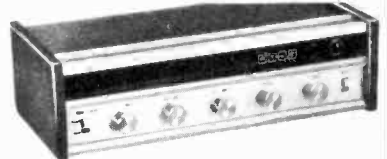

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms).

Inputs *4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES — Input — 1). Crystal mic, guitar or moving coil mic. 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12 1/2" x 6" x 3 1/2". **£20.00** + £1.35 p & p.


*8 TRACK HOME CARTRIDGE PLAYER



Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system, Unisound module and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV.

Yours for only **£16.20** + £1.70 p & p.


BUILD YOUR OWN STEREO AMPLIFIER*

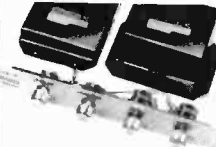

For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7" x 4") **£10** + £1.75 p & p. **£8.95** + £1.05 p & p. Also available with the 'Compact' (see opposite page) easy build speaker kit **£13.50** + £2 p & p.

PORTABLE DISCO CONSOLE*

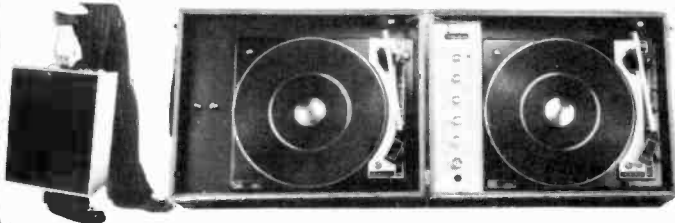

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

TECHNICAL SPECIFICATION:

Pre-amp — Output — 200mV. Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation. **Turntables capacity** — 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than — 35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaumont kalee meter). **Finish** — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size —

Unit Closed — 17 1/2" x 13 1/2" x 8 1/2" (app.)
Unit Open — 35 1/2" x 13 1/2" x 4 1/2" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.
The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only

£49.00 + £6.50 p & p.



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.D. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

Leaflets available for all items listed thus* Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Aug 1975 and subject to change without notice.


All prices include VAT at current rates




21D HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs
ACTON: 9.30a.m.—5p.m. Closed all day Wed.

Kit inspection

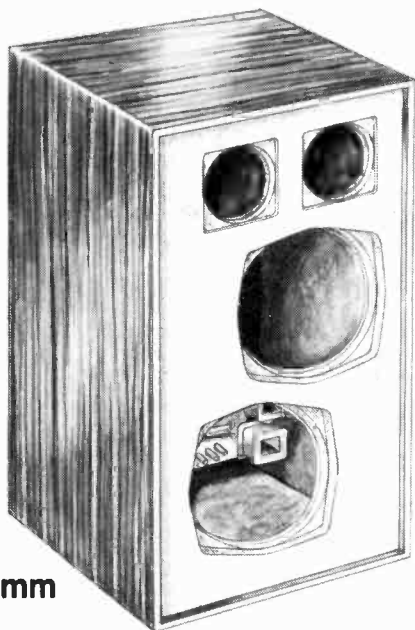

Dimensions
410 × 260 × 190mm

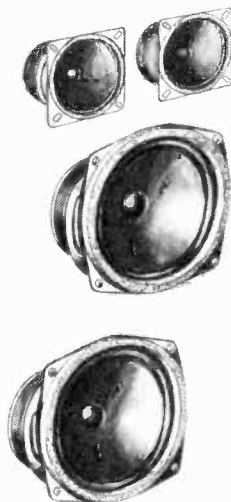

STUDIO ELECTRONICS EASIKIT

We invite your closest inspection of our loudspeaker kits. Here at last is a kit which doesn't require you to be either an electronic genius or a master carpenter. The assembly is simplicity itself, taking barely 15 minutes and requiring only a soldering iron, screwdriver and our easy to follow instructions, the cabinet being already built. 4 drive units provide excellent reproduction free from colouration, cabinet resonance and listening fatigue. In teak or white. Based on an original design as also selected for the outstanding Practical Electronics Rondo Quadraphonic system.

SPECIFICATIONS

Impedance 4-8 ohms.
Power Handling 20W r.m.s.
Crossover Frequencies 250Hz, 5kHz.
Frequency response 30Hz to 20kHz ± 5dB.
4 Drive units, Bass (13cm dia.), Bass/Mid-range (13cm dia.), 2 Tweeters (6.5cm dia.).

£42.50 per pair. Post free. Plus VAT.

*ready assembled £49.50 per pair. Post free.
Plus VAT.*

Trade enquiries welcomed.

Demonstrations by telephone appointment.

SOUND SPHERES


The little speaker with the big sound! Only 4½in diameter and weighing 700 grams, it is capable of handling 10W. A very versatile little performer, ideally suited to rear channel systems, in the car, extension speakers, etc. The magnetic base enables them to be mounted virtually anywhere. Superbly finished in black, white or orange.



SPECIFICATIONS

Impedance 4-5 ohms.
Power Handling 10W.
Response 100Hz to 16kHz.

£19.95 per pair. Post free.
Plus VAT.

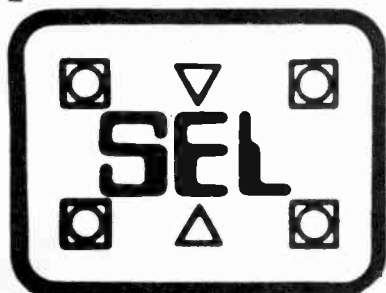

NAME PE10

ADDRESS

Please forward by return

..... I enclose cheque/PO/Cash


Barclaycard or Access welcomed.

Reg. No. in London 11 82 359


Studio Electronics Ltd

P.O. BOX 18, HARLOW, ESSEX CM18 6SH.

Tel. 416771

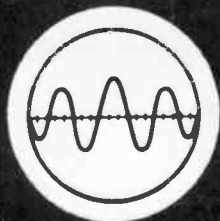


TUAC

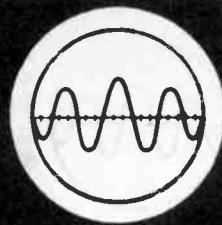

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137 9080

TUAC POWER MODULES offering more power and quality than ever before

● 125 watts RMS continuous sine wave output

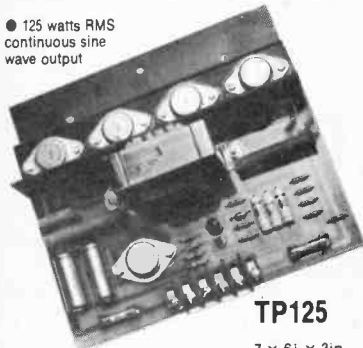


TP125

7 x 6½ x 3in

£19.50

● 4 R.C.A. 150 watt 15 amp output transistors

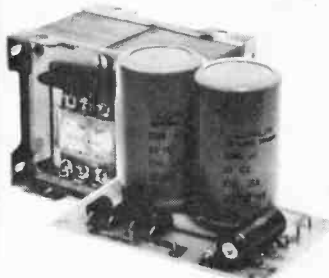Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:



PS 125 ± 45 volts for TP125

£12.25

PS 100 ± 43 volts for TL100

£11.25

PS 60 ± 38 volts for TL60


£10.00

PS 30 ± 25 volts for TL30

£5.90

PSU 2 for supplying disco mixer

£4.75

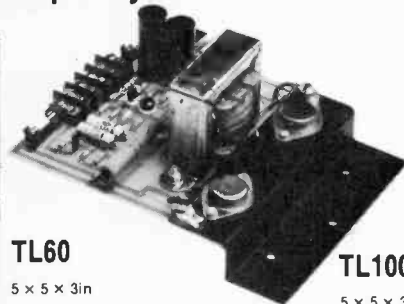

TL60

5 x 5 x 3in

● 60 watts RMS continuous sine wave output
● 2 R.C.A. 110 watt 15 amp transistors

£12.50

TL100

5 x 5 x 3in

● 100 watts R.M.S. continuous sine wave output
● 2 R.C.A. 150 watt 15 amp transistors

£15.00

- Rugged layer wound driver transformer
- Short—Open—and Thermal overload protection
- Only 6 connections

Specification on all power modules: All output power ratings ± 0.5dB; Output impedance 8-15 ohms; THD at full power 2% typically 1%; Input sensitivity 60mV into 10kΩ; Frequency response 20Hz-20kHz ± 2dB; Hum and noise better than -70dB.

TUAC DISCOTHEQUE MIXER WITH AUTO FADE



Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth; auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.

Specification: Deck Inputs—50mV into 1MΩ; Deck Tone Controls—treble +20 -10dB at 12kHz, Bass +22 -15dB at 40Hz; Mic Input—200 ohms upwards, 2mV into 10kΩ; Mic Tone Control—Total Variation Treble 15dB, Total Variation Bass 10dB; Tape Input—30mV into 47kΩ; Power Requirements—30-50 volts at 50mA.

£31.50
PANEL SIZE
18 x 4½in
DEPTH 3in

HOW TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD (PE10/3)
or quote Access/Barclay Card No.
and post to TUAC LTD (PE10-3)
163 Mitcham Road, London, SW17 9PG
We accept phone orders against
Access/Barclay Card Holders
Phone: 01-672 3137/9080


STOCKISTS—CALLERS ONLY

Arthur Sallis Ltd., 28 Gardner Street. Tel. Brighton 65806
Bristol Disco Centre, 86 Stokes Croft. Tel. Bristol 41666
Socodi, 9 The Friars. Tel. Canterbury 60948
Cookies, 132 West Street. Tel. Crewe 4739
Calbarrie Audio, 88 Wellington Street. Tel. Luton 411733
Al Music Centre, 88 Oxford Street. Tel. Manchester 236 0340
Damon Electronics, 99 Carrington Street. Tel. Nottingham 53880
Electra Centre, 58 Lancaster Road. Tel. Preston 58488
Mitchell Electronics, 64 Winchester Street. Tel. Salisbury 23689
Wec Lighting, 10 Commercial Road. Tel. Southampton 28102


ALL PRICES INCLUDE V.A.T. (8%) AND POSTAGE AND PACKING

ACCESS & BARCLAY CARDS ACCEPTED—JUST SEND OR PHONE US YOUR NUMBER

HP ENQUIRIES INVITED

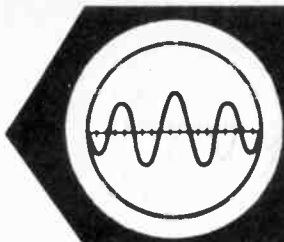


TUAC

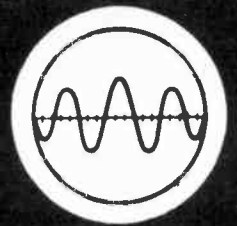

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137 9080

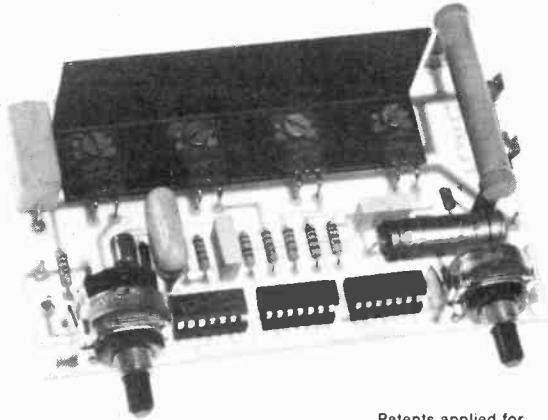NEW !!! 4 CHANNEL SOUND TO LIGHT SEQUENCER—4LSMI



- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from $\frac{1}{2}$ W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry optical isolation for amplifier protection
- Full wave control
- 13 easy connections

Patents applied for

£22.00


3 CHANNEL LIGHT MODULATOR

- R.C.A. 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 100W
- Full wave control
- 12 easy connections.


Single Channel Version 1500 Watts

£15.50

£7.25

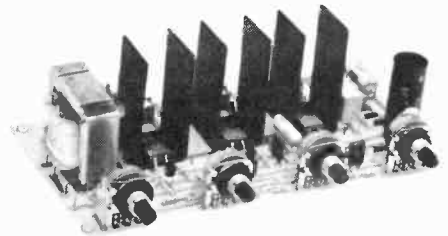

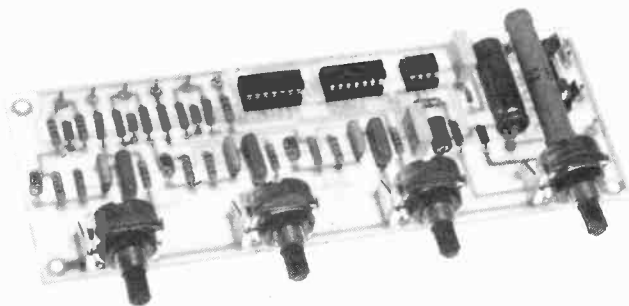ADD SEQUENCE AND DIMMING EFFECTS TO YOUR TUAC 3 CHANNEL LIGHT MODULATOR



SEQUENCE DIMMER MODULE—3SDMI

Speed Control 3 per min. to 10 per sec.
Full logic integrated circuitry
Dimmer control to each channel
9 easy connections

£9.50



DIMMER MODULE—LMDI


Dimmer control for each channel
7 easy connections

£4.25

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT OPEN 6 DAYS A WEEK 9.30am-6.00pm



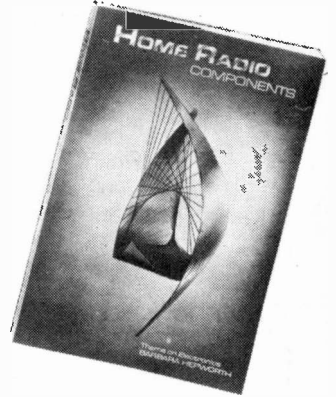We've been together now for nearly thirty years!



No—I'm not referring at the moment to My Old Dutch, but to the fact that for almost thirty years I've been getting my radio and electronic bits and pieces from Home Radio. *Hundreds* of orders I've sent them, and I've always been delighted with the courteous and efficient service I've received. What's more, on the many occasions when I've called at their Mitcham shop, I've found the same friendly, business-like atmosphere. On the *few* occasions when they've slipped up (they don't claim to be infallible) they have really gone out of their way to put things right and to ensure my satisfaction.

If you've been reading these adverts during the last few months you'll know that a young friend of mine has experienced the same satisfaction. Perhaps we two typify the thousands of electronic fanatics, young and old, who have found Home Radio Components a wonderful back-up service for a fascinating hobby.

If you are not yet with us why not join us right away? Your first step of course is to invest in the famous Home Radio Components catalogue. It's an eye opener!

From the moment you remove the wrapper and gaze on the beautiful colour picture of Barbara Hepworth's "Theme on Electronics" until you reach the Index at the back you'll find it as absorbing as a first class thriller. The 240 pages are packed with details of over 6,000 items, nearly 2,000 of them illustrated.

If you're a meany like me you'll probably use the same catalogue for several years (Home Radio keeps me up to date on prices by sending me new price lists *free*); but if you're keen to keep up with all the latest developments in electronic components then you'll get each edition as it's published. In any case, when you start ordering components you can recoup 70 pence of your 108p investment by using the 'save-money' vouchers supplied with the catalogue. You can't lose.

So why delay? Send the Coupon below *today* with a cheque or P.O. for 108 pence, and look forward to at least thirty years of happy co-operation with Home Radio Components!

75p plus 33p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 108p.

Please write your Name and Address in block capitals

NAME

ADDRESS



HOME RADIO (Components) LTD., Dept. PE
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd. No.
912968, London

The price of 108p applies only to customers in the U.K. and to BFPO Addresses.

HOME RADIO (Components) LTD., Dept. PE, 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422

MICRO MASTER MINDS

WHEN one hears lavish claims made in respect of some contemporary development in technology and predictions concerning its likely profound effect upon life in general in the future, one tends to be a little cautious and tries to avoid the temptation to get "carried away". This *may* or *may not* be a milestone in the making. Time alone will tell. Yet in the face of known facts, it is hard to resist the thought that a new chapter in electronic expansion is upon us, *right now*. Certainly it is evident that the total domination of machinery—in the widest sense of the word—by electronic control and supervisory systems has become much closer to reality with the arrival of the microprocessor. This device—virtually a minicomputer of great programming flexibility which may be contained within just four l.s.i. packages—appears to offer the key to the widespread and uninhibited use of powerful computing systems. It is a force to be reckoned with, and we endeavour to put readers in the picture with a special introductory article which commences this month.

U.S. semiconductor manufacturers are now producing, between them, a variety of different microprocessors. These devices have already been installed in aircraft; more recently they have been incorporated in advanced types of oscilloscopes, and now the search for additional areas for their profitable and useful employment is on. Other actual, or seriously proposed, applications range from automated industrial plants to sewing machines; from automobiles to washing machines; and from bowling alleys to vending machines.

Was it clever timing by the microprocessor makers or was it just chance that these devices made their first appearance during the onset of the present fuel and energy crisis? Certainly conditions at this time are very propitious for any device or system that will enable greater mileage to be obtained from a gallon of petrol—to say nothing of reducing the amount of pollution. There can be little doubt that microprocessors will be built into cars of the future.

Exciting, and full of promise all this may be—yet we have to end on a despondent note. What are the British semiconductor manufacturers doing about microprocessors? Very little it seems.

ENGINE ANALYSER

Until the day when we all drive computerised motor cars, we have to motor-on as best we can in face of ever-increasing fuel costs and garage servicing charges. Yet some assistance is here at hand—this month—for all our motorist readers. Through prevailing economic conditions more and more private motorists are being forced to do their own car maintenance. Here electronics can offer aid in the very practical form of a piece of test equipment known as an Engine Analyser. Constructors who run a car will be wise to make the PE Engine Analyser the first job they tackle this autumn, as the major and busiest season for home construction gets under way. This instrument could repay its cost many times over in the months ahead.

F.E.B.

Editor
F. E. BENNETT

Editorial
R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
R. W. LAWRENCE, B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
D. J. GOODING
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301


Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202

PE Engine Analyser

FOR ECONOMY MOTORING

By D. HALEY

PART ONE

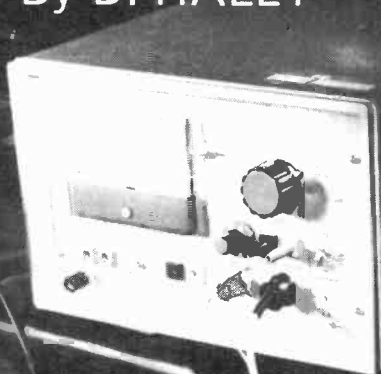

WITH the ever soaring costs of motoring more and more people are turning to do-it-themselves servicing of their own motor cars. Whilst much of this servicing can be carried out with the aid of a handbook and a few tools, the electrical components need a more sophisticated approach. The P.E. Engine Analyser described in this series of articles is designed for people with electronics as their hobby, who also wish to service their own car. The unit is quite simple and should not be any trouble to readers of this magazine. It is much simpler than the equipment garages use, but it is a lot cheaper, very easy to use and relatively easy to build. The cost of building the equipment can probably be recovered by hiring the Analyser, for a nominal charge, to friends and neighbours.

The Engine Analyser provides in one box a number of facilities to optimise the efficient and economical running of a car engine. Later, details are given for setting up procedures but for now a brief run-down of the functions provided will be given.

IMPORTANCE OF TIMING

Improper ignition timing may cause overheating, loss of power, poor acceleration and performance and may even shorten the life of an engine. It is for these reasons that accurate timing adjustment at the correct r.p.m. is vital. In the Analyser this is achieved with a very bright Xenon flash which allows timing to be achieved even in bright sunlight.

The dwell angle is the angle through which the distributor shaft turns while the points are closed and current is able to flow through the coil primary. Normally the points are 50 per cent closed and 50 per cent open, however when dwell time is specified there is no need to use feeler gauges, just set to the correct reading on the dwell meter to ensure maximum efficiency.

The voltmeter and ohmmeter is extremely useful for fault location and regulator adjustment.

The Analyser need not lay idle between services, since it may also be used as a batter charger. Frequent starting of the engine, with short journeys, will reduce the life of a battery. This can be offset with frequent topping-up by the charger. Two charging rates are provided.

BLOCK DIAGRAM

A block schematic diagram of the Engine Analyser is shown in Fig. 1.1. A battery charger transformer and bridge rectifier provide full wave rectified output at 12V for charging the battery at 4A. The rectifier can also be switched to half wave for a low charge of 2A. The 12 volt output can also be used to drive the Engine Analyser circuits or if mains supply is not available, these will work equally well from the car battery.

A voltage regulator circuit is included to regulate the supply to the circuits at 10 volts, so that outputs and meter calibrations will remain constant.

SPECIFICATION . . .

- **Ignition timing** By strobe lamp fired from inductive coupling to No. 1 spark plug lead.
- **Tachometer** 0 to 2500 r.p.m. on 1, 2, 4, 6 or 8 cylinder engines.
- **Dwell measurement** 10 per cent to 80 per cent at 1000 r.p.m.
- **Ohmmeter** 0 to 1000 ohms. 150 ohms centre scale.
- **Battery Charger** 12 volt 4A (High rate) or 2A (Low rate) or 6 volt 4A (High rate) or 2A (Low rate).
- **Voltmeter** 0 to 25 volts d.c. ± 5 per cent f.s.d.
- **Condenser check** 0.22 μ F condenser is substituted across contact breaker.
- **Power input** 240V a.c. at 50Hz or 12-16V d.c. at 1A.

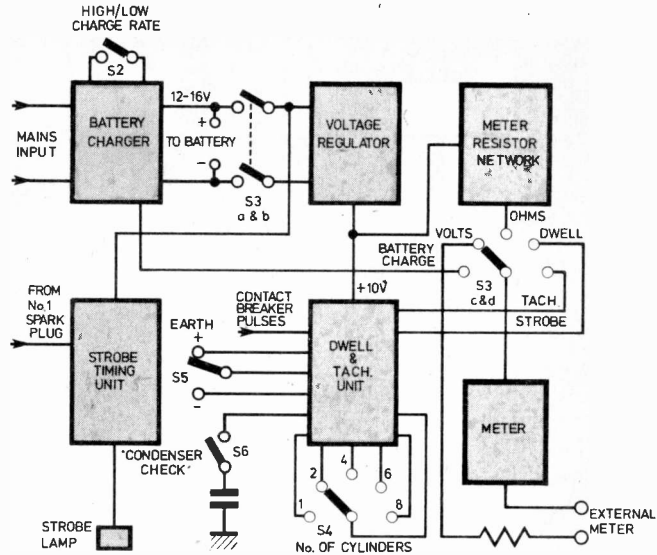


Fig. 1.1. Block diagram of Engine Analyser

The meter is switchable to the various functions as indicated in Fig. 1.1. The "Volts" and "Ohms" positions connect in circuit the necessary resistor networks for meter calibration. On battery charge the meter is connected across a shunt in the negative lead to read charging current from 0 to 5A.


The dwell and tachometer unit derives its information from the contact breaker pulses. Dwell is metered by cleaning up the contact breaker pulses and applying them to the meter to give a reading proportional to the "contacts closed" period. For tachometer readings, standard pulses are produced from the c.b. pulses, which give a meter reading proportional to their repetition rate.

The strobe timing unit produces a high voltage supply and triggering for a stroboscopic discharge lamp. When triggered from No. 1 spark plug, the lamp is used to illuminate the timing marks on the engine and fan belt pulley while the engine is running. The stroboscopic light pulse freezes the motion of the engine at the instant of firing of No. 1 cylinder, enabling the timing to be checked under dynamic conditions.

CONTROL PANEL

The photograph shows the control panel of the finished instrument. The meter is a 0-1mA moving coil meter with scale length just over 3 inches. There are five calibrated scales to indicate d.c. volts (0 to 25), dwell angle (0 to 100 per cent), r.p.m. (0 to 2500), amps (0 to 5) and ohms (0 to 1000). The dwell scale is calibrated in per cent rather than angle in order that the same scale shall apply for all types of engine. The maximum angle varies with number of cylinders, but the circuit is designed to produce deflection proportional to dwell angle for all engines.

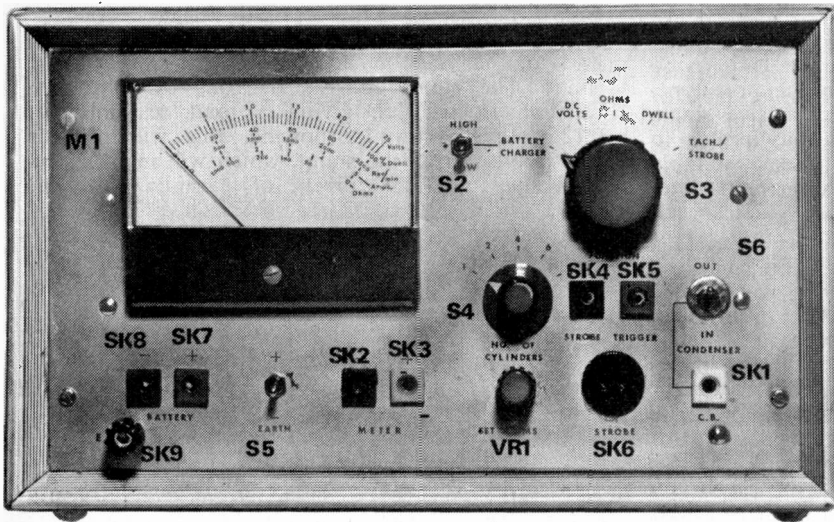Below the meter are two pairs of sockets. The pair marked "Battery" are for use in either charging the battery from the mains or powering the instrument from the car battery. The other pair,




The Engine Analyser front panel showing layout of controls and sockets

marked "Meter" are for use for voltage and continuity or resistance tests. The switch between the two, marked "Earth," should be set to whichever of the two battery terminals is connected to car chassis. The earth terminal (E) is provided to connect instrument chassis to car chassis.

The five position selector switch S3 on the top right hand side of the panel, switches the meter to the appropriate circuit and also switches power to the circuit boards when required. Associated with the battery charger is a "High/Low" charge rate switch which allows a low rate (2A) for overnight charging, or to limit initial charge current into a flat battery. The "No. of Cylinders" switch adjusts

the r.p.m. and dwell circuits for the type of engine under test. "Set Ohms" is adjusted so that the meter reads zero on ohms setting with the two meter leads shorted together. The strobe socket connects to the strobe lamp unit and the two trigger sockets above it to a small coupling coil, L1, for picking up a trigger pulse from No. 1 spark plug lead.

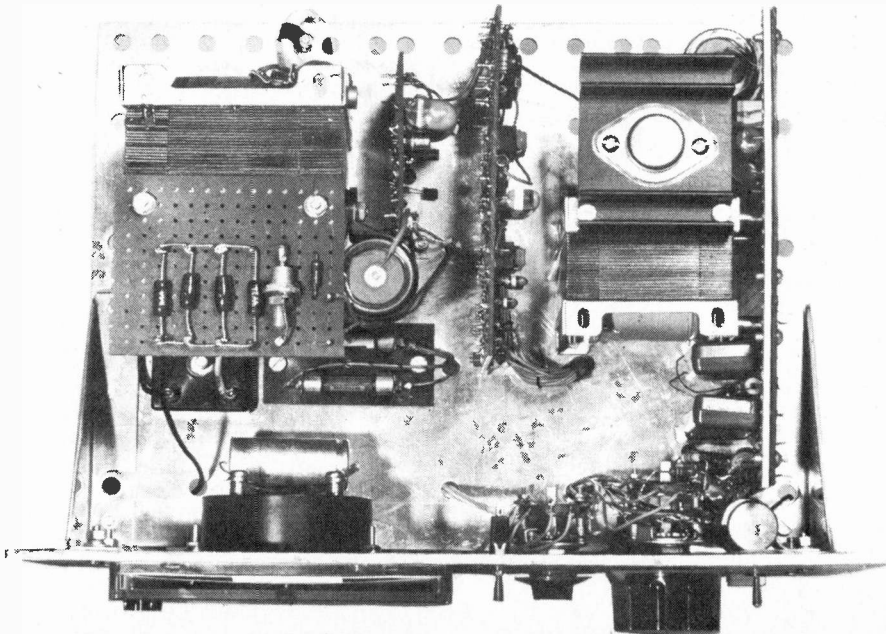Finally, the c.b. socket in the bottom right hand corner is for connection to the contact breaker terminal on the ignition coil. Associated with this socket is a standard ignition condenser which can be switched into circuit by the switch above the socket, thus enabling a test to be made for a faulty condenser.



FRONT PANEL AND CHASSIS ASSEMBLY

The actual front panel dimensions and layout can be varied slightly to suit the particular case to be used. An R.S. Type 1 was used in the prototype. Since the case is about the most expensive single item in the kit, many constructors may prefer to build their own wooden case, or use a suitable housing already to hand. The components and printed circuit boards are mounted on a flat chassis $9\frac{1}{4}\text{in} \times 7\frac{1}{4}\text{in}$ ($235 \times 190.5\text{mm}$) fixed to the rear of the front panel by two right-angled brackets.

A photograph shows the chassis layout, and the circuit diagram for the main wiring is shown in Fig. 1.2. The mains transformer, T1, is mounted at the rear left hand side of the chassis, with the bridge rectifier and fuse-holder in front of it. To obtain the half charge rate, a diode D1 is connected in series with the bridge, on the a.c. side, converting the rectifier to half wave. D1 is a stud type power diode, and is mounted on one a.c. terminal of the bridge rectifier by means of a solder tag on its stud terminal. For high charge the diode is short circuited by the charge switch S2.

The positive output of the bridge rectifier connects through a 5A fuse to the battery positive socket, and to the last 3 positions, "Ohms," "Dwell" and "Tach/Strobe") of one section of the four pole.

five way selector switch S3. The negative output is similarly connected to the battery negative terminal and another section of S3, through the ammeter shunt. The shunt consists of four 0.5 ohm 3W resistors in parallel, giving a total resistance of 0.125 ohms. With 5A flowing, this will produce 0.625 volts across the shunt, which will in turn produce the full scale current of 1 milliamp in the meter and its series resistor R5. This voltage will also just bring D6 to the point of conduction, which will limit any excessive overload of the meter due to currents greater than 5A. The meter shunt and series resistors and the protection diode are mounted on a small piece of Veroboard which is bolted to the top of the mains transformer, and the meter is connected through position 1 of the remaining two sections of S3. This completes the battery charger section of the circuit. 5A capacity wire must be used for wiring the bridge rectifier and battery sockets.

D.C. VOLTMETER

On position 2 of the function switch the meter is connected to the external meter sockets via two series resistors R8 and R9, to give a 25 volt d.c. measuring facility. The value of R8 may need to be selected to suit individual meters. R8 and R9 are mounted on the rear of the selector switch S3, using

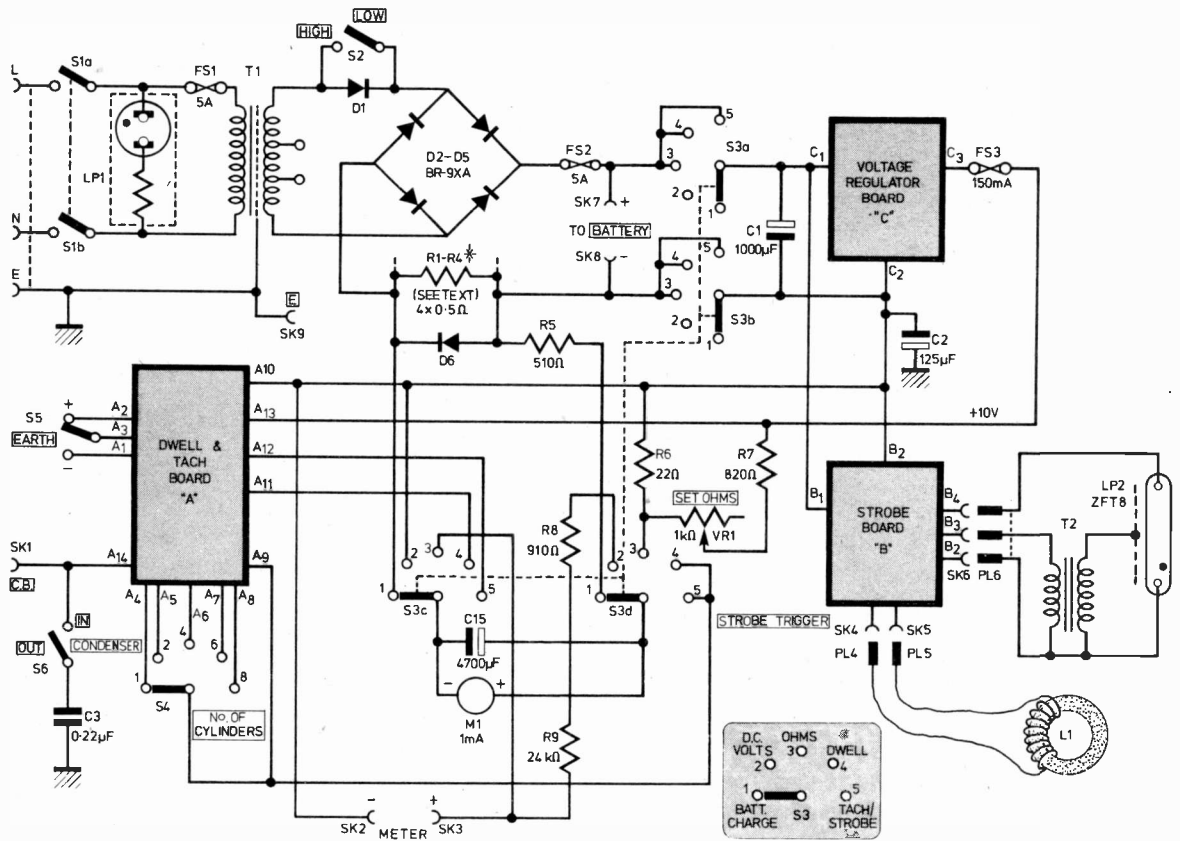


Fig. 1.2. Main wiring for Engine Analyser. Note that in the prototype S1, FS1 and LP1 are omitted

a spare tag for the junction. The remaining circuits require a d.c. power supply which will be described next.

POWER SUPPLY REGULATOR

Changes in engine speed will cause variations in generator voltage and hence the voltage appearing across the battery may be anything between 12.5 and 16 volts. As this will affect meter zero and calibration settings it is necessary to stabilise the supply for changes in battery volts. A simple series regulator circuit is used to produce a 10V 50mA regulated supply from the 12—16V input.

Fig. 1.3 shows the circuit diagram. A proportion of any variation in the output voltage is applied to the base of TR2, the emitter being held constant

by the reference potential on the base of TR1. The amplified error voltage at the collector of TR2 is applied to the base of series regulator transistor TR3, the phasing is such as to reduce the variation at the output, changes in input voltage are compensated by a corresponding change in the voltage drop across TR3. This circuit is built on a piece of printed circuit board $2\frac{1}{2}$ in \times $2\frac{1}{2}$ in at 0.1in (69.85 \times 63.5) pitch, with component layout as shown in Fig. 1.4. The assembled board is mounted by two small brackets on the chassis, adjacent to the mains transformer.

There are two electrolytic capacitors, C1 and C2, which are mounted separately from the board. C1 is bolted by a cleat to the side of the mains transformer and C2 is connected between the negative supply and chassis (positive terminal to chassis).

COMPONENTS . . .

Resistors

R1-R4	0.5 Ω 3W (4 off)	R20	1.8k Ω
R5	510 Ω	R21	2.2k Ω
R6	22 Ω	R22	120 Ω
R7	820 Ω	R23	330 Ω 5W
R8	910 Ω	R24	15k Ω 9W
R9	24k Ω	R25	1M Ω
R10-11	240 Ω	R26	1.2k Ω
R12	2k Ω	R27	150k Ω 1W
R13	3.3k Ω	R28	470 Ω
R14	10k Ω 2%	R29	820 Ω
R15	22k Ω 2%	R30	270 Ω
R16	16k Ω 2%	R31	2.2k Ω
R17	4.7k Ω 2%	R32	1k Ω
R18	3.3k Ω 2%	R33	1k Ω
R19	2k Ω 2%		

All $\frac{1}{2}$ W except where otherwise stated.

Potentiometers

VR1	1k Ω	} All linear
VR2	1k Ω	
VR3	3.3k Ω	

Capacitors

C1	1000 μ F elect. 25V
C2	125 μ F elect. 25V
C3	0.22 μ F
C4	0.1 μ F
C5	0.1 μ F
C6	1 μ F polyester
C7	16 μ F elect. 10V
C8	1.5 μ F polyester
C9	1 μ F polyester 400V
C10	1 μ F polyester 400V
C11	1 μ F polyester 400V
C12	0.1 μ F
C13	1000 μ F elect. 25V
C14	2.2 μ F polyester
C15	4700 μ F elect. 6V
C16	0.047 μ F

Transformers and Inductor

T1	240 pri. 12V sec. — Douglas battery charging transformer.
T2	TT51B (Henry's Radio)
L1	Trigger coil (see text) wound on Ferroxcube ring FX1588 (Home Radio)

Semiconductors

TR1-2	BC184 (2off)
TR3	2N3053
TR4	2N3055
D1	10A 100V
D2-D5	70V, 6A type BR-9XA
D6	10A 100V
D7	BZX85-5.1V 1.3W Zener
D8	BZY88-8.2V 400mW Zener
D9	BZY88-5.1V 400mW Zener
D10	1N4006 (800V rectifier)
D11	1N4006 (800V rectifier)
D12	150V 1W Zener
D13	BZX85-5.1V 1.3W Zener
CSR1	C106B silicon controlled rectifier (Henry's)
IC1	SN74121N
IC2	SN7402N

Switches

S1	Double-pole mains on/off
S2	S.p.s.t. toggle
S3	4-pole 5-way (made up of 2-pole, 6-way break-before-make wafers) (2 off) (R.S.)
S4	Single pole, 5-way
S5	S.p.c.o. toggle
S6	S.p.s.t. toggle

Xenon Tube

LP2	ZFT8 (Henry's Radio)
-----	----------------------

Meter

M1	1mA SEW model SD830
----	---------------------

Miscellaneous

FS1/FS2-5A fuses, FS3-150mA fuse, fuseholders (2 off) p.c.b. 3in \times 2.4in \times 0.2in (76.2 \times 60.96) (main chassis), p.c.b. 2.6in \times 2.7in \times 0.1in (66.04 \times 68.58) (10V regulator), p.c.b. 2.7in \times 4.8in \times 0.1in (68.58 \times 121.92) (tach. and dwell), p.c.b. 6.4in \times 3.4in \times 0.2in (162.56 \times 86.36 \times 5.08mm) (ignition timing) Veropins (31 off), 14 pin d.i.l. i.c. sockets (2 off), brackets: $2\frac{1}{2}$ in \times $3\frac{1}{2}$ in (2 off) (57.15 \times 88.9mm) (main chassis), ($\frac{1}{2}$ in \times $\frac{3}{8}$ in \times $\frac{3}{8}$ in) (Lektrokitt LK2321) (2 off) (tach. and dwell), paxolin tube for strobe 12in \times 1in (304.8 \times 25.4mm), Case-Type 1 instrument case (R.S.) SK2, SK3, SK4, SK5, SK7, SK8, SK9-4mm sockets (R.S.) (7 off). SK6, miniature socket (R.S.)

Its purpose is to complete the circuit for the contact breaker pulses to the dwell and tachometer circuits. The input to the voltage regulator board connects through the last 3 positions of S3a and b. A 150 milliamp fuse is connected in the 10 volt output line.

CONTINUITY METER

Position 3 of the function switch connects the meter for resistance and circuit continuity measurement. R6, R7 and VR1 ("Set Ohms") are connected across the 10-volt regulated supply, and VR1 adjusted so that with the meter leads short-circuited, full scale deflection (zero ohms) is produced. R6 plus the internal resistance of the meter should give

a total source resistance of 150 ohms. To check the calibration, set the zero control, and connect a 150 ohm resistor across the meter sockets, and the meter should read half scale. If not, a different value may be selected for R6, and the check repeated. If the reading is too high, reduce R6 and vice versa. When using the continuity tester on car wiring, the battery should be disconnected from the car to prevent possible short circuit or erroneous readings.

CONTACT CONDENSER

The test ignition condenser, C3, may be conveniently mounted by its flange to the chassis bracket bolt above the switch and contact breaker socket. A test for faulty condenser can be made by simply closing the switch. This completes the assembly of the static test circuits. In the next article we shall deal with the dwell and tachometer measurements.

CARS WITH 6 VOLT BATTERY

The engine analyser may be used on a car with a 6 volt system, provided it is supplied from 240 volt mains, or an independent 12 volt battery. If 6 volt battery charging is required, the a.c. input to D1 and the bridge rectifier must be moved to the 6 volt tapplings on the mains transformer secondary. This bridge will not then give sufficient d.c. output to supply the circuits, and an additional 25 volt, 1A bridge rectifier must be connected across the 12 volt tapplings. The input connections to S3a and S3b must be removed from the "Battery" sockets and taken to the d.c. output terminals of this second bridge. There may also be a change necessary in the dwell and tachometer circuit, and this will be mentioned when the circuit is described.

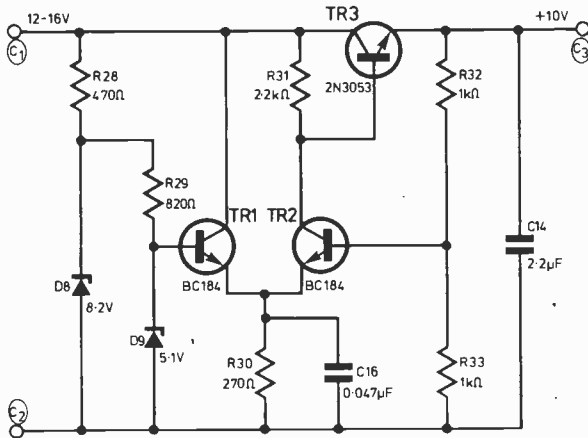


Fig. 1.3. Circuit of Voltage Regulator Board 'C'

NEXT MONTH: The remaining circuits involving dynamic engine tests

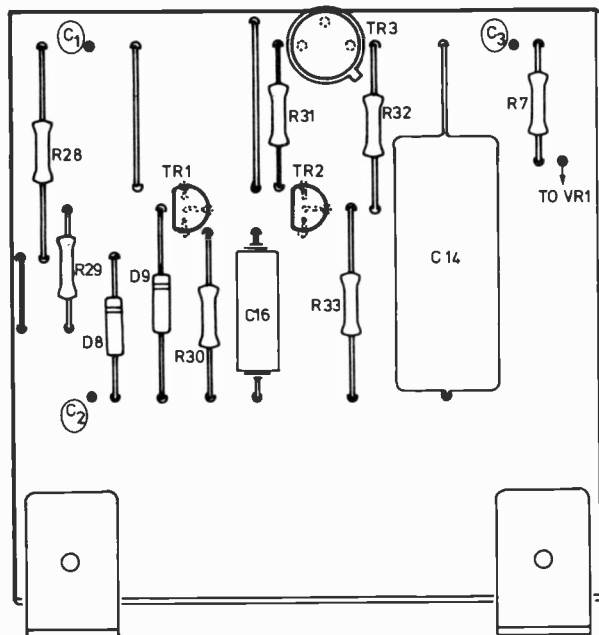


Fig. 1.4. Component layout and track cutting details for Board 'C'

PE

A VOLUME OF PRACTICAL KNOW-HOW

... can be made using these new-look self binders for **PRACTICAL ELECTRONICS** to become your most valuable source of reference. With the Easi-Binder current copies can be inserted as they are received, without waiting for the completion of twelve issues.

They are attractively made with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers, please advise year and volume and a separate set of gold transfer figures will be supplied.

At **£1.90** (including VAT and postage), they are obtainable from:

Post Sales Department, IPC Magazines Ltd.
Carlton House, 66-68 Great Queen Street
London, W.C.2

I enclose P.O./cheque value for binders at £1.90 each for Practical Electronics Vol. No's.

Name.....
 Address.....
 Date.....

PE



DIGITAL WATCH

ASSEMBLING THE SABCHRON I.E.D. WRISTWATCH KIT

If you want to be really with it, no doubt the digital watch is the thing of the moment. But, before you rush ahead and buy that expensive kit, make certain you have both the tools and the skill needed to undertake this deceptively simple task.

ANYONE with an interest in electronics will have noted the trend over recent years towards miniaturisation of almost everything. We have gone from large to small radios, computers and pocket calculators at an ever-increasing pace.

The latest development is the truly electronic watch. Made possible by the development of c.m.o.s., with its low power consumption and compact packaging density, this concept has in two short years managed to go from development prototype to kit construction in one of the fastest development curves in our exploding technology.

Various watches are coming on to the British market but these are mostly in the ready-made form and the prices are a little awe-inspiring to the would-be owner. For example there is one rather large item which boasts solar power and the ability to cope with both normal and leap-year counting once set. This is available at around £300.

At the other end of the scale at the time of writing there is a fairly simple ready-built unit which is capable of indicating merely hours and minutes, with a flashing hyphen to give some idea of seconds. Apparently such a device can be obtained for around £50.

Of course all these equipments come from overseas at this time and so they are subject, in price terms, to the vagaries of international financial adjustments, usually to the British purchaser's detriment, so it is heartening to see a kit appearing on the market with an associated lower cost.

Euray Trading Inc. of Dallas have started to advertise a kit for a watch which incorporates most of the features the non-specialist would need. Called the Sabchron Digital, the watch offers the ability to indicate, on one depression of a small button in its side, hours and minutes, the month and day numbers on a second depression, and minutes and seconds if the button is initially held down for three seconds.

THE SABCHRON

Using an l.e.d. display with up to four digits and housed in an attractive case of only slightly larger than a normal wrist-watch thickness dimension, the Sabchron when completed is certainly a reasonable project to undertake.

This kit makes use of current m.o.s. l.s.i. technology in the form of one small 24-lead chip which houses all the logic and basic electronics. The display is only switched on for a matter of seconds after the operating the main push-switch and is, in addition, strobed to reduce power consumption. Battery life is claimed to be about one year.

An additional function is the automatic control of l.e.d. brilliance dependent on ambient light. This is achieved by using an l.d.r. (light-dependent resistor) positioned inside the case to measure the amount of light falling on the display. This feature is optional.

CIRCUIT DESCRIPTION

The component count is kept fairly low by designing the integrated circuit in such a way that it is capable of driving the display directly rather than through driver transistors as can be seen from the general block circuit diagram of Fig. 1. Here the layout is for drafting convenience, obviously the i.c. pin numbers follow in order on the board used, as seen from Fig. 2 and Fig. 3.

The built-in oscillator circuit (input at pins 16 & 17) works in conjunction with the quartz crystal, C1, C2 and C3. The trimmer capacitor, C3 is included to adjust for accurate frequency. C1 and C2 are included to further stabilize the frequency, but the circuit would work without them. However, it is recommended that they be used. The oscillations are counted and divided by the i.c.

Power for the complete circuit is supplied by silver-oxide $1\frac{1}{2}$ V cells, B1 and B2. The l.d.r. varies the current available to the display drive circuitry. The l.d.r. resistance increases in bright light, permitting more current flow to this circuit, in total darkness, the resistance increases to reverse the effect.

Outputs from the i.c. are provided through pins 2, 3, 4, 5, 6, 7, 8, 19, 20, 21 and 22 for driving the display, thus omitting the need for additional driver transistors. Time display is made via S2 on an on-demand basis to conserve battery power. Internal logic elements within the i.c. keep the display lighted for about 1 to $1\frac{1}{2}$ seconds after demand is made. The logic elements are always powered and driven; only the display is on-demand. Since the i.c. draws only 18 μ W of power, the two silver-oxide cells will last up to one full year or more, depending on how frequently display demand is made.

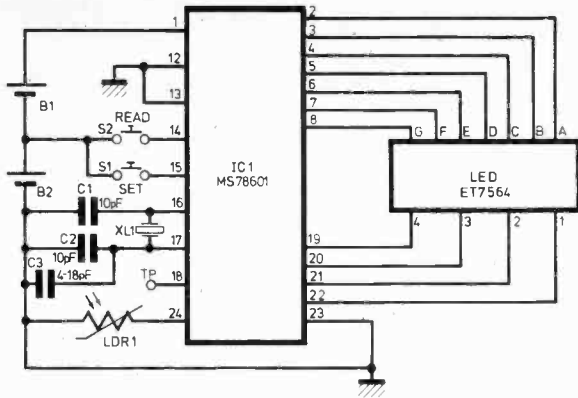




Fig. 1. Circuit diagram of the Sabchron digital wristwatch

Once the complete watch is assembled, operation is simple and uncomplicated. Depressing S2 once, displays the hours and minutes. Keeping S2 depressed after that, causes the minutes and seconds to be displayed. Depressing S2 twice in succession causes the month and date to be displayed, in that order (e.g. a display of 1204 indicates the 12th month and 4th day of the month). This is the way dates are written in the United States.

PRECAUTIONS


Before any construction at all is considered there are several precautions which need to be taken.

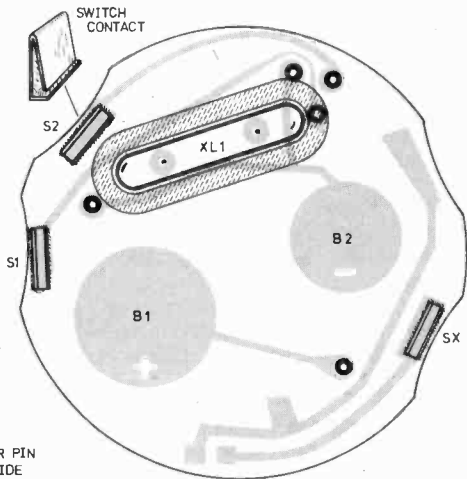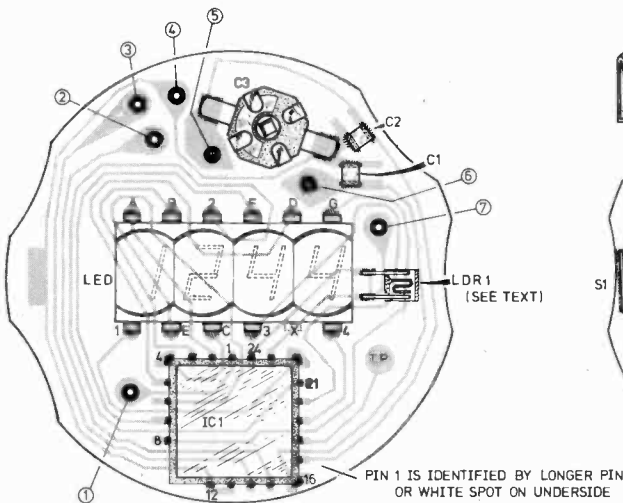First of all there is the question of skill level required. No doubt someone with a reasonably mechanical bent could cope if he followed the instructions painstakingly and laboriously. However, as both miniature soldering and the handling of an m.o.s. l.s.i. is involved there is considerable risk of damage to the product in the process.



Figs. 2 and 3. Components mounted on the double-sided printed circuit board

Components...

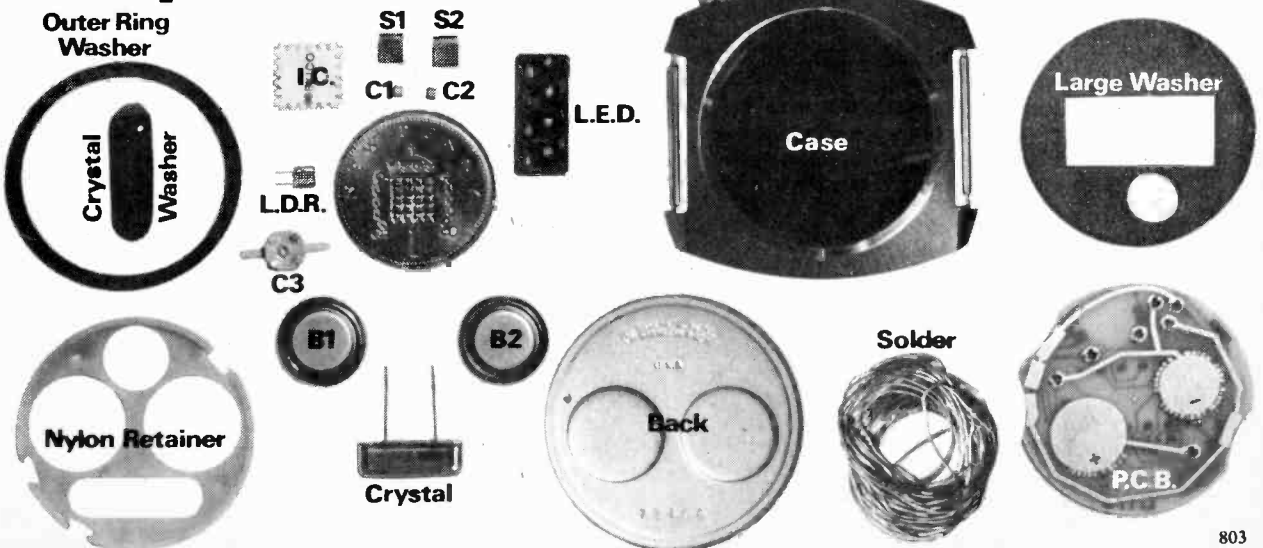

Thus it would be advisable that a prospective constructor have at least some experience with quite small soldering problems and the handling of c.m.o.s. with its attendant danger of electrostatic damage.

TOOLS

Then there is the matter of suitable tools. No doubt most enthusiasts have a fairly miniature iron but here it is really necessary for the bit to be smaller than 3/64in diameter, so for many this will involve the purchase of a suitable iron and miniature bit. In fact a pointed rather than a chisel end might be found more suitable.

The kit calls for a plastic tweezers but, as anyone who has tried to purchase a pair will know, there are very few around so it behoves one to make them as the writer did.

Finally, there is provision for speed adjustment through a tiny trimmer capacitor which has to be set using a very small square socket tool. To the best of our knowledge there is no version of this available in the U.K., so one will have to be made.

With these thoughts in mind and dealt with one way or another construction can be considered.

THE KIT

The Sabchron kit comes complete with quite comprehensive instructions and all the parts carefully packaged in small plastic bags. The first words on the instructions say "Read before starting assembly" and we heartily endorse this. Currently there is also some Addenda material which bears similar careful scrutiny.

First of all the watch specification is discussed and then a list of required tools is noted. Here it might be sensible to add a pair of small snipe-nosed pliers and a pair of side cutters for holding small objects and cutting leads to length respectively.

KIT INSTRUCTIONS

As in most kits, the instructions are written in a numbered step-by-step sequence which any constructor will find easy to follow. The only steps which might cause some baulking are those concerned with a repetition of a series of resistance checks which, on the face of it, seem unduly laborious. However, they are none-the-less absolutely necessary.

Starting from an untouched p.c.b., the first stage involves a decision to use the optional light level control for the l.e.d.s. If one decides, as we did, to make use of this facility then a small section of track shorting the location of the l.d.r. has to be removed.

FIRST SOLDERING

The board is 'double-sided, with interconnection between the sides provided by so-called "bif" rivet. These have to be soldered to both sides of the board and in fact this step provides good practice in handling the small iron before more important components are attached.

After this first soldering exercise a series of continuity tests is carried out between both sides of the board and various pads for the i.c. and l.e.d. to ensure proper soldering and no damaged tracks. This and similar checks are very important and should not be skipped no matter how convinced of one's soldering ability one might be. Any fault now can become very embarrassing later.

FIDDLY BITS

Probably for many, the hardest task will be the next step, involving attaching two tiny capacitors in the oscillator circuit.

Again, the use of these components is optional in that without them the watch maintains a claimed accuracy of 3 minutes per year whilst with them this figure can be considerably bettered.

Two points come up at this time. One is the use of so-called reflow soldering in which both parts of a joint are first tinned and then subsequently placed together, heated and thus bonded. The second is the nature of the solder compound used in the tiny chip capacitor which, in the prototype, appeared to be a somewhat pasty material when heated, rather than a free-flowing solder. Thus it behoves the constructor to apply solder to the capacitor joints when making them rather than relying only on the solder on the capacitor themselves as is suggested in the instructions.

The trimmer, C3, comes with longer leads than necessary and these need trimming to suit the board prior to tinning, a step not mentioned in the instructions.

Handling the tiny C1 and C2 capacitors is quite a problem and the writer found that any excess of pre-tinning on the board copper caused them to lie at odd angles when assembling before soldering. A bit of solder wick is handy in this case for removing excess solder, but probably some extra solder will be needed to obtain a good bond. In fact, in a second assembly operation no pre-tinning was done and this was found to be an easier operation.

After assembling the capacitors, the l.d.r. is soldered on, taking care to watch orientation both in terms of the exposed side of the tiny chip and in terms of orientation with respect to the edge of the board as the l.e.d. display has to be subsequently assembled in the centre of the board.

CONTINUITY CHECKS

At this point a comprehensive continuity check is carried out and again one must emphasise that this step is imperative since the next steps involve mounting the rather sensitive circuitry which, if some lines are not connected or are shorted, can be damaged on applying power.

CRITICAL STEPS

Now we come to the trickiest part of the assembly. Tricky because even if damage is done to the i.c. you will not know till you power the watch. And it is very easy to do damage because of static electricity. Thus the suggestions as to earthing everything to a common earth are most important. This is dealt with in the instructions in some depth.

The writer used a normal desk for assembly, overcoming the earthing problem by using two sheets of aluminium foil to work on. Wearing cotton clothes (nylon can create a great deal of static electricity, and working with bare arms on the working surface at all times makes certain both you and the tools are grounded.

The soldering iron must be connected to this ground surface and it is advisable, when handling the i.c., to keep it insulated from every thing until the soldering is done. The writer applied the first solder joints to the chip whilst the p.c.b. was resting on a sheet of cardboard on the aluminium foil and

Construction

1

2

3

4

5

- 1 — *Cutting the l.d.r. shorting strip out (Step. 1)*
- 2 — *Soldering the BIF rivets to provide the conductive path through the board (Step. 2). An Antek 15W iron with a No. 6 tip being used. The kit supplier recommends a smaller tip*
- 3 — *Soldering C3 in position. C1 and C2 can be seen already soldered on the board and the size of finger gives some idea of the scale involved*
- 4 — *The most important operation is soldering on the integrated circuit. The solder and iron tip are displayed for scale only, as the i.c. and l.d.r. have been soldered in position*
- 5 — *Soldering the l.e.d. in position*

completed some of the soldering after the first three steps whilst holding the p.c.b. with the hand.

The orientation of the chip is obviously important and care should be taken to ensure it is both the correct way up and with pin 1 facing the pin 1 pad on the p.c.b. before the final pressure is applied to make the double-sided adhesive sheet used to temporarily hold it down actually stick firmly.

Patience at this stage is imperative. Do not do more than one joint at a time between inspection steps. The delay in the sequence introduced by each examination is very useful as it allows things to cool down after heat from the iron has been applied. In this way the chip does not become too hot and heat, it should be remembered, can destroy the chip.

The soldering operation itself at this stage requires quite a lot of dexterity and great care must be exercised to avoid too much solder as well as too much heat. It is very easy to run solder over more than one track on the p.c.b. but a good loupe (magnifying glass) will show such an error fairly clearly.

FINISHING ASSEMBLY

From this point on the assembly is fairly simple with the possible exception of the application of three small switch contacts. These latter are in the form of bent-up phosphor-bronze strip which has to be soldered to the p.c.b. at three points on the periphery. In itself the soldering is not difficult providing one can hold the spring steady whilst the solder cools.

The three switch contacts engage in three slots formed in a nylon moulding which serves to locate the board and contacts in the watch body. The engagement is very tight and some relieving with a small file or, indeed, the hot iron bit, is needed to finally get the assembly to go together smoothly.

After all components are assembled on the p.c.b. and prior to power application, a further and final continuity check is carried out.

FIRST TRIAL

The instructions now lead the constructor through the first trials of the watch, including powering the unit up, checking it out and finally closing up the case.

In the writer's case the prototype worked first time round on all tests, apart from one l.e.d. segment which was clearly due to a faulty l.e.d. No doubt, the kit being a prototype explains this particular item. The second, final form, kit operated properly the first time power was applied.

Measurements on the two models made up were quite interesting. The first, prototype version, without any alteration at all gained some 15 seconds in 14 days according to TIM. The second version, the final form of model, lost some 30 seconds in 48 hours, clearly a matter for heavy adjustment. Indeed both watches constructed need adjustment to meet the claimed accuracy and this brings up the matter of the tool required for this job.

To the writer's knowledge there is no available device so again one has to be made up and could be filed from a length of steel or brass rod to give the required very small rectangular end shape. In fact, the adjustment can be effected using any fairly small object which is shaped so as to engage with the flats or the diagonals of the square hole in the capacitor spindle. ★

NEWS BRIEFS

A Stitch in Time . . .

THE latest domestic sewing machine introduced by Singer in the United States, the Athena 2000, is controlled electronically by a m.o.s. l.s.i. system produced for Singer by AMI Microsystems.

Designed to Singer's own specification, the AMI module operates in conjunction with touch contact controls to replace as many as 350 mechanical parts, including the manual levers and dials conventionally used for the selection of the various machine functions.

Pattern selection, for example, is effected simply by touching the relevant contact; the appropriate machine settings are then made automatically by the m.o.s. control system. This facility also allows one unit of a selected pattern to be sewn, following which the machine automatically stops. Similarly, the AMI module causes the adjustment of machine settings according to the selected stitch length and width, and the fabric in use.

At present, the Athena 2000 is available only in the US domestic markets. A version of the machine for Europe is currently under development.

TV Innovations

FOR those of us who like to watch t.v. but find following a programme difficult when others start talking in the room, a recent innovation from Germany may help put an end to our plight. Mounted on the front of the new set from Loewe Opta GmbH is an array of l.e.d.s which transmit a frequency modulated beam of infra-red to a photo diode mounted on a pair of headphones; the beam being modulated with the t.v. sound. The headphones are thus completely independent of the t.v.

Infra-red was chosen since light in that frequency band tends to be reflected around the room and therefore can be picked up by the receiving photo diode without it having to be in line of sight with the transmitter. One is able to listen to a programme without being disturbed by others talking, and without fear of anyone tripping over leads to the headset.

Besides their sophisticated ultrasonic control system (see Inter Navex '75 report) Grundig are to incorporate yet another new feature in their latest range of t.v.s. On pressing either a control on the ultrasonic control unit, or a plate on the t.v. itself, four-centimeter high light-green digits giving the time in hours and minutes appear on the bottom of the screen. Also, whenever the channel is changed a similar display giving the programme number is shown on the screen. The digits automatically disappear after ten seconds.


Going Dutch

THE Wilhelmina Gasthuis Hospital in Amsterdam is the first hospital in Holland to be equipped with an EMI-Scanner, a revolutionary X-ray machine for the diagnosis and investigation of brain disorders.

The order was placed with EMI's Dutch Company ANRU, and followed a visit by Professor Westra of the hospital, to the Company's X-ray Systems division at Hayes, Middlesex and to several existing clinical installations of the system in UK hospitals.

The EMI-Scanner produces pictures of brain tissue with exceptional clarity and high definition, giving doctors 100 times more information on tissue than is possible with conventional X-ray techniques.

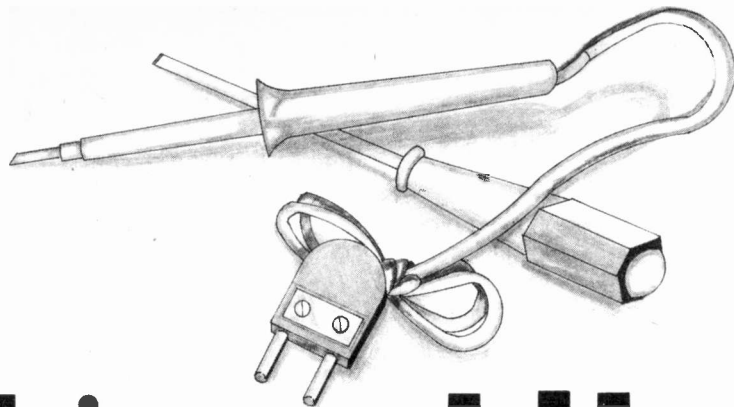As patients can frequently be accepted for examination by the EMI-Scanner on an out-patient basis this contributes greatly to reduced patient anxiety.



This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you


how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.

1

Build an oscilloscope.


As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

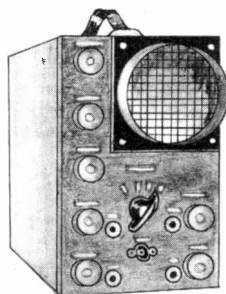

2

Read, draw and understand circuit diagrams.

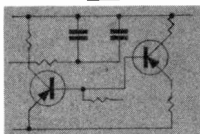
In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.




3

Carry out over 40 experiments on basic circuits.

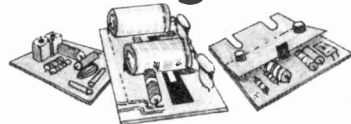We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.



PLUS

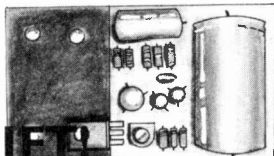

FREE GIFT

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE


To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept EL105
P.O. Box 156, Jersey, Channel Islands.

NAME.....

ADDRESS.....

(Block caps please)

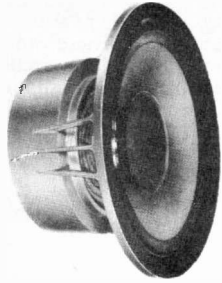

WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 253, 8 or 15 ohm £10-25
 Baker Group 35 3, 8 or 15 ohm £14-00
 Baker Group 50 12 8 or 15 ohm £13-75
 Baker Deluxe 12in d/cone £11-87
 Baker Major 12in d/cone £10-00
 Baker Regent £18-12
 Baker Superb £16-25
 Baker Auditorium 12 £10-31
 Castle Super 8 RS/DD £10-95
 Celestion MF1000, 8 or 15 ohm £3-75
 Celestion PS8 for Unilux £12-00
 Celestion G12M 8 or 15 ohm £15-00
 Celestion G12H 8 or 15 ohm £24-00
 Celestion G13C 8 or 15 ohm £33-00
 Celestion G19C 8 or 15 ohm £30-00
 Decca London and crossover £37-50
 Decca DK30 and crossover £24-00
 EMI 13in x 8in 150 d/c 8 ohm £2-94
 EMI 13in x 8in type 350 8 or 15 ohm £9-56
 EMI 13in x 8in 20W base £7-89
 EMI 6 1/2in 93850 4 or 8 ohm £2-50
 EMI 5in 14A 7030 mid range 8 ohm £0-77
 EMI 2 1/2in tweeter 97492AT £8-31
 Eagle DT33 30W tweeter £4-40
 Eagle HT15 horn tweeter £2-06
 Eagle CT5 cone tweeter £3-00
 Eagle CT10 tweeter 8 or 16 ohm £4-44
 Eagle MHT10 horn tweeter £1-75
 Eagle crossover CN23, CN28, CN216 £6-12
 Eagle FR4 £9-82
 Eagle FR5 £12-31
 Eagle FR8 £3-44
 Elac 3 x 5 59RM109 15 ohm, 59RM114 8 ohm £4-06
 Elac 6 1/2in 6RM171 d/c roll surr £3-12
 Elac 6 1/2in 6RM220 d/cone £1-75
 Elac 4in tweeter TW4 £3-12
 Elac 10in d/cone 10PRM239 8 ohm £2-87
 Elac 8in 8CS175 3 ohm £5-25
 Fane Pop 15W 12in £7-50
 Fane Pop 25T 30W 12in £12-00
 Fane Pop 50W 12in £13-95
 Fane Pop 55 60W 12in £14-75
 Fane Pop 80W 15in £25-95
 Fane Pop 100W 18in £34-50
 Fane Crescendo 12A 100W 12in £36-50
 Fane Crescendo 12B bass £47-50
 Fane Crescendo 15in 100W £62-95
 Fane Crescendo 18in 150W £8-12
 Fane 801T 8in d/c roll surr £5-75
 Fane 807T 8in d/c roll surr £3-44
 Fane 808T 8in d/c £40-50
 Fane 701 twin ribbon horn £14-95
 Fane 910 horn £33-85
 Fane 920 horn

Goodmans 8P 8in 8 or 15 ohm £5-50
 Goodmans 10P 8 or 15 ohm £5-80
 Goodmans 12P 8 or 15 ohm £13-95
 Goodmans 12P-D 8 or 15 ohm £18-95
 Goodmans 12P-G 8 or 15 ohm £15-95
 Goodmans Audiomax 12AX 100W £36-50
 Goodmans Audiomax 15AX £40-25
 Goodmans 15P 8 or 15 ohm £21-00
 Goodmans 18P 8 or 15 ohm £36-00
 Goodmans Hifax 750 £18-00
 Goodmans Axent 100 tweeter £8-44
 Goodmans Audiom 100 12in £13-90
 Goodmans Axiom 402 12in £20-00
 Goodmans Twinaxiom 8 £10-14
 Goodmans Twinaxiom 10 £10-75
 Jordan Watta Module £17-06
 Kef T27 £8-06
 Kef T15 £8-94
 Kef B110 £8-37
 Kef B200 £9-50
 Kef B139 £16-50
 Kef DN8 £2-31
 Kef DN12 £5-75
 Kef DN13 £3-87
 Peerless Dome Tweeter KO10DT £8-06
 STC 400G Super Tweeter £8-56
 Radford BD25 £18-44
 Radford FN11a £13-56
 Radford FN12a and 12b £12-44
 Radford MD9 £11-50
 Radford TD3 £8-06
 Richard Allan CGBT d/c r.surr £7-37
 2 1/2in 64 ohm, 70mm 80 ohm, 70mm 8 ohm £0-77
 2 1/2in 75 ohm £9-50
 7in x 4in 3 or 8 ohm £1-83
 8in x 5in 3 or 8 ohm £1-75
 10in x 6in 3, 8 or 15 ohm £2-89

SPEAKER KITS

Baker Major Module each £13-44
 Goodmans Mezzo Twinkit pair £47-19
 Helme XLK25 pair £25-44
 Helme XLK30 pair £17-19
 Helme XLK50 pair £48-25
 Kefkit 1 each £42-90
 Kefkit 3 each £18-37
 Richard Allan Twinkit each £15-94
 Richard Allan Triple 8 each £23-12
 Richard Allan Super Triple each £27-50
 Wharfedale Linton 2 kit pair £23-12
 Wharfedale Glendale 3 kit pair £40-82
 Wharfedale Doveedale 3 kit pair £83-12
 Baker, Linear and Eagle PA disco amplifiers in stock. Send stamp for list.

FREE with Speaker Orders over £7

Hi-Fi Loudspeaker Enclosures book.
 All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, 12in and up 50p each, speaker kits 75p each (£1 50 pair), tweeters and crossovers 25p.
 Send stamp for free booklet. Choosing a Speaker

Including VAT 25% on Hi-Fi, 8% on PRO and PA

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF.

Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow.

Discount TV, Hi-Fi: Swift of Wilmslow, 5 Swan Street, Wilmslow.



Cassettes

The best buy!

	1	5	10
Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!	C60 40p	£2 00	£3 90
	C90 54p	£2 70	£5 30
	C120 75p	£3 70	£7 38
AGFA HIGHDYNAMIC SUPER	C80 - 6 54p	£2 70	£5 35
	C90 - 6 70p	£3 30	£6 75
	C120 90p	£4 90	£9 85
AGFA STEREO-CHROM CHROMIUM DIOXIDE	C60 90p	£4 90	£8 75
	C90 £1 10	£5 90	£10 90

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO

(DEPT. PE)
 10 SWAN STREET, WILMSLOW,
 CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

SINCLAIR

IC20

AMPLIFIERS

SEND S.A.E. FOR FREE DATA BOOKLET

IC20 10 + 10W stereo amp. kit with free booklet and printed circuit £8-58.

PZ20 power supply kit for above £5-91.

VP20 volume, tone control and preamp kit £6-56.

SINCLAIR CALCULATORS

*****This months snip. Get the Sinclair Cambridge Memory Calculator at the same price as the normal Cambridge. Only £11-20 *****

CALCULATORS

Cambridge Memory £11-20
 Scientific £14-10
 Oxford 100 £9-95
 Oxford 200 £15-90
 Oxford 300 £22-98

MAINS UNITS

For Oxford Series £3-69
 For Cambridge, Cam. Mem. and Scientific £3-95



FERRANTI ZN414

IC radio chip with data £1-69. Also available kit of extra parts to complete a radio £3-38. Send S.A.E. for free leaflet.

SINCLAIR PROJECT 80

AFU £8-31 FM Tuner £14-91
 Z40 £6-55 Stereo decoder for above £9-69
 Z60 £8-31 Transformer for PZ8 £5-16
 Q16 £9-71 Stereo 80 £14-91
 PZ5 £6-21 Project 80S £38-22
 PZ6 £9-69 Project 80SSQ £46-65
 PZ8 £9-45 Project 80 Quadraphonic decoder £20-97

BATTERY Eliminator Bargains

6-WAY SPECIAL

The most versatile battery eliminator ever offered. Switched output of 3, 4, 6, 7, 9 and 12V at 500mA £5-45.

3-WAY MODEL

Switched outputs of 6, 7 1/2 and 9V at 250mA with unique 4-way multi-jack plug and socket output connector £3-55.

RADIO MODELS

50mA output with poppet battery connectors for transistor radios, etc. 6V £3-86; 9V £3-86; Double 4V + 4 1/2V £4-43; 6 + 6V £4-43; 9 + 9V £4-43.

TAPE RECORDER MAINS UNITS

7 1/2V output complete with 5 pin DIN plug to run cassette tape recorders from the a.c. mains £4-61.

HEAVY DUTY MODELS

500mA, British made to very high standards. Our best buy suggestion. 6V £4-90; 7 1/2V £4-90; 9V £4-90.



SINCLAIR IC12 6W IC power

amp and preamp with 44 page booklet and printed circuit £4-10.




SWANLEY IC TOMORROW

Similar to above. 10W into 15 ohms, but no printed circuit £2-12. SEND S.A.E. FOR FREE LEAFLET ON BOTH

S-DECS and T-DECS

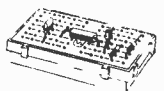S-DeC £2-34.
 T-DeC £4-15.
 H-DeC A £4-55.
 H-DeC B £7-85.
 IC carriers: 16 dil: plain £1-18; with socket £2-21.
 10 T05: Plain £1-09; with socket £2-08.



SWANLEY ELECTRONICS

P.O. Box 68, Swanley, Kent BR8 8TQ

Prices include post and VAT.

Official credit orders from schools, etc., welcome.

No VAT charged on overseas orders.

All prices are special offers.



THE EARTH AND EARTHQUAKES

Geophysicists have been working for some time on evidence of a number of related facts which suggest that an earthquake is but one of a number of manifestations of a chain of physical events.

Dr. Donald Anderson, Director of the Seismology Laboratory at the Californian Institute of Technology, has discovered a number of curious data relationships which occurred at the beginning of this century. Between 1897 and 1914 there was a 17 year period of seismic violence. During that time no less than 71 earthquakes were reported with an intensity greater than 8 on the Richter scale.

Coincident with these happenings there were volcanic eruptions and "Tsunamis". These "Tsunamis" are giant waves and in the time of the 17 year cycle of events some of these were more than 100 feet high. Perhaps surges are a more apt description of them for they are the result of earthquake crustal movement and not tidal effects.

Now at the same time as these events were operating, the "wobble", known as the Chandler Wobble after its discoverer, was at its peak. This wobble is a spinning top effect which varies in such a way that the north geographical pole describes varying diameter circles. This normally has a slight effect on the speed of the rotation of the Earth which over a period of time averages out.

However, at the period in question the length of the day changed because the Earth had slowed up. In five years the rotation decreased more than it had

previously done in the last 2000 years. At the same time the global temperature added to the phenomena by rising by 1.0 degree Centigrade, the sea level rose and the westward drift of the Earth's magnetic field accelerated.

During the last few years great strides have been made in the science of geophysics. As a result of refined measuring systems, the observations from satellites and probes and the revival of interest in plate tectonics, earthquake predictions have become more accurate.

The spin-off of space technology has had its part in this and we are thus able to learn more about the rather unstable globe on which life exists. Indeed, like so many of the things going on around us the facts are more exciting than fictional stories.

ON THE MOVE

The Earth's upper crust is not stable and solid, but is in fact made up of about a dozen tectonic plates which move in relation to each other. The upper surface of the crust is rather similar to a conveyor belt feeding new crust out at one end and consuming it at the other. Pressure builds up in the interior of the Earth and pushes new molten material out of the sea floor separating the plates and pushing them apart. If this occurs with the Pacific Plate and the North American Plate then one passes under the other returning material to the interior. Earthquakes occur at the lines where the plates meet.

This is but a part of the chain of events. The total energy cycle involves the atmosphere, for energy is transferred from it to the crust, to the core and back out again. For example, when the Earth slows down rotational energy is released and this could be transferred to the atmosphere or the core.

From his examination of the data Dr. Anderson believes that massive earthquakes release enough energy to affect the Chandler wobble and the Earth's rotation. There seems to be evidence of a 40 year cycle of the Chandler effect. The great earthquake of 1911 was near the Chandler maximum and so was the Assam event in 1950 and the Kamchatka event in 1952.

The efficiency of measurements now possible, of the tilt and bulge of the Earth, make predictions of earthquakes a more positive science.

EXPLORING THE MAGNETOSPHERE

Plans for a joint effort by NASA/SRC which would involve three satellites have been discussed in

London. The original project involved two satellites. These would have been put into a low circular orbit and the other in an elliptical orbit with an apogee varying between three to six Earth radii. Correlated measurements could thus be made.

Now thoughts are along the lines of three satellites. The third would be a UK vehicle unpropelled. The lower orbiting US satellite would be used to vary their separation.

There is considerable competition for space funds but there can be no doubt about the value of such missions. A great deal of work needs to be done at lower levels and the inter-level correlations have already shown their value.

The sunspot cycle seems to be directly related to tropospheric phenomena such as lightning, verticity rainfall and pressure.

SOVIET ACTIVITIES

The *Salyut 4* vehicle has been an unusually successful project. Apart from the long time occupation by cosmonauts, more than 60 days for the last pair, an enormous amount of data has been acquired.

A new method of spectral sounding was employed in the upper atmosphere using infra red and ultra violet techniques. This enables studies to be made of the distribution of water vapour, ozone and nitrous oxides. The optical observations were carried out by means of the OCT-1 orbital solar telescope. Also aboard were automatic installations for the growth of higher plants. The "beds" were sown with onions and peas. These have shown lavish development a month after launch.

The present parameters of *Salyut 4* are: Orbital period 91.3 min. Perigee 336km Apogee 362km and orbital inclination 51.6 degrees.

METEOR 2

Launched for meteorological studies, *Meteor 2* on board instruments include infra red experiments, an experimental optical-mechanical television scanning system and some rather complex radiometric equipment. The radiometric equipment is for the study of penetrating radiations in near Earth space.

The satellite has an advanced three axis system for the orientation of the satellite to the Earth. In addition there were the usual telemetry and other communications systems.

The parameters are: Orbital period 102.5 min. Perigee 872km. Apogee 903km and the inclination of the orbit 81.3 degrees.

ENVELOPE SHAPER

By E.F. FLINT



Two types of envelope shaper are found in commercial synthesisers: one gives control of attack and release times and is known as an "AR" envelope shaper: the other gives control of attack and release times and also allows, after the end of the attack period, a decay of variable rate to a preset level (sustain level). This type is known as an "ADSR" envelope shaper (Fig. 1) which has a far greater control potential and allows a wider range of effects to be produced.

The circuit comprises two exponential generators, a high impedance buffer stage, a Schmitt trigger and a unity gain differential adder.

CIRCUIT DESCRIPTION

The circuit diagram of the ADSR shaper is given in Fig. 2. When S1 is closed the emitter of TR1 rises to 8.5V, resulting in capacitor C1 charging through D1 and VR1 to approximately 8 volts, since about 0.5V is lost across D1. Half of the voltage on C1 is applied to the inverting input of IC1 via the divider R2 and R3.

F.E.T. BUFFER STAGE

This voltage is also applied to the gate of f.e.t. TR2, which has a high impedance and thus does not drain C1. The source of the f.e.t. connects onto VR3 whose slider position determines at what stage in the cycle the Schmitt trigger (TR3 and TR4) fires. This occurs when the base of TR3 reaches approximately 3V. When this happens TR4 is off and TR5 is held on with R8. Zener diode D3 (3.9V), D4 and VR4 provide a charging path for C2, the charging rate being determined by VR4.

A proportion of the voltage on C2, depending on the setting of VR5, is applied to the non-inverting input of IC1 via R11. Any voltage present at this input will result in a proportional reduction of the output voltage of IC1. The rate this reduction occurs is set by the decay control, and the level it reduces to by the sustain control.

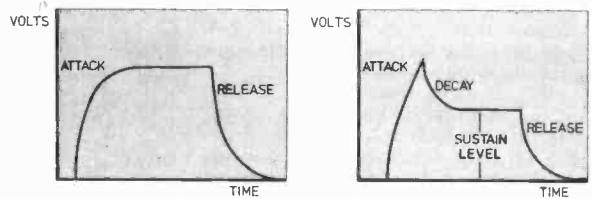


Fig. 1. "AR" and "ADSR" envelopes

COMPONENTS . . .

Resistors

R1	4.7k Ω	R5	270 Ω	R8	560 Ω
R2	1M Ω	R6	680 Ω	R9	4.7k Ω
R3	3.3M Ω	R7	560 Ω	R10-13	1M Ω
R4	390 Ω				
All $\frac{1}{4}$ W, 5% carbon					

Potentiometers

VR1, VR4	100k Ω lin.	VR5	1M Ω lin.
VR2	500k Ω dual ganged lin.		
VR3	10k Ω vert. mounting skeleton preset		

Capacitors

C1-2	10 μ F 16V elect.
------	-----------------------

Semiconductors

IC1	741 8 pin dil.
D1, 2, 4, 5	1N914
D3	BZY88 3.9V, 400mW, Zener
TR1, 3, 4, 5	2N3702, BC212 etc (any general purpose silicon or germanium pnp type)
TR2	2N3820 (p-channel f.e.t.).

Miscellaneous

S1	S.p.s.t. or trigger switch of keyboard
S2	D.p.s.t.
B1-2	PP9
	Veroboard $2\frac{1}{2} \times 4\frac{1}{2}$ in. (64 \times 115mm)
	8 pin dil. holder for IC1 (optional)

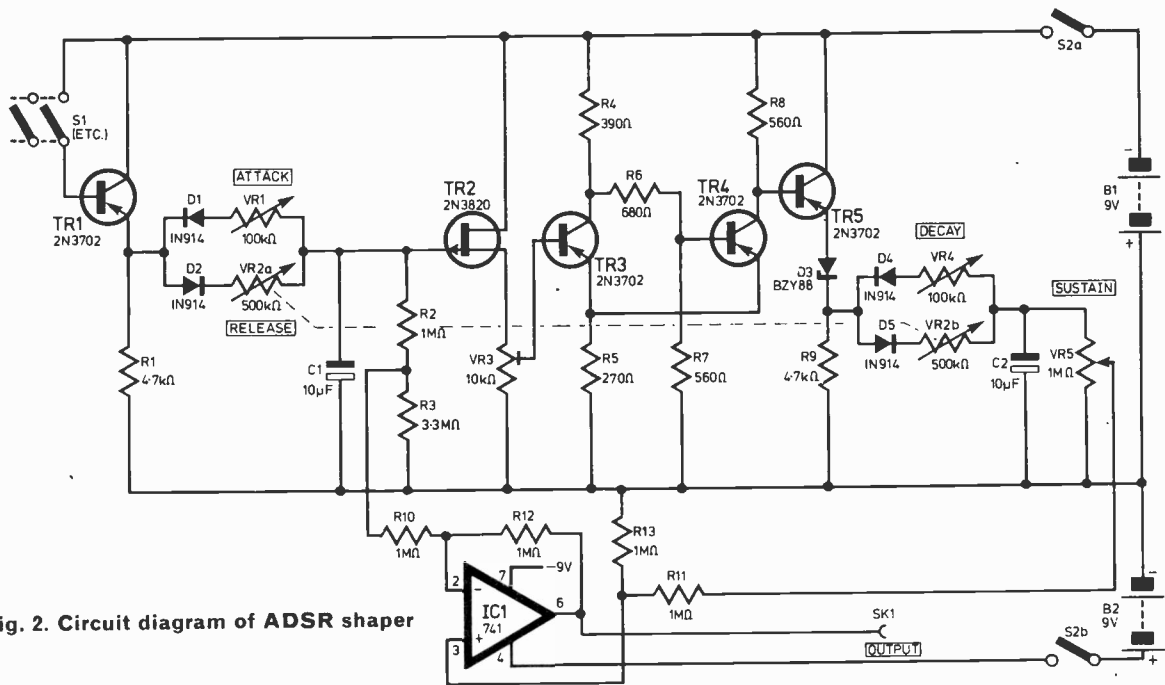


Fig. 2. Circuit diagram of ADSR shaper

RELEASE

When S1 is opened, TR1 switches off, the voltage on C1 falls, the Schmitt trigger switches off resulting in the voltage on C2 also falling. Capacitor C1 discharges through R1, D2 and VR2a; C2 through R9, D5 and VR2b. Thus both discharge with the same time constant.

CONSTRUCTION AND TESTING

A suitable Veroboard layout is given in Fig. 3. Note that pin 5 of the holder for IC1 should be snipped off so that it does not touch the copper strip connecting pin 4 to the negative voltage line. An oscilloscope or high resistance voltmeter is required to set VR3.

First monitor the voltage on C1 and ensure that it rises when S1 is closed. Now monitor the voltage on C2. Start with VR3 wiper at the ground end of its travel; close S1 and advance VR3 wiper until C2 starts to charge. If C2 is not at 0V with S1 open, change D3 for one of a higher Zener voltage.

If VR1 and VR4 are both set at minimum resistance the voltages on C1 and C2 will rise quickly.

USE WITH VOLTAGE CONTROLLED AMPLIFIERS


The module can be used with the VCA circuit published in PRACTICAL ELECTRONICS October '73. For this purpose connect a 4.7KΩ resistor between the output and ground, and connect the output to the input of the VCA.

ADSR SHAPER EFFECTS

Generally speaking, short attack and decay times will tend to give short, sharp, percussive sounding effects when used with, for instance, noise sources. With a little experimentation with the various controls, an ADSR shaper can be adjusted to closely simulate the envelopes produced by a wide variety of instruments (e.g. the piano, violin, guitar, etc) and thus adds a new dimension to a monophonic synthesiser.



Fig. 3. Veroboard and component layout details

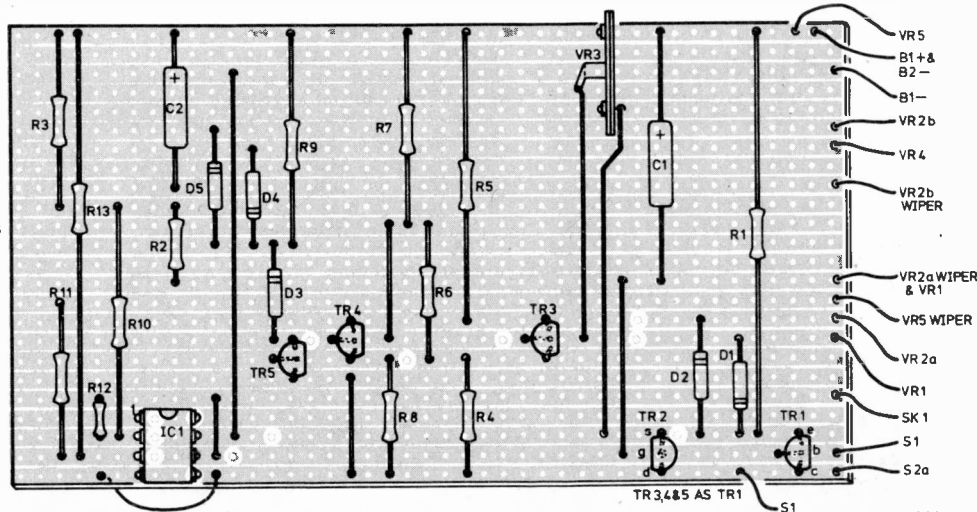

SEMICONDUCTOR UPDATE

By R.W. COLES

2416 MP9100
553 MP9200
554

MISTER SHIFTER

T.T.L. brought us the eight-bit shift register, and m.o.s. stretched this up to 128, and then an incredible 1024, bits per register during the last few years. A shift register 1024 bits long in a single dual in line package seemed pretty indredible to me, or anyway it did until the other day when I saw the preliminary data sheet on the new Intel 2416!

The 2416 is a charge-coupled m.o.s. device housed in a diminutive 18 pin package containing no fewer than 64 separate registers each 256 bits long, an amazing 16,384 bits in all! Even those who are numb to the customary excesses of m.o.s. technology will have to agree that getting that number of storage elements together on one piece of silicon is quite a revolution, and a revolution is just what its manufacturers want to start, because the 2416 is aimed at the bulk-storage end of the computer memory market, the traditional territory held by electro-mechanical devices such as magnetic tapes and discs.

If Intel are right, and the 2416 does start to replace its non-solid-state predecessors, it will be continuing a trend which began with the ousting of magnetic cores from computer work stores by the now familiar "Random-Access" m.o.s. chips. Semiconductor storage has already proved that it can be cheaper and more compact than rival magnetic devices at this high speed small capacity end of the market, but at first glance it seems a tall order to think of replacing things like disc-drives whose storage capacity is rated in Megabits. The key to success, as always, lies in the low price of semiconductor devices, and even at its introductory price of £30 each, the 2416 works out at only about 0.2 pence per bit.

The reason why the storage on the new chip is organised as 64 separate recirculating registers instead of one thumping great long one is not hard to find. Since shift register stores can only be accessed via their serial inputs and outputs, it would take an unacceptably long time to rotate the contents of a 16,384 bit device for access to a particular bit, even at high clock speeds. By splitting the store into separate loops of 256 bits each and using an address decoder to get at the separate registers,

average access time is reduced to less than 100 microseconds at a clock rate of 1 Mhz.

To prove that the 2416 really is a practical proposition Intel have put together a printed circuit board measuring 9in by 15in which has a storage capacity of 1,048,576 bits, the magic "Megabit" figure, which will have the manufacturers of the magnetic systems losing a lot of sleep if I'm any judge!

TIMELY QUADS

The 555 i.c. timer chip has been with us now for several years, and in that time it has become very popular, and has been used in many amateur projects. The popularity of this chip is well deserved because the 555 combines in one small package all the useful features one needs to build a wide range of ascillators and time delays, coupled with a wide availability and low price.

A dual version of the 555 was introduced, but not a lot was gained because the dual version came in a 14 pin d.i.l. instead of the little 8 pin "Mini-d.i.p." of the 555, but Signetics have now taken the cramming process a step further by putting four 555 type timers in a 16 pin d.i.l. which comes in two versions with type number 553 or 554.

To get four timers into such a restricted space, some reduction in available facilities has had to be made, the most fundamental being a reduction in the output drive capability. The original 555 can source or sink up to 200ma at its output pin, whereas the new quads come in two versions, one of which, the 553, sinks current, while the other, the 554, sources it, both at a reduced current level of up to 100ma. In addition, the 553/554 quads do not have the reset input which is available on the 555 to terminate an initiated time period, but since in many applications the reset is superfluous this is no loss.

The 553/554 have most of the other traditional timing features, such as good stability and wide range, and the duty cycle of all four timers can be varied by means of a single external control voltage.

The new quads really come into their own where sequential time periods are required, i.e. timer A triggers timer B, timer B triggers timer C and so on, making them ideal for such applications as traffic light

controllers, model train sequencers, etc.

DIAL STYLE

Two new i.c.s from Plessey demonstrate the way that large-scale integration can solve everyday problems as well as the more exotic problems of the mammoth computer industry.

The MP9100 and the MP9200 are m.o.s. i.c.s intended for use in push-button telephones, the first being a dial code generator and the second a store to enable a caller to recall previously entered numbers by pressing a single button.

The MP9100 comes in an 18 pin d.i.l. package, and has many novel features which make it attractive for amateur as well as professional applications. A four line binary code from a keyboard is accepted, up to twenty digits at a time, and from this input the MP9100 generates the necessary pulse sequences to drive the uniselectors of standard Post Office Strowger type exchanges. In addition to the digits 0 to 9, "Dial-tone-waits" may be keyed in anywhere in the number sequence, to force a pause in the output pulse sequence.

This unfamiliar-sounding operation is normally carried out by the telephone user himself, and is required, for example, when a private exchange has a dial-out facility. In situations like this it is necessary to dial, say 9, and then wait for the "outside-line" dialling tone before dialling in the normal way.

With the MP9100 there is no need to pause during the keying sequence, all that's necessary is to key in a "dial-tone-wait" after the 9, and then the rest of the number, the chip will send out the 9 and then wait until a dial-tone arrives before continuing.

The MP9200 is a sort of optional extra to go with the MP9100 in a telephone system, bringing with it a facility which did not exist at all with traditional instruments, namely the ability to store up to ten, separate, 22 digit telephone numbers, for later recall. Each complete number is recalled and dialled out via the MP9100, by pressing the appropriate single key.

A system using these chips could be the long awaited electronic replacement for the "little-black-book" for space-age batchelors!

1st GRADE COMPONENTS

FROM
MOTOROLA · MULLARD · SIGNETICS
MONSANTO · FERRANTI · GIM

We hold £250,000 worth of components and all items listed in this advertisement are ex-stock at the time of going to press • All products guaranteed • No minimum order charge

SIGNETICS 74 series TTL

N7400	14p	N7453	18p	N74148	£1-26
N7401	14p	N7454	18p	N74150	£2-45
N7402	14p	N7460	18p	N74151	£1-44
N7403	18p	N7470	36p	N74153	68p
N7404	18p	N7472	24p	N74154	£1-44
N7405	20p	N7473	36p	N74155	72p
N7406	41p	N7474	30p	N74156	72p
N7407	41p	N7475	54p	N74157	68p
N7408	41p	N7476	37p	N74158	68p
N7409	20p	N7480	50p	N74160	99p
N7410	15p	N7483	99p	N74161	99p
N7411	21p	N7485	£1-17	N74162	99p
N7413	29p	N7486	32p	N74163	99p
N7414	45p	N7490	63p	N74164	£1-26
N7416	27p	N7491	90p	N74165	£1-26
N7417	27p	N7492	63p	N74166	£1-26
N7420	15p	N7493	48p	N74170	£1-80
N7421	21p	N7494	90p	N74174	£1-13
N7426	23p	N7495	72p	N74175	81p
N7430	15p	N7496	£1-63	N74180	90p
N7432	23p	N74100	£1-35	N74181	£3-24
N7433	27p	N74107	32p	N74182	90p
N7437	27p	N74109	54p	N74190	£1-44
N7440	18p	N74116	£1-35	N74191	£1-44
N7442	70p	N74121	36p	N74192	£1-44
N7443	£1-35	N74122	50p	N74193	£1-44
N7444	£1-35	N74123	90p	N74194	£1-80
N7445	£1-35	N74125	43p	N74195	90p
N7446	£1-35	N74126	43p	N74198	£1-98
N7447	£1-12	N74128	45p	N74199	£1-80
N7448	£1-35	N74132	45p	N74221	90p
N7450	18p	N74145	90p	N74279	72p
N7451	18p	N74147	£1-44	N74298	£1-26

LINEAR ICs

SIGNETICS

LM301AV Ext. comp. operational amplifier	36p
LM307V Int. comp. operational amplifier	45p
MC1458V Dual Comp. operational amplifier	£1-80
NE510A Video amplifier	85p
*NE540L Audio power driver	£1-17
NE555V Timer	44p
NE556A Dual 555 14 pin	95p
NE561B Phase locked loop with A.M. demod.	£2-70
NE562B Phase locked loop with V.C.O.	£2-70
NE566V Phase locked loop function gen.	£1-50
*PA239A Dual low noise stereo pre-amp.	95p
µA741CV Op. amp.	42p
µA747CA Dual op. amp.	90p

MOTOROLA

MC1303L Dual stereo pre-amp.	£1-47
*MC1306P 1W audio amp.	64p
MC1304P F.M. multiplex stereo demodulator	£1-12
*MC1301P Stereo demodulator	£1-92
*MC1312P	£3-31
*MC1314P Quadrophonic decoder kit	£3-31
*MC1315P	£3-59
*MC1330P Low level video detector	67p
MC1496G Double balanced mixer	77p
MFC6040 Electronic attenuator	77p

G.I.M. CONSUMER CIRCUITS

AY-5-1224 12/24 hour digital clock circuit	£4-25
AY-5-3510 3 1/2 digit DVM circuit	£6-10
*AY-1-0212 Master tone generator	£5-55
*AY-1-5051 4 stage divider	£1-20
*AY-1-6721/5 5 stage divider	£1-30
*AY-1-6721/6 6 stage divider	£1-45
*AY-1-5050 7 stage divider	£1-75
C550 B digit calculator chip	£6-50
C500 B digit calculator chip	£3-25

SIGNETICS MEMORIES

N82506B 256 bit bipolar RAM	£4-50
2602B MOS 1024 bit static RAM	£3-00

FERRANTI ICs

ZN1040E Universal counter/display cct	£12-00
ZN1034E Precision timer cct	£2-99
ZN414 A.M. radio circuit	£1-00
Data and circuits on ZN414	5p

MOTOROLA

C-MOS	MC14002CP	19p	MC14003CP	£1-31
	MC14000CP	19p	MC14032CP	£1-70
	MC14001CP	19p	MC14034CP	£3-59
	MC14002CP	19p	MC14035CP	£1-34
	MC14006CP	£1-45	MC14038CP	£1-70
	MC14007CP	19p	MC14040CP	£1-21
	MC14008CP	£1-54	MC14042CP	£1-14
	MC14009CP	91p	MC14046CP	£1-67
	MC14010CP	91p	MC14049CP	53p
	MC14011CP	19p	MC14050CP	53p
	MC14012CP	19p	MC14071CP	£1-60
	MC14013CP	53p	MC14076CP	£1-19
	MC14014CP	£1-42	MC14081CP	19p
	MC14015CP	£1-17		
	MC14016CP	53p		
	MC14017CP	£1-13		
	MC14021CP	£1-17		
	MC14022CP	£1-54		
	MC14023CP	19p		
	MC14024CP	19p		
	MC14025CP	19p		
	MC14027CP	78p		

MC14500 series

MC14510CP	£1-26
MC14511CP	£1-95
MC14528CP	87p
MC14543CP	£2-00
MC14536CP	£2-90
MC14553CP	£4-07
MC14558CP	£1-79
MC14585CP	£1-46

COMPLETE LIST
AVAILABLE ON
MC14500 SERIES.
SEND S.A.E.

SPECIAL INTRODUCTORY OFFER

FREE! 10 G.I.M. IN4001 rectifier diodes with every order over £5. Clip this box and send with order to qualify. Offer ends 31 December, 1975.

MULLARD CONSUMER ICs

*TAA350A	£1-96
*TAA550	60p
TAA570	£2-19
TAA630	£3-80
*TAA700	£4-03
*TAD100	£1-35
*TBA480	£1-75
*TBA480Q	£2-84
*TBA500	£2-42
*TBA500Q	£2-52
*TBA510	£2-43
*TBA510Q	£2-23
*TBA520	£2-99
*TBA520Q	£2-08
*TBA530	£2-63
*TBA530Q	£2-62
*TBA540	£2-88
*TBA540Q	£2-97
*TBA550	£4-14
*TBA550Q	£4-23
*TBA560C	£4-14
*TBA560CQ	£4-23
*TBA570	£1-38
*TBA570Q	£1-47
*TBA673	£2-19
*TBA690	£2-23
*TBA690Q	£2-35
*TBA700	£1-84
*TBA700Q	£1-96
*TBA720AQ	£2-23
*TBA750	£2-23
*TBA750Q	£2-23
*TBA920	£3-68
*TBA920Q	£3-77
*TBA990Q	£3-77
*TCA160B	£2-84
*TCA160C	£1-93
*TCA270	£4-09
*TCA270	£4-19
*TCA290A	£2-76
*TCA420A	£1-96

MULLARD AUDIO AND RADIO MODULES

*LP1162 5W Audio Amp	£4-20
*LP1173 10W Audio Amp	£6-68
*LP1181 RF-IF	£3-94
*LP1183/2 Stereo Pre-amp Module	£4-12
*LP1184/2 Very low distortion pre-amp stereo	£7-18
*LP1185 FM IF Amplifier	£5-56
*LP1186 FM Tuner Module	£6-88
*LP1400 Stereo Decoder Module	£7-22

Data and suggested circuits available price 5p per Module.

TRANSISTORS, DIODES, ETC.

AC1276/1	12B	61p	AF121	20p	BC121	16p	BC268A	11p	*BC350A	12p
AD161/1	162	93p	AF125	14p	BC131C	16p	*BC307	11p	*BC350B	13p
AA119	9p	AF239	40p	*BC136	20p	*BC307A	12p	*BC351A	11p	
AA215	19p	BA102	16p	*BC137	20p	*BC307B	13p	*BC351B	13p	
AC122	19p	BA114	9p	*BC147	10p	*BC308	10p	*BC352	11p	
AC126	19p	BA154	8p	*BC148	8p	*BC308A	11p	*BC352A	11p	
AC127	18p	BA155	9p	*BC148B	12p	*BC308B	12p	*BC352B	13p	
AC128	13p	BA156	9p	*BC149	8p	*BC309	11p	*BC352L	10p	
AC153	8p	BA163	78p	*BC152	11p	*BC309A	14p	*BC388	28p	
AC175K	30p	BA182	18p	*BC158	11p	*BC317	14p	BC445	99p	
AC176	18p	BAV10	9p	*BC159	13p	*BC318B	13p	BC446	15p	
AC176/181	18p	BAW62	8p	*BC175	18p	*BC319	14p	BC447	15p	
AC187/188/1	65p	BAW63	35p	*BC176	18p	*BC320B	16p	BC448	15p	
AC188	30p	*BAX16	10p	*BC179	20p	*BC322	16p	BC449	16p	
AC191	30p	*BB105B	20p	*BC208A	10p	*BC327	15p	BC485	15p	
AC198	30p	*BB105G	19p	*BC214K	10p	*BC328	15p	BC486	15p	
AC202	16p	*BC107	11p	*BC237	11p	*BC332	15p	BC487	15p	
AD140	31p	*BC107A	13p	*BC237A	12p	*BC337	15p	BC488	17p	
AD149	45p	*BC108	13p	*BC237B	12p	*BC338	12p	BC489	17p	
AD162	36p	*BC108B	13p	*BC238	10p	*BC347	11p	*BC352	13p	
AD162	36p	*BC108C	13p	*BC238A	10p	*BC347B	12p	*BC351	11p	
AD162	36p	*BC109	15p	*BC238B	10p	*BC348	10p	BCX46	15p	
AD162	36p	*BC109B	17p	*BC238C	10p	*BC348A	11p	BCX47	15p	
AD162	36p	*BC109C	18p	*BC239	12p	*BC348B	10p	BCX48	16p	
AD162	36p	*BC113	10p	*BC239C	12p	*BC349	10p	BCY70	24p	
AD162	36p	*BC113	10p	*BC261	12p	*BC349B	10p	BCY71	24p	
AD162	36p	*BC115	16p	*BC261A	15p	*BC349L	9p	BCY72	22p	
						*BC350	11p	BD115	34p	



COMPONENTS

Terms of Business

Cash with order

Postage 20p U.K.

£1 Overseas

Dept. P.E., 5 Northfield Industrial Estate
Beresford Avenue, Wembley, Middx. HA0 1SD
Telephone 01-903 3168

PRICES EXCLUSIVE OF V.A.T. WHICH MUST
BE ADDED AS SHOWN BELOW

V.A.T. 8% except where marked thus * these items 25%



AUDIO FAIR '75

— The truest sounds you'll ever hear

Choose the right hi-fi and you're constantly rewarded. Choose the wrong hi-fi and you live with a costly mistake.

Audio '75 helps you arrive at the right buying decision, by bringing together under one roof, the finest equipment for you to see, hear and compare.

Audio Fair '75 lets you become acquainted with new products, new ideas and new refinements in your price range.

Don't miss Audio Fair '75 — it could save you a lot of money and anxiety.

Sponsored by **THE OBSERVER**

THE 1975 INTERNATIONAL AUDIO FESTIVAL & FAIR.

OLYMPIA LONDON 20th-26th OCTOBER.
Admission 75p (live-theatre show FREE)

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious men to move up into higher paid more secure jobs in the field of electronics — now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour T.V. Servicing
- Electronic Engineering & Maintenance
- Computer Engineering and Programming
- Radio, T.V. and Audio, Engineering & Servicing
- Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept. S20, Intertext House,
London SW8 4UJ
or telephone 01-622 9911 (all hours)

INTER NAVEX 75 REPORT

AN exhibition designed to cater for the ever expanding Audio and Visual Aids industry, Inter Navex 75 was held at Olympia from July 8 to 10. Most exhibitors were showing equipment in some way associated with education, but an enormous range of peripheral gear was also displayed.

PROJECTION T.V.

Trying to show a large number of people a t.v. programme, whether taped or live, can be difficult unless one happens to have a large number of monitors available. A new colour t.v. projection system launched by Advent should help solve a few problems from this point of view. Providing a $4\frac{1}{2} \times 5$ -ft. screen, the system can give comfortable viewing for as many as 40 people.

The system employs three separate "Light Guide" projection tubes each having its own optical system within the tube (thus eliminating the cleaning and alignment problems usually associated with this sort of equipment). A built-in cross-hatch generator allows for quick and easy convergence adjustment. With the growth of the video-recording industry, the system is sure to find popularity with schools and industrial training courses as a means of showing programmes to classes.

Still on the t.v. front, Grundig were displaying their new television (Color 2252) which features an extremely comprehensive ultrasonic control system, and a 110 degree in-line slot mask tube. The control system allows instantaneous selection of any channel, plus the usual volume, brilliance and colour contrast up-down controls. In addition a button is provided on the unit to allow one to cut the sound. Pressing it again returns the volume to its original level.

The service engineers should like it too, as plugging a gadget called a Diagnostic Adapter into the main printed circuit board, in theory reveals faulty modules in the set under breakdown conditions.

ANIMATED DISPLAYS


Have you ever wondered how those "animated" displays work which depict such things as flows in chemical processing plants, or the movement of fluids round the body? The displays themselves appear to have zones that are actually moving along. The effect is generated by using a special plastic film which, although transparent, is in fact composed of strips which are "sequentially polarized", i.e. the direction of polarisation is sequentially rotated strip after strip. If one views this through a rotating disk on which the angle of rotation of polarisation varies through 360 degrees around it, the dark zones formed when the two polarisations are at right angles to each other, will move down the film due to the sequential polarisation of the film. This causes the effect of apparent motion on the display.

Technamation had some impressive displays of charts of widely differing subject matter using the principle. The charts are easily made up with ordinary coloured self-adhesive plastic film and the special polarised



material (also self adhesive). The system is ideal for overhead projectors where the rotating wheel is merely placed between the chart and the projector lens to give the animation effect.

VIDEO CASSETTES

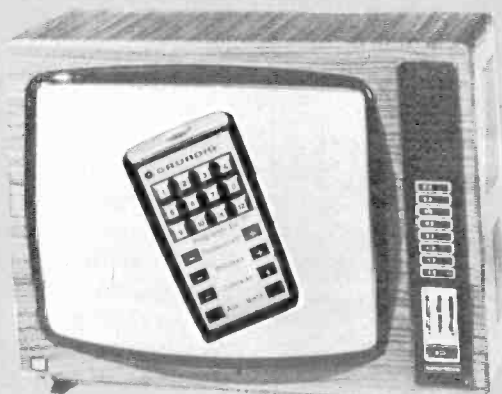A number of video cassette recorders were on display; amongst others the increasingly popular Phillips model, and surprisingly, an all British recorder with a sophisticated digital clock arrangement to allow accurate time switching (from Radio Rentals Contracts). ★




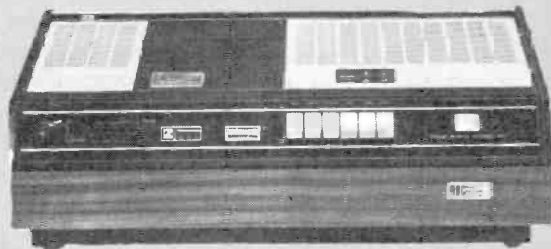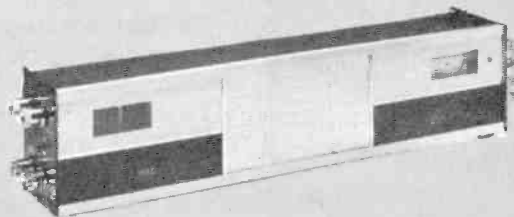Grundig's new ultrasonically controlled t.v.



The Radio Rentals Contracts vcr and timer






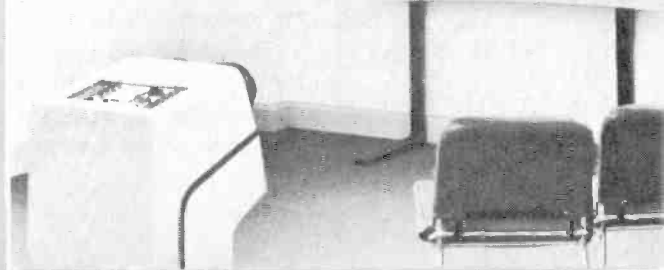
The Video-Beam colour t.v. projection system from Advent



MICROPROCESSORS

PART 1

By V. YATES*

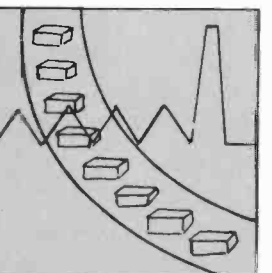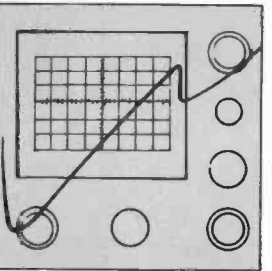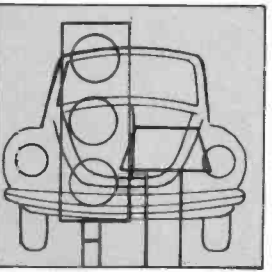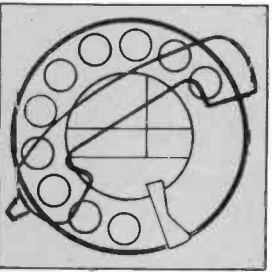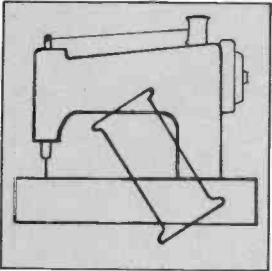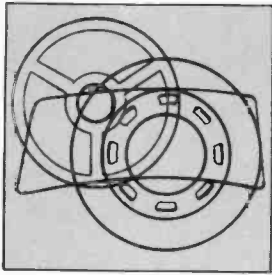

A word heard more and more in electronics today is "microprocessor". Although a comparatively recent innovation, this device is now finding its way into extremely diverse fields of application.

The word "microprocessor" describes a complex integrated circuit package which forms the heart of a digital processing system. The concept has been designed in order to provide a basic, flexible system which can be "programmed" to perform functions normally requiring large numbers of standard TTL devices. The essence of the system is flexibility however, and this is one of the many reasons for their rapid increase in popularity.

The automobile industry, for instance, has turned to microprocessors to cope with the task of optimising engine performance under all conditions, and with the price of fuel soaring, this is obviously a highly favourable feature. Microprocessor on-board diagnostic systems (i.e. letting the driver know where a fault has occurred) and "anti-skid" braking systems are among other applications in this field.

Domestic equipment will benefit by this new technology. Sewing machines and washing machines are examples of consumer products which will make use of microprocessors.

Electronic games will soon be (some already are in fact) incorporating microprocessors, which are bound to greatly increase their sophistication. An electronic bowling-alley exists now which uses a complex microprocessor system not only in scoring, but also in giving the right "feel" to the game as far as the roll of the "ball" and knocking the pins down.

These devices have already entered the field of electronic instrumentation and some of the more advanced types of oscilloscopes and signal generators already incorporate microprocessors.

Industry has been exploiting microprocessors in such fields as factory automation systems, machine tool control, electronic scales, conveyor-line control, robot manipulation of piece parts and component insertion. A microprocessor-based metal stretching machine can monitor operations performed on a piece of metal (via various A-D converters) commit them to a "memory" and then can duplicate the operation as many times as is required.

Traffic control is another area where microprocessors are bound to excel. The complex logic required to control an intricate main road intersection can be relatively easily carried out using a microprocessor.

Telephones and telephone systems will greatly benefit from the use of microprocessors. Research is being carried out at present to reduce the bandwidth necessary to transmit a telephone channel by having an "intelligent" transmitter and receiver system.

On a more practical basis a microprocessor controlled memory arrangement for a 'phone could be envisaged which would not only automatically dial a number when perhaps a name or symbol was entered, but also have facilities for redirecting calls to holiday addresses.

The above examples show how microprocessors can become the heart of intelligent systems, and also indicate their great flexibility.

The following article is concerned with the operation of the device itself and also some of the associated equipment.

THE microprocessor is one of the most exciting new products to be announced by semiconductor manufacturers and, even though microprocessor technology is still in its infancy, a bewildering choice of some 30 different types is now being offered to electronics design engineers. Before examining the microprocessor in depth, it is worth briefly looking at the development of the digital integrated circuit to see exactly how and why the microprocessor evolved.

DEVELOPMENT

In the early days, all digital integrated circuits were integrated copies of the discrete component circuitry they replaced. They were made up of resistors and bipolar transistors diffused into a single chip of silicon and only a very few individual logic elements (gates, flip flops, etc.) could be built into a package. Therefore, a typical digital system employing these circuits consisted of a very large number of separate packages.

As bipolar semiconductor technologists learned how to increase the complexity of the circuit in each package, integrated circuits employing *p*-channel, and more recently *n*-channel, m.o.s.f.e.t.s. were introduced. The mos technologies opened the way to integrating thousands of transistors on a single chip and enabled circuits of an unprecedented complexity to be contained in a single small package.

PROBLEMS

At this stage a very difficult problem arose. A great deal of money is needed to design and produce one complex l.s.i. (large scale integration) circuit, say, several tens of thousands or hundreds of thousands of pounds. If a large number of each particular integrated circuit is ultimately to be produced, the development cost can be spread over a sufficiently large number of units to become insignificant. In addition, it is important to note that semiconductor manufacture is essentially a mass production undertaking as the more integrated circuits of one type that can be produced the lower the production cost per unit.

The potential advantages of large scale integration were in danger of not being fully realised because it was found that as the complexity of an integrated circuit was increased the more specialised became its uses. What was needed was a universal digital integrated circuit that could be used in an unlimited number of different applications. That universal i.c. was developed and was called the microprocessor.

MICROPROCESSOR FUNDAMENTALS

Any conventional digital circuit consists of a number of gates and flip-flops connected in such a way as to perform the required function. Such a

circuit accepts digital inputs, performs some kind of processing and provides digital outputs. The function performed by many digital systems is determined by the way in which the various gates and flip-flops are interconnected.

PROGRAMMING

The microprocessor differs from the "hardwired" digital circuit discussed above in that the function performed is determined by a sequence of instructions which are stored in a memory in much the same way as a conventional digital computer. A change in the programme will alter the function carried out by the microprocessor.

PRACTICAL MICROPROCESSORS

To enable readers to more fully grasp the detail involved in microprocessor system design, one microprocessor—the Motorola M6800—will be described in some depth. Following this, basic details will be given on some other microprocessors which are available to industry.

The Motorola M6800 is a family of six integrated circuits that can be interconnected in a variety of different ways. The set comprises the microprocessor itself (MPU), a Random Access Memory (RAM), a Read Only Memory (ROM), a Peripheral Interface Adapter (PIA), an Asynchronous Communications Interface Adapter (ACIA) and a Low-speed Modem (LSM).

SECTIONS

All microprocessors can be divided into four basic sections: a memory, an input/output unit, a control unit and an arithmetic logic unit. The entire operation of such a system can be likened to a man adding up numbers written on a sheet of paper and writing the result on the same piece of paper.

In this analogy the sheet of paper becomes the peripheral device—the source and destination of the data to be processed. The man's eyes are the input system enabling the numbers to be read into the memory. The man's hand forms the output unit enabling the results of a calculation to be written down. The memory of both the man and machine perform the same function—both store the sequence of instructions (algorithm) for performing addition. The part of the brain which performs the addition can be likened to the arithmetic logic unit and the brain's co-ordination centre to the machine's control unit.

BYTES

In the Motorola microprocessor, instructions and alphanumeric data are represented by eight-bit

*Director, MOS Marketing, Europe. Motorola Inc.

GLOSSARY OF TERMS...

ACIA	Asynchronous Communications Interface Adapter	GROM	Control Read Only Memory	PROM	Programmable Read Only Memory
ACU	Arithmetic Logic Unit	DMA	Direct Memory Access	RAM	Random Access Memory
Byte	8-bit binary word	IRQ	Interrupt Request	RALU	Register, Arithmetic and Logic Unit
CCR	Condition Code Register	MPU	Microprocessor	ROM	Read Only Memory
		NMI	Non Maskable Interrupt	RTI	Return from Interrupt
		PIA	Peripheral Interface Adapter		

binary words, called bytes, which are stored in the memory. Each location within the memory has a numerical address (in the same way as houses in a street) and each location is capable of holding one byte of information.

With one byte (eight bits) it is possible to count up to the equivalent of 256 in decimal and, therefore, with one byte it is possible to individually address up to 256 memory locations. For the majority of microprocessor applications much greater memory capacity is required, therefore all the registers within the microprocessor concerned with addressing have a length of 16 bits.

This means that up to 65,536 separate locations within memory can be addressed (since a 16-bit binary word can have a value of up to this figure in decimal). Every location within memory will hold one 8-bit binary word, which means that the memory can consist of $65,536 \times 8 = 524,288$ bits. However, there is no need to have a memory as large as this to make the MPU function.

HEXIDECIMAL CODING

In binary, memory location number one would be referred to as location 0000000000000001, location number two would be 0000000000000010 and location 32,769 would be 1000000000000001, which, you will agree, is all rather tedious.

To avoid using such long strings of 1s and 0s, the hexadecimal code is often used when referring to numbers within the MPU, as conversion between binary and hexadecimal is easier to perform and more convenient than conversion between binary and decimal.

The conversion between binary and hexadecimal first involves splitting the binary word up into blocks of 4-bits as follows:

01101101 becomes 0110 1101

Table 1: Hexadecimal Code

Decimal	Binary	Hexadecimal
0	= 0000	= 0
1	= 0001	= 1
2	= 0010	= 2
3	= 0011	= 3
4	= 0100	= 4
5	= 0101	= 5
6	= 0110	= 6
7	= 0111	= 7
8	= 1000	= 8
9	= 1001	= 9
10	= 1010	= A
11	= 1011	= B
12	= 1100	= C
13	= 1101	= D
14	= 1110	= E
15	= 1111	= F

Each block of four bits has 16 possible values. In the decimal system we only have ten symbols to use (0 to 9) so, in the hexadecimal system, counting continues using letters of the alphabet as follows:

Returning to our earlier example, 01101101 in hexadecimal is equal to:

01101101
0110 1101
6 D (from Table 1)

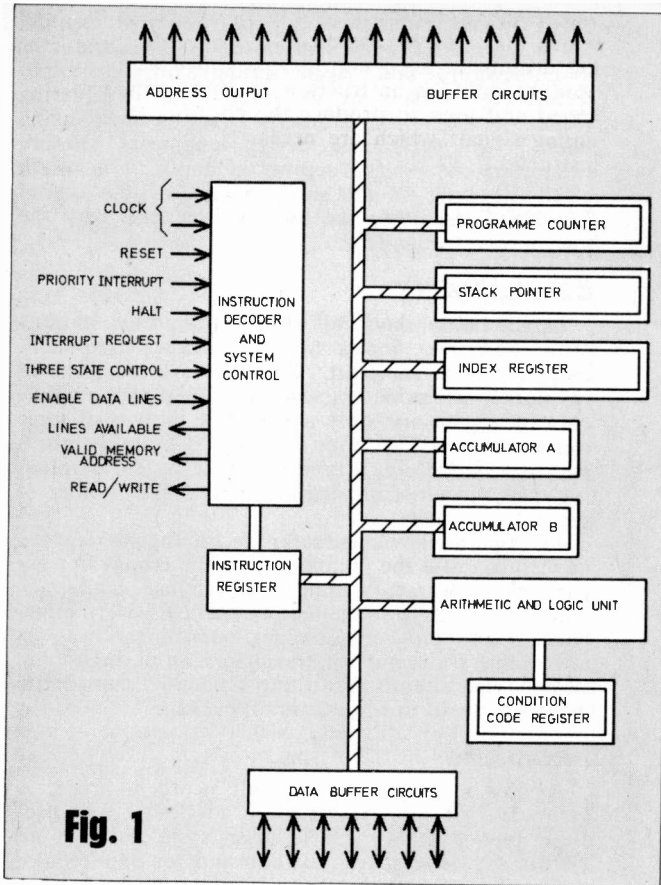


Fig. 1

Fig. 2

0001	86	Load accumulator A with
0002	05	the number 05 (Hex).
0003	B9	Add contents of accumulator
0004	00	A to the contents of the
0005	27	Memory location 0027.
0006	B7	Store the contents of accumulator
0007	00	A at memory
0008	28	location 0028
0027	03	Operand
0028	08	Result

In other words 01101101 is equivalent to 6D in hexadecimal. If you wish to work it out you will find that 6D in hexadecimal is equivalent to 109 in decimal.

Using the hexadecimal system is confusing at first. Numbers like CF2C do not seem to make much sense. However, after a little practice working in 16s with the hexadecimal system, it becomes as familiar as working in tens.

SIMPLIFIED VIEW

A much simplified block diagram of the Motorola microprocessor is shown in Fig. 1. The blocks labelled programme counter, stack pointer and index register are all registers capable of holding 2 bytes (16 bits) which are used to hold the addresses of instructions or data stored in the memory.

Accumulators A and B are each 1 byte registers which are primarily used to hold data for and from the arithmetic logic unit. The instruction register is used to hold an instruction (1 byte) which is decoded and used to produce the control, routing and timing signals which are necessary to carry out the instruction.

EXAMPLE SEQUENCE

With the aid of Fig. 1 and Fig. 2 it is possible to trace a complete sequence of events within the microprocessor.

Fig. 2 shows a number of memory locations containing instructions which are to be performed by the microprocessor. For convenience the instructions are shown in hexadecimal instead of binary. To the left of the memory locations are the four digit hexadecimal memory location addresses. On the right of the memory locations are the plain English explanations of the instructions stored in the memory locations.

The programme counter is set to the address of the first instruction in the programme which is situated at memory location 0001. This is done by loading the programme counter with the number 0001.

The address in the programme counter is sent to the memory along the address bus and, as a result, the contents of memory location 0001 are sent to the MPU along the data bus to be stored in the instruction register. The programme counter is now incremented by 1 to 0002.

The content of the instruction register (86—the instruction to load accumulator A with data represented by the byte in the next memory location) is decoded and the control system causes the byte addressed by the programme counter to be transferred along the data bus from memory to accumulator A in the MPU. The programme counter is again incremented (now holds 0003) and accumulator A holds the numerical value 05 (hexadecimal).

NEXT INSTRUCTION

The MPU fetches the next instruction from memory that is addressed by the programme. This is B9—an instruction which causes the numerical value contained in accumulator A to be added to the content of the memory location specified in the following two bytes of the instruction and to place the result of the addition in accumulator A. The programme counter is incremented to 0004.

The MPU fetches the first byte of the second operand address (00) from memory location 0004, increments the programme counter to 0005 and fetches the second byte of the address (27) from location 0005. The programme counter is incremented to 0006.

The MPU now holds the first operand (05) in accumulator A, holds the address 0027, which is the location of the second operand, and has the instruction to add (B9) in the instruction register. The MPU fetches the data at address 0027 (the numerical value 03), adds it to accumulator A and stores the result in accumulator A.

Having completed instruction B9, the MPU fetches the next instruction (B7) addressed by the programme counter and then increments the programme counter. Instruction B7 will cause the

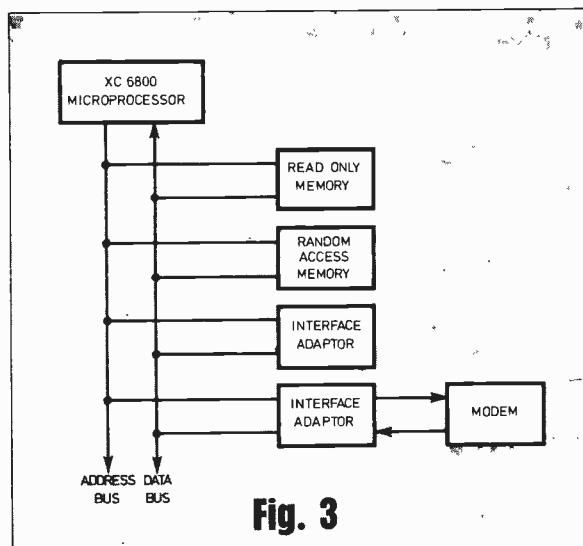


Fig. 3

contents of accumulator A (the result of the addition of 05 and 03) to be transferred to the location specified by the next two bytes. These two bytes 00 and 28 are fetched one at a time by the MPU and the numerical value 08 is transferred to memory location 0028.

The sequence of instructions we have just traced caused the numbers 03 and 05 to be added together and the result to be stored in a known memory location.

The purpose of the various registers and counters in the MPU are summarised below.

Programme counter: The programme counter holds a two byte address and is used by the MPU to proceed through a programme step-by-step.

Stack pointer: A section of the memory is called "the stack". Each new byte to be stored in the stack will be stored at a location which is on top of all the other bytes which have previously been stored in the stack. Reading information from the stack is done one byte at a time starting with the byte that is on the top. Sometimes the stack is described as a "last in first out memory". The stack pointer is a register which contains a two byte address that specifies the vacant location on top of the stack. The use of the stack will be discussed later.


Index register: The index register is also used to store a two byte address and its use will be discussed in a later section of the article.

Accumulators: The two accumulators are used primarily to hold operands for, and results from, the arithmetic logic unit (ALU).

Condition code register: The condition code register (CCR) provides extra information on the results of operation performed by the ALU. It enables the MPU to be programmed to make decisions. When the ALU performs an operation the result of that operation is stored in accumulator A, accumulator B or the memory.

Additionally, various flip-flops (or bits) may be set in the CCR to indicate that, for instance, the result is negative, the result is zero or that overflow occurred. Two bits are set aside to indicate if a carry (or half carry) has occurred and one bit is called the "Interrupt Mask Bit"—more about that later.

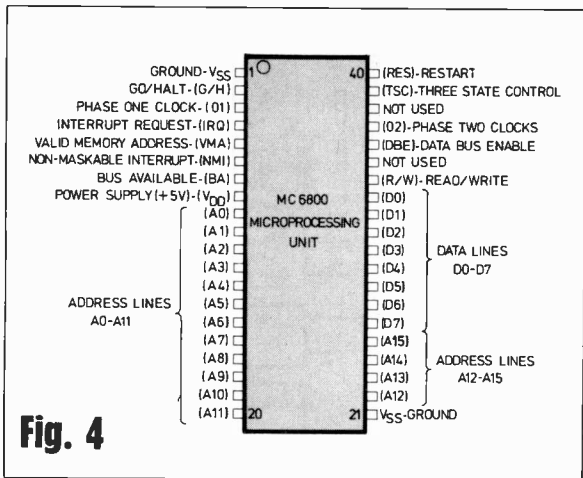It is possible, under programme control, to examine (or test) the state of individual bits within



the $\overline{\text{HALT}}$ input is at logic "0" (machine halted) or the three-state control input is high (DMA), the MPU read/write output will be put into a high-impedance state.

Pin 5. Valid memory address (VMA): When the MPU has placed a memory address on the address bus, the VMA output goes to logic "1". This signal is used for control purposes.

Pin 36. Data bus enable: When this input is in the logic "0" state the data bus driver circuits are held in a high impedance state for DMA applications. Normally this input is driven by the clock. Additionally, the data bus drivers within the MPU are also disabled internally every time the MPU goes into the read condition.

Pin 7. Highway available: This output is normally in the logic "0" state unless either the $\overline{\text{HALT}}$ line is at logic "0" (halt machine) or the MPU has just executed an instruction to "wait." In both of these two conditions the Highway available output will go to logic "1"—indicating to other circuits the MPU has stopped and that the address highway is vacant, and all "three-state" output drivers will be put in their high impedance condition. The MPU is removed from the "wait" state when a valid interrupt occurs (see later).

the CCR following an operation. For example, bit N in the CCR is set to "1" if the result of an operation is negative. A programmer could say:

- A. Carry out instructions 1, 2 and 3.
- B. Instruction 4. Does bit N = 1? (bit test). If N = 0 return to instruction 1. If N = 1 proceed with instruction 5. In other words, the sequence of instructions being carried out by the machine was made dependent on the sign of the result through the use of a CCR bit test.

Fig.3 shows the main interconnections in a typical MPU system. The address bus is 16-bits wide and provides the means by which the MPU selects a particular memory location or output device. The data bus is 8-bits wide and is bi-directional. That is, the buffers in each integrated circuit connected to the data bus can function as either inputs or outputs.

The MPU itself is housed in a 40-pin dual-in-line package as shown in Fig. 4. In all, 26 of these pins are taken up by the previously discussed address and data highways, and the +5V and common lines of the power supply. Another two are used by the 1MHz two-phase clock generator needed by the system. The functions of the remaining pins are as follows:

Pin 2. HALT: When this input is taken to logic "0" all activity in the machine is stopped.

Pin 39. Three-state control: A logic "1" input on this pin will cause all of the address bus buffers and the Read/Write line (pin 34) to go into a high impedance state—in other words turning them off. External equipment can now use the address bus to directly access the memory without involving the MPU in the process (Direct Memory Access—DMA).

Pin 34. Read/Write: The MPU has two basic modes of operation—read and write. In the read mode the MPU is in a condition to accept information from either the memory or from input/output devices. In the write mode the MPU will send out information to either the memory or the input/output circuits. The MPU informs the rest of the system that it is in the read mode by applying logic "1" to the read/write output.

When the MPU is in the write mode the read/write output is at logic "0". Normally, when the MPU is in the standby mode (waiting for work) the read/write output will be logic "1". When either

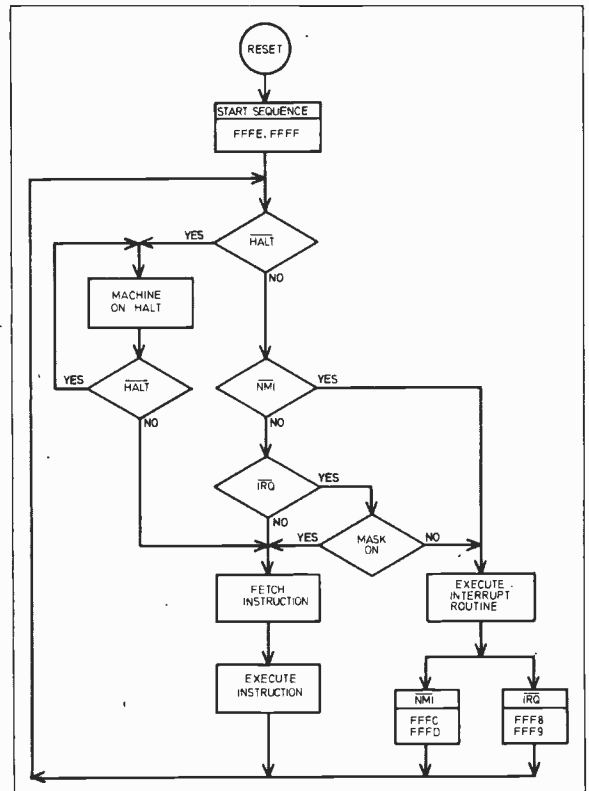


Fig. 5

Pin 4. Interrupt request (IRQ): A logic "0" on the IRQ input will cause the following sequence of events:

1. The MPU will complete the instruction it is currently processing.
2. The Interrupt mask bit in the condition code register is examined. If this bit is "1" it means that the processor is processing a previously requested interrupt and the MPU will, therefore, ignore the new interrupt request until it has completed all the instructions in the interrupt programme it is currently servicing. If the Interrupt mask bit is at logic "0", the MPU enters an interrupt routine.
3. The contents of the index register, programme counter, accumulators and the condition code register are stored in the memory in the previously mentioned stack.
4. The MPU now responds to the interrupt request (having ensured that all the information it was processing has been safely stored away) by setting the mask interrupt bit to logic "1". This ensures that the MPU cannot respond to any new interrupt request.
5. The MPU now addresses a known location in memory where the first instruction for the interrupt service programme will have been previously stored.
6. The last instruction in the interrupt programme will be RTI (Return from Interrupt).
7. On receipt of this instruction—having completed the interrupt programme—the MPU recalls the data it stored away in the stack and continues from where it left off.

Pin 40. Reset: Whenever the MPU is first switched on, or after a power failure, the MPU has to go through an initialisation routine before it can commence operations. A positive going pulse on the Reset input causes the processor to begin its restart sequence. During the sequence the interrupt mask bit in the code condition register is set to "1" to prevent interruption. At the end of the sequence the MPU will output a known address to provide the MPU with the address of the first instruction to be performed.

Pin 6. Non maskable interrupt (NMI): The application of a logic "0" on this input begins a chain of events which is very similar to the interrupt request sequence, but which has one major difference. The NMI input is used to inform the MPU that a task awaits which has the highest possible priority.

The MPU, on receipt of the NMI signal, enters the interrupt routine without regard for the condition of the interrupt mask bit. However, the MPU completes its present instruction and stores the contents of the various registers away in the stack before starting the high priority programme.

At the end of this programme, when it encounters the RTI instruction, the MPU will return to its previous task.

The whole operation of the MPU is summarised in the flow chart of Fig. 5.

Next month:

The language and programming of the MPU

APRS 75

Some of the highlights from the Association of Professional Recording Studios exhibition held recently in London.

THE APRS exhibition offered its usual spectacular display of state-of-the-art professional audio equipment. Although one would expect the general poor economic situation to severely affect development in this field, if it has it was not obvious at the exhibition. With over 70 stands almost every aspect of sound processing was covered.

C.R.T. LEVEL MONITORING

An impressive display of various forms of program level monitoring equipment was given by the Danish firm N.T.P. One such device uses a conventional colour t.v. monitor as a multi-channel display unit. Keeping an eye on a large number of programme meters (as is required in multi-track recording) can be extremely difficult. This unit, however, makes the process much easier by bringing all the channels together on a t.v. screen. Channels may be grouped together and/or colour coded for easy identification. They have even incorporated an overload arrangement which causes the overload portion on the display to go red.

DELAY UNIT

H.H. Electronics, makers of high quality power amplifiers, have recently added a portable echo delay unit to their range. It is capable of single or multiple echoes with the facility of variable time delay. Working on a tape-loop system with a fixed recording and moveable replay head, it can achieve continuously variable delays (or times between echoes) of between 100 and 720ms. The unit also incorporates a compressor to allow a large range of input levels to be accommodated.

AUDIO PROCESSING

Audio & Design were demonstrating their range of audio processing equipment. An interesting new product in this line is a band-selective compressor. A normal compressor attenuates the whole programme signal when operating. With this unit, however, one can select a particular frequency band and only operate on that. It can, for instance, act as an extremely effective "de-esser" (a device which removes high level sibilants thus reducing the possibility of associated distortion). It will no doubt find popularity in the disc-cutting field.

TAPE RECORDERS

The new Studio 8 tape recorder from Ferrograph (Wayne Kerr were responsible for most of the development work) was on display. It has been well received by the professional recording field and such features as state-of-the-art logic systems, fibre optics, and choice of editing facilities no doubt help it along in this respect.

Leavers-Rich have introduced a new $\frac{1}{4}$ inch tape recorder known as the Proline 2000. Servo controls in its capstan and tape tensioning systems as well as optoelectronic techniques are a few of its prominent features. Also from Leavers-Rich is a cassette transport system aimed at Broadcasting, Studio, and Educational use.

FREE ENTRY COMPETITION

...Practical Electronics & Plessey
issue a challenge

over
£500!


HOW INVENTIVE ARE YOU?

PRIZES

- ★ 1st Prize £250
- ★ 2nd Prize £100
- ★ 3rd Prize £50

Fifty Other Prizes for
Runners Up

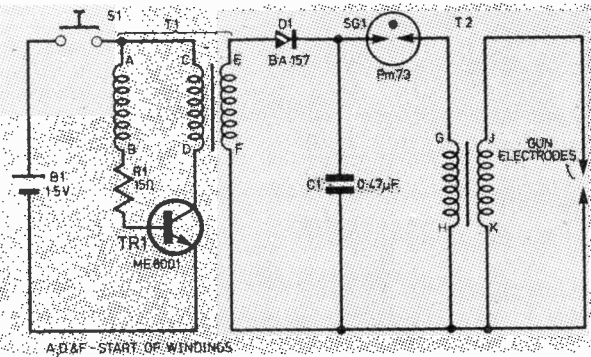- ★ 25 Magispark Gas Ignitors
- ★ 25 One-Year Subscriptions
to Practical Electronics



When you saw the Portable Gas Ignitor in the July issue of *Practical Electronics* did you immediately think of other applications for this particular circuit? Can you suggest any ways in which the device could be put to other uses in industry or in the home? If so, here's an opportunity to put your ideas to good advantage. And if you missed the July issue, not to worry—the circuit and the essentials of its operation are given on this page.

In association with the Plessey Company, we present this fascinating challenge and offer prizes totalling over £500 in value for really practicable and ingenious ideas. And a chance, possibly, to see your idea in production! So get that grey matter plus your know-now of electronics working, and meet our challenge right away!

HOW TO ENTER

The contest is for practical applications of the Portable Gas Ignitor Circuit—either utilising the original circuitry or including design modifications to increase its scope.

To remind you, the operation of the Ignitor is:

The application of a high voltage across a pair of electrodes produces an electric field in the gas between them, this leads to ionisation and breakdown of the gas producing a spark across the gap. When the circuit of the ignitor is completed current flows from a battery into a transistor oscillator circuit and the resultant pulses of energy charge a capacitor to approximately 300 volts. The capacitor is then discharged by an electronic switch into the primary of an H.T. transformer which produces the necessary voltage to cause the sparks at the electrode. The design enables a steady stream of sparks at 10,000 V to be generated with complete safety and employing only a single 1.5V dry cell as the power source.

Entries must be written/drawn clearly on one side of plain paper with the entrant's full name and address at the top of every sheet. Each entry to comprise:

- (a) a brief summary of the idea (about 25 words)
- (b) any such further lucid description, drawings, sketches or circuit diagrams you consider the judges may need to form the best appraisal of your idea. **DO NOT** send actual models.

Each entry must have a properly completed entry coupon firmly affixed to the **BACK** of the summary.

SECOND CHANCE!

The closing date is Monday October 13, 1975, to allow plenty of time for you to obtain the second entry coupon from our next issue and post two different ideas in one envelope if you wish.

RULES AND CONDITIONS

There is no entry fee nor limit to the number of entries a reader may submit but each entry must be accompanied by a proper printed entry coupon, cut from PRACTICAL ELECTRONICS, and must bear the entrant's own full name and address. Entries will also be accepted from groups—in which case the entry coupon must be completed by one of the group and the names and addresses of all the other members listed on a separate piece of paper affixed, with the entry coupon, to the back of the summary.

All accepted entries will be examined by a panel of expert judges, including Plessey engineers and the Editor of *Practical Electronics*, and assessed on (a) originality of the idea, (b) technical merit, (c) practicability, (d) economic viability, (e) market potential. The prizes will be awarded for the best entries in order of merit. No entrant may win more than one award. In the event of the same idea being submitted by two or more entrants, presentation of the entry (clarity, best expression, etc) will decide such winner(s) or winning order.

In the event that the judges consider there are not enough entries of a sufficiently high standard, the Editor reserves the right not to award any prize(s) at his discretion.

Entries arriving after closing date will not be considered, nor will any received that are illegible, not wholly understandable, are not accompanied by a properly completed entry coupon or in any other way do not comply exactly with the instructions and rules.

No responsibility can be accepted for entries lost or delayed in the post or otherwise; proof of posting will not be accepted as proof of receipt. No entries can be returned.

Copyright of all entries shall become the property of IPC Magazines Ltd., publishers of *Practical Electronics*. Ideas submitted may be used or adapted by the competition sponsors for production or other commercial use. Where appropriate, additional payment will be automatically negotiated with the entrant. Entries will not be published prior to evaluation in order to comply with legal safeguards.

Decisions of the judges, and of the Editor in all other matters affecting the competition, will be final and legally binding. No correspondence will be entered into nor interviews granted.

Winners will be notified by post and brief details of winning entries published later in *Practical Electronics*. The Editor

reserves the right to amend and/or re-draw any sketches or diagrams of prizewinning entries for publication purposes.

The contest is open to all readers in Great Britain, Northern Ireland, Eire, Channel Isles and Isle of Man except employees of IPC Magazines Ltd., the Printers of Practical Electronics, and the Plessey Co. Ltd. and its subsidiary companies; and the families of all such employees.

Post your entry in a sealed envelope to: Ignitor Application Contest, PRACTICAL ELECTRONICS, 136 LONG ACRE, LONDON, WC2E 9QP, to arrive not later than October 13, 1975 the closing date.

FREE ENTRY COUPON

NAME (Mr/Mrs/Miss)
(Block Letters)

ADDRESS

Telephone Number, if any

I certify that

* delete clause NOT applicable

* (a) this entry is of my own original idea and has not been copied from any other source.

* (b) this entry is made on behalf of the group members listed, and is our own original idea not copied from any other source.

(c) this idea has not been published—or offered for publication elsewhere.

I/We agree to abide by the rules and conditions, and to accept the published result as final and legally binding.

SIGNED



BOOK REVIEWS

HI-FI FOR THE ENTHUSIAST

By M. L. Gayford

Published by Pitman

235 pages, 222 m.m. × 140 m.m. Price £5.00

THIS is the second edition of a work first published in 1971 and the contents have been expanded to take in developments such as quadraphonic sound.

This book ranges over the whole gamut of equipment from input to output. But first it deals with the *end*—to which all these items are but the *means*. The first chapter explains simply the nature of human speech and hearing; the human vocal and auditory systems are examined; psycho-acoustical factors such as perception of pitch and sound pressure, the need for two or more channels for exercise of our full psycho-acoustical powers, stereophonic and quadraphonic systems, room acoustics and placement of loudspeakers are discussed.

The bulk of the book is concerned with hardware, and sets out to serve the needs of would-be purchasers of audio equipment who lack any extensive technical knowledge by indicating the features and performance that should be looked for when selecting complete units or kits for home construction, to form a sound reproduction system.

The description of f.m. broadcasting and reception and the typical f.m. tuner specification given are more suited to the technically knowledgeable; to the non-technical person the terms and expressions will be largely meaningless, although a nodding acquaintance as gained through a study of this book will possibly help when

reading manufacturers' sales literature or listening to salesmen.

This point also applies to the sections dealing with other programme input sources and with amplifiers. A few typical circuits for commercial tuners and amplifiers are included, but component values are omitted—at the instance of the proprietors, no doubt.

The two chapters dealing with loudspeakers and enclosures are likely to be particularly valuable to the lay reader and merit close study. This final link is perhaps the most important, and choice and selection of loudspeakers must be based very considerably on personal preferences.

Recommendations are included on planning a complete high-quality system. There are diagrams of commonly used audio connectors and cables. A Glossary of Hi Fi and radio terms, lists of recommended books, and a list of gramophone test records are useful appendages to this book.

J.V.

A GUIDE TO AMATEUR RADIO (16th Ed)

By Pat Hawker, G3VA

Published by Radio Society of Great Britain.

112 pages, 248 m.m. × 182 m.m. Price 90p.

THIS latest edition is as welcome as all its fore-runners. Those who are not addicts of amateur radio will find this an illuminating read. It could convert them before the final page is reached.

No one is better able to "sell" home radio than Pat Hawker—an ardent activist in the game and an acknowledged authority in the related technical matters.



Those who already have a hankering after radio communication will find the answers to all their immediate queries in this publication.

The recent changes in UK amateur regulations are covered. Guidance on the latest developments in technique and equipment is given, and a new chapter on popular amateur radio equipment is incorporated.

PE NEXT MONTH...

ELECTRONIC TUNING FORK

Completely simplifies the tuning of musical instrument by providing 84 frequency-accurate tones which can be instantly switch selected. All beat note adjustments are clearly visible on a l.e.d. monitor

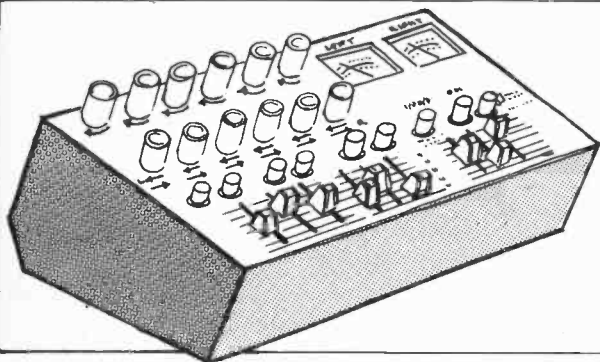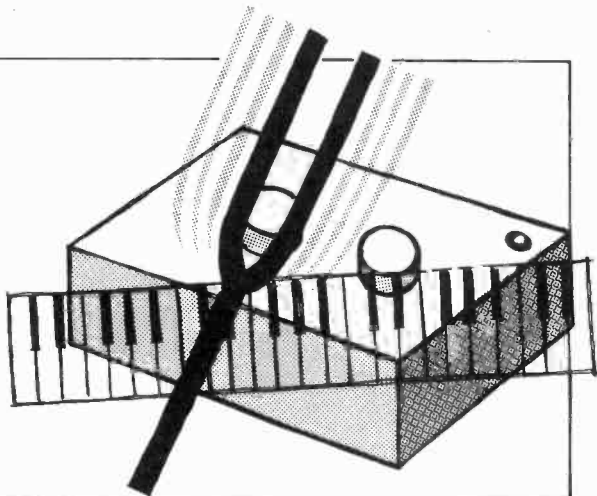

MINIMIX 6

A compact low cost, battery operated, six-channel stereo mixer with such features as: panning controls, comprehensive headphone monitoring facilities, twin VU meters, and prefade monitoring on all channels. Although designed with synthesizers (such as the P.E. Minisonic) in mind, the unit is nevertheless capable of a much wider range of applications

ENGINE ANALYSER

This month's article contains full constructional details for building the dwell/tachometer unit complete with calibration procedures

**Ensure YOUR
future issues**



To
(Name of Newsagent)

Please reserve/deliver the NOVEMBER issue of Practical Electronics (35p), on sale October 10 and continue every month until further notice.

NAME

ADDRESS

.....

PRACTICAL

ELECTRONICS

NOVEMBER ISSUE ON SALE OCTOBER 10, 1975—PRICE 35p

CONSTANT CURRENT LOAD

By D. W. LLOYD

An easily adjusted load for p.s.u.s and amplifiers

WHEN experimenting, particularly with power units and amplifiers, a constant current load is often required. The unit described here was designed to serve just that purpose being easily adjusted by a potentiometer to give the required loading effect.

The load is constant for a.c. as well as d.c. inputs within the range of 4–30V. As the unit is not polarity conscious it may be used with d.c. circuits either way round, that is, the positive and negative terminals on the circuit being loaded may be reversed and the constant current load will still work correctly. The a.c. loading capability of the unit makes it ideal for checking transformers by simply connecting the load across the secondaries and adjusting the unit to draw from the required current.

REFERENCE LEVEL

To enable a constant current to be generated a reference level must be obtained which should be very stable, this can be obtained from across a Zener diode fed with a series resistor from the supply being loaded. For good constant current stability this method will not produce the best results, because as the input voltage varies so the current through the Zener will vary which will in turn vary the Zener level very slightly. So for the best results the supply to the Zener should be stabilised. This starts to increase the cost of the unit so to overcome this problem it was decided that the only way to ensure a constant voltage to supply the reference Zener was to use an internal battery.

The battery chosen to do the job was a 9V type which fed a 3.3V Zener diode which meant dropping 6V across a resistor. As batteries are being used it is essential that the current to the reference Zener is kept to a minimum so a current of 2.5mA was chosen. This gave a low drain on the battery.

A switch is incorporated into the unit to switch the battery out, this will save the battery and a life of 12 months can be reckoned on.

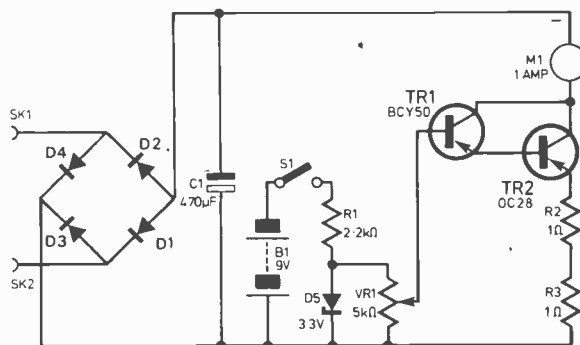


Fig. 1. Circuit of Constant Current Load

COMPONENTS . . .

Resistors

- R1 2.2kΩ ½W
- R2-R3 1Ω 2.5W vitreous wirewound (2 off)

Capacitor

- C1 470μF elect. 100V

Rectifiers

- D1-D4 Bridge Rectifier (1A)

Potentiometer

- VR1 5kΩ

Transistors

- TR1 BCY50
- TR2 OC28

Meter

- M1 1A d.c.

Diode

- D5 3.3V 400mW Zener

Sockets

- 2mm terminal sockets (2 off)

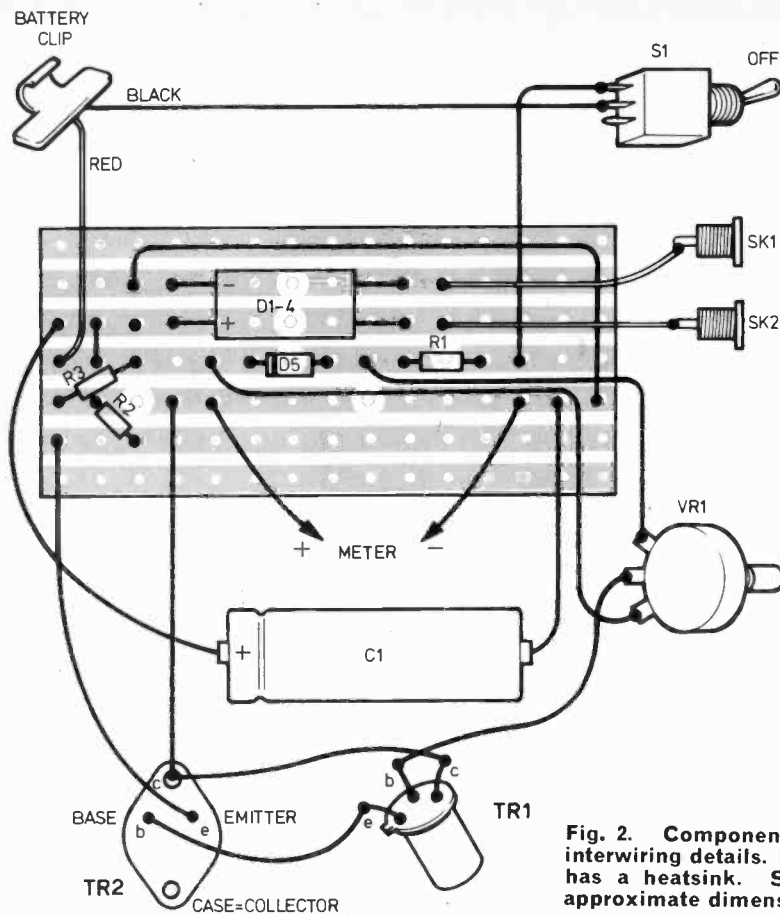


Fig. 2. Component layout and interwiring details. Note that TR2 has a heatsink. See photo for approximate dimensions

The circuit operation is very simple and with the transistor specified a constant current of 1A can be drawn from a circuit of 25V this can be increased

by paralleling another power transistor with the one already in circuit, this will enable the voltage to be doubled at the same current or the voltage can remain at a maximum of 25V and the current may be doubled, see Fig. 1.

Keeping to the very basics in this design has enabled the price of the unit to be very low and if all of the components were to be purchased new then the total cost will not exceed £5.


ZENER RESISTOR VALUE

The Zener resistor value is calculated to draw from the battery a current of only 2.5mA. Which can be switched off when the unit is not in use. To enable the unit to be fairly universal the load is formed by arranging TR2 to take a constant current of 1A maximum. With a gain of only 20 for the transistor used, a base current of 50mA would be required which is far too much current for B1 to supply. A further transistor connected to form a super-alpha pair gave an overall gain equal to the gain of TR1 times the gain of TR2 that is, 50×20 so that an input of only 1mA will give 1A which is well within the capabilities of the small battery.

EMITTER LOAD

As the unit represents a load which draws 1A resistance is necessary in the emitter of TR2 to enable the circuit to function properly. R2 and R3 are each 1ohm, which will develop an emitter voltage drop of 2V. With 2V at the emitter of TR2 a base

continued on page 831

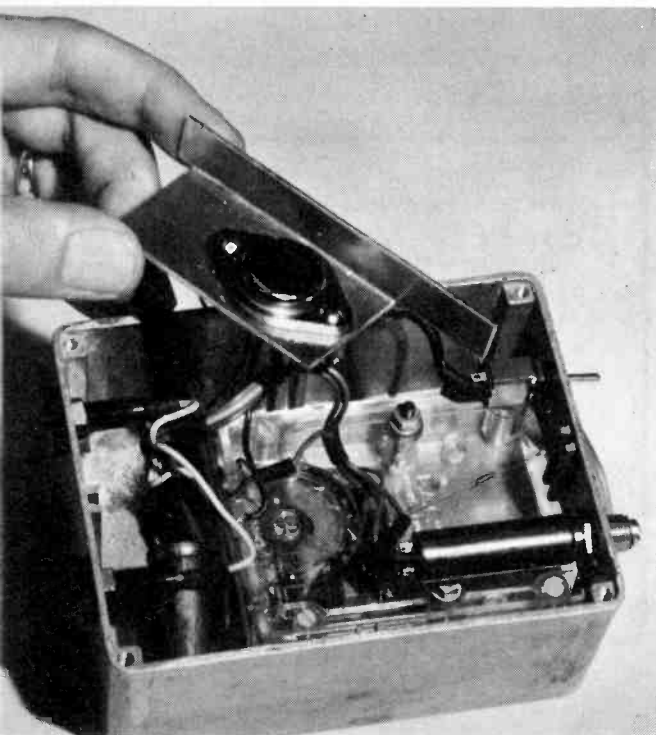

TEACH=IN 76

**DO YOU KNOW
SOMEONE WHO
WOULD LIKE
TO LEARN
ELECTRONICS?**

Next month Everyday Electronics (a companion magazine to P.E.) starts a new series designed to teach the beginner the basics of electronics



**PLUS! FREE INSIDE...
DATA CHART-COMPONENTS
IDENTIFIED AND EXPLAINED**


PLUS! *These easy to build projects*
TREMULO·TRANSISTOR TESTER· DOORBELL BLEEPER

PLUS! *All the regular features
including our monthly look
at careers in Electronics!*

Don't miss out... Place your order NOW!

everyday electronics

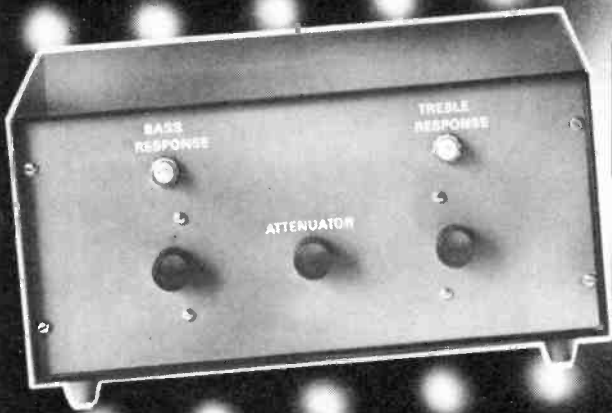OCTOBER ISSUE
ON SALE FRIDAY
SEPTEMBER 19
PRICE 30p



LIGHT MODULATION UNIT

By S.R. BEECHING

A Two-channel Sound to Light Converter

THE main features of this Light Modulation Unit are its simplicity, reliability and accurate transformation of audio input to audio modulated 50Hz 240V mains current. Before any description of the circuit it is felt that the choice of a two-channel unit as opposed to three should be defended. The two-channel light unit described provides good separation of the bass and treble frequencies without the use of complex filters, which may require high stability low tolerance components.

With a larger number of three-channel systems it is often difficult to discern which channel is which, as they all appear to be behaving similarly. With the middle channel removed the difference between the two channels can be readily seen with the added advantage of the electronics being simpler.

ISOLATING TRANSFORMER

The circuit is shown in Fig. 1. The input is isolated by a speaker isolating transformer rated at 5W with a series resistor incorporated to prevent damage both from and to high powered amplifiers. (This can be increased in case of doubt).

The input sensitivity is about 1V r.m.s. and a suitable signal can be obtained from the speaker outputs of the power amplifier.

The common line of the electronics is mains neutral, and it must be borne in mind that since the live side of the supply can easily be made common by a simple mistake in the wiring extreme care must be taken. The signal is taken from T2 secondary to VR1 which acts as an input attenuator. Attenuators VR2 and VR3 then adjust the treble and bass light levels respectively.

CIRCUIT DESCRIPTION

TR1 and TR2 and associated components form the filter stages. The bass filter operates in the "Miller Integrator" fashion with C7 connected between the collector and base of TR2.

Capacitor C2 and the input impedance of the stage comprising TR1, R3 and R4 form the high pass

COMPONENTS . . .

Resistors

R1 75Ω	R7 2.2kΩ	R13 1kΩ
R2 68Ω	R8 22kΩ	R14 470Ω
R3 22kΩ	R9 2.2kΩ	R15 470Ω
R4 2.2kΩ	R10 1kΩ	R16 220kΩ
R5 1kΩ	R11 68Ω	R17 220kΩ
R6 68Ω	R12 1kΩ	

All resistors $\frac{1}{2}$ W 10% carbon

Potentiometers

VR1-VR3 10kΩ 1in. plastic slider controls—see text (R.S. Components)

Capacitors

C1 1000μF 25V elect.
C2 4.7nF plastic or ceramic
C3 4.7nF plastic or ceramic
C4 0.1μF plastic or ceramic
C5 10μF 6V elect.
C6 22μF elect.
C7 0.1μF plastic or ceramic
C8 0.1μF plastic or ceramic
C9 470μF 10V elect.
C10 22μF 25V elect.
C11 22μF 25V elect.
C12 0.1μF 400V polyester
C13 0.1μF 400V polyester

Semiconductors

TR1-TR2	BC107
D1-D4	IN4001 (or bridge rect.)
D5-D6	IN4148
CSR1-CSR2	BRY39
CSR3-CSR4	40430

Miscellaneous

T1	240V to 12V 100mA (R.S. Components)
T2	Universal speaker isolating transformer (R.S. Components)
L1-L2	3A t.v. chokes (R.S. Components)
Case	—see text, wire and solder etc.

filter for the treble channel. Capacitor C3 causes the response of the filter to fall off at higher frequencies to prevent spurious responses to spikes generated in the triac circuitry.

If it is found that instruments with predominantly h.f. output are not causing the treble channel to respond, C3 may be reduced; but the above point must be borne in mind.

SILICON CONTROLLED SWITCHES

The filter outputs pass via C4 and C8 to the triac drive circuitry. This consists of two BRY39 silicon controlled switches (CSR 1 and 2) which conduct giving a pulse of current to the triac gate when their anode (pin 4) is driven more positive than their anode gate (pin 3). Resistors R14 and R15 load the BRY39 and hold the triac gate to the common line to prevent spurious triggering.

During continuous switching, the voltage across C10 and C11 will reduce. Gate current to the triacs will then be determined by the value of R12 and R13. These are therefore chosen to be able to provide this current since if they are too large the triacs may fail to trigger under conditions of continuous firing.

DIODES

Diodes D5 and D6 prevent C4 and C8 from charging up with the firing current of the SCS's. On negative signals the diodes conduct so that positive signals can be passed through the capacitors into the gates of the SCS's.

R.F. CHOKES

The r.f. chokes have been incorporated in the circuit to reduce any r.f.i. from the triacs. Three amp types were used in the prototype but if the full current capacity of the triacs is to be exploited these should be uprated to 6A.

MONITORING

Each channel drives a neon bulb to allow monitoring of the state of the display bulbs if they are remote from the unit. The neons also provide a means of checking that the displays are connected, since they will glow dimly without the displays due to the small current passed through C12 and C13. As soon as the displays are in circuit the neons will no longer glow as the small leakage current will then be shunted via the displays to neutral.

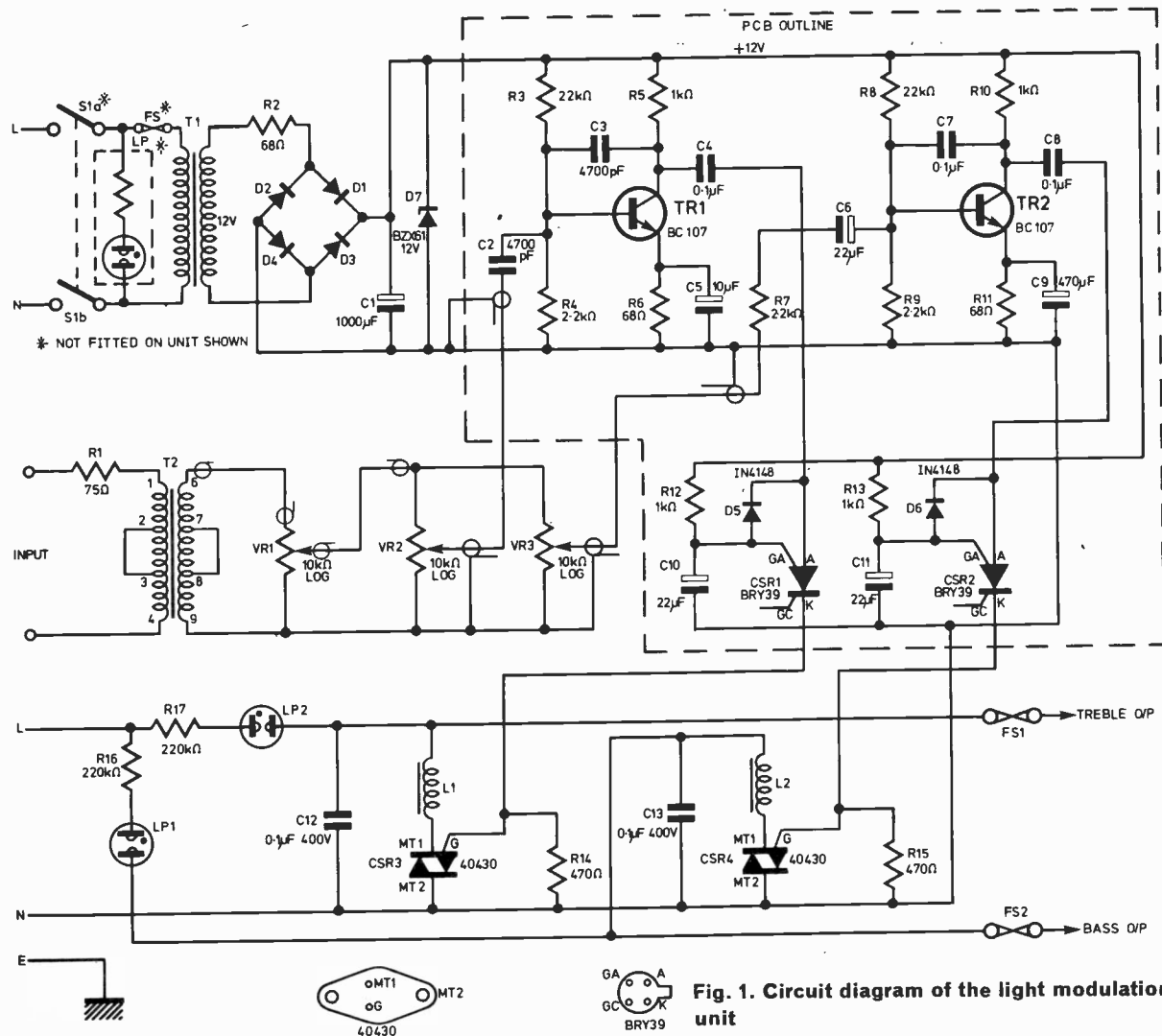


Fig. 1. Circuit diagram of the light modulation unit

CIRCUIT BOARD DETAILS


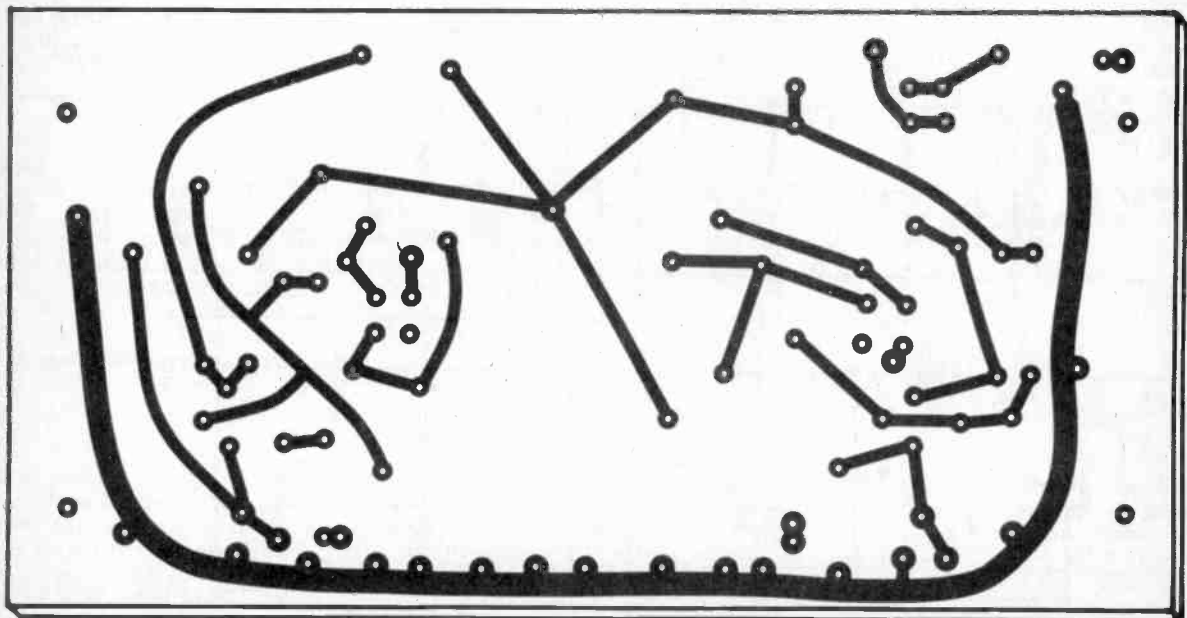
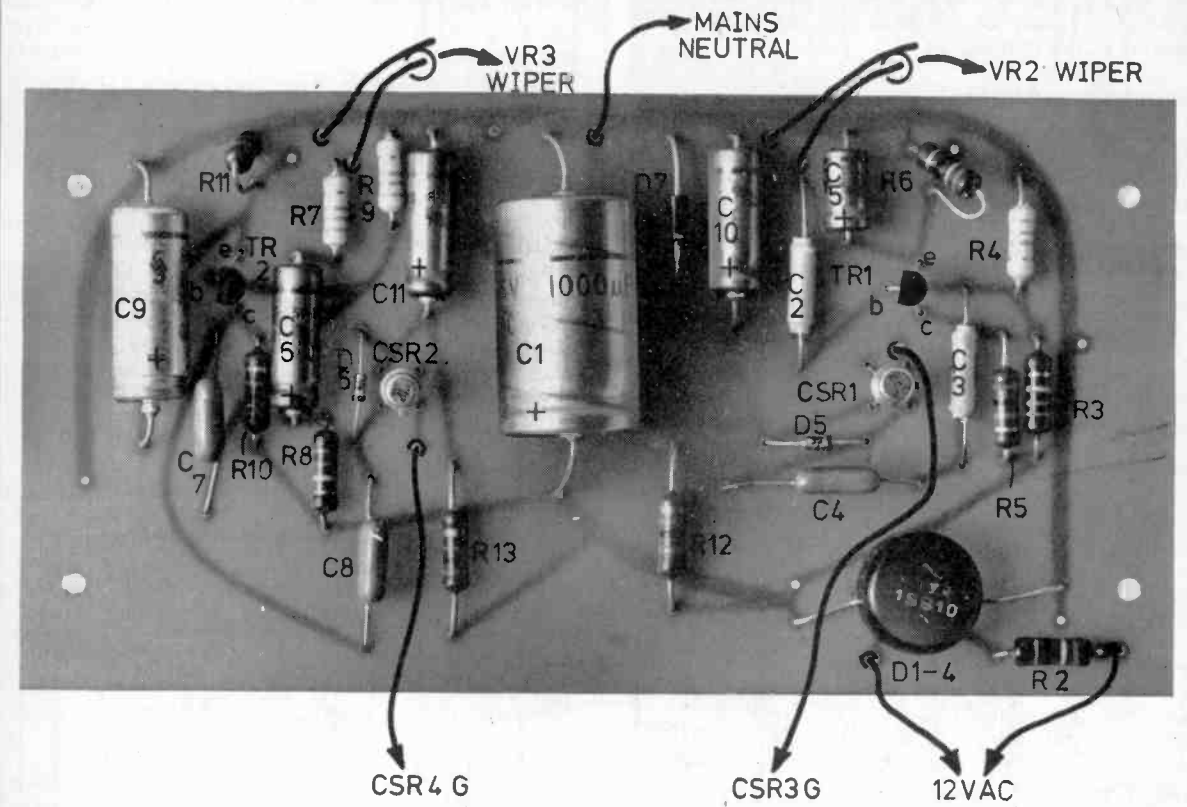


Fig. 2. Component layout and printed circuit board master (full-size)

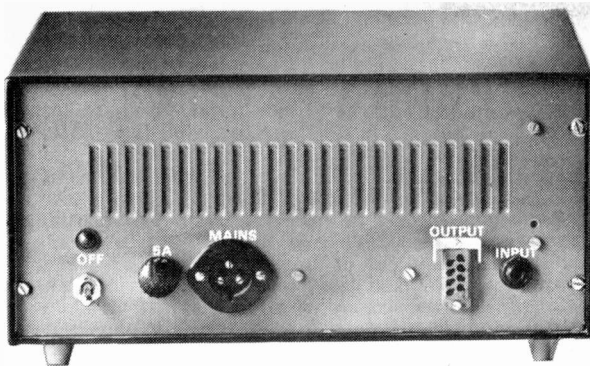

CONSTRUCTION

The printed circuit board master and component layout is given in Fig. 2.

During construction remember that a *live* chassis technique is used and so extreme care must be taken. A wooden or metal case may be used but the metal case must be earthed and the electronics and wiring insulated from it. The output sockets should be 5A or 13A and insulated from the case. For the input attenuators R.S. slider controls are recommended as they are plastic. If rotary potentiometers are used however, they should have nylon shafts. Care must be taken with the wiring of these components as screened cable is used; *the screening is live and must be insulated from the metal case.*

Wiring details of the unit are shown in Fig. 3. The common (neutral) line is wired from the input to the triacs which are mounted on a heatsink. The cable used should be able to withstand the current (6A) and be adequately insulated. The live mains is wired straight to the output sockets and to the bulbs; it is also wired to the neons and transformer. Both triacs are mounted on the same heatsink. They are insulated by mica washers and as a further precaution it is recommended that the heatsink is insulated from the chassis by pillars or nylon nuts and bolts.

Resistors R14 and R15 are mounted across the triac pins. If wiring to the pins is difficult then insulated mounting tags can be used. The chokes can be mounted between the triac cases and the fuseholders.

DISPLAYS

Finally a word about the displays that have been used. Small wattage bulbs (15W-60W) produce a very rapid 'flashy' effect, whilst the higher wattage bulbs (100W-500W) are much slower due to filament heating time (thermal inertia). Two 500W spots with colour change wheels focussed on the same white wall will produce an ever-changing colour, which varies according to the colour wheel, and the amount of colour mix dependent on the quantities of bass and treble.

At the other end of the scale large numbers of 15W pygmy bulbs in a matrix can produce an exciting display. An enhanced effect can be obtained by wiring the bulbs in fixed patterns which can be switched by relays as well as driven by the light unit. One similar to this was built into an old t.v. cabinet with frosted glass and used as a mobile discotheque. There are no limitations to the display technique and the constructor will be able to spend many hours devising his own. ★

CONSTANT CURRENT LOAD

continued from page 826

voltage of $2V + V_{be}$ of TR2 + V_{be} of TR1 must be present at TR1 base. The V_{be} of an average transistor is around the 0.3V level so the base voltage of TR1 = $2V \pm 0.3V + 0.3V = 2.6V$. This determines the Zener level which must not fall below this level and so a Zener of 3.3V was used to ensure adequate forward bias at a loading of 1A.

To allow the level to be adjusted the voltage to the base of TR1 is obtained from the wiper of VR1 which is connected across the Zener diode thus as the potentiometer is rotated anticlockwise the voltage at the base of TR1 decreases until zero is reached. At this point the transistor is reverse biased and so cut off and represents no load. As VR1 is rotated the transistors become forward biased and will conduct more and more until the full load of 1A is reached. The dissipation of TR2 must be kept to around the 30W region and so the maximum voltage applied must be limited to 30V. It is connected to a heat sink in direct contact with the diecast box.

BRIDGE CIRCUIT

How does the unit act as a constant load for both a.c. and d.c. circuits. If we consider the unit being used with a d.c. supply first of all it can be seen that with a positive supply at socket SK1 and negative at SK2 then conduction will be via D4 and D1. If the d.c. supply was reversed that is with the negative line at SK1 and the positive at point SK2 then the negative supply to the transistors will be provided by D2 conducting and the positive will be supplied via D3 once again ensuring that the polarity of the supply is correct for the load circuit.

Diodes arranged in this form are said to be in a bridge network and they will provide a rectifying circuit for an a.c. supply that may be connected across the input sockets. After some smoothing from C1 a d.c. signal is obtained and supplied to the transistors as described before. The ammeter connected in series with the super-alpha circuit so that the load current is displayed continuously.

CONSTRUCTION

Constructional layout is determined by the meter used. In the prototype unit an edge meter was used. Of course terminals can be arranged so that an external meter may be used or an Avometer. The transistor TR2 is mounted onto a heatsink, using insulators to ensure that there is no electrical connection to the case. This can be checked by connecting an ohmmeter across the transistor and the heatsink the reading obtained should be infinity.

Vero board has been used for the circuit assembly and requires cutting in the places indicated in Fig. 2.

TESTING

With the reference voltage switched on check with a voltmeter that the voltage across the Zener diode is greater than 2.6V. With an ammeter in series with the unit connect it to a d.c. supply of approximately 15V and adjust VR1. Both meters should coincide over the full range of the unit. Now reverse the leads from the power supply and check that the meters still track together. Remove the test meter and the unit is now ready for use. ★



BOOK REVIEWS

THE STORY OF RADIO (8 Volumes)

By W. M. Dalton

Published by Adam Hilger

Each Vol.: 150 pages, 215 mm × 150 mm

Price £4.50

THE STORY OF RADIO is intended to extend to eight volumes in all. To date Volumes 1, 2 and 3 have been published.

Each volume is a first-class hardback production, with many line diagrams and photographs of technical and historical interest. The price of each volume makes this add up to a formidable total for the complete work. One is inclined to question the publishing policy: few readers are likely to be interested only in part of the overall story, so there seems little justification for separating the work into so many volumes. Fewer volumes with more pages should have resulted in some economy in binding materials resulting therefore, one would expect, in a lower selling price.

What kind of story? Well this certainly is no romanticised tale, nor is it a ponderous exposition of scientific and technical development. The author has settled very successfully it seems (judging from these first three volumes) on a mid course and has produced a well researched account of pertinent scientific and technical discovery and invention before and since the advent of radio, or wireless telegraphy to use the more meaningful term.

In this story personalities are treated in a formal fashion, being introduced summarily (by surname alone) as their contributions to knowledge or invention are described. The objective and crisp style of presentation adopted undoubtedly avoids unnecessary distractions to and flow of the essential story. Yet the lack of a bibliography or an appendix giving key facts or source references for the work of these pioneers—some are very well-known figures, some lesser known—will be rather a disappointment to the more inquisitive student of technical history wishing to explore in more detail some of these discoveries, experiments, or inventions. This apart, this work should prove to be popular and provides a useful record of the technical landmarks in the history of radio. Those old enough will certainly relish wallowing in nostalgia, which will be further enlivened by the excellent photographs of equipment of bygone days and once-familiar circuits which are reproduced, together with many other line diagrams, in these volumes.

Vol. 1. How Radio Began

The first chapter retells concisely the principal known events in the long history of magnetism and electricity, the second describes the first practical and commercial uses of electricity—for signalling and for power. These two chapters are a prelude to the real story: this opens with accounts of the earliest investigations into electromagnetic radiation and first experiments in wireless telegraphy, the subsequent successes, and the kind of apparatus used. The final chapter covers the thermionic valve and the earliest valve circuits in the period up to the outbreak of the First World War.

Vol. 2. Everyone An Amateur

The story is taken up from the post World War 1 years. There are details of wartime uses and developments: especially notable—radiotelephony in aircraft

and directional finding. Amateurs had to wait until 1920 before restrictions on their activities were lifted. Then followed a period of great activity—technical and political. Both amateurs and commercial interests play their part in spurring along new improved circuits and new devices for transmitting and receiving radio signals. The amateurs' vital part is faithfully recorded, not least the agitation which finally lead to the creation of a broadcasting service, then to be followed by an epidemic of home construction of receiving sets. The important distinction between the large host of set constructors and the smaller band of transmitting and experimenting amateurs is made clear in the final chapter which deals with the rediscovery of short waves by amateurs and the ultimate usurping of these waves by government and commercial bodies.

Vol. 3. The World Starts To Listen

This volume is chiefly devoted to the rapid and extensive technical advances in commercial receivers during the period 1925-1930. The coming of mass-production, the emergence of many new types of valves and new circuit designs based on them. Developments in broadcasting techniques; the loudspeaker and the gramophone pickup.


The final chapter entitled "Telephones, Talkies and Television" introduces these and other new fields (as distinct from radio) where "radio-techniques" were also being applied at this time. What is outlined is in fact the dawn of "electronics" but that word has yet to enter *The Story of Radio*. Doubtless it will though, in some later volume of this immensely enjoyable, technically informative and (no doubt to the majority of present-day readers) quite revealing account of those past years of brilliant and exciting endeavour and achievement, which include a period when the amateur held a proud position as a pioneer and frequently set the pace for the professionals.

F.E.B.

PUBLISHER'S ANNOUNCEMENT

The contents of PRACTICAL ELECTRONICS is fully protected by international copyright and reproduction of it in any form is prohibited without our consent.

With effect from this announcement any application for permission to reproduce, or use our material in any way or part of, must be made to the Editor. Under no circumstances will permission be given to reproduce material in a similar or competitive publication, without payment. No application need be made in the case of a private constructor, constructing one item for his/her own enjoyment and interest.

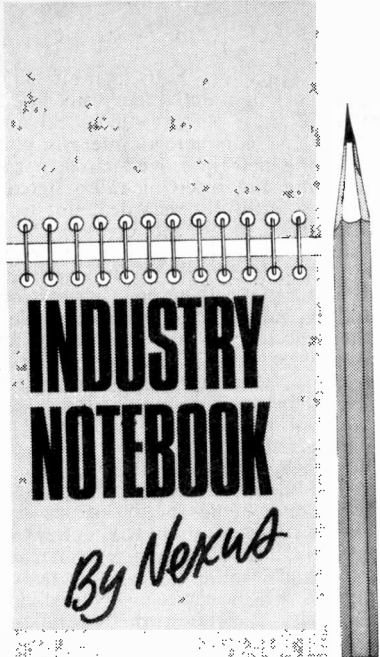

INDUSTRY NOTEBOOK

By Nexus

BOOM OR BUST?

There has never been a more confusing time for industry watchers like myself. From all sides one hears gloom and doom and there is some truth in these stories. But not the whole truth. Consumer electronics has taken its biggest knock for years as forecast by myself and others earlier this year. Deliveries of colour t.v. sets have dropped severely following the imposition of higher taxes. But for the same reason monochrome sales have had a boost. Hi-fi and radio sales were also down.

But what is the norm? Might it not be the case that this year's sales are normal and last year's exceptional? Growth is bound to slow down once the market is saturated.

Well managed companies are not suffering. Those in professional electronics who also have a good export business are at their wits end to recruit staff and maintain deliveries. I have often stated in this column that in times of stress the little company with a flexible response to market changes has a better chance of survival. The big companies are, however, still performing not only well but admirably.

Plessey reports almost £320 million in sales, £27.3 million pre-tax profits, £40 million export. Not bad. Chairman Sir John Clark also commented on Britain's membership of the EEC and how it affected Plessey. In 1972 exports to EEC countries were £3 million. They are now £9 million.

With a courageous look in his crystal ball, Sir John suggests they may well be £40 million by 1979. Consumer components and Garrard record players have been hit by the

consumer market slump but with overall trade figures so healthy, every Plessey business will survive and most are clearly prospering.

With sales of £1,500 million, profits up by £23 million to a record £174 million GEC is flourishing. Capital investment for the year was £78 million and this might have been more but for £85 million snatched in taxes by the Government.

With heavy dependence on the consumer market, Thorn Electrical pushed sales up to £807 million but all the headlines concentrated on the profit slump. Profit tumbled by £8.7 million. Sounds an awful lot until you realise that the "huge" drop still left Thorn with £65.4 million profit in what is officially described as "difficult market conditions".

SOLDIERING ON

Then there's Racal, soldiering on through boom, depression, recession. This company has again made record profits and has thus successfully achieved 20 consecutive years of record growth and record profits.

With still only £50 million turnover and 6,000 people employed Racal remains a medium sized company but is world leader in what it does best. The formation of Racal-Tacticom Ltd. in July brought together Racal-Mobilcal and Racal-BCC to form easily the strongest military manpack and mobile radio supplier in the world with a customer list of well over 100 armies.

More than 70 per cent of all Racal sales were overseas last year and in ground radio equipment Racal exported more than all its UK competitors added together. In 1970 Racal turned over £14.3 million with £1.7 million profit. Latest figures are £50.2 million with £9.5 million profit.

Look at British Aircraft Corporation with its record breaking Rapier missile and other aerospace interests. Turnover up from £174 million to £271 million and profits up from £13.7 million to £24.2 million. And the forward order book stands at a record £815 million.

An indifferent performer for a number of years, Ultra Electronics reports a £13 million forward order book. An all-time record. With £9 million turnover profits were £550,000, £142,000 up on the previous year.

The main British subsidiary of ITT, Standard Telephones and Cable, reports record sales of £333 million which included a sharp rise in export business. Profit was £33.8 million.

Naturally these figures, mostly a reflection of trading in 1974, need

treating with some reserve because the effects of inflation tend to show "growth" where none exists. But the picture can hardly be regarded as gloomy.

The really dull spot is the instrument industry. The 60 leading companies, according to a recent analysis, after allowing for inflation are showing zero growth or even a loss in sales figures and many are only on the margins of profitability.

LADIES' YEAR

Mrs Mary Griffin has become president of the Scientific Instrument Manufacturers' Association (SIMA). She has served for several years as a SIMA council member and has been the association's spokesman on statistics and economic affairs.

Professionally she is a special director of Smiths Industries Ltd. and was awarded the MBE for services in export in 1970. With a background as a chemist and mathematician perhaps she will prepare an elixir to revive the fortunes of Britain's instrument makers followed by more heartening statistics during her period in office.

Dr Elizabeth Laverick has been appointed to serve on the Engineering Design Advisory Committee of the Design Council. After a distinguished academic start in life she was in industry for 20 years as a radar and microwave expert, rising to be technical director of Elliott Automation Radar Systems Ltd. In 1971 she left industry to become deputy secretary to the Institution of Electrical Engineers.

It seems extraordinary that so few ladies enter electronics on the engineering side. I know of two qualified lady engineers at the M-OV division of the GEC Electronic Tube Co. Ltd., and a lady scientist at English Electric Valve Co. In Sweden recently I met the general manager of a semiconductor plant who was a she.

Here and there one comes across a lady craft apprentice but they are always demonstrated to visitors as being something of a novelty. At a recent international conference in Holland there were 200 engineer delegates of whom only one was a lady, French and slightly embarrassed at the preponderance of males.

And yet, of the total workforce in electronics, the majority are women but generally only engaged on the more menial tasks of assembly, although a few do emerge climbing the ladder of promotion in inspection and test departments.

How about it, girls? Unless you improve your performance in electronic engineering we shall have to conclude you are not as equal as you would have us believe.

INGENUITY UNLIMITED



A selection of readers suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

CAR ANTI-THEFT DEVICE

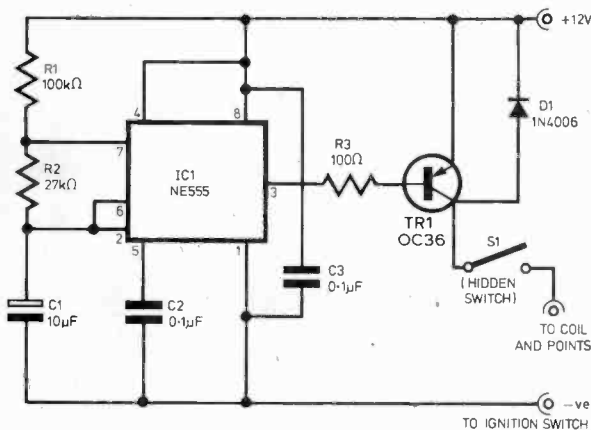


Fig. 1

MOST car anti-theft devices use one or both of the following two principles:

- (1) The ignition circuit is completely disabled, usually by means of a hidden switch.
- (2) Any attempt to break into the car sounds the horn, flashes the headlamps, etc.

The first of these two approaches suffers from the disadvantage that the ignition circuit can usually be remade under the bonnet, using a piece of wire. The second approach leaves the car owner with the possibility of returning to his vehicle to find a flat battery and a group of disturbed local residents.

The device described here works by upsetting the timing of the car engine, causing it to run extremely roughly. It is assumed that any car thief would soon abandon a vehicle which refused to accelerate properly, performed kangaroo motions and generally appeared to be in need of some serious repair.

The circuit shown in Fig. 1 works as follows: IC1 is connected as an astable multivibrator, driving TR1. TR1 is turned on for about 0.25S then off for a further 0.95S repeatedly. If the points open when TR1 is on, no spark is generated and the engine does not fire. Due to the parallel connection of the points and TR1 there is no danger of the engine firing in the middle of a compression stroke or inlet stroke.

The circuit still operates even if a piece of wire is used to connect the battery negative to the ignition coil. The wire from S1 to the coil is best made as inconspicuous as possible.

For a negative earth car TR1 could be replaced by an *npn* device (2N3055). TR1 needs no heat sink as it is either fully on or cut off and dissipates little power.

P. J. Tyrell,
Ilford.

SIMPLE TIMER

THE 741 and C1 form an operational integrator, the integration current being determined by the current flowing through TR1, see Fig. 1.

This in turn is determined by the setting of VR1 (R1 limiting the maximum base drive to a safe value). The integrator output is fed to R3 and R4 which turns TR2 on when the output reaches about 5 volts.

The circuitry around TR2 can be altered to suit the constructor's needs. For example, a relay could be operated instead of the l.e.d.

The timing range of the circuit as it stands is from less than a second to about 12 minutes.

A. MacNeil,
Great Bookham.

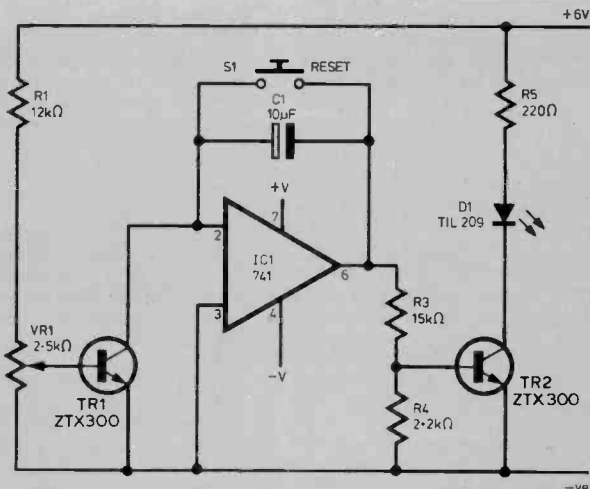


Fig. 1

SPECIAL OFFER

TO PRACTICAL ELECTRONICS READERS

SABCHRON DIGITAL

LED WRISTWATCH

As featured in this issue **SAVE ABOUT £8.75***

(SPECIAL OFFER VALID UNTIL 15th OCTOBER 1975 ONLY)

- SINGLE BUTTON OPERATION.
- DISPLAYS HOURS, MINUTES, SECONDS, MONTH AND DATE (DAY OF MONTH).
- GOLD PLATED SWISS MADE CASE WITH STAINLESS STEEL BACK COVER.
- ACCURACY TO WITHIN 5 SECONDS PER MONTH.
- AUTOMATIC READOUT INTENSITY CONTROL: BRIGHTENS DISPLAY IN BRIGHT LIGHT; DIMS DISPLAY IN SUBDUED LIGHT OR TOTAL DARKNESS.
- BATTERIES LAST UP TO 1 YEAR WITH NORMAL USAGE.
- WATER RESISTANT, SHOCK PROTECTED, ANTI-MAGNETIC.

COMPLETE KIT

(with batteries but without bracelet). Airmail post paid.

£36.25*

ASSEMBLED WATCH

(with leather band and 12 month guarantee on the electronics). Airmail post paid.

£45.50*



ACTUAL SIZE

SABCHRON WATCHES ARE AVAILABLE ONLY FROM THE U.S. MANUFACTURER

EURAY TRADING INC.

P.O. BOX 64683, DALLAS, TEXAS 75206, U.S.A.

★ IMPORTANT INFORMATION ABOUT PRICES

The above prices shown in British Pounds are approximate equivalents of the actual U.S. Dollar prices: Kits (with coupon): U.S. \$80.00. Kits (without coupon) U.S. \$99.50. Assembled (with coupon) U.S. \$100.00. Assembled (without coupon) \$119.50. ALL PRICES INCLUDE AIRMAIL POSTAGE AND INSURANCE. REMITTANCE BY U.S. DOLLAR BANK DRAFTS OR U.S. DOLLAR MONEY ORDERS. DO NOT SEND PAYMENT IN ANY OTHER CURRENCY PLEASE.

SPECIAL OFFER COUPON

(valid until 15/10/75 in U.K., valid until 15/11/75 other countries)

To: EURAY TRADING INC., P.O. BOX 64683, DALLAS, TEXAS 75206, U.S.A.

Please Send via Insured Airmail

I enclose Bank Draft International Money Order in U.S. Dollars for \$.....

Name

Address

(country)


All orders (received with payment) shipped within 72 Hours, 27 Minutes and 53 Seconds!

EXTRA SPECIAL! You can have your SABCHRON DIGITAL personalized with any name or initials (maximum 12 letters and spaces) engraved with gold coloured letters on the watch face for U.S. \$10.00 additional. Print or type clearly the name or initials to be engraved on the coupon. (Allow 48 hours additional for personalized watch cases.)

The above prices do not include taxes leviable by a purchaser's country of residence.

SONY HALF PRICE

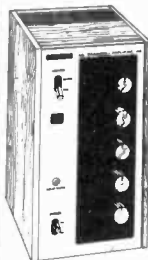These top quality SQ Decoder/Amplifiers are offered at half price while stocks last. Brand new in manufacturers' cartons with one year guarantee.



SQA 100
SQ DECODER/AMPLIFIER
SQA 100. A versatile and space saving SQ decoder/amplifier which can convert your existing stereo system (providing your amplifier has a tape source monitor switch) to exciting 4-channel realism—just add model SQA 100 and a pair of rear speakers. Other features include tone controls, balance controls, and power amplifier giving 8W RMS output per channel, master volume control for simultaneous adjustment of 4 channels and decoder output controls for independent use of decoder. Many of your favourite artists are now recording albums in SQ—ask at your local record shop.

REC. RETAIL £52.00 incl. VAT
OUR SPECIAL HALF PRICE OFFER
ONLY £26.00 incl. VAT
Please add £1.50 P. & P. and insurance

SQA 200
OUR SPECIAL HALF PRICE OFFER
£38.80 incl. VAT
REC. RETAIL PRICE £77.68 incl. VAT
Please add £1.50 P. & P. and insurance



SQA 200
SQ DECODER/AMPLIFIER
SQA 200. Providing an output of 8W RMS per channel for the rear speakers. SQA 200 is a decoder/amplifier designed specifically to work with those complete audio units systems provided with a tape-source monitor switch. Now that so many of your favourite artists are recording SQ albums, the addition of SQA 200 plus a pair of rear speakers will add a new dimension to your stereo system.

DECLON FOAM SPEAKER FRONTS
as used by leading manufacturers

18½ x 10 x ½ black or brown £2.00 each
22 x 12 x ½ brown £2.50 each
29 x 11 x ½ brown £3.00 each
26 x 15½ x ½ brown £3.00 each

Prices include VAT and Post and Packing.
Can be easily cut to suit any loudspeaker enclosure.
Pattern as illustrated.



THE FABULOUS SANSUI 210 TUNER AMPLIFIER



REC. RETAIL PRICE
£111.85 incl. VAT
OUR PRICE
£74.95 incl. VAT
+ £1.50 P. & P. and insurance

210
Sansui 210 34W AM/FM Stereo Multiplex Tuner Amplifier. Equipped with an FET front end for exceptionally sensitive FM reception, linear scale FM dial for precise tuning and automatic FM stereo/mono switching, this model also provides a full system of accessory circuits, wide 30 to 25,000Hz power bandwidth and holds distortion to less than 1%.

CHEQUES, P.O.s AND
MONEY ORDERS TO

medway mail order co.

P.O. BOX 4G
GILLINGHAM
KENT, ME7 5LB

Dimmit range of light dimmers and lighting control systems

Illustrated is the popular PMSD1000 module. A 1kW slider control dimmer, interference suppressed, 60mm slider range size 4½ x 2 1½in. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £8.60 inc. VAT and postage and packing.

Complete compact light dimmer systems for stage, club and disco lighting, etc.

DD61 (illustrated). Six 1kW channels, six outlet sockets, master control, mains on/off switch, size 23 8½ 5in. Price £97.20 inc. VAT.

DD261. As above but with two-preset arrangement, i.e. two slider controls per channel, two master controls. Size 23 10 5in. Price £117.72 inc. VAT.

DD61-B. Six 1kW channels, using module PMSD1000, lowest cost system. Size 16½ 8 5in. Price £59.50 inc. VAT.

DD62. Six 2kW channels, six outlet sockets, mains on/off switch. Size 25 x 10½ x 6in. Price £156.60 inc. VAT.


Add £2.20 postage and packing for all systems.

The Dimmit range includes rotary and slider control dimmers and sound to light converters for home, entertainment and professional applications. Ratings 1kW, 2kW, 31-VV.


All products are guaranteed and are supplied with full instructions and applications. Full after-sales service. Technical advice given.

For full information on all modules and lighting control systems send 15p for our illustrated catalogue and price list. Callers welcome, visit our showroom for a demonstration of any of the modules or systems. Mon.-Fri. 9.30 to 6.0 p.m. Sat. by arrangement.

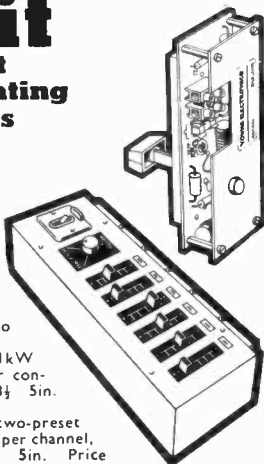YOUNG ELECTRONICS LTD.
184 Royal College Street, London NW1 9NN Tel. 01-267 0201



NEW! THE HOT ONE

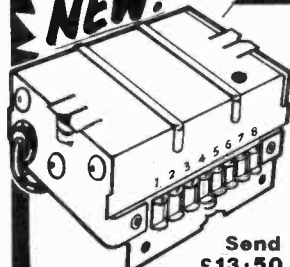


DX FRONT END
VTO3 88-108 MHz

- * 2 DUAL GATE MOSFETS
- * SILVER CLAD CHASSIS
- * A.G.C. and A.F.C.

A 4 stage Front End. Will pull out stations which on conventional receivers would be lost in the noise. Gain 30dB + at 100 MHz. Noise 6-5dB Typ.

Send
£13.50

V.H.F. FRONT END/CONVERTER

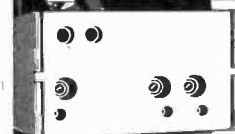

- VTO1
- * ADVANCED DESIGN
 - * DUAL-GATE MOSFET FIRST STAGE
- Covers: AIRCRAFT · WEATHER · SATELLITES · AMATEURS

VARICAP TUNED:
Input 118-150 MHz
I.F. Output 10.7 MHz

Send £10.90

I.F.T.O. HIGH PERFORMANCE DE-LUXE I.F. STRIP

NOW with 70dB gain **Send £8.60**

- * SHARP SKIRT SELECTIVITY
- * CONTROLLABLE SQUELCH
- * CENTRE ZERO TUNING METER + SIGNAL STRENGTH METER OUTPUT

ALL PRICES
QUOTED
INCLUDE VAT
AND P. & P.

Send 8p + S.A.E. for Data Sheets.
Sole U.K. Agents

REEDHAMPTON LTD.
182-184 Addington Road, Selsdon, Surrey CR2 8LB

LOW VOLTAGE PULSE GENERATOR

THE CIRCUIT (Fig. 1) generates pulses in the audio range with very fast rise and fall times even when the supply voltage is as low as 0.8 volts, thus making it ideal for signal injector purposes.

In commercial injectors an unbalanced multivibrator is often employed which results in slower transitions. Typical wave forms are shown in Fig. 2.

Transistors TR2, 3 and 4 form an oscillator whose frequency largely depends on C and R4. With the values shown the frequency is about 300Hz. This can be altered so that the output is in the range 0.1Hz to 5kHz, with an almost constant mark space ratio of 1:28. At the collector of TR2 negative going pulses are available, while after inversion at TR1 positive going pulses are also available.

The output from the circuit was fed into a u.h.f. television resulting in an audible tone from the loudspeaker and a dot pattern on the screen, thus showing that very high frequency harmonics must be present. Current consumption is only 0.3mA at 1.5 volts.

D. C. Dyer,
Coventry.

Fig. 1

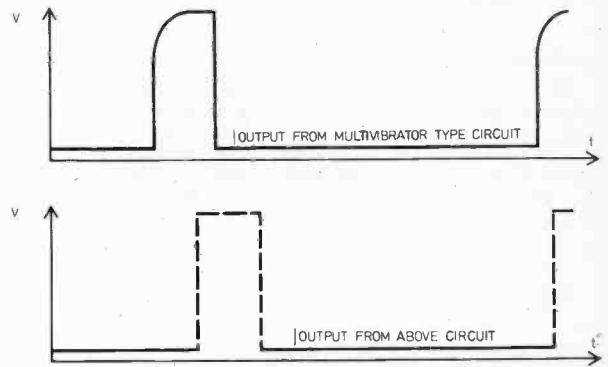
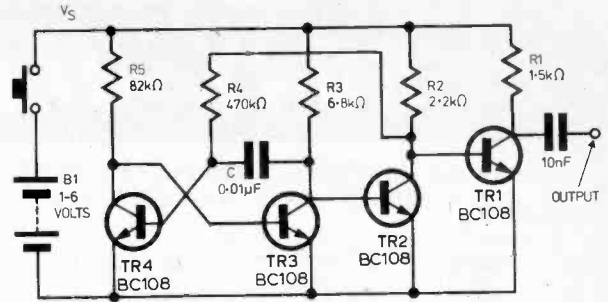


Fig. 2

FREQUENCY DOUBLER

THIS circuit in Fig. 1 was devised to demonstrate the frequency-doubling of sine-wave voltages over a wide frequency range. The output voltage waveform is sufficiently sinusoidal to suggest its use, after a stage of amplification, as the input to a similar frequency doubling circuit. The circuit may find application in electronic musical instruments as a means of extending the upper frequency range of any instrument which uses sine-wave oscillators.

The circuit (Fig. 1) comprises a phase-splitter amplifier, TR1, driving two point-contact diodes, D1 and D2, which are connected to give full-wave rectification of the anti-phase voltages from the emitter and collector of TR1. The potentiometer VR1, initially set at its midpoint, is adjusted to give an output which is free of the input frequency. VR2 controls the output voltage and the symmetry of the output waveforms, though a fixed resistor of 470 ohms will give satisfactory results. With VR2 at its midpoint, and an input of 700mV pk-pk, the output voltage at double the input frequency is 100mV pk-pk within 1dB over the

input frequency range 35Hz to 100kHz. The upper limit of input frequency was set by the available test oscillator.

Transient distortion associated with changes in d.c. level of the output voltage waveform implies that the circuit is best used with inputs of amplitude, but the duration of transient distortion will be

reduced if the capacitors C1, C2, and C3 are reduced for operation at frequencies above 35Hz.

This circuit is readily adapted for use with other transistors, provided that R1 is selected to give a collector current in TR1 of 5 to 10mA.

D. Letts,
Camberwell.

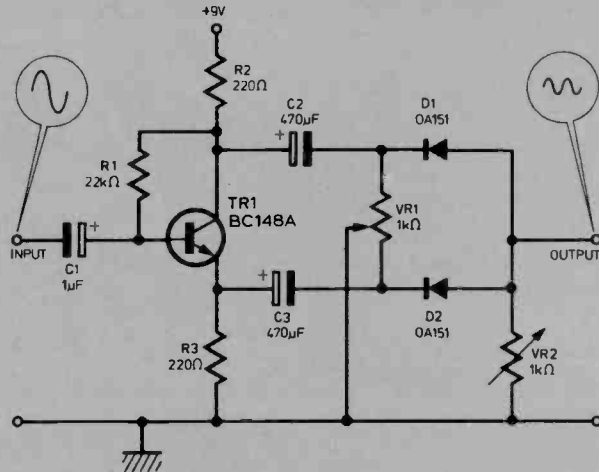


Fig. 1

VOLTAGE CONTROLLED OSCILLATOR

THE v.c.o. circuit has a dynamic range of 4 decades, for inputs of 10V down to 1mV, and with care, down to 0.1mV. The timing is reliable, and the ramp output is very linear.

A positive voltage applied to the input causes the amplifier to start integrating. When the trigger voltage of TR1 is reached (this is an avalanche device) the capacitor is discharged and the process starts again.

R3 and D1 ensure that the amplifier cannot integrate "backwards" and destroy TR1.

The trigger voltage of TR1 is dependent on the interbase voltage, and R4, VR2 are thus used as a control for setting the frequency range initially.

The outputs are thus obviously effected by loading, and this must be taken into account.

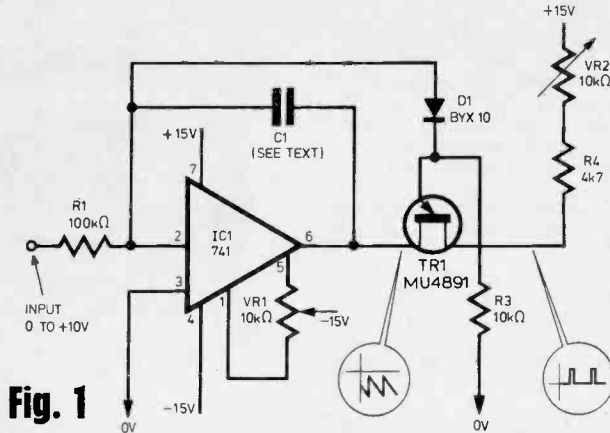


Fig. 1

C1 has been tried with values from 0.01μF to 10μF, the latter giving a reliable period of about 1½ hours. Obviously C1 must be very low leakage.

To compensate for offset errors in the 741 earth the input and adjust the offset control at VR1 for minimum voltage drift at pin 6.

A. W. Diverall, Ashtead.

SHORT CIRCUIT PROTECTION

A SHORT circuit protection device for fixed voltage d.c. power supplies like rechargeable batteries is shown in Fig. 1.

The relay is used to cut out the power supply. When a short circuit occurs no current flows through the relay and thus it falls off to the normal closed position. R1 is chosen experimentally such that enough current flows through the relay to hold the normal open contacts closed, but *not* enough current to operate the relay when S1

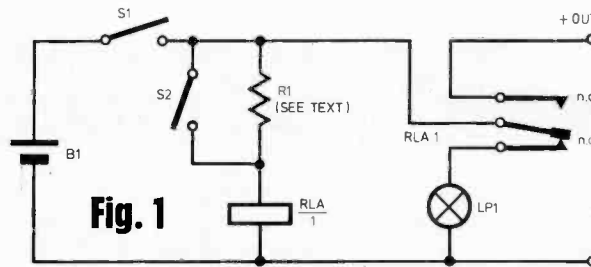


Fig. 1

is closed. If R1 were not used the relay would chatter in the short circuit condition. S2 serves to reset

the relay, and LP is a lamp to indicate when the relay has cut out.

S. Bygraves, Norwich.

THE 7413 is a dual Schmitt trigger, and is excellent for producing the fast rise time necessary to drive TTL integrated circuits. With the addition of a few components, indication and memory can be added.

All inputs are normally at logical "1" (+5V), when any input goes to logical "0" the output of 7413 rises to logical "1", and removal of the sink current drives the transistor on. One input to the 7413 is coupled to the transistor collector, so that the Schmitt latches on, and the bulb indicates signal failure. Simultaneously, a fast negative transition is produced at the 7413 output. The latch may be reset, simply by grounding the base of the transistor.

R. Bratby, Headington.

SIGNAL FAILURE INDICATOR WITH MEMORY


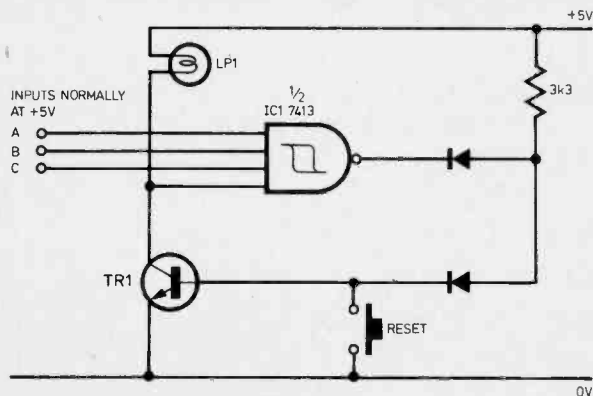


Fig. 1

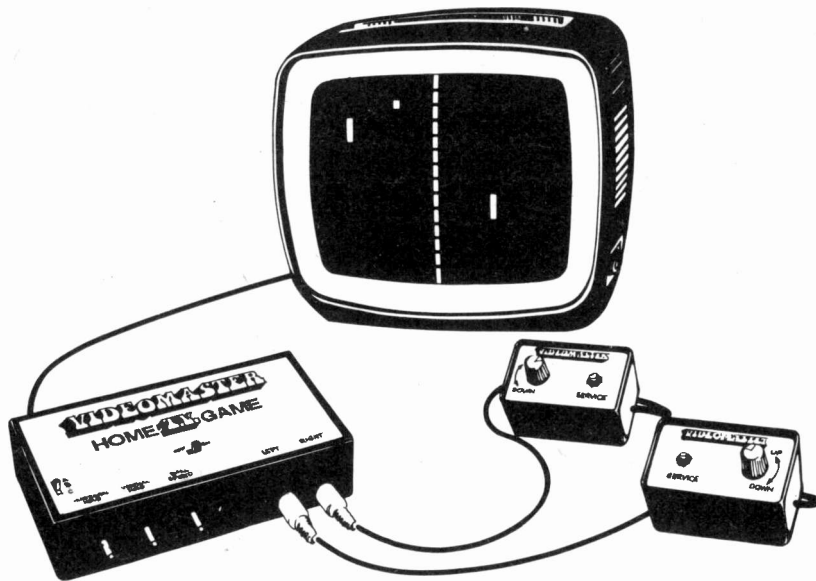

Videomaster urge all good electronics enthusiasts to play the game

The best thing about the Videomaster Home T.V. Game Mk. III is that the sheer pleasure of building it is immediately followed by the excitement of playing three fascinating games.

The famous Videomaster is now available for you to make. It plugs into any standard UHF 625 line TV set, and it shouldn't take you longer than a few hours to build.

In detail . . . The Videomaster Mk. III has eleven integrated circuits . . . four transistors . . . eleven diodes . . . is easy to build . . . with no alignment necessary because with ready-built and tested transistorized UHF modulator, is complete with all parts . . . including fully drilled and prepared p.c.b. . . . handsome plastic box . . . control leads . . . complete step by step assembly instructions . . . Runs on a PP7 9 volt battery . . . and has logic and analogue "state of the art" circuitry all with National Semiconductors CMOS devices . . . with full specification.

The cost? Only **£19.95** (+ VAT)

POST TODAY TO:

Videomaster Ltd

119/120 Chancery Lane, London WC2A 1QU

Please send me (insert no.) Videomaster Mk. III kits at £21.55 ea. inc. VAT. P & P

I enclose my cheque/money order for £.

Tick if VHF Modulator required -£1 extra

NAME

ADDRESS

ALLOW 14 DAYS FOR DELIVERY



PE/1

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
1 ST. MICHAELS TERRACE, WOOD GREEN
LONDON N22 4SJ Phone 888-4474

BARGAIN PROJECT BOX

A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied).

An ideal box to give a small project a professional finish. SIZE (Internal 81mm x 51mm x 28mm).

OUR PRICE 40p. + 8%.



"CRESCENT BEAT BRITTE" SINGLE CHANNEL SOUND TO LIGHT UNIT
This fantastic little box

approx. 4" x 3" x 2 1/2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at £7.50 plus 10p P. & P. + 8%.

MINIATURE RELAYS

Brand new range of British made relays, size: 1 1/4in x 1in x 1 1/4in. All two changeovers with 250V 1-5A contacts and suitable for fitting on 0-1in veroboard. Type Volts Current Ohms
27/A 12V 17mA 700 All
21/A 12V 28mA 430 £1-30
12/A 6V 33mA 185 each + 8%.

MINI LOUDSPEAKERS

2 1/2in 80 ohm, 50p; 2 1/2in 40 ohm, 60p. Please include 5p P. & P. on each L.S. + 25%.

MIDGET

MAINS TRANSFORMER

Varnish Impregnated
Size 45mm x 36mm x 31mm
PRI 840V
Sec 3.0-3 100mA
Sec 6.0-6 100mA
Sec 9.0-9 100mA
Sec 12.0-12 100mA
Sec 20.0-20 100mA
£1-23 10p P. & P. + 8%.

CRESCENT BUBBLE LIGHT SHOW

This budget system compares very favourably with more sophisticated and higher priced models.

Specification:
Projector—150W convection cooled. At 30ft the projected image is 16ft.
Motor—1 rev. per 2 min.
Liquid Wheel—6in diameter multi colour.

The motor is fitted to the projector and can only be purchased as a single unit.

The liquid wheel is our standard model and may be purchased separately.

A bargain at: Projector, £15; Wheel, £5; Total £20. Plus 75p cart. + 8%.

CABLE LESS SOLDERING IRON WAHL "ISO-TIP"

* Completely portable.
* Solders up to 180 joints per charge.
* Recharges in its own stand.
* Fine tip for all types of soldering.
* Only 8in long and weighs just 6 ozs.

OUR PRICE £9.75 + 8%. (Spare bits are available)

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD. IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ THE POWER AMP MODULE
170W r.m.s. eq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm).

★ THE PRE-AMP MODULE
Four control pre-amp, Vol. Bass, Treble, Middle controls. Designed to drive most amplifiers using F.E.T. first stage.

★ THE POWER SUPPLY
Is supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain, £25, carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers. + 8%.

12-0-12V 500M/A

240V primary transformer bargain. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our price £1-20. + 8%.

FERRIC CHLORIDE

Anhydrous ferric chloride in double sealed one pound poly packs. Our Price 60p per lb. + P/P + VAT @ 8%.

LOW NOISE, LOW PRICE CASSETTES

Good quality tape in well made screw type cassettes. Presented in single plastic cases.
C60 3lp C90 42p C120 55p
10% discount on ten or more cassettes of one type. + 8%.

ABS PLASTIC BOXES

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels. 1005, 105mm x 73mm x 45mm 55p; 1006, 150mm x 75mm x 47mm 72p; 1007, 184mm x 124mm x 60mm £1-28; 1021, 106mm x 74mm x 45mm (sloping front) 55p. + 8%.

P.C. ETCHING KIT

This kit contains all that the constructor will need to etch the circuits of his own design. Contents: Plastic etching dish. Sample copperclad board. Lamininate Cutter. 1 lb Ferric Chloride. Large Plastic Spoon. Etch Resist Pen. Full Etching Instructions. Complete and Big Kit Value at £3.75 + 8% VAT.

2in. PANEL METERS

Size 59mm x 46mm	
0-50µA —ME6	0-100mA—ME13
0-100µA—ME7	0-500mA—ME14
0-500µA—ME8	0-1A —ME16
0-1mA—ME9	0-50V —ME16
0-5mA—ME10	0-300V a.c.—ME17
0-10mA—ME11	S meter —ME18
0-50mA—ME12	V.U. meter—ME19

£3 each. 10p P. & P. + 8%.

POWER PACKS


PP1 Switched 3-4j-6-7j-9 and 12V at 500M/A with on/off switch and pilot light. Size 130M/M x 53M/M x 75M/M, only £4.
PP2 Switched 6-7j-9V Battery Eliminator. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Ideal for cassette recorders, £3-25.
PP3 Car converter. From 12V Pos. or Neg. to ± 6-7j-9V. Easy to fit and transistor regulated, £3-80. + 8%.

TELESCOPIC AERIAL

Nine section fully swivelling telescopic aerial with 4BA single bolt fixing or two hole fixing bracket. Fully extended 4'3". Fully closed 7". Our Price 50p + P/P + VAT @ 8%.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

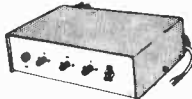Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18-50 plus 38p P. & P. + 8%.



Low cost circuit assembly



5 assembly boards plus 500 solder pins (Approx.)

ONLY £4

Plus VAT Inc. post and packing


'Lektrokit' offers you a re-usable Circuit Assembly kit at a price you can afford. Designed for double sided circuitry, these unique assembly boards and pins are continuously re-usable—cutting your development time and material costs. With the 'Lektrokit' system, circuitry is so simple to modify time and time again.

Send cash with order to:-

LEKTROKIT LTD.

Trafford Road, Reading, Berks. RG1 8JR.

Trade enquiries invited.

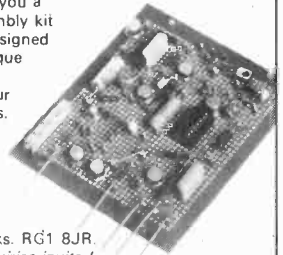

Make light work of wiring

with the NEW SELF ADHESIVE WIRE STAPLES



Countless uses in industry and offices

*QUICK AND EASY TO APPLY — EVEN IN AWKWARD PLACES

*SAVES DAMAGE TO WOOD AND PAINTWORK
*STICKS ON INSTANTLY: HOLDS WIRE FIRMLY

You'll save enormous time and trouble with the new Brandauer adhesive staple. Just peel off the backing strip and press staple into place. Then bend clips over to hold wire firmly in position. No messing with pins, tacks, soldering or drilling. No damage to woodwork, e.g. skirting boards. Use the Brandauer Staple for any wall, frame or cabinet wiring jobs — it's wonderfully easy for fitting in those awkward corners.

Send now for details to:

SPECIAL PRODUCTS DISTRIBUTORS LTD.
81 Piccadilly, London W1V 0HL: Tel: 01-629 9556.

U.K. CARRIAGE 20p UNLESS OTHERWISE STATED

VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

SEND 30p FOR A CRESCENT CATALOGUE

PATENTS REVIEW...

RESCUE TRANSMITTER/RECEIVER

In BP 1 382 732, Autophon AG, of Switzerland, describes an electronic system to facilitate the rescue of people buried or trapped, for instance by a landslide or avalanche.

The system requires that both the searcher and the searched be equipped (in advance of course) with matching equipment. It is suggested that where this has been previously tried difficulties have arisen because of the very wide range of field strength intensities that must be handled. The receiver must pull in a strong signal from a remote transmitter but must also accurately process a strong signal from the same source when local.

The circuit diagram for the transmitter/receiver is shown in Fig. 1. The ferrite aerial forms with C1 an input circuit tuned approximately to the same transmitter and receiver frequency. The multivibrator intermittently switches the transmitter primary input stage on and off to save battery power.

A manually operated switch S1 has ganged segments, each with nine positions. The oscillator crystal X1 is connected to earth by R5 and C6 and to the primary input stage via switch contacts S1, 1K. TR1 functions as the output stage of the transmitter when under the control of primary input stage.

The input amplifier is connected to a tap on aerial coil and, as long as the amplifier is powered, the base of switching transistor TR3 receives a voltage which causes it to conduct. The circuit elements between TR2 and R8 act as a symmetrical crystal filter, of which the output leads to adjustable attenuation or damping resistors R8, R9, R10.

Signals of three different intensities are delivered to R8, R9 and R10 at their three junction points and each point is connected to two terminals of S1b. Thus the output of the symmetrical crystal filter reaches the input of the mixer after being damped to a degree dependent on the switch position. The mixer also receives a signal from the receiver oscillator, which differs only slightly from the receiver frequency. The resultant signal is filtered, passed to the control element, a.f. amplifier and finally to the earphone.

The circuit gives the following function option with the single switch, S1. Unit on and off, switching between a transmitting function and a receiving function (switch positions S and E). Adjustment of the receiver to the best suited sensitivity range (switch positions E with varying damping effect). Overall performance check (position K with voltage supply to the transmitter and receiver stages with the

signal processed as a low frequency signal under normal conditions. so that the earphone produces a sound signal). Thus the same unit is carried by anyone feeling themselves to be at risk (e.g. climbing potholing or skiing) and by a searcher subsequently on a rescue operation if the risk is realised.

CAR MIRROR DEFROSTING BP 1 387 436

A technique for electrically defrosting or demisting car wing mirrors is described by the Sprague Electric Co. of Massachusetts in BP 1 387 436.

Whereas it is necessary to embed a heating element in a car window to provide for defrosting or demisting, a mirror of necessity incorporates a conductive element at its reflective backing.

In accordance with the invention, a glass surface has a reflective nickel-chromium alloy resistance film evaporated or sputtered on the back. In practice approximately 25 or 30W of power is obtained with a coating 300-400 Å thick having a resistance of about 4 to 6 ohms and fed from a 12V battery supply. A thermostat can be used to provide automatic control of the heating dependent on ambient temperature.

One suggestion is that an alloy of 80 per cent nickel and 20 per cent chromium be applied and the electrical supply connected via contacts formed from conductive epoxy resin attached directly to the alloy coating. A small piece of ceramic material with a positive temperature coefficient of resistivity (PTCR) is incorporated in one resin contact to serve as a thermostat. As a suitable PCTR it is suggested that a material composed of 65 per cent $BaTiO_3$ (including 0.15 per cent Nz_3O_5) and 35 per cent $SrTiO_3$.

Readers with enquiring minds may wish to experiment on the effects of connecting conventional wing mirror coatings to the 12V supply.

BP 1 382 732

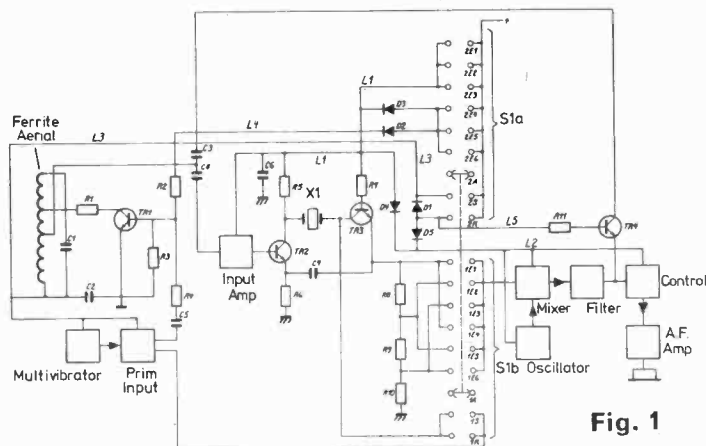


Fig. 1

Copies of Patents can be obtained from the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price 33p each.

Readout —

A SELECTION FROM OUR POSTBAG

Readers requiring a reply to any letter must include a stamped addressed envelope. We regret that we cannot answer any technical queries on the telephone.

Touch tuning

Sir,—Further to my article titled "Touch Tuning Unit", published in the May 1975 issue, I have made some simple modifications to the circuit which may be of interest to your readers. These modifications improve the sensitivity of the unit, since in the original circuit, when the person operating the touch buttons was earthed, the unit could not switch channels correctly.

The modification requires there to be a negative supply voltage of approximately 5V to the unit, as well as the positive supply. The modification is as follows:

1. Remove C3, D9, and D10; replace by short-circuit.
2. Connect pin 4 of IC2 to negative rail.
3. Connect emitters of TR2, TR4, TR6, TR8, TR10 and TR12 to negative rail.

In addition, I would like to point out some printing errors in the article. These are: Component List—D17 should be BZY88C6V8. Component List and Fig. 2—IC4 to be DL707. Page 394, column 2, line 2—R12 to read R11.

R. J. Bonfield,
Hampton, Middx

Matchless!

Sir,—I read with interest your article by Mr Bullen, on the "P.E. Portable Gas Lighter". As Mr

Bullen says, it would have been rather difficult to light the gas with flint and steel. However, about 50 years ago, when a young man, I was given an old non-working gas lighter. This was operated by frictional electricity. It so happens that this year I decided to recondition and repair it and had only finished it about 8 weeks before your article appeared.

A sketch is enclosed (see Fig. 1) and shows a finger lever near the handle. It takes three depressions of the lever to energise to sparking condition. The spark is about 0.020in and quite brilliant. Internally the ebonite circular box contains one 3in diameter Wimshurst type revolving disc with six metal foil plates stuck upon it. This is driven by the finger lever via a quadrant and a small free wheeling pinion. In the base of the ebonite box is the "Leyden Jar" (capacitor today); this comprises two semi-circular lead foil plates cemented to the bottom of the box.

I do not have gas so I am unable to try it, but feel doubtful if it would be very successful on town gas. A very gentle squeeze of the tripper is sufficient to produce maximum sparking. Its overall length is 12½in, the ebonite box being 4¼in dia. by 1½in high. The name of the machine is "The Matchless Electric Gas Lighter" (I assume no pun intended!) Molisons Patents, and I guess the date circum 1900.

E. J. Bright,
Weybridge, Surrey

Sound track

Sir,—I would like to back up Mr Scargill's statement (Readout, June) and add that Mr Lenton-Smith should listen to the following pieces:

"Dark Side of the Moon" by Pink Floyd (Harvest SHVL 804)

Side 1, track 2 "On The Run"

Side 2, track 3 "Any Colour You Like"

"The Two Sides of Tony (T.S.) McPhee" by Tony McPhee (W.W.A. 001)

Side 2 "The Hunt"

The Pink Floyd tracks are played on E.M.S. Synthesisers (V.C.S.3's and a Synthi Hi Fli guitar model), and Mr McPhee's suite is played on two ARP2600's, an electric piano and a "Rhythm Ace" drum synthesiser.

It may be of interest that Mr McPhee's work was recorded in a studio which he built himself in his garage and until 3 years ago he only played the guitar professionally.

Further examples of good synthesiser work can be found on the recordings of the following groups and musicians:

Gentle Giant (Vertigo/W.W.A.), Peter Hammill (Charisma), Rick Wakeman (A&M), Van Der Graff Generator (Fontana/Charisma), Genesis (Charisma), Manfred Mann's Earthband (Vertigo), Yes (Atlantic), Groundhogs (United Artists/W.W.A.) and Jethro Tull (Chrysalis).

Incidentally, how about a reprint of the P.E. Sound Synthesiser as there must be many people who missed this series as I did.

Steven F. J. Smith,
Coatbridge, Lanarkshire

Eaton Audio can supply reprints (see advertisers index).


SS Convention

Sir,—I think your readers may be interested in the special "Slow-Scan TV Convention" being organised by the British Amateur Television Club.

The convention will take place at Aston University, Birmingham on Saturday, October 11, from 1000 to 1800 hrs. This convention is open to all who are interested in this fascinating topic, whether they belong to the B.A.T.C. or not. There will be lectures and display of equipment and plenty of opportunity for the exchange of ideas.

There is a small charge of 50p to cover expenses, and tickets may be obtained from Mr M. Crampton, G8DLX, 16, Percival Road, Rugby, CV22 5JS:

C. G. Dixon,
Ross-on-Wye, Herefordshire

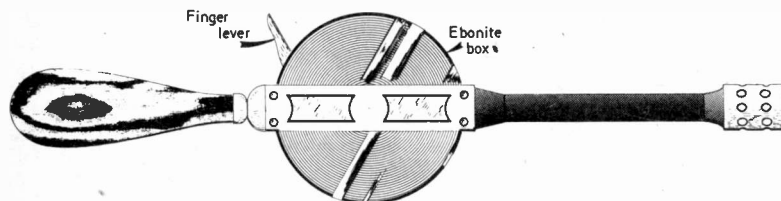

Mr Bright's 50 year old "Matchless Electric Gas Lighter"

NEWS BRIEFS

Solar Cells Becoming Popular

AT long last interest is being shown more actively in solar power. The Government has made moves to support Ferranti in their research on the subject and another active company, Lucas, have been releasing information on applications in Australia for their range of solar energy systems.

The latter includes railway signalling, fire protection, radio repeater stations, a pipeline cathodic protection set-up and a Ham transmitter on Mt. Sugarloaf near Melbourne.

Now that Lucas have proved solar cells in use in the Western Isles, Scotland for transmitter/receiver use it is to be hoped that a lowering of price and increase in availability for the many obvious uses in the U.K. will occur.

British Instrumentation

NORTH Sea Oil is all the rage these days so it is not surprising that electronic companies are fast becoming involved in this market area.

The latest is Transducers (CEL) of Reading who is now offering a specialist service to companies in the offshore oil fields in conjunction with Banchory Instruments of Scotland.

The two companies are jointly offering a comprehensive pressure and load/tension measuring, X monitoring and control facility. They are able to either simply supply the equipment or provide all follow-up facilities including servicing and maintenance.

Inspectors Talk To Computers

QUALITY assurance inspectors probably spend as much time noting their observations as they use in carrying out the observations in the first instance. Now EMI Threshold Ltd have come up with a computer solution to this problem in which the computer is able to recognise a vocabulary of selected words.

In this way an inspector can instruct the computer to effect various functions whilst his hands are free to manipulate the object under inspection.

The vocabulary used is normal factory terminology and not only does the system display the inspector's findings as he speaks them but it also shows the correct values for any specific parameter. In addition, a record is kept of all operations for future use.



MAIL BAG

The on-going increase in postal and telephone charges does not seem to have made any difference to our post bag or our telephone bell. Enquiries continue to flood in.


We find that there are two points we are constantly mentioning. In the first place we just cannot afford to reply to any *readers' letters*, particularly those not associated with projects we have published, unless they are accompanied by a *stamped addressed envelope*. Were we to undertake to do so our post bill would become astronomic.

We cannot deal with *technical enquiries by telephone*. Readers should write in, giving details of symptoms and perhaps some test point readings, when requesting technical help so that we can at least give the relevant author some idea of the problems involved.

Finally, whilst we normally supply details as to source of components in each project we do assume that the constructor refers to advertisements and has an awareness of general sources. Thus, where goods are generally available we do not specify a source. You could save the cost of a letter by reading the advertisement pages first.

FREE Brochure on New KITS

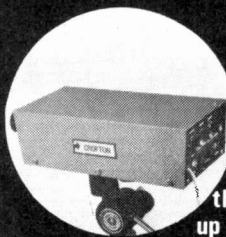Whether professional, student, teacher or amateur, the field of electronics can open up a new world for you.



CROFTON don't just sell kits, we offer you a technical back up service to ensure your success


The following is a selection of some of the more popular kits -

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ PE Rondo Quadraphonic Four Channel Sound (Designer Approved)
- ★ Electronic Ignition
- ★ Electronic Flash
- ★ P.W. Tele-Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobbulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE: PC Bs for most published projects available to order

CROFTON ELECTRONICS LTD

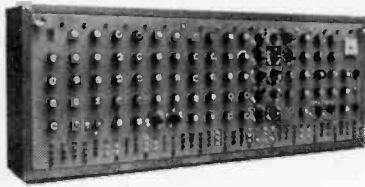Dept 'E' 124 Colne Road, Twickenham, Middx O1 898 1569



P.E. SYNTHESISER

(P.E. Feb. 1973 to Feb. 1974)

The well acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits. All function circuits may be used independently, or interconnected. The greater the number of circuits, the greater the versatility. Other circuits in our lists may be used with the Synthesiser to good advantage.

THE MAIN SYNTHESISER

Stabilised Power Supply	£12.05
Two Linear Voltage Controlled Oscillators and one Inverter—all 3 circuits:	£16.28
PCB (2 are required)—each	£1.48
Two Ramp Generators and Two Input Amplifiers—all 4 circuits	£5.62
PCB (holds all 4 circuits)	£1.38
Sample-Hold and Noise Generator—PCB (holds both circuits)	£6.52
Tone Control, £2.43; PCB, 72p	£1.64
Reverberation Amplifier	£6.26
Spring Line unit for Reverb Amp	£4.95
Ring Modulator	£3.44
Peak Level Meter Circuit	£1.50
100µA Panel Meter	£3.75
PCB for Rev., R-Mod. & Meter Ccts.,	£1.86
Envelope Shaper, £5.24; PCB, £1.42	
Voltage Controlled Amp. and Diff. Amp.	£6.70
PCB (holds both circuits)	£1.26
THE SYNTHESISER KEYBOARD CIRCUITS	
Can be used without the Main Synthesiser to make an independent musical instrument)	
2 Log. Voltage Controlled Oscillators	£2.32
PCB for both Log VCO's	
Divider, 2 Hold Circuits, 2 Modulation Amplifiers, Mixer and 2 Envelope Shapers	£19.46
PCB (Holds the first 6 circuits)	£1.80
PCB for both Envelope Shapers	£1.50
Keyboard Stabilised Power Supply	£7.30
Printed Circuit Board	94p

SYNTHESISERS AND KEYBOARDS

P.E. JOANNA

(P.E. May to Aug. 1975)

The new electronic piano that has switchable alternative voicing of Piano Honky-Tonk and Harpsichord. All PCB's are "as published".

Power Supply	£8.85
Tone Generator and Top C Envelope Shaper	£10.26
PCB for above	£1.30
Envelope Shapers	
12 sets (full requirement)	£32.16
Set of 12 PCB's (full requirement)	£15.00
Voicing and Pre-Amplifier Circuits	£7.99
PCB for above circuits	£1.80

Remaining circuits: prices in lists.



P.E. MINISONIC

(P.E. Nov. 1974 to March 1975)

A portable, battery or mains operated, miniature sound synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser, the functions offered by this design give it great scope and versatility.

Two Voltage Controlled Oscillators	£5.14
Voltage Controlled Filter and Voltage Reference Circuit	£3.35
Two Envelope Shapers and Two Voltage Controlled Amplifiers	£7.25
Keyboard Controller and Hold Circuits	£2.62
Keyboard Divider Resistors (select type to suit keyboard used, all are 2% tolerance), 2 Octave, £1; 3 Oct., £1.48; 4 Oct., £1.96; 5 Oct., £2.44.	
H.F. Oscillator and Detector	£1.66
Ring Mod., Noise Gen. & Env. Inverter	£4.96
Two Power Amplifiers and Two Mixers	£3.51
Battery Eliminator	£5.68
Temperature Stabiliser	£1.47
PCB to hold 2 VCOs, VCF and V-Ref	£1.84
PCB to hold 2 ESs, 2 VCAs, 2 Mixers, Ring Mod, Keyboard Control and Hold	£1.99
PCB to hold 2 Power Amps, Noise Gen, Envelope-Inverter, HF Osc. and Detector	£1.32
PCB for Battery Elim. & Temp. Stab.	£1.25

KEYBOARDS

Kimber-Allen Keyboards as required for many published circuits, including the P.E. Joanna, P.E. Minisonic and P.E. Synthesiser. The manufacturers claim that these are the finest moulded plastic keyboards made.

3 Octave Keyboard (37 notes C to C)	£20.50
4 Octave Keyboard (49 notes C to C)	£23.50
5 Octave Keyboard (61 notes C to C)	£27.00
Contact Assemblies for use with above keyboards:	
Single-pole change-over (SP) as for P.E. Joanna and P.E. Minisonic. Two-pole normally-open make-break (2P) as for P.E. Synthesiser. Special contact assembly (4PS) having 4 poles, 3 of which are normally-open make-break contacts and the fourth is a change-over contact—this special assembly enables the same keyboard to be used with the P.E. Synthesiser, P.E. Minisonic, and P.E. Synthesiser simultaneously thus avoiding the cost of more than one keyboard.	


Contact	3 Octave	4 Octave	5 Octave
Each Set	Set	Set	Set
SP	20p £7.40	£9.80	£12.20
2P	24p £8.88	£11.76	£14.64
4PS	48p £17.76	£23.52	£29.28

Printed Circuit Boards for use with the above contacts and thus eliminating most of the interwiring required, are available—details in our lists.

PHONOSONICS

FOR ADDRESS, INFORMATION REGARDING POST AND PACKING, VAT, LISTS AND EXPORT TERMS SEE OUR OTHER ADVERTISEMENT ON OPPOSITE PAGE

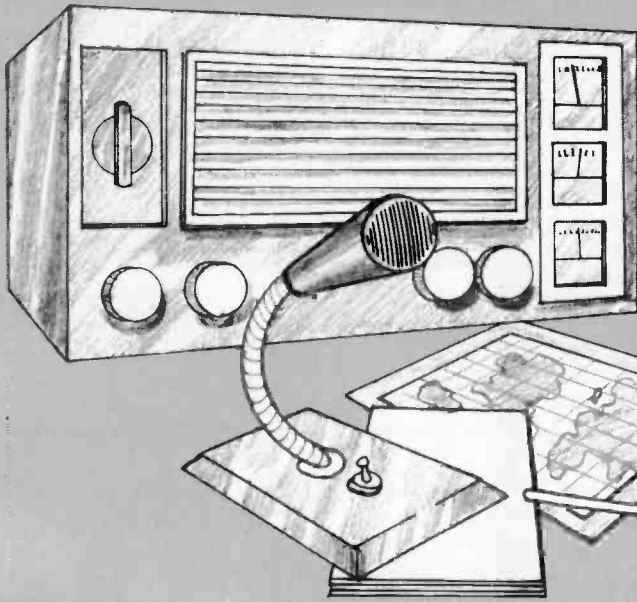Photos: 2 of our units containing some of the P.E. projects built from our kits and PCBs. (The cases were built by ourselves and are not for sale.)



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept.,
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

E10/75

Free!

PHONOSONICS

**SUPPLIERS OF QUALITY PRINTED
CIRCUIT BOARDS, KITS AND
COMPONENTS TO A WORLD-WIDE MARKET**

SOUND-TO-LIGHT (P.E. Apr./Aug. 71)

The ever-popular AURORA—4 or 8 channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities. A MUST for any Disco, and a fascinating visual display for the home.

- 4 channel component set (excl. thyristors) £12.83
- 8 channel component set (excl. thyristors) £22.16
- Power supply component set £4.86
- PCB for 4 frequency channels £3.32
- PCB for power supply and 8 lamp drivers £1.56
- 1 Amp 400V thyristors (1 per chan. req.) each 75p
- Panel meter (1μA) (optional) £3.75

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over", particularly useful for Disco work or for home-movie shows.

- Component set incl. PCB £2.95

TAPE-NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings.

- Component set (incl. PCB) £2.50
- Regulated power supply (incl. PCB) £3.98

P.E. SYNTHESISER

SEE OUR ADVERTISEMENT ON OPPOSITE PAGE

GUITAR EFFECTS PEDAL (P.E. July 75)

Will modify an audio signal not only from a guitar but from any audio source, producing 8 different switchable effects that can be further modified by manual controls. Possibly the most interesting of all the low-priced sound effects units in our range.

- Component set with special foot operated switches £6.16
- Alternative component set with panel mounting switches £4.60
- Printed Circuit Board £1.10

HI-FI TAPE-LINK (P.E. Mar./Apr. 73)

Designed for use with reasonable quality tape-decks, this high performance pre-amp includes record, playback and metering circuits.

- Stereo component set (excl. panel meter) £23.48
- Mono component set (excl. panel meter) £14.19
- Power supply component set £5.93
- Stereo main PCB £2.74
- Stereo sub-assembly PCB 98p

P.E. GEMINI 30W STEREO AMPLIFIER

An exceptionally high quality Stereo Amplifier system. Further details are in our lists. WHILE STOCKS LAST.

- Main Amplifier: £5.96
- Set of resistors, capacitors and presets £1.28
- Stereo printed circuit board

- Pre-Amplifier: £10.57
- Set of resistors, capacitors, potentiometers and switches— £2.20
- Standard tolerance set
- Stereo PCB (as published)

- Regulated Power Supply £4.58
- Set of resistors, capacitors and preset

VOLTAGE CONTROLLED FILTER (P.E. Oct. 74)

An independently designed VCF that can be used with the P.E. Synthesiser.

- Component set £3.41
- Printed circuit board £1.20

Transistors	BFY51	22p	2N3055	48p	
AC128	20p	BFY52	24p	2N3702	12p
AC176	20p	BSY95A	22p	2N3703	12p
BC107	13p	MJE2955	11p	2N3704	12p
BC109	13p	MJE3055	75p	2N3819	35p
BC148	12p	OC28	60p	2N3823E	39p
BC149	12p	OC71	14p	2N4060	12p
BC149	12p	OC72	14p	2N4871	36p
BC157	13p	ORP12	66p	2N5245	51p
BC158	13p	ZTX107	11p	2N5777	45p
BC159	13p	ZTX108	11p		
BC182L	12p	ZTX501	13p	1N914	4p
BC184	12p	ZTX503	15p	1N4001	6p
BC187	25p	ZTX531	23p	1N4002	7p
BC204	14p	2N706	13p	1N4004	8p
BC209C	14p	2N914	22p	1N4006	9p
BC212L	15p	2N1304	22p	1N4007	10p
BC213	15p	2N2219	27p	OA91	7p
BC478	25p	2N2905	27p	OA200	8p
BCY71	22p	2N2907	22p	OA202	8p
BF178	40p	2N3053	18p	Z5J (ZIL)	75p
BFY50	22p	2N3054	66p	Z5I71	16p

RHYTHM GENERATOR

(P.E. Mar./Apr. 74)

Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and soft cymbal), and with variable time signatures and rhythm rates. Really fascinating and useful. Tempo, Timing and Logic circuits £12.57
PCB for above circuits (double-sided) £2.84
Component set for all 8 effects circuits £10.49
Set of 4 PCB's to hold all 8 effects £4.74
Simple mixer (no PCB available) £2.76
Alternative mixer with external volume controls and adjustable gain (independently designed), including PCB £9.22
Power Supply, including PCB £6.32

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, velocity operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl. SWs) £6.36
Printed circuit board £1.54
Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce "jungle-drum" rhythms.

- Component set (incl. PCB) £2.47

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

- Component set (incl. PCB) £2.40

PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

- Component set (incl. PCB) £3.65

P.E. JOANNA

SEE OUR ADVERTISEMENT ON OPPOSITE PAGE

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

- Component set incl. PCB £2.63

POWER SUPPLIES

Sophisticated low-noise highly-stabilised power supply kits complete with PCB's and detailed information are now available. Details in list.

Other PCBs (all "as published") While stocks last
Bench Power Supply (P.E. Sept. 1974) 70p

- CCTV:
 - Master Logic, Video Amp., Sync Mixer and Cathode Switch PCB (P.E. Oct. 1974) £2.20
 - PCB for remaining Circuits (P.E. Oct. 1974) £2.20
 - Digital Power Supply (P.E. Aug. 1972) 50p
 - Electronic Piano:
 - Pre-amp PCB (P.E. Oct. 1972) 85p
 - Power Supply PCB (P.E. Oct. 1972) 60p
 - Power Slaves: Power Supply PCB (P.E. Aug. 1974) 55p
 - Rondo:
 - CBS SQ Decoder PCB (P.E. Sept. 1973) 60p
 - Pre-Amp PCB (P.E. Oct. 1973) 60p
 - Tone, Balance and Volume Control PCB (P.E. Oct.) £1.40

Integrated Circuits	Zeners	Electrolytic Capacitors (μF/V)
709 TOS 40p	3.3V 400mW 15p	0.47/63 8p
709 8-pin DIL 40p	3.9V 400mW 15p	1.0/63 8p
723 TOS 40p	4.7V 25p	1.5/63 6p
741 8-pin DIL 32p	5.1V 400mW 15p	2.2/63 6p
747 14-pin DIL 115p	5.1V 1W 25p	4.7/63 6p
748 TOS 63p	5.6V 400mW 15p	6.8/40 6p
748 TOS 63p	5.6V 1.3W 20p	10/25 6p
748 8-pin DIL 63p	6.2V 400mW 15p	13/50 6p
748 14-pin DIL 63p	6.8V 400mW 15p	15/40 6p
μA7805 TO220 165p	9.1V 400mW 15p	22/10 6p
μA7815 TO220 165p	10V 400mW 15p	22/25 6p
AY-1-0212 550p	11V 1W 25p	33/6.3 6p
CA3046 71p	12V 400mW 15p	33/16 6p
MC1312P 205p	12V 1W 25p	33/40 6p
MFC4000B 73p	15V 400mW 15p	33/50 6p
MFG6040 83p	18V 1W 25p	47/10 6p
SG3402N 202p	18V 1W 25p	47/25 6p
3015FEP27 135p	20V 400mW 15p	47/40 6p
(7-segment numeric display)	20V 1W 25p	47/63 7p
	27V 400mW 15p	100/10 6p
		100/25 6p

Polyester (μF)	Tantalum (μF/V)
0.01 3p	0.1/35 13p
0.015 3p	0.22/35 13p
0.022 3p	0.47/35 13p
0.033 3p	1.0/35 13p
0.047 3p	1.5/35 13p
0.068 3p	2.2/35 13p
0.1 4p	4.7/35 16p
0.15 5p	10/16 16p
0.22 5p	10/25 18p
0.33 7p	15/6.3 18p
0.47 9p	22/16 18p
0.68 11p	47/6.3 18p
1.0 14p	47/16 30p
2.2 24p	100/3 18p

SEE OUR LIST FOR OTHER GOODS STOCKED

Prices are correct at time of press. E. & O.E. deliveries subject to availability.

LIST
Send S.A.E. with all U.K. requests for free list giving fuller details of PCBs, kits, and other components.
Overseas enquiries for list:
Europe—send 20p.
Other countries—send 30p.

POST AND HANDLING
U.K. orders: under £15 add 22p. over £15 add 40p.
Optional: Fee for compensation against loss or damage in post (U.K., Eire & C.I. only): 35p.

VAT
Add 25% (or current rate if different) to full total of goods, post and handling.
Overseas—VAT does not currently apply.

Overseas—will be charged extra. minimum charge 70p. Details of kit weights, and postage rates will be sent with list.
Eire and Channel Isles classify as overseas for posting purposes.

PHONOSONICS, DEPT. PE30, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW MAIL ORDER AND C.W.O. ONLY DON'T FORGET VAT!


SAXON ENTERTAINMENTS LTD.

NEW PROFESSIONAL QUALITY MODULES TO SAVE YOU £ £ £s

THE NEW POWER AMPLIFIERS

Three brilliant new power modules employing the same circuitry use 10 transistors, three diodes and one zener diode, with electronic over temperature cutout as well as normal thermal protection, load line short circuit and wrong load protection, integrally mounted output capacitor, etc. Fused supply and output terminals. Solder or screw connected. The input impedance is high enough to accept all types of mixer having an output of 250mV.

- * NEW 90°C overtemperature electronic cut-out, not mechanical.
- * NEW integral output capacitor means no external components normally required.
- * Short circuit load line type protection with twin summing amplifiers.
- * Inherently open circuit proof.
- * Input sensitivity - 10dBm (240mV into 100k) permits use with most mixers.
- * Frequency response 20Hz-40kHz \pm 1dB.
- * Distortion typically 0.4%. Noise - 80dB.
- * Compact: only 15cm x 8cm x 3cm.
- * Suitable for all public address, discotheque, and group applications.
- * Fused supply and output terminals.
- * Single supply line (split supply not required).

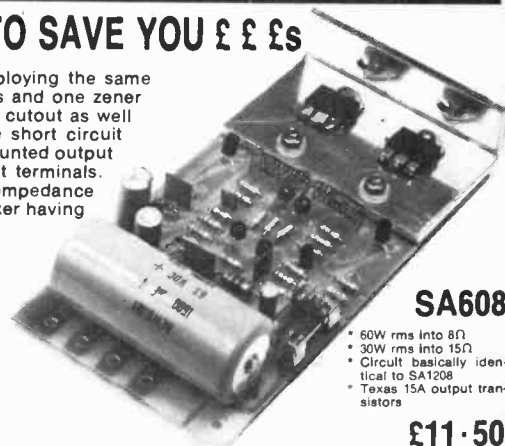

SA608

- * 60W rms into 8 Ω
- * 30W rms into 15 Ω
- * Circuit basically identical to SA1208
- * Texas 15A output transistors

£11.50

CONSTRUCTIONALLY AND ELECTRONICALLY IMPROVED: MULTIPLE TESTED: GUARANTEED

SA1208

120W rms into 8 Ω , or 60W rms into 15 Ω . Glass fibre pcb for strength and hard wear. Texas 15A output transistors.

£16.00

SA308

30W rms into 8 Ω , or 15W rms into 15 Ω . Circuit is basically identical to that of SA1208. 10A "Plastic Power" output transistors, etc.

£9.00

THE NEW POWER SUPPLIES

One piece units, ready to wire assembly with integral glass fibre pcb, size 10 x 8 x 10cm (PM1201 10 x 8 x 13cm). Grain oriented laminated transformers are used for compactness. Also facilities for preamp supply. Fully fused.

PM1201 95V for one SA1208

£11.00

PM1202 95V for two SA1208

£14.00

PM601 65V for one or two SA608

£9.00

PM301 45V for one or two SA308

£7.50


SAXON SUPERFECT

(illustrated)

All these features in ONE UNIT:

No other commercially available module to our knowledge, offers all these facilities in one complete unit.

Sequential display with variable speed, frequency dependent channels—individually fused, and continuously variable function control to give uninterrupted light display in absence of signal. Electronic override on each channel. RCA 8A triacs handling 1,000W per channel, plus timer circuitry to reduce "flicker". Individually controlled bass middle and treble plus master audio control for ease of adjustment.

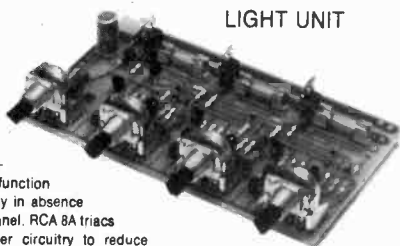

LIGHT UNIT

£19.75

SAXON SOUND-LITE

Our ever popular 3000 watt unit is now available in module form at only £13.50. Gives individual control of bass middle and treble plus master control for ease of adjustment. 1,000W per channel—individually fused. Negligible load on amplifier. RCA 8 AMP triacs for reliability.


£13.50

The ultimate in mixer modules

* Inputs for two decks (ceramic cartridge) plus tape, with overall bass and treble controls.
 * Hi/lo imp. mic. input with separate volume bass and treble controls. * Continuously variable autofade depth plus preset threshold control. * Up to 0.5W from low distortion push pull monitor amplifier. * Frequency response 20Hz-50kHz -1dB. * Low noise (-80dB) virtual earth mixing circuitry. * Low power consumption (20mA at 18 volts). * Size: mono 40 x 6 x 3cm, stereo 40 x 10 x 3cm. * Output - 10dBm (240mV) suits all Saxon and most other amplifiers.

MODULAR PRE-AMPS

Mono and Stereo
 Up to 20 x IM7001 input modules may be used with mixer module IM17002. Each input module has various types of equalisation and monitor path outlets.

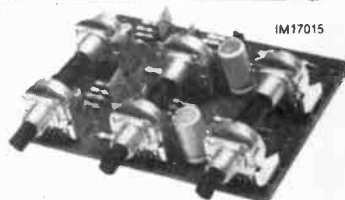

IM17015

* With equalisation to suit ceramic AND magnetic cartridges, low and high imp. mic. and all musical instruments. * Mono and stereo. * Mono module may be matrixed into a stereo system. * Carbon film resistors in low noise circuitry. * 20Hz-50kHz \pm 1dB response. * Wide range bass and treble controls—zero noise with volume at min. * For 18V operation. * Outputs for monitoring and echo send. * May be used with the discotheque mixers and Minotaur amplifiers.

IM7001M (mono) £5.50

IM7001S (stereo) £9.00

IM7002 MIXER MODULE with output suitable for most amplifiers PLUS up to 1W of monitoring power.

- * Accepts up to twenty IM7001 input modules.
- * Mono or stereo.
- * Up to 3V output—will feed loads down to 600 ohms.
- * Up to 1W into 8 Ω for monitoring (will feed higher impedance).
- * Accepts echo and other effects return signals.

IM7002M (mono) £5.50

IM7002S (stereo) £9.00

SAXON MONO AND STEREO DISCOTHEQUE MIXERS WITH AUTO FADE



MONO VERSION £18.50

STEREO VERSION £27.50

SAXON ENTERTAINMENTS LTD. 327 WHITE HORSE ROAD, CROYDON, SURREY, CR0 2HS

SYSTEM 7000

PROFESSIONAL STANDARD COMPLETE UNITS

A total range project to satisfy the most discerning

Note these compelling features:

- Stainless Steel Escutcheons†
- Totally compatible with all Saxon modules.
- Tough easily-read facts.
- Plug/socket terminations throughout.
- 100W rms into 8Ω.
- Two mixed inputs, wide range bass and treble controls.
- May be operated as a slave amplifier.
- Amazingly compact (27 x 16 x 10cm).




* Fully protected against all incorrect loads and short circuits.

MINOTAUR 100 £47.50

† Except Minotaur (anodised aluminium)

SYSTEM 7000 DISCO CONTROL UNIT

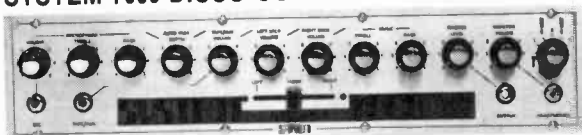

- Mono or stereo versions.
- Two deck and one tape inputs. Individually controlled plus deck fader (ineffective in central position).
- Wide range bass and treble controls plus separate mic. vol. bass and treble controls. Overall master control.
- Continuously variable autofade depth and threshold.
- Five position monitoring switch with two mute positions—ample headphone power.
- Noise -80dB response 20Hz-50kHz ±1dB.
- Complete, cased with all terminations by plug socket, etc.

MONO VERSION £28.50


STEREO VERSION £45.00

SYSTEM 7000 MODULAR MIXING

COMPLETE VERSIONS OF THE IM7001 AND IM7002 modules shown in our advertisement.

Let you make a professional quality versatile mixer to your requirements using these modules. Mono and stereo inputs may be combined.

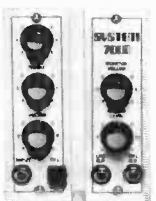- The mixing modules split mono signals.
- Each input module has own monitor switch.
- Stainless steel panel on 15 x 5cm matrix (approx.)
- Input equalisation for all types of signal inc. magnetic cartridge.
- Complete system may comprise twenty channels, mono or stereo with ample monitoring power.
- May be patched in with disco mixers or Minotaur amplifier.



MONO INPUT MODULE £8.50
STEREO INPUT MODULE £12.00
MONO MIXER MODULE £8.50

STEREO MIXER MODULE £12.00
POWER SUPPLY UNIT FOR UP TO 20 MODULES £7.50

SYSTEM 7000 LIGHTING CONTROL UNIT

1,000W per channel. Sound light and SEQUENTIAL and OVERRIDE.
Individual bass, mid, and treble controls.
Master control.
Plug/socket terminations.
Slider control for function, for sound/light, sequencing or both combined.
Stainless steel front panel matching to disco control unit.
Compact (17 x 10 x 10cm approx.).
Electronic override eliminates clicks.
High sensitivity, negligible input power.



£35

All Saxon Modules are guaranteed for two years from date of purchase
To order, telephone 01-684 6385 now or call 01-684 0098 for more details.
WE ACCEPT TELEPHONE ORDERS FOR C.O.D. AND ACCESS/BARCLAYCARD ACCOUNT HOLDERS

If ordering by post please send cheque/crossed postal orders made payable to Saxon Entertainment Ltd. or simply enclose your Access/Barclaycard number.
Shop hours Mon.-Sat. 9.00-5.00 p.m. Tel. 01-684 6385

All prices include postage and packing, but V.A.T. at 8% must be added to total value of order.

Trade enquiries
Saxon products are available from Norman Rose Electrical Ltd.

Branches in:
London. Tel: 01-837 9111
Manchester. Tel: 061-273 1498

Birmingham. Tel: 021-236 4710
Bradford. Tel: (0274) 24006

TRANSFORMERS

ALL EX-STOCK

MAINS ISOLATING 115V or 240V Sec. only Centre Tapped and Screened				12 AND OR 24 VOLT PRIMARY 240-250 VOLTS			
Ref. No.	VA (Watts)	£	P & P	Ref. No.	Amps	£	P & P
07	20	2.80	38	111	0.5 0.25	1.35	23
149	60	4.37	45	213	1.0 0.5	1.74	30
150	100	4.89	45	71	2 1	2.66	38
151	200	8.13	53	18	4 2	4.12	45
152	250	9.83	73	108	8 4	4.56	45
153	350	11.88	73	72	10 5	5.14	53
154	500	13.65	91	116	12 6	5.52	53
155	750	20.51	BRS	17	16 8	7.28	60
156	1000	29.15	BRS	115	20 10	10.39	73
157	1500	33.23	BRS	187	30 15	13.59	83
158	2000	37.07	BRS	228	60 30	16.83	BRS

30 VOLT RANGE Secondary Taps 0-12-15-20-24-30			
Ref. No.	Amps.	£	P & P
112	0.5	1.81	30
79	1.0	2.40	38
3	2.0	3.49	38
20	3.0	4.35	45
21	4.0	5.13	53
51	5.0	6.41	53
117	6.0	7.16	60
88	8.0	9.87	67
89	10.0	9.90	73

50 VOLT RANGE Secondary Taps 0-19-25-33-40-50			
Ref. No.	Amps.	£	P & P
102	0.5	2.58	30
38	1.0	3.38	38
103	2.0	4.68	45
104	3.0	5.81	53
105	4.0	7.60	67
106	6.0	12.10	67
107	8.0	12.98	85
118	10.0	16.99	BRS

60 VOLT RANGE Secondary Taps 0-24-30-40-48-60			
Ref. No.	Amps.	£	P & P
124	0.5	2.33	38
126	1.0	3.41	38
127	2.0	5.08	45
125	3.0	7.52	60
123	4.0	8.75	67
40	5.0	9.75	73
120	6.0	11.30	85
121	8.0	15.00	BRS
122	10.0	17.52	BRS
189	12.0	19.98	BRS

AUTO TRANSFORMERS			
Ref. No.	VA (Watts)	£	P & P
113	20 0-115-210-240	1.67	30
64	75 0-115-210-240	2.90	38
4	150 0-115-200-220-240	4.12	45
66	300 0-115-200-220-240	5.82	53
67	500 0-115-200-220-240	8.82	67
84	1000 0-115-200-220-240	13.58	91
93	1500 0-115-200-220-240	18.11	BRS
95	2000 0-115-200-220-240	24.20	BRS
73	3000 0-115-200-220-240	35.09	BRS

SCREENED MINIATURES			
Ref. No.	mA	Volts	£ P & P
238	200	3-0-3	1.54 10
212	1A, 1A	0.6-0.6	1.44 30
13	100	9-0-9	1.41 13
235	330, 330	0.9-0.9	1.56 19
207	500, 500	0.8-0.8	1.92 30
208	1A, 1A	0.8-0.8	3.20 38
236	200, 200	0-15-0-15	1.43 30
214	300, 300	0-20-0-20	1.93 30
221	700 (d.c.)	20-12-0-12-20	3.48 38
206	1A, 1A	0-15-20-0-15-20	3.00 38
203	500, 500	0-15-27-0-15-27	3.85 38
204	1A, 1A	0-15-27-0-15-27	3.85 38
S112	500	12-15-20-24-30	1.88 37

CASED AUTO TRANSFORMERS
240V mains lead input and U.S.A. 2-PIN outlets 20VA £3.23 P & P 38p. 113W 150VA £6.70 P & P 62p. Ref. 4W 500VA £10.45 P & P 80p 67W 1000VA £17.51 BRS 84W

HIGH VOLTAGE MAINS ISOLATING Prim. 200/220 or 400/440 Sec. 100/120			
Ref. No.	VA	£	P & P
60	243	4.37	63
350	247	10.41	95
1000	250	27.06	BRS
2000	252	41.07	BRS

PLUS

BRIDGE RECTIFIERS		30p
50V	2A	30p
100V	2A	35p
200V	1A	40p
400V	4A	60p
600V	2A	45p
500V	10A (PM 7A6)	£2.35

POWER UNITS
CC12-05 Output Switched
3-4-5-6-7 5-9-12V at 500mA. £4.08. P & P 30p

TEST METERS		£50-80
AVO 8 MK5		£19.75
AVO 72		£11.80
U4313*		£13.85
U4315*		

CAPACITORS
MINIATURE CERAMIC
50V 22pF—0.047 mF 30p per DOZ.
PAPER (MCTAL CASED)
1000V 0.01-0.025-0.050-0.1 mF
85p per DOZ. P & P 15p

MAINS KEYNECTORS
£3.25 P & P 25p

MAINS TIMER
Delay 1-30 minutes
(Adjustable)
£5.95 P & P 25p

PLEASE ADD VAT AFTER P & P
ELECTROSIL AND SEMICONDUCTOR STOCKIST.
Send stamp for lists

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

TRANSISTORS	
BC182	10p
BC184	11p
BC204	11p
BC209C	11p
BC212	14p
BC213	15p
BC214	16p
MPS-L01	39p
MPS-L51	41p
MPS-U07	69p
MPS-U57	85p
SDT9203	210p
ZTX300	15p
ZTX500	17p
2N2219	22p
2N2484	24p
2N2904	30p
2N2905	27p
2N3054	100p
ARRAYS	
CA3046	75p
CA3096AE	120p
DIODES	
BA148	25p
1GP7	10p
1N914	5p
1N5401	21p
1SJ50	12p
NOISE DIODES	
Z5J (Z1J)	75p
Z1M	120p
RECTIFIERS	
EA100/10	100p
MDA942A	210p
REC41A	120p
REC46	255p
REC70	40p
OP. AMPS	
709 (8-dii)	39p
710 (70S)	39p
741 (8-dii)	37p
748 (8-dii)	48p

EXCLUSIVE TO EATON AUDIO—a professional quality modular constructional case system by VERO ELECTRONICS LTD, designed with the amateur's project in mind. Wide choice of modules from ½in to 8in wide. Send large S.A.E. or 10p stamp for illustrated leaflet and price list before you start your next project.

DON'T BUY ANYTHING . . .
 UNTIL YOU HAVE ALL THE FACTS ABOUT THE MINISONIC. Without any doubt, the best value for money in synthesisers today. Performance and versatility equal to ready made instruments costing over five times as much. Very high stability log oscillators (2); filter; noise generator; versatile keyboard control system; envelope shaper and V.C.A. (2 each); ring modulator and headphone/L.S. output.
Hear It—Exclusive C20 demonstration cassettes still available. "AUDIO FAIR 1974", an introduction to the MINISONIC by G. D. Shaw, and "SYMBIOSIS", an experimental composition for the MINISONIC by Malcolm Pointon.
 Each tape, £1.06 post free Together, £1.86 post free. VAT 8%
See It—At the AUDIO FAIR 1975.
Play It—SYNTHESISER MUSIC SERVICES, 12 Holland Park Road, W11, Tel. 01-221 5665, have the MINISONIC on permanent demonstration.
Read It—Reprints of the MINISONIC series are available *only* from EATON AUDIO, details in lists.
Buy It—A top line Synthesiser in its own right, or a worthy addition to any music studio—you cannot fail to be impressed, not least by our new lower prices!
 BASIC COMPONENT KIT, £38.00, UK post free
 POWER SUPPLY KIT, £8.90, UK post free
 Lists—send S.A.E. or 10p stamps.

LINEARS	
MFC6040	100p
SG1495D	290p
SG3402N	174p
SG3402T	174p
UA7815	220p
723	180p
RESISTORS	
Triple rated high stability carbon film, 5 for 7p. Metal oxide half watt, 5 for 16p. Both types, E12 values from 4R7 to 3M9.	
POTENTIOMETERS	
Carbon 24mm, lin and log, 5kΩ to 1MΩ, 25p. Wirewound 1W, lin only, 10Ω to 25kΩ semi-precision, 82p.	
PRESETS	
Carbon, horizontal miniature, all values 10Ω to 2MΩ, 10p. Cermet, horizontal miniature, all values 10Ω to 1mΩ, 45p. Cermet, rectilinear 20 turn, all values 100Ω to 500kΩ, 128p.	
RESISTANCE WIRE	
Constantan, 0.0293Ω per metre: 20cm 10p Per metre 40p	

C.MOS LOGIC
 Now available at bargain prices.
 Examples:
 MC14011C 21p
 MC14016C 55p

EXTRA SPECIAL LINEARS			
Device	Description	Manuf.	Case Cost
LM318N	Very high speed, high gain, op. amp. (70V/μS)	N.S.	T05 257p
LM381N	Very low noise, dual, audio preamp. (0.7μV noise)	N.S.	14-dii 174p
LM1306P	Half-watt, 8 ohm, audio preamp, and amplifier	N.S.	8-dii 75p
MC1741SCP	High speed 741, compensated, direct replacement	Mot.	8-dii 107p
ZN424E	High speed, low noise, operational amplifier	Fer.	14-dii 130p

DATA SHEETS, all devices, 10p extra

ZENERS—SPECIAL OFFER
 Standard values: 2.7V to 15V, 400MW devices, only 8p

EATON AUDIO


DEPT. PE, P.O. BOX 3
 ST. NEOTS, CAMBS.
 PE19 3JB

TERMS: MAIL ORDER ONLY, C.W.O. MINIMUM ORDER £1. VAT: Please add 25% to value of order inc. P. & P. unless otherwise stated. Cheques or P.O.s payable to Eaton Audio. Orders over £5 free of P. & P., otherwise please add 10p in the £1.

GIVE YOUR TELEVISION HI-FI SOUND

-exclusive tuner constructional design

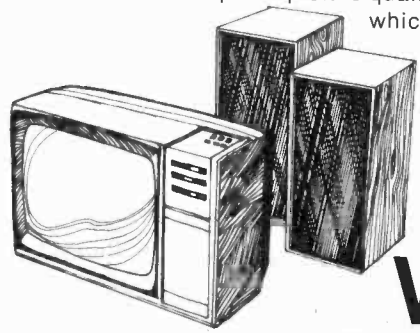Our TV tuner receives the signal from the TV aerial and produces an audio signal which can be fed into your hi-fi equipment. The result is not only high quality sound but also a high quality video signal which can be fed back into your set to improve picture quality. The tuner consists of a printed circuit board



which can be either mounted in a small cabinet or installed in existing equipment. Full details in this issue. We've also got a feature on progress in multiphonic organs and a resistor survey.

Wireless World

OCTOBER ISSUE 35p

Marshall's

A. Marshall (London) Ltd Dept: PE
 42 Cricklewood Broadway London NW2 3ET
 Tel: 01-452 0161/2 Telex: 21492
 & 85 West Regent St Glasgow G2 2QD
 Tel: 041-332 4133
 & 1 Straits Parade Fishponds Bristol BS16 2LX
 Tel: 0272 654201/2
 & 27 Rue Danton Issy Les Moulineaux Paris 92
 Tel: 642 2985

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat
 Trade and export enquiries welcome

Catalogue price 25p

Top 500 Semiconductors From the Largest Range in the U.K.

2N4556	0-80	Orange	0-12	2N5192	1-24	AF106	0-40	BC184	0-13	BF153	0-25	LM308	2-50	OC35	0-60
2N4564	0-85	2N3053	0-25	2N5195	1-46	AF109R	0-40	BC184L	0-13	BF154	0-20	LM309K	1-88	OC42	0-50
2N457A	1-20	2N3054	0-60	2N5245	0-47	AF114	0-35	BC186	0-25	BF159	0-27	LM381	1-50	OC45	0-32
2N490	4-14	2N3055	0-75	2N5294	0-48	AF115	0-35	BC187	0-27	BF160	0-23	LM381	1-20	OC71	0-20
2N491	4-38	2N3390	0-45	2N5295	0-48	AF116	0-35	BC207	0-12	BF165	0-32	LM702C	0-75	OC72	0-25
2N492	5-00	2N3391	0-28	2N5296	0-48	AF117	0-35	BC208	0-11	BF166	0-40	LM709	0-75	OC81	0-25
2N493	5-20	2N3391A	0-29	2N5298	0-50	AF118	0-35	BC212K	0-16	BF167	0-25	TO99	0-48	OC83	0-24
2N596	0-22	2N3392	0-15	2N5457	0-49	AF124	0-30	BC212L	0-16	BF173	0-27	8DIL	0-38	ORP12	0-55
2N597	0-16	2N3393	0-15	2N5458	0-46	AF125	0-30	BC214L	0-18	BF177	0-29	8DIL	0-38	R53	1-80
2N598	0-82	2N3394	0-15	2N5459	0-49	AF126	0-28	BC237	0-18	BF178	0-35	LM723C	0-90	SL414A	1-80
2N599	0-59	2N3402	0-18	2N5492	0-58	AF127	0-28	BC238	0-15	BF179	0-43	LM710	0-47	SL610C	1-70
2N706	0-14	2N3403	0-18	2N5494	0-58	AF139	0-65	BC239	0-15	BF180	0-35	LM710	0-47	SL611C	1-70
2N706A	0-18	2N3440	0-59	2N5496	0-61	AF166	0-48	BC251	0-25	BF181	0-36	LM710	0-47	SL620C	2-60
2N708	0-17	2N3441	0-87	2N5777	0-45	AF200	0-65	BC253	0-25	BF182	0-35	LM710	0-47	SL621C	2-60
2N709	0-42	2N3442	1-10	2N6027	0-45	AF239	0-65	BC257	0-16	BF183	0-55	LM747	1-00	SL623	4-59
2N711	0-50	2N3444	0-20	3N128	0-73	AF240	0-90	BC258	0-16	BF184	0-30	LM748	1-00	SL640C	3-10
2N718	0-23	2N3415	0-21	3N139	1-42	AF279	0-70	BC259	0-17	BF185	0-30	8DIL	0-60	SL641C	3-10
2N718A	0-28	2N3416	0-34	3N140	1-00	AF280	0-79	BC261	0-25	BF194	0-12	14DIL	0-75	SN75003N	1-85
2N720	0-57	2N3417	0-24	3N141	0-81	AL102	1-00	BC262	0-25	BF195	0-12	LM3900	0-70	SN76023N	1-80
2N814	0-39	2N3538	0-15	3N200	2-49	AL103	1-00	BC263	0-25	BF196	0-12	LM7805	2-00	SN76033N	2-60
2N816	0-28	2N3638A	0-15	40361	0-40	BC107	0-14	BC300	0-38	BF197	0-15	LM7812	2-50	ST2	2-20
2N818	0-32	2N3639	0-27	40362	0-45	BC108	0-14	BC301	0-34	BF198	0-18	LM7815	2-50	TAA263	1-10
2N929	0-37	2N3641	0-17	40363	0-88	BC109	0-14	BC302	0-29	BF200	0-20	LM7824	2-50	TAA300	1-80
2N930	0-22	2N3702	0-12	40389	0-48	BC113	0-15	BC303	0-54	BF225J	0-43	MC1303	1-50	TAA550	0-60
2N1302	0-19	2N3703	0-13	40394	0-58	BC115	0-17	BC307	0-17	BF244	0-21	MC1310	2-92	TAA550	0-60
2N1303	0-19	2N3704	0-15	40395	0-58	BC116	0-17	BC308A	0-16	BF245	0-45	MC1330P	0-60	TAA611C	2-18
2N1304	0-26	2N3705	0-15	40406	0-44	BC166A	0-18	BC309C	0-20	BF246	0-58	MC1351P	0-60	TAA621	2-03
2N1306	0-31	2N3707	0-18	40408	0-50	BC118	0-21	BC237	0-32	BF247	0-65	MC1352P	0-60	TAA661B	1-32
2N1307	0-30	2N3708	0-14	40409	0-52	BC119	0-29	BC337	0-20	BF255	0-19	MC1466	3-50	TBA641B	2-25
2N1308	0-47	2N3709	0-15	40410	0-52	BC121	0-25	BC338	0-20	BF257	0-47	ME0402	0-20	TBA651	1-89
2N1309	0-47	2N3710	0-15	40411	2-80	BC125	0-16	BCY30	0-80	BF258	0-53	ME0404	0-19	TBA800	1-50
2N1671	1-54	2N3711	0-15	40554	0-74	BC126	0-23	BCY31	0-85	BF259	0-55	ME4102	0-11	TBA920	4-00
2N1671A	1-67	2N3712	1-20	40595	0-84	BC132	0-30	BCY32	1-15	BF259	0-55	ME4104	0-11	TIL209	0-30
2N1671B	1-85	2N3713	1-20	40601	0-67	BC134	0-13	BCY33	0-85	BF279	0-24	MJ481	1-45	TIP29A	0-49
2N1711	0-45	2N3714	1-38	40602	0-61	BC135	0-13	BCY34	0-79	BF521A	2-30	MJ481	1-45	TIP29C	0-80
2N1907	5-50	2N3715	1-50	40603	0-53	BC136	0-17	BCY38	1-00	BF528	0-92	MJ490	1-05	TIP29C	0-80
2N2102	0-64	2N3716	1-80	40604	0-56	BC137	0-17	BCY39	1-50	BF561	0-27	MJ490	1-05	TIP30A	0-85
2N2147	0-78	2N3717	1-20	40636	1-10	BC138	0-24	BCY40	0-47	BF598	0-25	MJ295S	1-00	TIP31A	0-82
2N2148	0-94	2N3772	1-80	40669	1-00	BC140	0-58	BCY42	0-28	BF599	0-30	MJ340	0-48	TIP31C	1-00
2N2160	0-90	2N3773	2-65	40673	0-73	BC141	0-68	BCY58	0-30	BFX30	0-27	MJ340	0-48	TIP32C	1-74
2N2162A	0-22	2N3789	2-06	AC126	0-20	BC142	0-23	BCY59	0-32	BFX84	0-24	MJ295S	1-00	TIP32A	0-75
2N2219	0-24	2N3790	2-46	AC127	0-20	BC143	0-25	BCY60	0-17	BFX85	0-20	MJ305S	0-75	TIP32C	1-24
2N2219A	0-26	2N3791	2-35	AC128	0-20	BC145	0-21	BCY71	0-22	BFX87	0-28	MJ370	0-65	TIP33C	1-45
2N2220	0-25	2N3792	2-60	AC151V	0-27	BC147	0-14	BCY72	0-15	BFX88	0-25	MJ371	0-75	TIP33A	1-51
2N2221	0-18	2N3794	0-24	AC152V	0-49	BC148	0-14	BD115	0-75	BFX89	0-90	MJ520	0-75	TIP34A	1-45
2N2221A	0-21	2N3819	0-37	AC153	0-35	BC149	0-15	BD116	0-75	BFY50	0-23	MJ521	0-70	TIP34C	2-60
2N2222	0-20	2N3820	0-84	AC153K	0-40	BC153	0-18	BD121	1-00	BFY51	0-23	MP8111	0-32	TIP35A	2-80
2N2222A	0-25	2N3823	0-78	AC154	0-25	BC154	0-18	BD123	0-82	BFY52	0-21	MP8112	0-40	TIP36A	3-70
2N2368	0-25	2N3904	0-27	AC176	0-30	BC157	0-16	BD124	0-87	BFY53	0-18	MP8113	0-47	TIP41C	1-40
2N2369	0-20	2N3906	0-27	AC176K	0-40	BC158	0-16	BD131	0-40	BFY90	0-75	MPSA05	0-28	TIP42A	1-80
2N2646	0-55	2N4037	0-42	AC187K	0-35	BC160	0-80	BD132	0-50	BSX20	0-21	MPSA06	0-31	TIP42C	0-80
2N2647	0-98	2N4058	0-18	AC189K	0-40	BC167B	0-15	BD135	0-43	BSX21	0-29	MPSA12	0-35	TIP49C	0-70
2N2904	0-22	2N4059	0-15	ACY19	0-27	BC168C	0-15	BD136	0-49	BSX21	0-29	MPSA15	0-35	TIP53	1-70
2N2904A	0-24	2N4060	0-15	ACY20	0-22	BC169B	0-15	BD138	0-63	BU105	2-25	MPSA56	0-31	TIP295S	0-88
2N2905	0-25	2N4061	0-15	ACY21	0-26	BC169C	0-15	BD139	0-71	CI06D	0-65	MPSU05	0-65	TIP305S	0-50
2N2905A	0-26	2N4062	0-15	ACY28	0-20	BC170A	0-15	BD140	0-87	CA3018A	1-00	MPSU55	0-63	TX300	0-13
2N2906	0-19	2N4126	0-21	ACY38	0-58	BC171	0-16	BD159	0-80	CA3020A	1-00	MPSU56	0-80	TX301	0-13
2N2906A	0-21	2N4289	0-34	AD142	0-57	BC172	0-17	BD530	0-80	CA3028A	0-79	MPSU56	0-80	TX302	0-18
2N2907	0-22	2N4919	0-95	AD143	0-68	BC177	0-28	BDY20	1-05	CA3035	1-36	NE555V	0-70	TX300	0-20
2N2907A	0-24	2N4920	1-10	AD149V	1-20	BC178	0-27	BF115	0-30	CA3046	0-70	NE556	1-30	TX302	0-15
2N2924	0-20	2N4921	1-83	AD150	1-15	BC179	0-30	BF117	0-55	CA3048	2-11	NE560	4-48	TX301	0-13
2N2925	0-20	2N4922	1-00	AD161	0-50	BC182	0-12	BF121	0-35	CA3052	1-62	NE561	4-80	TX302	0-18
2N2926	0-24	2N4923	1-00	AD162	0-50	BY182L	0-12	BF123	0-35	CA3089E	1-62	NE565A	4-48	TX350	0-23
Green	0-12	2N5190	0-92	AD161	0-50	BC183	0-12	BF125	0-35	CA3090Q	4-23	OC23	1-35		
Yellow	0-12	2N5191	0-98	AD162	0-50	BC183L	0-12	BF152	0-20	LM301A	0-48	OC28	0-78		

OC35	0-60
OC42	0-50
OC45	0-32
OC71	0-20
OC72	0-25
OC81	0-25
OC83	0-24
ORP12	0-55
R53	1-80
SL414A	1-80
SL610C	1-70
SL611C	1-70
SL620C	2-60
SL621C	2-60
SL623	4-59
SL640C	3-10
SL641C	3-10
8DIL	0-60
14DIL	0-75
LM3900	0-70
LM7805	2-00
LM7812	2-50
LM7815	2-50
LM7824	2-50
MC1303	1-50
MC1310	2-92
MC1330P	0-60
MC1351P	0-60
MC1352P	0-60
MC1466	3-50
MC1469	2-75
ME0402	0-20
ME0404	0-19
ME4102	0-11
ME4104	0-11
MJ481	1-45
MJ490	1-05
MJ295S	1-00
MJ340	0-48
MJ370	0-65
MJ371	0-75
MJ520	0-75
MJ521	0-70
MP8111	0-32
MP8112	0-40
MP8113	0-47
MPP102	0-34
MPSA05	0-28
MPSA06	0-31
MPSA12	0-35
MPSA15	0-35
MPSA56	0-31
MPSU05	0-65
MPSU55	0-63
MPSU56	0-80
NE555V	0-70
NE556	1-30
NE560	4-48
NE561	4-80
NE565A	4-48
OC23	1-35
OC28	0-78

PW TELE TENNIS KIT
 As featured on BBC Nationwide and in the Daily Mail 2 Oct. 74. Ideal game for whole family. No need to modify your TV set just plug in to aerial socket.
 Parts list as follows: A Resistor Pack £1.25 P & P 20p. B Potentiometer Pack £1.25 P & P 20p. C Capacitor Pack £3.10 P & P 20p. D Semiconductor Pack £14.50 P & P 20p. E IC Sockets £4 P & P 20p. F Transformer £1.15 P & P 25p. G PCB's £7




TRAMPUS

Electronics Ltd.
WINDSOR, BERKS.
58/60 GROVE RD:
SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p. EXPORTS 60p.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. CALLERS WELCOME.
CATALOGUE/LIST FREE SEND SAE.
BARCLAYCARD & ACCESS x POST.

Digital Displays

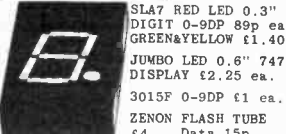

LEDS red 13P

LEDS 209 STYLE ONLY 13p ea
TIL 209 WITH CLIP RED 15p ea
TIL 211 & CLIP GREEN 29p ea
LARGE 0.2" & CLIP RED 17p ea
LARGE 0.2" CLIP GREEN 30p ea
209 STYLE OR .2" ORANGE 29p ea
INFRA RED LED £1.2N5777 33p.

PHOTO IC 81P

TEC12 PHOTO AMP/SCMITT/RELAY
DRIVER or LED TTL INTERFACE 81p



FLUORESCENT LIGHTS 12V MADE IN UK
8 WATT 13" £3. 13W 22" £3.50

DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75
MM5311/4 6 DIGIT CLOCK £7

CASSETTE mechanics £13.75

NEW 8tk CARTRIDGE MECHANISM £8
STEREO CASSETTE MECHANISM £13.75
Suitable for 'PW ASCOT' recorder
with heads etc. SEND 15p for DATA

INTEGRATED CIRCUITS

709 D1L4 29p	LM377 2x2Wf2.87
565 TIMER 54p	LM380 2W AF 89p
703 RF/IF 28p	LM381 2xPre £2
709 T099 23p	LM3900 4xOPA69p
709 DIL 14 28p	MC1303 £1.20
710 DIL 14 34p	MC1306 49p
723 Reg. 54p	MC1310&LED£2.65
741 DIL 8 27p	MC1312 SQ £2.10
741 DIL 14 29p	MC1330 69p
741 T099 29p	MC1339 2xPre £1
747 2x741 70p	MC1350 55p
748 DIL 8 33p	NE536 fetOPA £2
7805 5V £1.40	NE540 Driver £1
7812 & 15 £1.40	NE550 2vRef 79p
76013 6W AF £1	NE555 Timer 55p
8038 SIG GEN £3	NE556 2X" £1.20
CA3028 £1	NE560 PLL £3.15
CA3046 55p	NE561 PLL £3.15
CA3048 £2	NE562 PLL £3.10
CA3052 £1.50	NE565 PLL £2.69
CA3054 £1	SN72709 709 28p
LM300 2-20V £2	SN72741 741 26p
LM301 OPA 45p	SN72748 748 33p
LM304 0-40V £3	SN76660 1F £1.25
LM307 OPA 49p	SN76611 1F £1.25
LM308 HiCo 95p	TAD110 & IF £2
LM309K 5V £1.48	TB8910 78AF 99p
LM372 1F £1.80	ZN414 RX £1.09

SPECIAL OFFERS

2N3055 FULL HIGH SPEC 115W 37p
741C 8PIN DIL 27p. MFC4000B 33p
NE555 TIMER 55p. ZN414 RX £1.09
BC109 9p. 2N3819e 16p. BFY51 15p

749 TTL

7400 GATES 13p	7473/74/76 29p
7404 INVERT 17p	7475 45p
7401/2/10etc14p	7490 52p
7413 SCMITT 31p	7491/2/3/4 59p
7440 BUFFER 14p	74100 74175 £1
7447 DRIVER 89p	74121 32p
7470 & 7472 29p	74123 59p
	74141 (& 7441) 73p

TRANSISTORS & DIODES

Price each	MATCHING	16p
AC127 & 128 16p	INS, BUSH SET10p	
AC187 & 188 19p	TIP 41 70p	
AD149 43p	TIP 42 88p	
AD161 & 162 39p	TIP 2955 90p	
BC107 & 108 9p	TIP 3055 55p	
BC109 10p	TIS43 aae2N2668	
BC147/8/9 10p	ZTX109A301 13p	
BC157/8/9 12p	1N4001 4p	
BC167/8/9 12p	1N4004 & 7 7p	
BC177/8/9 18p	1N4148 & 914 4p	
BC182/3/4A&L10p	2N697 14p	
BC212/3/4A&L11p	2N70688 11p	
BCY70/1/2 17p	2N2646 UJT 32p	
BD131 & 132 39p	2N2904 & 5 20p	
BFR51 2N2926trovgy 9p	BFR50/51 23p	
BFR50/51 23p	2N3053 17p	
BFR88 250V 29p	2N3055 115W 37p	
BFY50/1/2 15p	2N3563 & 64 16p	
BSX19/20/21 16p	2N3614 49p	
MJE2955 90p	2N3702 & 3 9p	
MJE3055 65p	2N3704 & 5 10p	
MFU131 PUT 49p	2N3706 & 7 9p	
OA81 OA81 6p	2N3708 & 9 8p	
OA81 & OA91 6p	2N3710 & 11 10p	
TIP 29 & 30 52p	2N3819E FET 16p	
TIP 31 & 32 69p	2N3823E FET 17p	
	2N3904/5/6 15p	

NEW TRAMPUS FULL SPEC PAKS

PAK A 10 RED LEDS our choice £1
PAK B 4 741 OP AMP " £1
PAK C 4 2N3055 £1. D 12 BC109 £1
PAK E 10 BC182 £1. F 11 2N3704 £1
PAK G 8 BFY51 £1. H 9 2N3819e £1
PAK J 9 2N3053 £1. K 40 1N914 £1

BZY88 400mW	1A/50V SCR 86p
ZENER DIODES 9p	TAG1/400 65p
BRIDGE RECT	C106 & 7 SCR D1
1A 50V 20p	4A/400V 58p
	SC148D TRIAC
BR100 DIAC 25p	10A 400V 75p

vero

VERO PINSx36 28p
COPPER CLAD VERBOARD 0.1"
24"x5" 29p 24x3 1/2" 26p. 31x3 1/2" 31p.
31"x5" 31p 31x 1 1/2" £1.50

DIL IC's BOARDS 6x4 1/2" £1.50
24 way edge connector 60p.
36 way 90P. PLAIN 3 1/2"x1 1/2" £1.
FACE CUTTER 45p. PEC ETCH PAK 50p

DALOpen69p

PRINTED CIRCUIT BOARD KIT £1.69
DECON NO MESS ETCH PAK NEW 69p
DECON DESOLDER BRAID REEL 50p
HEATSINKS
5F/T05 & 18F/T018 5p ea. TV4 15p.
TV3/T03 16p. EXTRUDED 4" 4Y1 29p.
TGS308 GAS DETECTOR £1.80 ea.
LOGIC PROBE TTL TESTER PEN £5

CAPACITORS

CERAMIC 22pf to 0.1uf 50v 5p.
ELECTROLYTIC: 10/50/100 uf 1in
10v 5p. 25v 6p. 50v 8p. 2uf/10v 5p.
1000 uf/25v 18p. 200/500 25v 9p.
POTENTIOMETERS (POTS) AP or EGIN
LIN or LOG ROTARY 13p. SWITCH 14p
DUAL 45p. SLIDERS 29p. STEREO 57p
KNOBS 7p. PRESETS 6p. RESISTORS 11p
SWITCHES: SPST 18p. DPDT 25p.

DIN PLUGS ALL 12p. SOCKETS 10p.
ALI CASES AB5/AB7 50p. AB13 65p.
TRANSFORMERS 1A 6v6v or 2x12v
Only £1.34. 100mA type CT 15p.

OIL sockets

TEXAS GOLD
LOW PROFILE ea
8, 14, & 16 PIN 13p
SOLDERCON STRIPS:
100 PINS 50p. 1K £3

MAIL ORDER PROTECTION SCHEME

The Publishers of Practical Electronics are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund moneys sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund moneys owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with Practical Electronics within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered." Classified and catalogue mail order advertising are excluded.

INTRODUCING THE CUB COMBI BLOWTORCH up to 2,500°F

Vest pocket size, yet will braze, silver-solder small jewellery items, etc; soft solder, stop paint, putty, burn-off, oiled spark plugs, etc. Burns up to 13ron tiny gas cylinder. 'Cub' complete with 2 cyls., instruction book & soft-solder bit.



£4.25 incl. VAT. P. & P. Spare cyls. 80p per 2. incl. P. & P.

'CRAFTSMAN'S' TORCHES up to 6,000°F

A range of mini-torches for all gases, incl. Oxy/Acetylene. Operates from standard gas cyls. or our own mini-packs for all ultra-fine welding, brazing, fusion or cutting, incl. steel, glass, ceramic in labs or workshops. 0.002-1in. capacity.

SEND 5p STAMPS, NOT SAE, FOR ILLUSTRATED LEAFLET

MICROFLAME (UK) LIMITED

Freepost, Rickingham, Diss, Norfolk, IP22 1BR, Tel. Botesdale (037-989) 555



Precision tool using combination of butane and compressed oxygen or micronox. A pencil lead thin flame size. Adjustable to 5,000°F. Cuts metals, welds, brazes and solders gold, silver. Ideal electricians, opticians, dentists, silversmiths, modelling, jewellery, clockmakers. Up to 40 minutes use on fuel supplied. Replacement set of 2 micronox, 1 butane cylinder. £1-50 extra incl. post. Our Price £14-95 + 65p p. & p. Send £15-60.

Please send cash with order—we despatch promptly by post. Access accepted—send name, address and number.


BINOCULAR MAGNIFIER

FOR PRECISION CLOSE-UP WORK—LEAVES BOTH HANDS FREE
See close-up work with less eye strain and fatigue. Lightweight adjustable headband. Powerful optically ground lenses from Continental glass-works. Can be worn over normal glasses. An essential aid in modelling, industry, home and workshop. Stamp collecting, Jewellers, watchmakers and any fine work. 2x magnification. £7-65 + 40p p. & p. 3x model £8-85 + 40p p. & p. State model. Also deluxe model with hinged lenses. Mount £1 extra.

Please send cash with order—we despatch promptly by post. Access accepted—send name, address and number.

JOHN DUDLEY & CO. LTD. (Dept. PE11), 301 Cricklewood Lane, Finchley Road, London, NW2. Tel. 01-458 5917. Callers welcome. Easy Parking.

Wireless World DOLBY NOISE REDUCER

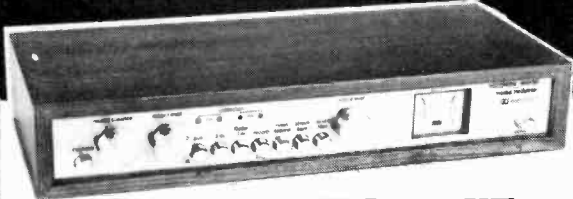

CONSTRUCTION KIT AVAILABLE ONLY FROM WIRELESS WORLD

Complete kits for the Wireless World Dolby B noise reducer are available through the address given below. The two-channel design features:

- *a weighted noise reduction of 9dB
- *switching for both encoding (low-level h.f. compression) and decoding
- *a switchable f.m. stereo multiplex and bias filter
- *provision for decoding Dolby f.m. radio transmissions (as in USA)
- *no equipment needed for alignment
- *suitability for both open-reel and cassette tape machines
- *check tape switch for encoded monitoring in three-head machines

The kit includes:

- complete set of components for a stereo processor
- regulated power supply components
- board-mounted DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, two meters, front panel, knobs, mounting screws and nuts.

Price is £43 inclusive.

A single-channel printed-circuit board, with f.e.t. costs £2.50 and £8.63 with all components inclusive (excluding edge connector, £1.37 extra). Selected field-effect transistors cost 68p each inclusive, £1.20 for two and £2.20 for four.

Calibration tapes are available, costing £1.94 inclusive for 9.5cm/s open-reel use and for cassette (specify which).

Send cash with order, making cheques payable to:

IPC Business Press Ltd, to: Wireless World Noise Reducer, General Sales Department, Room 11, Dorset House, Stamford Street, London SE1 9LU. Allow three weeks for delivery.

DOLBY KIT ORDER FORM

Please supply me with the complete Wireless World kit for a Dolby noise reducer.

I enclose remittance value £43.00 inclusive.

Name

Address

Additional items required

I enclose remittance value £

payable to IPC Business Press Ltd.

Wireless World



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments.)

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK



To: ALDERMASTON COLLEGE, DEPT. CPE05
READING RG7 4PF

CPE05

Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel: 01-628 2721

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS


POSTCODE



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

BD139-240 | BR257,8,9-240 | BD140-240

INVERTORS

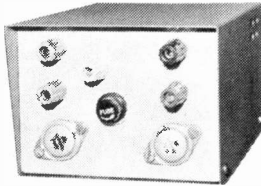

240v-50Hz from your 12v car battery.

25 watt—£4.20 150 watt—£19.10
40 watt—£7.35 300 watt (12v)—£29.85
75 watt—£10.71 300 watt (24v)—£23.75

All above invertors are in kit form but may be purchased built up in metal case & ready for use. Price list sent on receipt of s.a.e. Prices include post & packing.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £22.50 + £1.10 p. & p.

FLOURESCENT LIGHT INVERTOR KIT
8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats & secondary lighting for factories, hotels, etc.
12"-8 watt—£2.90 + 25p p. & p. Built up—£4 + 25p.
21"-13 watt—£3.30 + 30p p. & p. Built up—£4.50 + 30p.


TRANSFORMERS & COILS

Both high volume & small order capacity available.

Special offer. Miniature mains transformer 12-0-12v-6V.A.—85p plus 10p p. & p.

TRADE & EXPORT ENQUIRIES WELCOMED

P.E. ORION STEREO AMPLIFIER

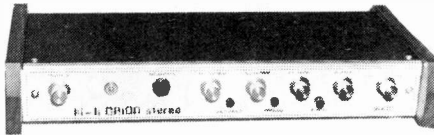


20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response ± 1 dB 20 Hz to 20 kHz. Hum level virtually nil with vol. full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.

Complete kit of parts including slim line bookend case, silk screened front panel & knobs. £43 incl. VAT & p. & p.

The bookend case, I.C.s & semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information

ASTRO IGNITION

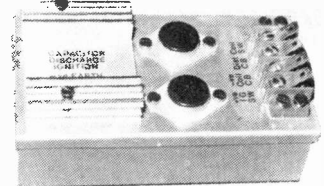

ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £9.50 incl. VAT. Ready built with only two connections to alter £12.50 incl. VAT. Thousands have used this system both home and abroad. Consider these *advantages* more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark, the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth. Trade and export enquiries welcomed.

ASTRO ELECTRONICS

Spring Bank Road, West Park Chesterfield.

PRINCIPLES OF TRANSISTOR CIRCUITS

by S. W. Amos Price £3.45

110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston Price £2.00

ELECTRONICS SELF-TAUGHT WITH EXPERIMENTS AND PROJECTS by J. Ashe Price £2.10

TRANSISTOR POCKET BOOK by R. G. Hibberd Price £3.00

RADIO AND LINE TRANSMISSION by D. C. Green Price £4.25

ELECTRONICS AN ELEMENTARY INTRO. FOR BEGINNERS by L. W. Owens Price £1.65

ELEMENTARY TELECOMMUNICATION PRACTICE by J. R. G. Smith Price £1.50

SCR MANUAL INCLUDING TRIACS AND OTHER THYRISTORS 5th edition by G.E. Price £1.90

SOLID STATE HOBBY CIRCUITS by R.C.A. Price £1.20

INTEGRATED ELECTRONICS by Millman Price £4.95

TEST EQUIPMENT FOR THE RADIO AMATEUR by H. L. Gibson Price £2.05

WORKING WITH THE OSCILLOSCOPE by A. C. W. Saunders Price £3.70

★ PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books
**19-21 PRAED STREET
LONDON W2 1NP**

Phone 01-723 4185
Closed Saturday 1 p.m.


BRIDGE ELECTRONICS COMPONENTS

	E		E		E
AC126	0-13	BD138	0-28	2N2218A	0-18
AC127	0-13	BF135	0-29	2N2219	0-17
AC128	0-11	BD140	0-32	2N2219A	0-18
AC151	0-18	BDV56	1-00	2N2221	0-17
AC152	0-25	BF115	0-20	2N2221A	0-18
AC153	0-27	BF200	0-25	2N2222	0-17
AC176	0-14	BF194	0-09	2N2846	0-30
AC187K	0-27	BF195	0-09	2N2904	0-18
AC188K	0-27	BF198	0-12	2N2905	0-18
AD181	0-35	BF199	0-32	2N2906	0-18
AD182	0-35	BF257	0-24	2N2907	0-18
BA102	0-10	BF258	0-24	2N2926G	0-09
BAX13	0-03	BF259	0-24	2N3053	0-20
BAX16	0-04	BEX29	0-22	2N3054	0-40
BC107	0-09	BFX30	0-22	2N3055	0-45
BC108	0-09	BFX34	0-20	2N3393	0-12
BC109	0-09	BFX85	0-27	2N3441	0-56
BC147	0-09	BFY50	0-19	2N3442	0-96
BC148	0-09	BFY51	0-19	2N3638	0-10
BC149	0-09	BFY52	0-19	2N3638A	0-10
BC167	0-10	BY126	0-11	2N3702	0-10
BC168	0-10	BY127	0-11	2N3704	0-10
BC189	0-10	OA47	0-06	2N3706	0-10
BC182	0-09	OA90	0-04	2N3708	0-10
BC183	0-09	OA91	0-04	2N3771	1-25
BC184	0-09	OA200	0-05	2N3772	1-35
BC212	0-09	OA202	0-06	2N3773	2-00
BC213	0-09	IN814	0-05	2N5260	0-11
BC214	0-91	IN404	0-05	2N3906	0-12
BC237	0-08	IN4007	0-06	2N5294	0-35
BC238	0-08	IN4148	0-03	2N5296	0-35
BC239	0-08	IS920	0-05	2N3794	0-20
BC297	0-09	2N697	0-15	2N5260	0-25
BC308	0-09	2N698	0-14	2N4036	0-55
BC309	0-09	2N706	0-10	2N4037	0-40
BC327	0-12	2N708	0-10	2N4821	0-80
BC328	0-12	2N718	0-23	2N5260	0-25
BCY70	0-13	2N1305	0-25	2N4289	0-25
BCY71	0-13	2N1307	0-25	2N5447	0-12
BCY72	0-12	2N1308	0-25	2N5449	0-12
BD135	0-25	2N1513	0-15	2N5457	0-30
BD136	0-26	2N1711	0-15	2N5458	0-27
BD137	0-27	2N2218	0-17	2N6027	0-40

FULLY GUARANTEED

Mail order only V A T extra p & p 20p
Bridge Electronics
PO Box No. 10 Fishponds Bristol BS16 2LX

VEROBOARD

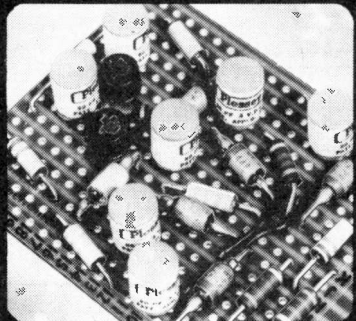

VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK

0.1" and 0.15" pitch, plain and copper clad universal circuit boards.

AVAILABLE FROM YOUR LOCAL RETAILER

TRADE DISTRIBUTOR N Rose (Electrical) Ltd. London, W.C.1



VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford,
SO5 2TB Tel: Chandler's Ford 393



GIRO NO. 331 7056. Access accepted.
C.W.O. only. P. & P. 15p on orders below £5
Discount: £10-10% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT AT 8%

DOE TO RECENT V.A.T. CHANGES PLEASE ADD 15% TO TOTAL ORDER VALUE EXCEPT TEST METERS AND VEROBOARD

SPECIAL RESISTOR KITS (Prices include post & packing)
10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net
Due to current world shortages, resistor kits may contain some wattage and value substitutions.

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3½p, 0.068µF, 0.1µF, 4½p, 0.15µF, 5p, 0.22µF, 6p, 0.33µF, 8p, 0.47µF, 10p, 0.68µF, 13p, 1µF, 16p, 1.5µF, 24p, 2.2µF, 27p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V, 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 3p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3½p, 0.047µF, 0.068µF, 0.1µF, 4½p, 0.15µF, 7p, 0.22µF, 9p, 0.33µF, 13p, 0.47µF, 15p.
160V: 0.01µF, 0.15µF, 0.22µF, 3p, 0.047µF, 0.068µF, 3½p, 0.1µF, 4½p, 0.15µF, 5½p, 0.22µF, 6p, 0.33µF, 7p, 0.47µF, 9p, 0.68µF, 13p, 1µF, 15p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, 10K, 12µF 0.01, 0.015, 0.022, 0.033, 0.047, 2½p, each. 0.1, 30V, 5p.

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 4½p.

RESISTORS

CF—High Stab Carbon Film, 5%	MF—High Stab Metal Film, 5%	Size mm		
V. Type Range	1-99	100-999	1000+	
± CF 12-1M	1	0.80	0.60	2.4x7.5
± CF 22-2M2	1	0.80	0.65	3.9x10.5
± CF 22-1M	1	0.80	0.65	0.60
± MF 10-2M7	2	1.7	1.4	1.2
± MF 10-2M2	2	1.6	1.3	1.1
± MF 10-10M	3	1.98	1.81	1.65
± MF 10-10M	3	1.98	1.81	1.65
± MF 10-10M	4.5	3.52	3.08	2.75

(Price in pence each).
VALUES AVAILABLE—E12 Series only. (Net prices above 1.00.)

PRESET SKELETON POTENTIOMETERS

MINIATURE 0.25W Vertical or horizontal 7p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω
SUB-MIN 0.05W Vertical, 100 Ω to 220K Ω 7p each.



B. H. COMPONENT FACTORS LTD.

(P.E.), LEIGHTON ELECTRONICS CENTRE,
59 NORTH STREET, LEIGHTON BUZZARD,
LU7 7EG. Tel: Leighton Buzzard 2316 (Std. Code 02523).

Miniature Mullard Electrolytics

1.0µF 63V 7p	68µF 16V 7p
1.5µF 63V 7p	68µF 63V 14p
2.2µF 63V 7p	100µF 10V 7p
3.3µF 63V 7p	100µF 25V 7p
4.0µF 40V 7p	100µF 16V 7p
4.7µF 63V 7p	150µF 16V 7p
6.8µF 63V 7p	150µF 63V 17p
8.0µF 40V 7p	220µF 6.4V 7p
10µF 16V 7p	220µF 10V 7p
10µF 25V 7p	220µF 16V 8p
10µF 63V 7p	220µF 63V 21p
15µF 16V 7p	330µF 16V 8p
15µF 63V 7p	330µF 63V 25p
16µF 40V 7p	470µF 6.4 14p
22µF 25V 7p	470µF 40V 26p
22µF 63V 7p	680µF 16V 8p
32µF 10V 7p	680µF 40V 25p
33µF 16V 7p	1000µF 16V 17p
33µF 40V 7p	1000µF 25V 28p
32µF 63V 7p	1500µF 6.4V 25p
47µF 10V 7p	1500µF 16V 28p
47µF 25V 7p	2200µF 10V 17p
47µF 63V 8p	3300µF 6.4V 28p

VEROBOARD

0.1 0.15	36p 36p
2½ x 5"	33p 25p
3½ x 5"	42p 46p
3½ x 3"	36p 36p
2½ x 1"	10p 9p
2½ x 5" (Plain)	— 19p
2½ x 3" (Plain)	— 29p
5 x 3" (Plain)	— 29p
Insertion tool	73p 73p
Track Cutter	56p 56p
Pins, Pkt. 25	22p 22p

TRANSISTORS

AC127 21p	BC212L 13p
AC128 22p	BC213L 13p
BC107 12p	BC214L 18p
BC108 12p	OC44 19p
BC109 13p	OC71 13p
BC148 13p	OC81 17p
BC149 13p	OC170 29p
BC182L 13p	TIS43 34p
BC183L 13p	2N2926 13p
BC184L 14p	2N3702 14p

POTENTIOMETERS

Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 17½p Dual Gang 48p. Log single with switch 28p. Slider Pots. 60mm, 5K, 10K, 25K, 50K, 100K, 250K, 500K, log or lin. Single 45p. Dual 55p.

DIODES

IN4001 6½p	Din 2 Pin	12p
IN4002 7½p	3 Pin	13p
IN4003 9p	5 Pin 180°	16p
IN4000 9p	5 Pin Jack	20p
IN4005 12p	2.5mm jack	13p
IN4006 14p	Phono	7p
IN914 7p	Din 2 Pin	10p
IN916 7p	3 Pin	10p
BA100 10p	3 Pin	10p
OA5 42p	5 Pin 180°	12p
OA47 9p	Std. Jack	18p
OA81 11p	2.5mm Jack	13p
OA200 8p	Phono	7p

PLUGS

IN4001 6½p	Din 2 Pin	12p
IN4002 7½p	3 Pin	13p
IN4003 9p	5 Pin 180°	16p
IN4000 9p	5 Pin Jack	20p
IN4005 12p	2.5mm jack	13p
IN4006 14p	Phono	7p
IN914 7p	Din 2 Pin	10p
IN916 7p	3 Pin	10p
BA100 10p	3 Pin	10p
OA5 42p	5 Pin 180°	12p
OA47 9p	Std. Jack	18p
OA81 11p	2.5mm Jack	13p
OA200 8p	Phono	7p

ELECTROLYTIC CAPACITORS, Tubular & Large Cans

(µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 7p, 50/50, 8p, 100/50, 200/25, 10p, 250/50, 18p, 500/10, 8p, 500/25, 17p, 500/50, 25p, 1000/10, 17p, 1000/25, 25p, 1000/50, 40p, 2000/10, 20p, 1000/100, £1.10, 2000/25, 35p, 2000/100, £1.20, 2500/25, 38p, 2500/50, 68p, 5000/25, 68p, 5000/50, £1.20.

SOCKETS

Din 2 Pin 10p
3 Pin 10p
5 Pin 180° 12p
Std. Jack 18p
2.5mm Jack 13p
Phono 7p

METALLISED PAPER CAPACITORS

250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7½p, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 7½p, 0.5, 9p, 1000V: 0.01, 11p, 0.022, 13p, 0.047, 0.1, 19p, 0.22, 28p, 0.47, 36p.


LEIGHTON ELECTRONICS CENTRE

Our New Electronics Centre is now open in Leighton Buzzard and all callers are welcome. As well as our normal stock of over 3,000 products we have a large range of surplus bargains and calculators, etc. Open 6 days. 9-12.30. 1.30-5 p.m.



MULTIMETER U4323

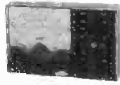22 Ranges plus AF/IF Oscillator, 20,000 Ω/Volt.
Vdc—0.5—1000V in 7 ranges
Vdc—2.5—1000V in 6 ranges
Iac—0.05—500mA in 5 ranges
Resistance—5 Ω—1M Ω in 4 ranges.
Accuracy—5% of F.S.D.
OSCILLATOR—1 KHz and 465KHz (A, M.) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE £68.64 net P. & P. 50p.



U4323

MULTIMETER U4324

34 Ranges. High sensitivity. 20,000 Ω/Volt. Overload protected.
Vdc—0.6—1200V in 9 ranges.
Vdc—3—900V in 8 ranges.
Iac—0.06—3A in 6 ranges.
Iac—0.3—300mA in 5 ranges.
Resistance—25 Ω—5M Ω in 5 ranges.
Accuracy—dc and R—2½% of F.S.D. ac and db—4% of F.S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case, test leads, spare diode, and battery.
PRICE £10.64 net P. & P. 50p.



U4324

MULTIMETER U4341

27 Ranges plus Transistor Tester. 16,700 Ω/Volt. Overload protected.
Vdc—0.3—900V in 8 ranges.
Vdc—1.5—750V in 6 ranges.
Iac—0.06—600mA in 5 ranges.
Iac—0.3—300mA in 4 ranges.
Resistance—2K Ω—2M Ω in 4 ranges. Accuracy—dc—2½%. ac—4% of F.S.D.
hfe—10—350 in 2 ranges.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £11.88 net P. & P. 50p.




U4341

MULTIMETER U4313

33 ranges. Knife edge with mirror scale. 20,000 Ω/Volt. High accuracy. mVdc—75mV.
Vdc—1.5—600V in 9 ranges.
Vdc—1.5—600V in 9 ranges.
Iac—60—120 microamps in 2 ldc—0.6—1500mA in 6 ranges.
Iac—0.6—1500mA in 6 ranges.
Resistance—1K Ω—1M Ω in 4 ranges. db scale—10 to +12db.
Accuracy—dc—1½%, ac—2½%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £14.90 net P. & P. 50p.



U4313

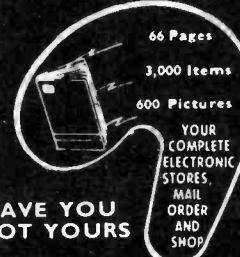

HAVE YOU GOT YOURS

CATALOGUE No. 4 NEW CONVENIENT SIZE, AND FULLY ILLUSTRATED
CONTAINS MANY HARD TO GET ITEMS

PAYS FOR ITSELF WITH DISCOUNT VOUCHERS WORTH 20p

- * DISCOUNTS
- * ALL NEW STOCK
- * SATISFACTION GUARANTEE
- * DEPENDABLE SERVICE

SPECIAL OFFER

FREE—741 Operational Amplifier I.C. with every copy of R. M. Marston's book "110 Operational Amplifier Projects for the Home Constructor", price £1.80. Includes circuits for musical instruments, fire alarm, burglar alarm, touch-activated switch and many other exciting projects.

ZN414 £1.10

Ferranti Application Booklet for ZN414, 25p

ZN1034E New Ferranti Precision Timer I.C.

£2.90

Ferranti Data Sheets for ZN1034E 10p

741 Operational Amplifier I.C. 33p

RADNAGE RADIO & ELECTRONICS

2 Bottom Road, Radnage, High Wycombe, Bucks.

Prices inclusive. Add 15p Post and Packing UK, 60p Exports. Mail order only



DECADE 4 resistance substitution box—a must for all engineers, students and experimenters. Full details on request. Trade enquiries welcome. £38 plus 8% VAT.

5W Chassis Stereo amp. (2.5W/CH) 12V d.c. output 2.5W/CH into 8 ohm. Input tape head 3mV or suitable 100mV mic/P.U. with external components. Slider controls. £4 plus 25% VAT.

8 track car stereo players 12V neg. earth. £14 plus 25% VAT.
12V d.c. Solenoids short duration. 55p inc. VAT.
12V Miniature Lamps with flying leads. Pack of 10 60p inc. VAT.
High Power Strobe Light—ideal Disco/Group use. £42 plus 8% VAT.

SCOTT ELECTRONICS

Estcourt House, Estcourt Road, Gt. Yarmouth, Norfolk

Tel. (0493) 58942

C.O.D. under £30

Practical Electronics Classified Advertisements

RATES: 13p per word (minimum 12 words). Box No. 35p extra. Semi-Display £10.00 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD. Tel. 01-634 4451.


RECEIVERS AND COMPONENTS

TTL at LOW PRICES!					
(Fast delivery. All prices include VAT)					
Type	1/24	25/99	Type	1/24	25/99
7400	0-14	0-13	7473	0-33	0-31
7401	0-14	0-13	7474	0-33	0-31
7402	0-14	0-13	7475	0-45	0-44
7403	0-14	0-13	7476	0-34	0-31
7404	0-16	0-15	7480	0-46	0-42
7405	0-16	0-15	7483	0-89	0-80
7408	0-16	0-15	7486	0-30	0-26
7410	0-14	0-13	7489	2-99	2-80
7413	0-32	0-31	7490	0-46	0-44
7417	0-30	0-29	7491	0-74	0-69
7420	0-14	0-13	7492	0-48	0-45
7427	0-27	0-25	7493	0-46	0-44
7430	0-14	0-13	7495	0-61	0-58
7432	0-27	0-25	7496	0-77	0-69
7437	0-29	0-26	74107	0-34	0-31
7440	0-14	0-13	74121	0-34	0-31
7442	0-69	0-63	74123	0-65	0-61
7445	0-89	0-82	74141	0-71	0-69
7447	0-81	0-79	74145	0-86	0-78
7450	0-14	0-13	74151	0-91	0-88
7451	0-14	0-13	74153	0-76	0-72
7453	0-14	0-13	74154	1-60	1-55
7454	0-14	0-13	74157	0-87	0-79
7460	0-14	0-13	74174	0-99	0-90
7412	0-27	0-25	74175	0-99	0-90
7472	0-28	0-25	74181	2-09	1-95

TTL may be mixed for quantity prices.
INTEL 2102 1K static random access memories £4.50 each.
All devices full spec. by famous manufacturers.
S.A.E. for full lists. All goods sent by 1st class post free. 10p P. & P. on orders below £2 otherwise post free.

J. C. JONES
(Dept. PE9) 46 BURSTALLS,
ST. IVES, HUNTINGDON, PE17 4XX
(Mail Order only)

BRAND NEW COMPONENTS BY RETURN.
Electrolytics 18V, 25V, 50V, 0.47, 1.0, 2.2, 4.7, 10mfd, 5p; 22, 47, 5p (50V, 8p); 100, 7p (50V, 8p); 220, 8p (50V, 10p); 500, 11p (50V, 10p); 1000/25V, 18p. Subminiature bead-type tantalums. 0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/35V, 10/20V, 22/16V, 47/8V, 100/3V, 11p. Mylar Film 100V, 0.001, 0.002, 0.005, 0.01, 0.02, 3p; 0.04, 0.05, 3p. Mullard tubular polyester 400V E8 series, 0.001-0.022, 3p; 0.033-0.1, 4p. Mullard polyester 160V tubular or 250V miniature for vertical mounting E8 series, 0.01-0.047, 3p; 0.068, 0.1, 4p; 0.15, 0.22, 6p; 0.33, 7p; 0.47, 9p; 0.68, 11p, 1.0, 14p; 1.5/250V, 18p; 2.2/250V, 22p. Mullard miniature C333 ceramics 63V E12 series 2% 1.8pF-47pF, 3p; 56pF-330pF, 3p. Plate ceramics 50V E8 series 470pF-47,000pF, 2p. Polystyrene 63V, E12 series 10pF-1,000pF, 3p; 1,200pF-10,000pF, 4p. Miniature highstab carbon film resistors 1/4W E12 series 5% (10% over 1MΩ) 1Ω-10MΩ, 1p; 1N4002, 6p; 1N4006, 6p; 1N4148, 4p. Postage 10p. Prices VAT inclusive. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.



DEPT. 29
23 AVERY AVENUE
HIGH WYCOMBE
BUCKS.

AXIAL PRODUCTS LTD.

SERIALS
4 ELEMENT FM STEREO
£3-80 + 25% VAT + 50 P. & P.
18 ELEMENT TV
£2-00 + 25% VAT + 50 P. & P.
10 ELEMENT TV
£1-75 + 25% VAT + 50 P. & P.

New design, superior quality, including mounting bracket and full instructions.

AC127	15p	Center Diodes			
AC128	15p	400mW	11p	TTL IC's	
BC107	11p	1W	18p	7400	15p
BC108	11p			7403	15p
BC109	12p	1N4001	6p	7405	20p
BC113	15p	1N4004	6p	7410	15p
BC147	11p	1N4070	6p	7412	17p
BC148	11p	1N4148	5p	7413	25p
BC149	12p	8 Pin Di		7417	17p
BCY70	22p	741 op amp	35p	7442	78p
BF194	12p	301 op amp	50p	7447	87p
BF195	12p	555 Timer	60p	7474	36p
BFY50	18p			7480	49p
BFY51	18p			74121	27p
2N2906	25p	14 Pin Di		74180	113p
2N2926	11p	Skit	19p	74192	140p
2N3819	31p				
2N3055	50p				

All Semiconductor prices include VAT at appropriate rates. P. & P. 10p per £ under £2
C.W.O. MAIL ORDER ONLY

R.T. SERVICES (MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.
Tapped Auto Transformer, 240V-110V, 80 watts, £2 P.P. New.
Tapped Auto Transformer, 240V-115V, 200 watts, £4-50 P.P. New.
100 Watt Valve Output Transformer. KT88s, etc. 8 or 15Ω or 100 volt line output, £13-60 P.P.
FM Tuner with R.F. Stage and A.G.C., 3 transistors, neon, earth, 2 1/2 x 2 1/2 in with circuit, £1-54 P.P.
Crouzet Geared Motors, 30 r.p.m. New, £1-75 P.P.
UHF TV Tuners. Transistorised, £2-10 P.P. Panels with I.C.'s on 8 1/2 per I.C. min. order 10 I.C.'s.
Transformers. 7.5V+7.5V 1A, £1-12 inc. P.P. 12-0-12V, 100mA, £1-25 inc. P.P. 9-0-9V, 100mA, £1-25 inc. P.P. 29V 50mA, 95p inc. P.P. 6-0-6V, 100mA, £1-25 inc. P.P.
Transformer. 24 volt, approx. 1 amp + 6-3V CT approx. 500mA, £1-60 inc. P.P.
Transformer. 20 volt, 1 amp, £1-40 P.P.
Transformer. 45 volt, 2 amp, £3-38 P.P.
P.C. Board, S/S, 5 1/2 x 5 1/2, 10 for £1-10 P.P.
Transistorised Timer. Variable delay. 110 or 250V A.C. input. With instructions.
Brand new, £2-25 inc. P.P. Size 3" x 2" x 2".
Power Unit Components Transformer. 18 volt 1 amp F/W bridge rectifier, 2 1250 mfd capacitors, all new £1-60 per kit. P.P.
Electrolytic Capacitors, 4,000 MF, 50V, 4 1/2 x 1 1/2 90p. inc. P.P.
Mixed Pack of C280 series Mullard capacitors. 100 for £1-30 inc. P.P.

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY - EXTREMELY LOW LEAKAGE

Value	±1%	±2%	±5%
0.1µF (27 x 12.7)	51p		
0.22µF (33 x 18)	84p	2µF	67p
0.25µF (33 x 18)	87p	0.47µF	95p
0.47µF (33 x 18)	89p	0.6µF	95p
0.5µF (33 x 18)	87p	4.7µF	£1-02
0.68µF (50.8 x 19)	89p	6.8µF	£1-96
1.0µF (50.8 x 19)	£1-08	10µF	£2-40
2.0µF (50.8 x 25.4)	1.4µF	22µF	£3-22
	£1-44	22µF	£4-28

TANTALUM BEAD CAPACITORS - Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10-100µF at 16V/20V or 25V; 22-200µF at 6V/10V or 16V; 33-300µF at 6V or 10V; 47-400µF at 3V or 6V; 100-100µF at 3V. ALL at 10p each, 10 for 95p, 50 for £4.

TRANSISTORS: BC183/183L 11p BFY50 20p
BC107/8/9 6p BC184/184L 12p BFY1 20p
BC114 12p BC121/212L 14p BFY52 20p
BC147/8/9 10p BC647/688A 12p AF178 30p
BC153/7/8 18p BF194 12p OC71 18p
BC182/182L 11p BF197 18p 2N3055 50p

POPULAR DIODES - 1N914 6p, 8 for 45p, 18 for 90p; 1N916 8p, 8 for 45p, 14 for 90p; 1844 5p, 11 for 50p, 24 for £1; 1N4148 6p, 6 for 87p, 12 for 45p; 1N4001 51p; 1N4002 6p; 1N4003 61p; 1N4004 7p; 1N4006 71p; 1N4006 8p; 1N4007 81p.

LOW PRICE ZENER DIODES - 400mW, Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. ALL at 7p each, 5 for 35p, 10 for 65p. SPECIAL OFFER: 100 Zeners (may be mixed) for £6-00. BFY52 20p.

RESISTORS - High stability, low noise carbon film 5% 1/4W at 40°C, 1W at 70°C. E12 series only - from 2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2-2Ω to 2.2MΩ (730 resistors) 85p.

SILICON PLASTIC RECTIFIERS - 1.5 amp, brand new wire ended D027: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS - 2 1/2 amp: 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS - 0-1W only: ALL at 5p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ, 5MΩ.

PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

MARCO TRADING
Dept. E.10, The Old School, Edinstanton,
Mr. Wem, Shropshire
Tel.: Whixall 464/465 (STD 0948 72)
(Proprs.: Minicost Trading Ltd.)

ELECTROLYTICS 6.3, 10, 18V 10, 25, 33, 50, 100mF 25, 50, 63V 1, 2.2, 4.7, 6.8, 10, 25, 33, 50mF. All at 50p each or £4-60 for 100. Resistors Carbon Film 5% E24 Range 1/4W 0-8p, 1/2W 0-1p, 1/2W 0-7p, 1W 1p (prices are in fractions of 1p). Send 10p for our catalogue for additional items and discounts. P. & P. 15p + VAT 25%. C. W. ELECTRONICS 10, Kingsley Path, Britwell Est., Slough, Berks. (All components are brand new.)

LED	S	0-125	0-2	INFRA RED
RED	15p	18p		550nm
G/Y	27p	33p		Axial lead 49p
OR	27p	33p		1.5mW
				TO46 £1-18

OPTO-ISOLATORS

IL74	1-5kV, 150kHz	£1	T051A	25p	27p	46p
4350	2-5kV, 5MHz	£2-25	T068 3A	27p	39p	50p

Data free with all OPTO

AC125/6/7/8	15p	2N2926(G)	12p	VOLTAGE REGS.
AD161/162	40p	2N3053	15p	5V 7805 Plastic
AF117	5p	N3055	41p	12V 7815 1 Amp
AF124/5/6/7	34p	2N3702/3/4	12p	15V 7815 all
BC107/8/9	9p	2N3904/5/6	16p	18V 7818 £1-50
BC109C	12p	2N2846	35p	723 T099 50p
BC147/8/9	10p	MPF102	40p	BRIDGE RECTS.
BC157/8/9	11p	2N3819	25p	2A 50V 30p
BC187/8/9	11p	2N3823	20p	2A 100V 36p
BC189C	12p			2A 200V 41p
BC177/8/9	17p	BR100 Diac	21p	2A 400V 46p
BC182/3/4/L	11p	IN914	3p	ZENERS BZV85
BC186/7	30p	IN4001	5p	2.7-33V 8p
BC212/3/4/L	12p	IN4002.3	6p	
BCY70/71/72	13p	IN4004.5	7p	
BF194/5	12p	IN4008/7	8p	
BF196/7	14p	IN4148	4p	NE555 £1-18
BFY50/51	16p	OA47	6p	LM380 50p
BFX29	30p	OA70 OA79	8p	ZN414 £1-18
BFX84	24p	OA81 OA90	7p	7400 16p
BSX19/20	16p	OA91 OA95	6p	D.I.L. SOCKETS
OC71	10p	OA200	8p	8-pin 12p
2N706	10p	OA202	7p	14-pin 13p
2N1711	20p			18-pin 14p
2N2219	20p	OP. AMPS		709 all 25p
2N2904/5/6/7	16p			741 8-pin 29p
2N2904/5/6A	18p			748 D.I.L. 36p
2N2926(R)	7p			

PRICES INCLUSIVE + 15p P. & P. (1st class)
ISLAND DEVICES, P.O. Box 11, Margate, Kent

VALVES, RADIO, TV, TRANSMITTING, INDUSTRIAL. 1930 to 1975. 2,200 types in stock, many obsolete. List 20p. Quotation S.A.E. Postal export service. We wish to purchase new and boxed valves. Dealers, wholesalers, etc., stocks purchased. COX RADIO (SUSSEX) LTD., The Parade, East Wittering, Sussex. Tel. West Wittering 2023.

BETA DEVICES

MANUFACTURERS BRANDED PRODUCTS

TRANSISTORS	I.C.'s	DIODES & RECT.
AC157/188	709C T099 0-80	1N914 0-04
FB	709C D.I.L. 0-80	1N4148 0-04
BC107/8	741C T099 0-38	OA202 0-05
BC108	741C D.I.L. 0-38	1N4001/2 0-08
BC109C	723C D.I.L. 0-80	1N4003/4/5 0-08
BC147/8/9	747C D.I.L. 0-85	1N4006/7 0-06
BCY70/71/72/18	748C D.I.L. 0-36	BRIDGES
BFX86/87/88		W01 1A
	555-8-Pin 0-60	100V 0-20
BFY50	18 555-14-Pin 1-00	W06 1A
BFY51/52	18 808-ATEB	600V 0-20
OC28	48 2N3055	0-38 ZENERS
OC35	0-48 D.I.L. SOCKETS	BZV85 3-3-
2N2946	0-80 8-Pin 0-18	33V 5% 0-09
2N3053	0-14 8-Pin 0-12	1Watt 6-8-
TIP29A	0-48 16-Pin 0-14	200V 6M
TIP31A	0-61	L.E.D.
TIP41A	0-74	Please add 209-Red 0-17
TIP42A	0-90	17% V.A.T. L.E.D. Clip 0-08

C.W.O. PLUS P.P. 15p to BETA DEVICES
4 High Bridge Street, Waltham Abbey, Essex

Bank of 20 Neons 74p (11p), 5 Figure Resactable Counter 18/22V works on 12, £2-50 (30p). Box with 20 x LA2 Pot Cores + 20 x 1% Caps, £1-50 (50p). Copper Clad Pax. Panels 5 1/2 x 5 1/2 in. 6-65p, 1 1/2 x 12 in. 65p, 16 x 9 1/2 in. 65p, 8 x 9 1/2 in. 3-£1. Fibre Glass Ditto, 1 1/2 x 7 in. 80p, 18 x 4 in. 75p, 1 1/2 x 13 in. £1-50, all C.P. 74 Series I.C. Op. Panels 1 1/2-80p (10p). Mains Transformer, Sec. 25V 1A 0.4-10V 4p. £1-60 (40p). Lists 12p Refund on purchase.

J.W.B. RADIO
2 Barnfield Crescent, Sale, Cheshire, M33 1NL
Postage in brackets Mail order only

CLEARING DISTRIBUTOR STOCKS, transistors, diodes, components, etc. Sample pack 65p incl. postage or send stamp for list. **REDEHAWK SALES LTD.**, 10 Maple Lodge Close, Rickmansworth, Herts. Mail order only.

BARGAIN BELPAK TESTED SEMICONDUCTORS
 R1. 10NPN, SIL, T092—75p IN4001—6p
 IN4006—13p R2. 10NPN, SIL, T092—75p
 IN4002—7p IN4142—6p R3. 10NPN,
 SIL, T018—75p Zeners—2 to 33V—9p
 R4. 10NPN, SIL, T018—75p Philips Pots:
 Lin: 1K to 2M2—16p. Lists 25p.
 Export enquiries welcomed. Deduct 8% VAT. Mail
 Order only. Satisfaction guaranteed or money back.
 P. & P. and VAT included.

RELTRAN LIMITED
 (Dept. P.E.), P.O. Box 18, Camberley
 Surrey

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact **COLES-HARDING & CO.**, P.O. Box 5, Frome, Somerset. Immediate cash settlement.

SITUATIONS VACANT

MEN!
£90 p.w.
can be yours

Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks!

It can pay around £35 p.w. as a starter and can reach over £90 p.w. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators Training Centre Y40, Oxford Hse. 9-15 Oxford St., W.1. Tel. 01-734 2874

COURSES

THE POLYTECHNIC OF NORTH LONDON

Department of Electronic and Communications Engineering

Interested in Electronics and Communications?

* Join our B.Sc. Degree course in Electronic and Communications Engineering.

** Become a member of a Professional Institution and a Chartered Engineer.

*** Entry requirements: 2 'A' levels (Mathematics and normally Physics).

**** Any recognised equivalent (ONC, OND, etc).

***** Write to the Dept. of Electronic and Communications Engineering, Polytechnic of North London, Holloway, London N7 8DB (or phone 01-607 6767)

AGENTS

MANUFACTURERS/WHOLESALEERS—Australian importer requires information on availability—prices—weights Electronic Parts/Assemblies. Air Mail Reply—GSCE, 18 Marie Street, Murarrie, Q4172 Australia. Telex AA41532/Code P. Y. (GSCE).

PROFESSIONAL SERVICES

PATENTS AND TRADE MARKS. KINGS PATENT AGENCY LIMITED (Est. 1886). B. T. King, Director, M.I.Mech.E., Registered Patent Agent, 146a Queen Victoria Street, London, EC4V 5AT. Booklet on request. Tel. 01-248 6161. Telex 883805.

FOR SALE

PRACTICAL ELECTRONICS Vol. 1-9. What offers. SPENCER, Garden Cottage, Warren House, Warren Road, Kingston upon Thames.

LIQUID CRYSTAL DISPLAYS

Norstron 7-segment dynamic scattering LCD's

- * Ready mounted with attractive bezel
- * Run from 15VDC, CMOS compatible
- * Single digit displays can be mounted side-by-side
- * Supplied with mounting socket pins
- * Supplied complete with data sheets and application notes

Prices:

Single digit (0-9 and Decimal Point) .. £1.80 each
 3-digit (000-999 and Decimal Points) .. £4.90 each
 3½-digit (0000-1999 with Overflow,
 ± signs and Decimal Points) .. £6.00 each

P. & P. per order 25p, offer at these prices limited to present stocks; please add 25% VAT to all orders
 Data sheets only ... 10p

From:

NIMROD ELECTRONICS LTD.
 85 High Street, Billingshurst, W. Sussex
 RH14 9QX
 (Mail Order only)

MULLARD TECHNICAL HANDBOOKS—fifteen volumes and six supplements giving specifications on Capacitors, Semiconductors, I.C. Tubes and Resistors. £12 including postage. **FRANK MORTON**, 24 The Chestnuts, 70 Cleantus Road, London, S.E.18.

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
 Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
 367 Kensington Street
 Bradford 8, Yorks.

SERVICE SHEETS

SERVICE SHEETS, radio, TV, etc. 10,000 models. Catalogue 24p plus S.A.E. with orders-enquiries. TELRAY, 154 Brook Street, Preston, PR1 7HP.

SERVICE SHEETS for radio, TV, tape recorders, stereo, etc., with free fault-finding guide, 50p and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

LADDERS

LADDERS, timber and aluminium. Tel. Telford 586644 for brochure.

MISCELLANEOUS

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

ALUMINIUM PROJECT BOXES, lids and screws included

Box No.	Length	Width	Height	Price
7	5½	2½	1½	47p
8	4	4	1½	48p
9	4	2½	1½	46p
10	5½	4	1½	49p
11	4	2½	2	46p
12	3	4	1	38p
13	6	4	2	58p
14	7	5	2½	75p
15	8	6	3	93p
16	10	7	3	£1.14

Prices include VAT (at 8%) but 18p should be added to the total order value for postage & packing.

8 WATT 12V FLUORESCENT LIGHT KIT Complete Kit including all components, heatsink, channel, tube, etc. Only £3.49 inc. VAT p. & p. Ready built £4.10 inc. VAT, p. & p. Diffuser 59p extra inc. VAT p. & p.
 Send cheque or P.O.S. with your order direct to:

ELECTRONICS DESIGN ASSOCIATES
 Dept. PE, 82 Bath Street, Walsall, WS1 3DE.
 Phone, Walsall 33652

PRINTED CIRCUIT BOARDS, all prices inclusive of P. & P. etc. No extras. We offer: "P.E." Joanna PCB's, full spec., ready to assemble, any £1.30p each. Also full spec., ready to assemble PCB's for "P.E." Orion £1.30p, Power-slaves (2 PCB's) £1.52, C.C. TV (2 PCB's) £2.15. "Practical Wireless" Easy-build organ (2 PCB's) £5.70, teletennis (6 PCB's) £3.68, sound effects £1.10, tricolour £1.35, Ferret locator 75p, many others available. C.W.O. Send S.A.E. for lists. Production space available for PCB production, silk-screen printing, tinning, plus all art/graphic, photographic and design facilities. We also sell direct art/graphic aids and supplies. Cat. 40p. Production estimates by return or phone: **W.K.F. ELECTRONICS**, Welbeck Street, Whitwell, Worksop, Notts., S80 4TD. Tel. Whitwell (Derby's) 695 or 544, STD 009974. Callers seen by appointment only at Station Road.

PCB DIY SUPPLIES. We offer ferric chloride as used in our own plant, 4 lb £2.50, 1 cwt £23, 1 ton £350. 1 lb makes 1 gall. good strength. Solid carbide PCB drill bits from 1 mm up, £2.50. Most supplies for PCB production available from: **W.K.F. ELECTRONICS**, Welbeck Street, Whitwell, Worksop, Notts. Tel. Whitwell (Derby's) 695.

BUILD THE TREASURE TRACER MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screw-driver, pliers and snips
- As seen on BBC-1 and BBC-2 TV

Send stamped, addressed envelope for leaflet

Complete kit £10.90 Built and tested £15.25
 Post 50p 92p VAT (8%) Post 50p 1.27 VAT (8%)

MINIKITS ELECTRONICS, 6g CLEVELAND ROAD
 LONDON E18 2AN (Mail Order Only)

CABINET FITTINGS

FOR

Stage Loudspeakers and Amplifier Cabs
 Fretcloths, Coverings, Recess Handles, Strap Handles, Feet, Castors, Locks and Hinges, Corners, Trim, Speaker Bolts, etc., etc.
 Send 2 x 7p Stamps for samples and list.

ADAM HALL (P.E. SUPPLIES)

Unit G, Starline Works, Grainger Road
 Southend-on-Sea, Essex.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Examples, Width, Depth, Height, 8" x 5" x 3" £1.55; 10" x 6" x 3" £2.20; 10" x 8" x 3" £2.75; 12" x 10" x 3" £3.60; 8" x 4" x 4" £1.80; 10" x 6" x 4" £2.70; 12" x 8" x 4" £3.60; 7" x 7" x 5" £2.65; 8" x 10" x 6" £3.60; 12" x 8" x 7" £4.12; 12" x 12" x 7" £4.40. Plus 8% VAT & 50p postage. Over 200 models to choose from. Prompt despatch. Free literature (stamp would be appreciated). **BAZELLI**, Dept. No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

BUILD YOUR OWN

YOU ARE INVITED TO SEND S.A.E. FOR LISTS ON OUR VERY EXTENSIVE RANGE OF HIGH QUALITY AMPLIFIERS, PRE-AMPS, F.M. TUNERS, INSTRUMENTS, RADIO CONTROL, IGNITION UNITS AND MANY OTHER KITS. STATE REQUIREMENTS.

TELERADIO ELECTRONICS
 325 Fore St., Edmonton, London N9

SCREWS, nuts and washers. Useful quality assortment. £1.50 per packet inclusive. Write: **C. BRITTAIN**, The Bungalow, Old Titness, Buckhurst Lane, Sunninghill, Ascot, Berks. SL5 7QB.

BUILDING YOUR OWN HI-FI AMPLIFIER?

WHY NOT USE A PROFESSIONAL CASE? We have a limited number of high quality case assemblies valued at over £15-00 which must be sold.

LOOK AT THESE FEATURES:

- ★ Ready punched steel chassis
- ★ 3 piece, teak veneered case
- ★ Screen printed front and rear plates
- ★ Supplied complete with push switches
- Overall dimensions 17" x 8 1/2" x 3".
- Fantastic value at only £8.95 (inc. VAT and P. & P.)

Send cheque or P.O. now to:

SOUND ELECTRONICS (NEWCASTLE) LIMITED

43 Heaton Grove, Newcastle upon Tyne, NE6 5NP
Tel. (0632) 651008

DIVIDERS from Selmer organ, 5 double triodes each, £10 for 12 or £1 each (gone solid state). 'Halo' Wahwah £8, 4-channel mixer £11, top-boost £7, all as new. JARVIS, Dall, Rannock Station, Perth.

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	1/2lb Reel
10-14	£2.05	£1.15
15-19	£2.15	£1.20
20-24	£2.20	£1.25
25-29	£2.25	£1.30
30-34	£2.35	£1.38
35-40	£2.50	£1.45

All the above prices are inclusive in U.K.

COPPER SUPPLIES

102 Parwood Rd., Withington, Manchester 20
Telephone 061-445 8753

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine, and other individual requirements, one-off's and small runs. Machine engraving in metals and plastics, contour milling. Send 2 4p stamps for catalogue. RAMAR CONSTRUCTOR SERVICES, Masons Road, Stratford on Avon, Warwick. CV37 9NF.

fibre optic suppliers

MARE'S TAILS. Build a decorative display with this professionally finished unit, 22in diameter with 7,000+ fibres. Looks immaculate. £10.
FIBROFLEX SIZE 1. Flexible 440 strand glass light conduit, bundle dia. 1.14mm. 40p per metre (£3 per 10m).
FIBROFLEX SIZE 4. 2.28mm bundle dia., 1,780 strand glass light conduit, £1.90 per metre (£12 per 10m).

CROFON 1618. 84-strand plastic light conduit, bundle dia. 1.8mm, O.D. 3.3mm, £1.50 per metre (£9 per 10m).
PLASTIC OPTICAL FIBROFIBRE. For multiple illumination from one source, displays, internal illumination, effects, optical coupling, etc.

FP20 (0.5mm dia.)—£0.90 per 10m; £4 per 100m.
FP40 (1mm dia.)—£2.10 per 10m; £15 per 100m.
FP80 (1.5mm dia.)—£4 per 10m; £30 per 100m.

OPTIKIT 103. Contains 2m Crofon 1618 plus 5m each FP20, FP40, FP80 plus polishing compound. A handy pack for the experimenter and laboratory. £4-80.

LENSSES AND REFLECTORS. We stock a range of 8 lenses and 5 reflectors for use in proximity detectors, intruder detectors, batch counters, tachometers, short range optical communications.

OPTIKIT LS. 1 each of 6 convex lenses. £3.

OPTIKIT RRS. 1 each of 5 retro-reflectors. £2-50.

CIRCULAR POLARISERS. Cut that glare. Reduce specular reflection by up to 20x—enhance contrast on CRTs. LED displays, nixies, instruments, etc. Available in red/amber/green/neutral. 50mm square 70p; 75mm £1-40; 150mm £4-50.
LIGHT SOURCES AND DETECTORS: MV54 Miniature (2mm) Red LED, 20p (10 + 17p); MLE0500 Y092 Red LED, 20p (10 + 17p); MLE092 infra-Red Emitter, 20p (10 + 25p); XC208-R 3mm Red LED, 20p (10 + 17p); XC209-Y or -G Yellow/Green, 30p (10 + 25p); 2N5777 High Sensitivity Photodetector Silicon Detector, gain x2,500, 50p (10 + 42p); MR150 Silicon Phototransistor—high speed, 40p good sensitivity, 70p (10 + 87p).

****NEW MLE003.** Latest Motorola Light Activated SCR. High sensitivity 10mW/cm²; high current 400mA (5A peak); 60V. Switch small motors or relay direct from optical control, up to 24W power. £1-20 (10 + £1-10).

SE05B-40T/R ULTRASONIC TRANSDUCER PAIR. Suitable for "Ultrasonic Doppler Shift Intruder Detector". Practical Electronics, March 1975. Tx/Rx pair £4.
SE05B-25T/R ULTRASONIC TRANSDUCER PAIR.

**** NEW **** The SE05B-40T/R has proved to be an extremely popular item in our range and we are therefore introducing the 25kHz version. Although bandwidth is less at ±500Hz, sensitivity is better by 10dB. Suitable for burglar alarm systems, proximity switches, counters, level meters, anti-collision devices. 25kHz Tx/Rx pair £4.

Please add 8% VAT to prices above (plus 2p on orders less than £3). Send 9in x 6in S.A.E. for short form list.

FIBRE OPTIC SUPPLIERS

(Dept. PE), 2 Loudoun Road Mews

London NW8 0DN

(Please note change of address)

DIGITAL CLOCK CHIP, AY-5-1224, with data and circuit diagram, £3-06 plus VAT. "Jumbo" LED digits (16mm high), Economy type. DL-747, only £2-04 each plus VAT, post free. GREENBANK ELECTRONICS, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

12 VOLT 21in 13 watt FLUORESCENT LIGHTING (by THORN/AEI) with diffuser and on/off switch. Ideal, caravan, boat, emergency lighting, etc.

£5-50

inc. VAT and post
List price £7-02 inc. VAT

SALOP ELECTRONICS Tel. 53206
25 Wyle Cop, Shrewsbury, Shropshire

LOW COST I.C. MOUNTING for any size DIL package. 100 pin sockets 50p. 7 and 8 hole plastic supports 5p pair. Quantity rates. S.A.E. details and sample. Trial pack 50p. (P. & P. 10p order). P.K.G. ELECTRONICS, Oak Lodge, Tansley, Derbyshire, DE4 5FE.

THE SCIENTIFIC WIRE CO.

Copper—Nickel Chrome—Eureka—Manganin Wires.

Enamelled—Silk—Cotton—Tinned Coverings.

No minimum charges or quantities. S.A.E. Brings List.

Trade and export enquiries welcome.

P.O. BOX 30, LONDON E4 9BW

"PE JOANNA"

BULK COMPONENTS LIST

(page 388 May '75 issue)

EVERYTHING LISTED FOR JUST £44.61 inc. VAT + OUR USUAL DISCOUNT VOUCHERS or WITHOUT DISCOUNT VOUCHERS

£41-61 inc. VAT BY RETURN OF POST ... of course!

These are all top quality brand new components Capacitors and Resistors by Mullard, Diodes by I.T etc. For keyboards etc. see our catalogue 40p.

* CT2 Transformer in stock £2.72 inc. VAT *

Maplin Electronic Supplies
P.O. Box 3, Rayleigh, Essex

I.C. EXPERIMENTER'S KITS.

Learn about modern electronics with our new series of Kits on digital logic techniques. Kits contain specially selected I.C.'s, Holders, Veroboard, L.E.D.'s, instructions and data. Now available at £3-50 each:

Kit One: Gates Kit Two: Flip-Flops

Kit Three: Shift Registers

Experimenter's Pak, I.C.'s of Gates, Flip-Flops, Inverters, Counters, Holders and data. £3-00.

S.A.E. for further details to:
AUTOMATED HOMES
69 High Street, Rytom, Coventry CV8 3FJ
(Mail Order only)

HOME SCIENTISTS

Get the key to a FANTASTIC WORLD of previously UNHEARD-OF PROJECTS. The NEW Boffin catalogue lists LOTS of HIGHLY UNUSUAL, LOW-COST BARGAINS, READY-BUILT MODULES.

Here are just a few examples, there are stocks more!

Dazzling MINI-STROBE (pocket size) £3-50
PEOPLE DETECTOR .. £4-20
Big-Ear SOUND-CATCHER .. £4-20
Mini DREAM LABORATORY .. £4-20

Don't take our word for it though! GET A COPY AND SEE! SEND ONLY 20p and we'll RUSH you a COPY YOU'LL GET THE 'GOODIES' JUST AS QUICKLY TOO!

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh

Ewell, Surrey


(Mail Order U.K. only)

FANTASTIC NEW MICROTEST 80

MEASURES

ONLY 90 x 70 x 18mm

ELECTRONIC ZERO Ω

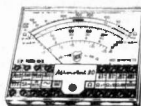

Amazing Value at £11-95
8 fields of measurement and 40 ranges

PRINTED CIRCUIT BOARD IS REMOVABLE WITHOUT SOLDERING

Volts d.c. 8 ranges: 100mV, 2V, 10V, 50V, 200V, 1,000V (20kΩ/V), 2% precision on d.c. and a.c.
Volts a.c. 5 ranges: 1.5V, 10V, 50V, 250V, 1,000V (4kΩ/V).
Amp. d.c. 8 ranges: 50μA, 500μA, 5mA, 50mA, 500mA, 5A.
Amp. a.c. 5 ranges: 250μA, 2.5mA, 25mA, 250mA, 2.5A.
Ohms 4 ranges: Low Ω, Ω x 1, Ω x 10, Ω x 100 (from 1/10 dΩ until 5MΩ).
V Output 5 ranges: 1.5V, 10V, 50V, 250V, 1,000V.
Decibels 5 ranges: +6dB, +22dB, +36dB, +50dB, +82dB.
Capacity 4 ranges: 25μF, 250μF, 2,500μF, 25,000μF.



SUPERMETER 680R ICE

20,000 Ohm per Volt sensitivity
Fully screened against external magnetic fields
Scale width and small case dimensions (128 x 95 x 32mm)
Accuracy and stability (1% in D.C., 2% in A.C.)
of indicated reading
Simplicity and ease of use and readability
Full ranges of accessories

1,000 times overload
Printed circuit board is removable without desoldering
More ranges than any other meter. Ask for free catalogue

£18-50

Accessories Extra

Accessories (extra) available to convert Microtest 80 and Supermeter 680R into following: LIGHTMETER, GAUSS METER, ELECTRONIC VOLT METER, AMPER-CLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR, Ω x 100kΩ Multiplier, SIGNAL INJECTOR—Send for details.

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324


A-DC 0-06-3A-6 Ranges
A-DC 0-3-3A-5 Ranges
V-DC 0-6-120V-9 Ranges
V-AC 3-300V-5 Ranges
Frequency in the range of 45 to 20kHz. Resistance: 500 ohm to 5 Mohm—5 ranges. Decibel: -10 to +12dB. Accuracy: ±2.5% DC ±4% AC. Dimensions: 167 x 98 x 63mm.



Only £9-25

ALPHANUMERIC NIXIE TUBES B7971

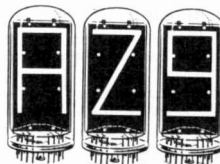The Alphanumeric NIXIE tube provides many unique benefits including: 170V-21mA * All d.c. operation * Uniform, continuous line characters of actual height * Memory with simple solid state drive circuits * Readability in high ambient light ... 200 footcandle brightness * Long life with no loss of brightness * Character height 2 1/2in.



Bases for above 80p each.
Price only 99p each plus 16p P.P.

JUST ARRIVED!!

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V d.c. Current 14mA. Pulse duration 100μs. Character height 0.51, overall size 1 1/4in.

Brand new, guaranteed. Surplus to manufacturer's requirements Type BS853et

1-25 £1-00; 25+ 90p; 100+ 80p;

1,000+ price on application.

Add 8% VAT to all items + 35p P. & P.
ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel. 01-837 7781

AERIALS	
Telescopic, 15-120cm	£1.50
Telescopic, H & V Swivel, 15-80cm	£2.25
Indoor FM antenna, Compact design	£2.45
Loft mounting FM dipole antenna	£2.45
CAPACITANCE SUBSTITUTION BOXES	
Single control for easy selection	
0001, 001, 0022, 01, 022, 047, 0.01, 0.22	£2.35
KEYNECTORS	
Rapid connect to mains. Built-in piano switches, neon & 13A fuse	£3.50
MULTIMETERS	
Vdc-10, 50, 250, 1,000. Vac-10, 50, 250, 1,000. Idc-100mA, R-150k	£4.95
PRINTED CIRCUIT KITS	
Contain all items necessary to produce printed circuits	£3.95
SIGNAL INJECTORS	
Audio through video signals, ideal -servicing amplifiers, radio & tv	£4.25
TEST SWITCHES	
5 miniature push to test switches	£1.00
VERNIER DIALS	
Positive logging to 1/10th of a degree, 8:1 ratio, clear scales	£2.45
YU METERS	
Calibrated -20 to +3, 0-100%, ideal -recording level or power output	£3.40



AUDIO PRODUCTS



AUDIO LEADS	
5p din plug to 5p din plug, 1.5m lead	£1.20
2p din plug to 2p din skt. 10m lead	£1.45
5 pin din plug to 2 phone plugs	£1.20
BIB HI-FI ACCESSORIES	
GROOV-KLEENS-Ref. 42	£1.95
1/4" TAPE EDITING KITS-Ref. 23	£1.50
CASSETTE EDITING KITS-Ref. 24	£1.65
CASSETTE HEAD CLEANERS-Ref. 31	£0.65
HI-FI STEREO TEST CASSETTES-Ref. 53	£2.15

CASSETTE WALLETS (HOLD 6)-Ref. 39	£0.90
CASSETTE HEAD DEMAGNETISERS	
Shaped pole piece-saves time	£3.65
EARPHONES	
Stethoscope style, 8 ohm dynamic	£1.20
Crystal earphone with lead & plug	£0.65
High resistance, 2000 ohm headphone	£3.20
FOOT SWITCHES	
Push on-push off, Anti skid base	£2.70
INTERCOMS	
2-station, ideal for the home-baby alarm, office, with cable & staples	£6.35
Door-phone 'Answer door before opening' Completely weatherproof	£9.95
MICROPHONES	
Dynamic, remote start/stop, 200 ohms, 100-10kHz, 6mV output	£2.15
MINIATURE TRANSISTOR MODULES	
Microphone pre-amplifier	£2.45
Power amplifier (Each plug-in with mounting socket)	£2.70
STEREO HEADPHONES	
Superb stereo listening in comfort and privacy, 30-15kHz, 8 ohms	£4.85
STEREO HEADPHONE JUNCTION BOXES	
3 way switch unit selects phones only, speakers only or both	£2.30
STEREO PRE-AMPLIFIERS	
In: 3-30mV, Equalise: RIAA. Out: 200-800mV flat. 20-20kHz. Supply: PP3	£7.30
SPEAKERS	
Miniature, 75mm dia, 8 ohms	£0.95
TWEETERS & CROSSOVERS	
Super Tweeters, 8 ohms, c/f 7kHz, For systems up to 30W RMS	£4.60
Cone Tweeters, 8 ohms, c/f 3kHz, For systems up to 10W RMS	£2.35
Crossovers, 8 ohms, c/f 800, 3kHz, 7kHz, For systems up to 40W RMS	£5.85
Crossovers, 8 ohms, c/f 3kHz, For systems up to 15W RMS	£2.10

BATTERY ELIMINATORS	
Miniature AC adaptor-provides 9V at 50mA DC output from mains	£4.35
POWER SUPPLY UNITS	
P1 Switchable between 6 & 9V (200mA) ideal-most small radios, etc.	£4.85
P2 Switchable to provide 6, 7.5, 9V at 400mA	£7.15
TRANSFORMERS	
Mains (miniature), 2 secondaries	
0-6V, 0-6V RMS, 280mA	£2.70
0-12V, 0-12V RMS, 150mA	£2.70
Mains (sub miniature)	
6-0-6V RMS, 100mA	£1.45
12-0-12V RMS, 50mA	£1.45
PERSONAL RADIOS	
Philips RL077 with earphone & case	£6.00
Philips RL020 with earphone & case	£7.50



TOOLS



COMBINATION TRY & MITRE SQUARES	
Cabinet/Chassis/P.C.B. work. One tool combining Try & Mitre Square, Depth, Height and Marking Gauges. 300mm/12in Rule. Spirit Level/Plumb & Steel Scriber	£2.35
HAND DRILLS	
Laytool compact, 5/16" chuck, Gears totally enclosed, S/L bearings	£3.99
SOLDERING IRONS	
Antex 25W, X25, 240V, Low leakage, 1/8" interchangeable long life bit	£2.05
3/32", 1/8", 3/16" spare bits-each	£0.47
X25 Elements	£1.10
Stands, ST3, High grade base, spring, sponges, accommodation-spare bits	£1.00
SOLDER -in handy 8lb dispenser	£0.43
WIRE STRIPPERS & CUTTERS	
8lb 8B, 8 gauge selector, automatic opening, easy grip handles	£0.85

SYNTHESISER
Modules by Dewtron®



The synthesiser illustrated was built using Dewtron modules, as sold to constructors for some years now. With over 10 years' experience in mail-order, we have supplied many famous people and groups. Over 30 types of synthesis modules, some of extremely precision design, e.g. VCO-2 log-law oscillator; 3-wave o/ps; sample/hold/envelope module; pitch-to-voltage module allowing a whole equipment to "play itself" in unison/harmony with any solo input or voice. Modules for sequencer construction, too. Famous "Modumatrix" patching system makes other patching a thing of the past! Send just 20p for full catalogue to:

D.E.W. LTD.

254 Ringwood Road, Ferndown
Dorset BH22 9AR

DIGITAL CLOCK KITS
SENSATIONAL OFFER

£2 OFF

FAST BUILDING, EASY TO FOLLOW INSTRUCTIONS. A VERY COMPLETE KIT



CLOCK DATA
SIZE 6½ x 3 x 2½ in
MAINS
OPERATION
50/60Hz
12/24 HOUR

USUAL PRICE TO P.E. READERS

NO KNOWLEDGE OF ELECTRONICS REQUIRED
LATEST 1975 DESIGN—ONLY £14
(including P. & P., VAT, Circuit)

COMPARE OUR PRICES IF PURCHASED AS SINGLE ITEMS (INCLUDING VAT AND P. & P.)

1 MOS Clock Chip 12-24 hr option	£ 95
4 0.63" LED Displays (latest HI BRI Type)	4.60
1 Segment Driver Chip	0.50
1 Pack Resistors, Caps., Transistors, Switch, etc.	1.60
1 Double Sided Glass Fibre P.C. Board	0.95
1 Double-wound Mains Transformer	1.50
1 Circuit/Assembly Manual	0.50
1 Futuristically-styled Case (state colour)—Yellow, Orange, Red, Black, White, Mauve, Green, Blue	4.40

Pulse Electronics Ltd

Dept. PE2, 202 Shefford Road, Clifton, Beds.
Tel. Hitchin (0462) 814477



TELEVISIONS AND SPARES TO THE TRADE

MONOCHROME TELEVISIONS

BBC 2 Dual Standard TVs (19in, 23in) in batches of 10—£2 each (makes include Bush, Thorn, Philips, Pye/Ekco, Baird). Many with transistorised tuners. GEC 2000, Thorn 950 series, Bush 141, Philips Style 70, Baird 600 and 700 series all at £6 each. Thorn 1400, Bush 160/170 series, Philips 210, Pye-Ekco Olympic, etc., Baird 673, Push Button—all at £12-50 each. 20in and 24in square screen Dual Standard sets—Thorn, GEC, etc., 20in—£15, 24in—£16-50. 20in and 24in Single Standard Thorn 1500, GEC, Bush Acoustic. 20in—£17-50, 24in—£19-50.

(1) Discounts for quantities. (2) All monochrome spares supplied free of charge. (3) All tubes guaranteed. (4) All cabinets very good. (5) All sets "walk and talk". (6) All sets guaranteed complete inside and out. (7) Delivery and VAT extra.

Portable TV: 16in Thorn UHF—£15 working, £12-50 untested.

COLOUR TELEVISIONS

Colour TVs 19in and 25in. Makes include Thorn 2000, Bush CTV25, Decca CTV 19/25in, Pye-Ekco, Baird 700 and 710 series, Philips G6, GEC 2028. All sets guaranteed complete inside and out—cabinets first class and tubes guaranteed. From £85 each. 20in and 22in Colour Televisions are always available in varying quantities—please telephone for availability and cost.

Please Note: (1) We deliver anywhere by our own transport. (2) All goods are blanket wrapped in our vans. (3) All orders with half deposit, balance on delivery after inspection. (4) Cheques most welcome. (5) Any quantity supplied. (6) We do not sell rubbish, and we stand by our guarantees. (7) We aim to please. (8) All spares supplied free of charge (mono only).

N.B. Special arrangements for delivery to North and South Ireland and world-wide exports orders welcomed.

TEST BENCH FACILITIES ALWAYS AVAILABLE

MISCELLANEOUS ITEMS

Large quantities of stereograms, fridges, deep freezers, Hoovermatics, radios, etc., always at hand—prices on request.

COLOUR SCAN COILS Mono
All dual standard £5 plus £1 P. & P. All makes £2 inclusive.

VALVES
All colour valves 40p each plus 5p All mono valves 10p each plus 2p each P. & P. per valve.

TUBES
19in—£15, 22in—£22, 25in—£20 (post. insurance, packing £5). 19in—£3, 20in—£4-50, 23in—£4, 24in—£6 (post. insurance, packing £3).

CABINETS
19in—£12, 22in—£16, 25in—£14 (post. insurance, packing £5). All cabinets—£5 including post. insurance, packing.

LOPTs
All dual standard colour £5-50 plus £1 P. & P. All makes available. All dual standard mono £2-50 plus £1 P. & P. All makes available.

PLEASE ALLOW 2 WEEKS DELIVERY. S.A.E. PLEASE FOR ENQUIRIES. ALL STOCK EX-EQUIPMENT
BARCLAYCARD, ACCESS AND PROVIDENT WELCOME

TRADE DISTRIBUTORS

5 COMMERCIAL STREET, HARROGATE, YORKSHIRE

Telephone: (STD 0423) 3498 and 62347

COLOUR PANELS Mono
IF, Decoder and Convergence—frame IF, Line timebase £3 plus £1 P. & P. All output for all dual standard models dual standard models in stock. from £7-50 plus £1-50 P. & P. All models available.

SLOT METERS
10p meters—£1-50 each including postage and packing.

SPEAKERS
6in x 4in, 5in Round, 8in x 2in 30p each plus 10p P. & P.

MAIL ORDER SERVICES

BLACK/WHITE TELEVISIONS
Working: 19in—£9-50, 23in—£12-50, 20in—£20, 24in—£24-50. Untested (but guaranteed complete with good tubes): 19in—£4, 23in—£5, 20in—£15, 24in—£18.

(Postage, packing and insurance £3-50 each; prices include VAT.)
N.B. All tubes guaranteed

COLOUR TELEVISIONS
Working: 19in—£85, 22in—£125, 25in—£130. Untested (but guaranteed complete with good tubes): 19in—£70, 22in—£90, 25in—£95.

(Postage, packing and insurance £9 each; prices include VAT.)
Thorn 2000, Bush CTV25, Philips G6, GEC2028, Baird 700, Decca CTV25

PORTABLE BBC2 16in TELEVISIONS (MONOCHROME)
Working £19-50. Untested £15. (Postage, packing and insurance £3; prices include VAT.)

MAIL ORDER SPARES. Special Offer—Brand new spares:
BRC 2000 panels, video, convergence, and regulator—only £12-50 plus £1-50 P. & P.

Bush CTV 25 Line timebase-tower unit including LOPT and valves Mk. 1 and II only—£18 plus £3 P. & P.

BRC single standard colour 4 button tuners colour and mono—£7-50 plus £1 P. & P.

UHF Vari-cap tuner units—£6-50 plus £1 P. & P.

VHF Vari-cap tuner units—£7-50 plus £1 P. & P.

Pye-Ekco CTV Tripler units—£6-25 plus 75p P. & P.

Philips G8 Tripler units—£7-50 plus 75p P. & P.

KB VC Series LOPT £2-50 including P. & P.

Bush 125 and 135 IF PANELS—£3-50 plus 75p P. & P.

Thorn 850 IF Panels—£2-50 plus £1 P. & P.

GEC 2000 IF Panels—£3-50 plus £1 P. & P.

EX-EQUIPMENT TUNERS:

Colour:
All dual standard colour push button—rotary and integrated models in stock at £4-50 plus £1 P. & P.

Mono:
All VHF tuners available at £2 plus £1 P. & P.
All UHF tuners for dual standard models in stock. Push button—£3-50 plus £1 P. & P.

Rotary—£2-50 plus £1 P. & P.
Integrated (UHF and VHF) £4-50 plus £1 P. & P.

Comprehensive list of capacitors, resistors, etc., too numerous to mention. Prices on request.

MAKE YOUR CALCULATOR RECHARGEABLE!

(Amongst other things!)

- ★ Ni-Cad. 1-2V rechargeable batteries
- ★ HP7 size
- ★ Charging 45mA/15h
- ★ Capacity 450mAh

only **£1-95** for TWO!! Including P. & P. & VAT

Write to Dept. PE

GUILDFORD CALCULATOR CENTRE
181 High St., Guildford, Surrey. Tel. (0483) 35014



DISCO PROJECTORS

Optikinetics Solar 100B Multi-Effect projector 100W QI lamp complete with oil wheel rotator and cassette rotator

£48-60 Postage £1

Bubblelite 150W complete with rotator and 6" oil wheel

£22 Postage £1

TUTOR 2 The most versatile effects projector available. 250W QI lamp complete with rotator and 6" oil wheel

£78 Postage £1-50

6" oil wheels £3-50 postage 25p, effects cassettes £5-85 postage 25p

Optikinetics, ICE, Pluto disco gear at discount prices. S.A.E. for list

4 FUNCTION MEMORY

Add or subtract from memory, display and retain or display and clear. Bright green display.

cbm GL997R

- ANTI-GLARE 8 digit display
- 4 function memory (MR, MT, M+, M-)
- Live percentage key
- Automatic constant
- Rechargeable

£16-55

+50p postage

A. E. Crew Electrical

56 MARKHAM ROAD, WINTON
BOURNEMOUTH, DORSET BH9 1HZ

Don't miss your copy of HENRY'S NEW 1975 CATALOGUE



only 50p
Plus 20p
P&P

- ★ **OVER 5,000 ITEMS** – largest UK range of electronic components for home constructors.
- ★ **200 PAGES** – every aspect of electronics and components for amateurs and hobbyists – kits, projects, test gear.
- ★ **DOZENS** of new lines and new ranges.
- ★ **MANY price reductions** throughout the new Catalogue.
- ★ **A Discount Voucher** with every copy, worth 50p.

ALL PRICES INCLUSIVE OF VAT

Write now for your copy, enclosing 70p remittance

MIDLANDS. NEW ELECTRONICS STORE
OPEN. 94/96 UPPER PARLIAMENT STREET,
NOTTINGHAM. TEL: 40403.

HENRY'S

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
354 PA-Disco-Lighting High Power Sound 01-402 5854
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Hi-Fi and
Electronics
Centres Open
9 am - 6 pm

Prices correct at time of preparation. Subject to change without notice £ & 0. £

ELECTRONIC FOOTBALL AND TENNIS WITH THE FABULOUS

VIDEO SPORT

ON YOUR OWN TV
Play three exciting electronic ball games. FOOTBALL, TENNIS, HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. Mains operated.



OUR INCREDIBLE PRICE
£29.50 incl. VAT
Demonstrations now in all CENTRES!

AM/FM MODULES

LP1179 LP1171
Combined AM/FM tuner modules, together with a small number of R's and C's and Ferrite Aerial, make up a sensitive FM/MW/LW tuner. 6 Volts supply, supplied with data and circuit sheets.
LP1171 combined IF strip £4.60.
LP1179 FM front end and AM gang £4.60.
£8.62 the pair.
Suitable Ferrite aerial 87p.



UHF TV TUNERS

625 line receiver UHF transistorised tuners U.K. operation. Brand new. (Postpacking 25p each)
TYPE A variable tuning slow motion drive £3.50.
TYPE B 4-button push button (adjustable) £4.60.
TYPE C variable tuning £2.90.
TYPE D 6-button UHF/VHF tuner £5.20

BUILD THE TEXAN + FM TUNER TEXAN 20 + 20W STEREO AMP

Features glass fibre PC board, Gardners low field transformer, 6-L.C.s, 10-transistors plus diodes, etc. Designed by Texas instruments engineers for Henry's and P.W. 1972. Overall size 15 1/2 x 2 1/2 x 6 1/2in. Mains operated. Free teak sleeve with every kit.



£29.95
(carriage 50p)
(also built and tested £39.95).

HENELEC STEREO FM TUNER


Features capacity diode tuning, lead and tuning meter indicators, mains operated. High performance and sensitivity. Overall size in teak sleeve 8 x 2 1/2 x 6 1/2in. Complete kit with teak sleeve.

£26.25 (carriage 50p)
(also built and tested £31.20)

JOIN THE LARGE BAND OF CONSTRUCTORS!

SPECIAL OFFER GARRARD CT4 STEREO CASSETTE TRANSPORT MECHANISM

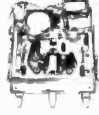Features: *Stereo heads *Built in motor stabiliser. *Auto stop + eject *Pause control. *12V d.c. operation.
Robust, precision engineered mechanism based on the STARR patented design. Ideal for use in car stereo cassette players, Hi-Fi stereo cassette recorders, industrial and many other applications.
Suitable for the PW Ascot Stereo Cassette Dock.



£13.50 INCL. VAT P. & P. 35p

FREE
Send now for our free list No. 36 for our complete range of over 2,000 semiconductor devices at new low prices.



Sparkrite MK2

The tried, tested, proven, reliable, complete, professional, capacitive discharge,
Electronic Ignition Kit

Sparkrite MK2 was voted best of 8 systems tested by Popular Motoring Magazine

PATENT PENDING

ORDER NOW

TO ELECTRONICS DESIGN ASSOCIATES DEPT PE10,
82 Bath Street, Walsall, WS1 3DE. Phone 33652.

FROM Name _____

Address _____

City _____

SPARKRITE MK 2 DIY Assembly kit	£10.93
SPARKRITE MK 2 Ready Built Negative earth	£13.86
SPARKRITE MK 2 Ready Built Positive earth	£13.86
Ignition changeover switches	£2.78
R.P.M. Limit systems in the above units	£2.42

I enclose cheque/P.O.s for £ _____

Cheque No. _____
(Send SAE if brochure only required)

Sparkrite MK2 is a high performance, high quality, capacitive discharge, electronic ignition system. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact-breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and therefore eliminates the possibility of blowing the transistors or the SCR. (Many capacitive discharge ignitions are not completely foolproof in this respect.)

Sparkrite can therefore give you—
up to 20% better fuel consumption, instant all weather starting, cleaner plugs — they last up to 5 times longer without attention, faster acceleration, higher top speeds, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.

THE KIT COMPRISES EVERYTHING NEEDED
Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heatsink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS
Electronic R.P.M. limitation.
This can be included in the unit to prevent over revving. An advantage to most companies, hire firms, high performance drivers etc.
Electronic conventional ignition switch.
Gives instant changeover from Sparkrite ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device. Includes switch, connectors, mounting bracket and instructions. Cables excluded.

PRICES
DIY assembly kit £10.93 incl. V.A.T. post and packing
Ready built unit £13.86 incl. V.A.T. post and packing (Both fit all vehicles with coil/distributor ignition up to 8 cylinders.)
Switch for instant changeover from Sparkrite ignition to conventional ignition £2.79 incl. V.A.T. post and packing
R.P.M. limiting control £2.42 incl. V.A.T. post and packing (Fitted in case on ready built unit, dashboard mounting on kit.)

CALLERS WELCOME

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

- 4 Transistor Earpiece Radio
- Signal Tracer
- Transistor Injector
- Transistor Tester NPN -PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier

- 7 Transistor Loudspeaker Radio MW/LW
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- One Transistor Radio

- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier

Components include:

- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 3 1/2" Loudspeaker ● Earpiece ● Mica Baseboard
- 3 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 2 818r Tuning Condensers ● 3 Knobs
- Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6 1/2 yards of wire ● 1 yard of sleeving, etc.
- Parts price list and plans 55p (free with parts)

TOTAL BUILDING COSTS

£10-30 P.P. & Ins. 65p
(Overseas Seamail P. & P. £3-40)

ROAMER TEN Mk. II

WITH VHF INCLUDING AIRCRAFT



10 TRANSISTORS.
9 TUNABLE WAVE BANDS.
MW1, MW2, LW, SW1, SW2, SW3.
TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND


Now with free earpiece and switched socket.

Latest 4" 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Chrome plated 6 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver beeking. Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 60p (FREE with parts)

TOTAL BUILDING COSTS **£11-87** P.P. & Ins. 65p
(Overseas Seamail P. & P. £3-50)

POCKET FIVE

NOW WITH 3" LOUSPEAKER

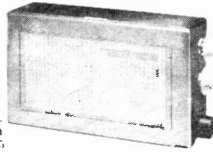

5 TUNABLE WAVEBANDS MW/LW and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive Black and Gold Case. Size 5 1/2in x 1 1/2in x 2 1/2in approx. Plans and parts price list free with parts.

Total Building Costs


£3-70

P.P. & Ins. 38p

(Overseas Seamail P. & P. £2-30)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

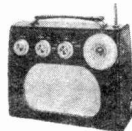

7 TUNABLE WAVEBANDS:

MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Chrome plated telescopic aerial can be angled and rotated for peak short-wave listening. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch, 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£8-73** P.P. & Ins. 65p
(Overseas Seamail P. & P. £3-50)

NEW JIFFY TESTER

Easy to build and operate, fits in the pocket. A quick checker for continuity of resistors, chokes, diodes, transistors, circuit wiring (not mains) and loudspeakers. Also for checking short circuits of capacitors, tuning capacitors and many other uses not listed here. See instruction sheet free with kit.

Complete with earpiece, jack plug and socket, resistors, capacitors, components, etc. Parts Price List and Easy Build Plans free with Parts

Total Building Costs

£2-81

P.P. & Ins. 22p (Overseas Seamail P. & P. £1-70)

NEW EVERYDAY SERIES EV6




Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 ins. approx. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull Output. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£4-98** P.P. & Ins. 50p
(Overseas Seamail P. & P. £2-30)

TRANS EIGHT

8 TRANSISTORS AND 3 DIODES

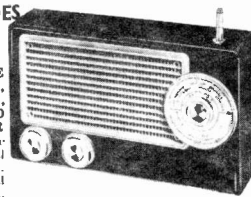

6 TUNABLE WAVEBANDS MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves.

3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

TOTAL BUILDING COSTS

£5-98

P.P. & Ins. 50p
(Overseas Seamail P. & P. £2-50)

"Edu-Kit"

Build Radios, Amplifiers, etc., from easy stage diagrams. Five units including master unit to construct.

Components include: Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine tone 3" moving coil speaker; Terminal Strip; Ferrite Rod Aerial; Battery clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 1/2in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£6-87** P.P. & Ins. 50p
(Overseas Seamail P. & P. £3-40)

ALL PRICES NOW INCLUSIVE VAT

- ★ Callers side entrance "Lavells" shop
- ★ Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE LTD

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52367 Reg. No. 788372

I enclose £ for

- | | | | |
|--------------|--------------------------|---------------|--------------------------|
| ROAMER TEN | <input type="checkbox"/> | EV6 | <input type="checkbox"/> |
| ROAMER EIGHT | <input type="checkbox"/> | TRANS EIGHT | <input type="checkbox"/> |
| JIFFY TESTER | <input type="checkbox"/> | MAJOR EDU-KIT | <input type="checkbox"/> |
| POCKET FIVE | <input type="checkbox"/> | EDU-KIT | <input type="checkbox"/> |

Name

Address

PE9

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/Sia) Ltd., South Africa—Central News Agency Ltd.

International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

More than just a catalogue

Projects for you to build.

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc. . . .

CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .


Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc. . . .

REALLY GOOD VALUE FOR MONEY AT JUST 40p.

**MAPLIN
ELECTRONIC
SUPPLIES**

**SUPERSONIC
SAME-DAY-SERVICE
QUALITY COMPONENTS
-FAST!**

ELECTRONIC ORGAN

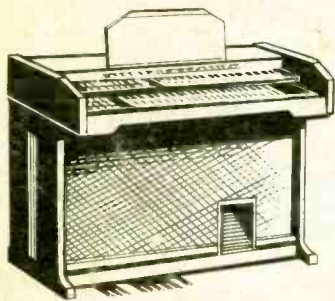

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops.

Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.

Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, priced at 35p.


No more doubts about prices

Now our prices are **GUARANTEED** (changes in VAT excluded) for two month periods—and we'll tell you about price changes in advance for just **30p** a year (refunded on purchases). If you already have our catalogue send us an S.A.E. and we'll send you our latest list of **GUARANTEED** prices. Send us **30p** and we'll put you on our mailing list—you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next **GUARANTEED** period before the prices are implemented!—plus details of any new lines, special offers, interesting projects—and clip-off coupons to spend on components to repay your **30p** when used as directed.

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to P.O. Box 3, Rayleigh, Essex, SS6 8LR.

SYNTHESISER

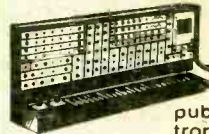

A reprint of the complete article giving full construction details published by "Electronics Today International" between January-September '74 of the International Voltage Controlled Synthesiser, developed as a "state of the art", now available, price £1.50. S.A.E. please for detailed price list.

GRAPHIC EQUALISER



A really superior high quality stereo graphic equaliser as described in the January edition of "Electronics Today International". We stock all the parts (except woodwork) including metalwork drilled and printed. It brings you a reprint of the article or a S.A.E. please for our detailed price list.

**MAPLIN
ELECTRONIC
SUPPLIES**

P.O. Box 3 Rayleigh Essex SS6 8LR.
Telephone: Southend-on-Sea (0702) 44101